
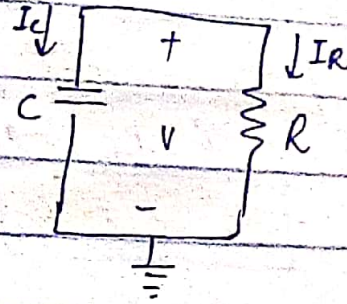
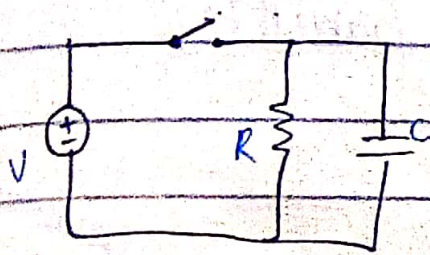


Ch#7: First order Circuits: → single element

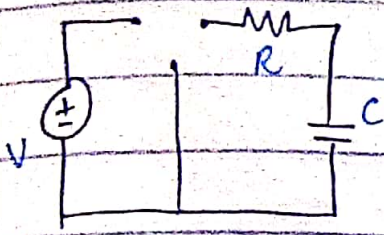7.2 The RC-source free ckt: - transient response.



applying KCL :-

$$i_C + i_R = 0$$

÷ by C on both sides: $\leftarrow C \frac{dv}{dt} + i_R = 0 \Rightarrow \frac{dv}{dt} + \frac{V}{R} = 0$

$$\boxed{\frac{dv}{dt} + \frac{V}{R} = 0}$$

→ 1st ODE (1st order differential eqn.)

$$\frac{dv}{dt} = -\frac{V}{R}$$

$$\frac{dv}{V} = -\frac{dt}{R}$$

voltage :-

integrate on both sides:-

$$\int \frac{1}{V} dv = -\frac{1}{R} \int (1) dt$$

$$\ln V = -\frac{t}{R} + \ln A/k/c \quad \text{const.}$$

⇒ when $t=0$; $V(t) = V_0$

So, $\ln V_0 = 0 + \ln A \Rightarrow \ln V_0 = \ln A \rightarrow \text{put in above.}$

$$\ln V - \ln V_0 = -\frac{t}{R}$$

$$\ln \left(\frac{V}{V_0} \right) = -\frac{t}{R}$$

$$\because e^{\ln x} = x$$

Taking exponential on both sides:-

$$e^{\ln(\frac{V}{V_0})} = e^{-t/RC}$$

$$V = V_0 e^{-t/RC}$$

V_0

or $V = V_0 e^{-t/RC}$

$\therefore \tau = RC \rightarrow$ time req. for response to decay to factor of 1/e or 36.8%

So, $V = V_0 e^{-t/\tau}$ — (1) Table # 7.1

When $t=0$:

$$V = V_0 e^{-0}$$

or $V = V_0(1)$

$$V = V_0$$

When $t = \tau = RC = 1$:

$$V = V_0 e^{-1}$$

$$V = V_0 e^{-1}$$

$$V = V_0(0.368)$$

~~$$\frac{V}{V_0} = 0.368$$~~

$$\frac{V}{V_0} = 0.368$$


or $\frac{V}{V_0} = 36.8\%$

discharge

if: $V = V_0 e^{-\infty}$

$$= V_0 \cdot \frac{1}{e^{\infty}} = \frac{V_0}{\infty}$$

$$= V_0 \cdot \frac{1}{\infty}$$

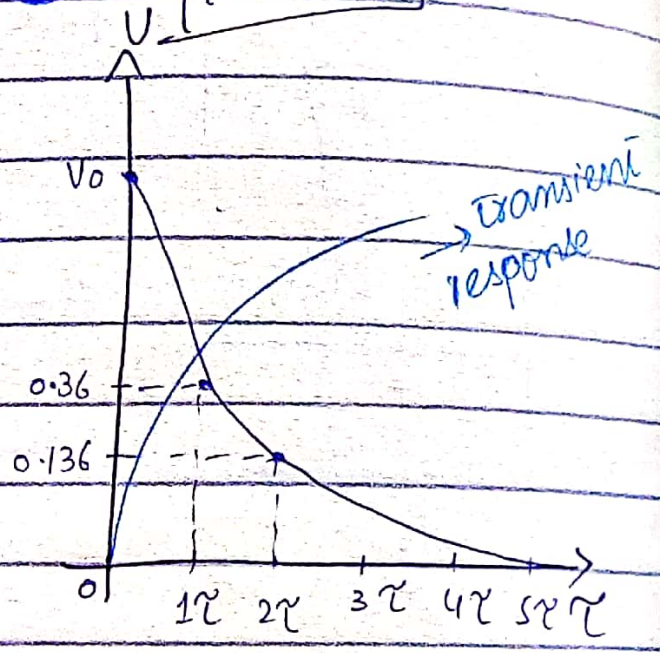

When $t = 2\tau$:

$$V = V_0 e^{-2}$$

$$V = V_0(0.136)$$

$$\frac{V}{V_0} = 13.6\%$$

When $t = 3\tau$:

$$V = V_0 e^{-3}$$

$$\frac{V}{V_0} = 0.049$$

$V = 0$ at $t = \infty$
 \hookrightarrow V starts from V_0 & decreases to zero. $t = \infty$

Current :-

$$i_R(t) = \frac{V}{R}$$

$$i_R(t) = \frac{V_0 e^{-t/\tau}}{R}$$

Power :-

$$P = I^2 R = V^2 / 4$$

$$\text{if: } P = I^2 \cdot R$$

$$= \left[\frac{V_0 e^{-t/\tau}}{R} \right]^2 \cdot R$$

$$P = \frac{V_0^2 e^{-2t/\tau} \cdot R}{R^2}$$

$$P = \frac{V_0^2 e^{-2t/\tau}}{R}$$

Energy :-

$$P = dw/dt$$

$$W = \int_0^t P \cdot dt$$

$$\tau = RC$$

$$W = \int_0^t \frac{V_0^2}{R} \cdot e^{-2t/RC} dt$$

$$W = \frac{V_0^2}{R} \cdot \left(\frac{e^{-2t/RC}}{-2/RC} \right) \Big|_0^t$$

$$W = \frac{1}{2} \cdot C V_0^2 e^{-2t/RC}$$

$$W = \frac{V_0^2}{R} \left[\frac{-RC}{2} \right] \cdot \left[e^{-2t/RC} - e^0 \right]$$



$$W = -\frac{1}{2} C V_0^2 \left[e^{-2t/RC} - 1 \right]$$

$$W = \frac{1}{2} C V_0^2 \left[1 - e^{-2t/RC} \right]$$

steady-state response.

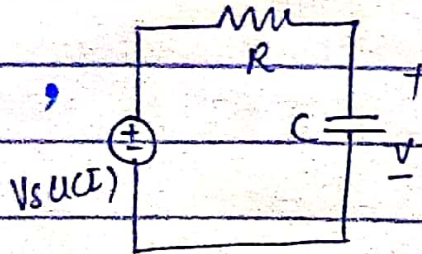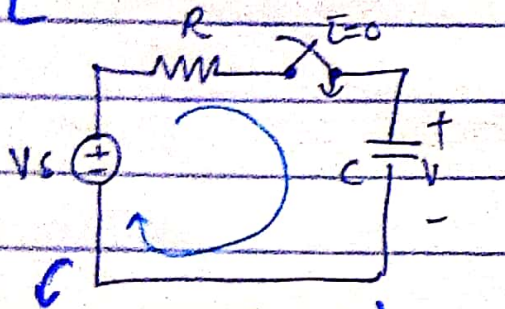7.5 Step-response of an RC ckt :- / RC-Transient response / temporary response / steady-state response

$$\left[\text{complete response} = \text{transient response} + \text{steady-state response} \right]$$



→ KVL :- (voltage)

Method #1

$$V_s = V_R + V_c$$

$$V_s - V_c = iR$$

$$V_s - V_c = C \frac{dV_c}{dt} \cdot R$$

rearrange :-

$$\int \frac{dt}{RC} = \int \frac{dV_c}{V_s - V_c}$$

$$\int \frac{1}{RC} dt = \int \frac{1}{V_s - V_c} dV_c \Rightarrow \frac{1}{RC} \int 1 \cdot dt = - \int \frac{-1}{V_s - V_c} dV_c \Rightarrow -\ln(V_s - V_c) = \frac{t}{RC} + K$$

$$-\frac{t}{RC} + K = \ln(V_s - V_c)$$

$$\left[\begin{array}{l} \text{at } t=0 :- V_c=0 \\ \ln(V_s - 0) = 0 + K \\ \ln V_s = K \end{array} \right]$$

So, $\ln(V_s - V_c) = -\frac{t}{RC} + \ln V_s$

$$\ln\left(\frac{V_s - V_c}{V_s}\right) = -\frac{t}{RC}$$

$$\text{So, } \frac{V_s - V_c}{V_s} = e^{-t/RC}$$

$$V_s - V_c = V_s e^{-t/RC}$$

$$-V_c = -V_s + V_s e^{-t/RC}$$

$$\text{or } V_c = V_s - V_s e^{-t/RC}$$

$\therefore e^{-t/RC} = \text{decay}$

$$V_c = V_s (1 - e^{-t/RC})$$

when $t=0$:-

$$\therefore e^0 = 1$$

$$V_c = V_s (1 - e^0)$$

$$V_c = V_s (1 - 1)$$

$$V_c = 0$$

$$\therefore \tau = RC$$

when $t = \tau = RC$:-

$$V_c = V_s (1 - e^{-1})$$

$$\frac{V_c}{V_s} = 0.6321 = 63\% \text{ charge}$$

when $t = 2\tau$:-

$$V_c = V_s (1 - e^{-2})$$

$$\frac{V_c}{V_s} = 0.8646 \text{ charge}$$

→ current:-

$$i = C \frac{dV}{dt}$$

$$i = C \cdot \frac{d}{dt} (V_s (1 - e^{-t/RC}))$$

$$i = C \cdot V_s \left(0 + e^{-t/RC} \cdot \frac{1}{RC} \right)$$

$$i = \frac{V_s}{R} e^{-t/RC}$$

Method #2:- (Step-response of RC ckt)


KVL:-

$$V_s = V_R + V_C$$

$$V_s = iR + \frac{q}{C}$$

$$\because q = CV$$

$$\frac{q}{C} = V$$

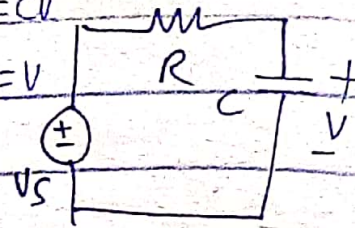

$$V_s = \frac{dq}{dt} \cdot R + \frac{q}{C} \Rightarrow CV_s = RC \frac{dq}{dt} + q$$

re-arrange:-

$$CV_s - q = RC \frac{dq}{dt}$$

multiply by -1:-

$$-RC \frac{dq}{dt} = q - CV_s$$

$$\because \text{at } t=0; q=0$$

$$\frac{dq}{q - CV_s} = -\frac{1}{RC} dt$$

$$\frac{q - CV_s}{CV_s} = -e^{-t/RC}$$

integrate:-

$$\int_0^q \frac{dq}{q - CV_s} = -\frac{1}{RC} \int_0^t dt$$

$$\frac{q}{CV_s} - 1 = -e^{-t/RC}$$

$$\frac{q}{CV_s} = 1 - e^{-t/RC}$$

$$\ln(q - CV_s) \Big|_0^q = -\frac{1}{RC} \Big|_0^t$$

$$q = CV_s (1 - e^{-t/RC})$$

$$\because \frac{q}{C} = V$$

$$[\ln(q - CV_s) - \ln(0 - CV_s)] = \frac{-t}{RC}$$

or $\because \frac{q}{C} = V$

$$V_C = V_s (1 - e^{-t/RC})$$

$$\ln\left(\frac{q - CV_s}{-CV_s}\right) = \frac{-t}{RC}$$

or $\frac{q - CV_s}{-CV_s} = e^{-t/RC}$

$$\frac{q - CV_s}{CV_s} = -e^{-t/RC}$$

current in capacitor:-

$$i_c = C \frac{dv}{dt}$$

$$i_c = C \frac{d}{dt} (V_s (1 - e^{-t/RC}))$$

$$i_c = \frac{V_s}{R} \cdot e^{-t/RC} \rightarrow \text{current decays.}$$

voltage across 'R':-

$$V_R = iR$$

$$V_R = \frac{V_s \cdot e^{-t/RC} \cdot R}{R}$$

$$V_R = V_s e^{-t/RC} \rightarrow V \text{ across } R \text{ decreases.}$$

$\& \text{ across } C \text{ increase}$

$$P = VI$$

Energy:-

$$W = \int_0^t P dt$$

$$W = \int_0^t i^2 R dt$$

$$W = \int_0^t \left(\frac{V_s \cdot e^{-t/RC}}{R} \right)^2 \cdot R dt$$

$$W = \int_0^t \left(\frac{V_s^2}{R^2} \cdot e^{-2t/RC} \cdot R \right) dt$$

$$\frac{V_s^2}{R} \cdot \frac{-t}{RC} \Rightarrow \frac{V_s^2 \cdot RC}{R \cdot -t}$$

$$W = \frac{V_s^2}{R} \int_0^t e^{-2t/RC} dt$$

$$W = \frac{-V_s^2}{R} \cdot e^{-2t/RC} \Big|_0^t$$

derivative of $-2t \leftarrow \frac{d}{dt} \left(\frac{-2t}{-2} \right) = \frac{1}{-2/RC} \Big|_0$

$$W = \frac{-V_s^2 C}{2} (e^{-2t/RC} - 1)$$

x by -1:-

$$W = \frac{1}{2} C V_s^2 (e^{-2t/RC} + 1)$$

Source-Free RL-circuit:-

at initial time $t=0$ inductor is charged. (by giving source and then

at $t=0$; $i(t) = I_0$ (take source away)

$$\Rightarrow i(0) = I_0$$

i) initial condition

ii) Time const. (T.C) = $\tau = L/R$

$$w(0) = \frac{1}{2} L I_0^2$$

KVL at ckt:-

algebraic sum of all voltages in closed loop = 0

$$\text{So, } V_L + V_R = 0$$

$$L \frac{di}{dt} + iR = 0$$

To remove L (co-efficient) :- (\div by L)


$$\frac{di}{dt} + \frac{iR}{L} = 0$$

$$\frac{di}{dt} = -\frac{iR}{L}$$

Integrate-arrange :-

$$\int \frac{1}{i} di = - \int \frac{R}{L} dt$$

$$\ln i \Big|_0^{i(t)} = - \frac{Rt}{L} \Big|_0^t$$

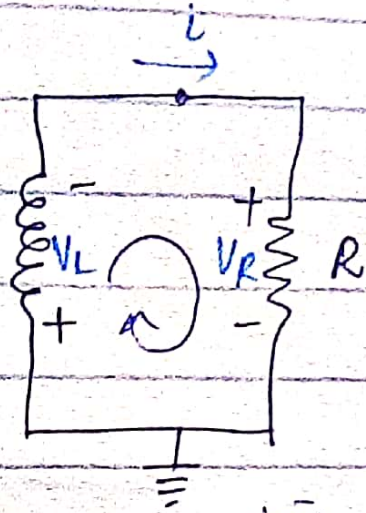

$i(0^-)$ \rightarrow before switching

$i(0^+)$ \rightarrow after switching

$i(0)$ \rightarrow switching

$$\ln i(t) - \ln i(0) = -\frac{R}{L}(t-0)$$

initial condition

$$\ln i(t) - \ln I_0 = -\frac{Rt}{L} \quad \because i(0) = I_0$$

at $t = 0$

$$\ln \frac{i(t)}{I_0} = -\frac{Rt}{L}$$

taking e both sides

$$\frac{i(t)}{I_0} = e^{-Rt/L}$$

$$i(t) = I_0 e^{-Rt/L}$$

$$\text{or } i(t) = I_0 e^{-\frac{R}{L}t}$$

max. vol. across R...

$$\tau = \frac{L}{R}$$

$$\frac{1}{\tau} = \frac{R}{L}$$

So, $i(t) = I_0 e^{-t/\tau}$

at $t=0$:-


$$i(0) = I_0 e^0 = I_0$$

$$\text{at } t = \tau: i(\tau) = I_0 e^{-1} = I_0 \cdot 0.368$$

$$\text{at } t = 2\tau: i(2\tau) = I_0 e^{-2} = I_0 \cdot 0.1358$$

$$\text{at } t = \infty: i(\infty) = I_0 e^{-\infty} = I_0 \cdot \frac{1}{\infty}$$

$\neq 0$

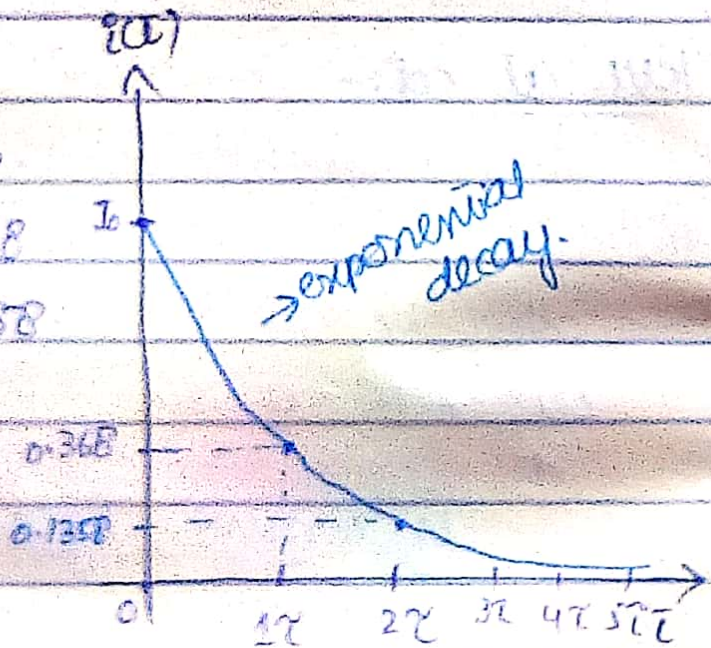

Transient state

Voltage across R (V_R):-

$$V_R = iR$$

$$\text{So, } V_R = R(I_0 e^{-t/\tau})$$

$$V_R = I_0 R e^{-t/\tau}$$

Power:-

$$P_R = i v_R$$

$$P_R = (I_0 e^{-t/\tau}) (I_0 R e^{-t/\tau})$$

$$P_R = I_0^2 R e^{-2t/\tau}$$

Energy:-

$$W = \int_0^t P dt$$

So,

$$W = \int_0^t I_0^2 R e^{-2t \cdot \frac{R}{L}} dt$$

$$W = I_0^2 R \int_0^t e^{-2t \cdot R/L} dt$$

$$= I_0^2 R \left| \frac{e^{-2t \cdot R/L}}{-2R/L} \right|_0^t$$

$$= -\frac{1}{2} L I_0^2 \left(e^{-2tR/L} - 1 \right) \quad \because e^0 = 1$$

x by -1.

$$= \frac{1}{2} L I_0^2 (1 - e^{-2t/\tau})$$

$$\because \tau = L/R$$

$$\frac{1}{\tau} = R/L$$

at $t=0$ $W = \frac{1}{2} L I_0^2 (1 - e^0)$

$$W(0) = 0$$

at $t=\infty$ $W(\infty) = \frac{1}{2} L I_0^2 (1 - e^0)$

So,

$$W(\infty) = \frac{1}{2} L I_0^2$$

→ (last para from book)


inductors & capacitor don't dissipate power, only resistor dissipate power.

7.6 Step-response of RL-cct. steady state.


→ RL with source :- $i_{total} = \left\{ \begin{array}{l} \text{discharge} \\ i_{trans.} + i_{steady} \\ \text{charge} \end{array} \right\}$

at $t=0$; $i(0)=0$ $t < 0 / i(0^-)$

before switching

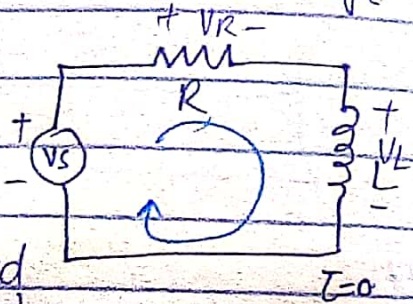

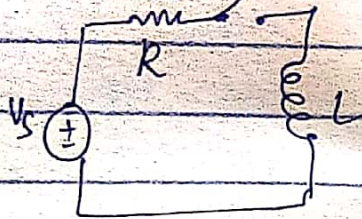at $i(0^+)$ → after switching (closed cct.)



KVL :-

$$V_s = V_R + V_L$$

$$V_s - V_R - V_L = 0$$

$$\text{or } V_s - iR = L \frac{di}{dt}$$

÷ by R on both sides :-

$$\frac{V_s}{R} - i = L \frac{di}{dt}$$

re-arrange :-

$$\left(\frac{V_s}{R} - i \right) dt = L di$$

$$\int_0^t \frac{R di}{L} = \int_0^t \frac{V_s - iR}{L} dt$$

$$\because \frac{V_s}{R} = \text{const} = 0$$

$$(t=0) \left[\frac{R \cdot i}{L} \right]_0^t = - \ln \left(\frac{V_s - i}{R} \right) \Big|_0^t$$

$$\Rightarrow - \frac{R \cdot i}{L} = \left[+ \ln \left(\frac{V_s - i(t)}{R} \right) - \ln \left(\frac{V_s - 0}{R} \right) \right]$$

$$\text{or } \ln \left(\frac{V_s - i(t)}{R} \right) = - \frac{R \cdot i}{L}$$

or take e both sides.

$$\frac{\left(\frac{V_s}{R} - i(\bar{t})\right)}{V_s/R} = e^{-\frac{R}{L} \cdot \bar{t}}$$

$$\therefore \tau = L/R$$

$$\frac{1}{\tau} = R/L$$

$$\frac{V_s}{R} - i(\bar{t}) = \frac{V_s}{R} \cdot e^{-\bar{t}/\tau}$$

$$-i(\bar{t}) = -\frac{V_s}{R} + \frac{V_s}{R} (e^{-\bar{t}/\tau})$$

x by -1

$$i(\bar{t}) = \frac{V_s}{R} - \frac{V_s}{R} (e^{-\bar{t}/\tau})$$

$$i(\bar{t}) = \frac{V_s}{R} (1 - e^{-\bar{t}/\tau})$$


Analysis:

at $t=0$: $i(0) = \frac{V_s}{R} (1 - e^0) = 0$

at $t=\tau$: $i(1) = \frac{V_s}{R} (1 - e^{-1}) = \frac{V_s}{R} \cdot 0.63$

at $t=2\tau$: $i(2) = \frac{V_s}{R} (1 - e^{-2}) = \frac{V_s}{R} (0.86)$

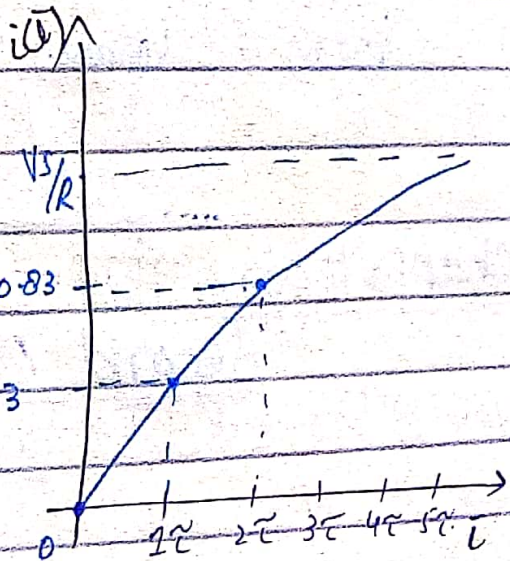at $t=\infty$: $i(\infty) = \frac{V_s}{R} (1 - e^{-\infty}) = \frac{V_s}{R} (\text{max})$



→ max. voltage across L.

V_R:-

$$V_R = iR$$

$$V_R = \frac{V_s}{R} (1 - e^{-\bar{t}/\tau}) \cdot R$$

$$V_R = V_s (1 - e^{-\bar{t}/\tau})$$

V_L :-

$$V_L = L \frac{di}{dt}$$

$$\tau = \frac{L}{R}$$

$$V_L = L \left[\frac{d}{dt} \left(\frac{V_s}{R} (1 - e^{-t/\tau}) \right) \right]$$

$$V_L = \frac{V_s \cdot L}{R} \left[-e^{-t/\tau} \right] \cdot \frac{d}{dt} \left(-\frac{Rt}{L} \right)$$

$$V_L = \frac{V_s}{R} \cdot \left[\ominus e^{-\frac{Rt}{L}} \right] \cdot \ominus \frac{R}{L}$$

$$V_L = V_s e^{-\frac{Rt}{L}}$$

or

$$V_L = V_s e^{-t/\tau}$$

So,

$$i(\text{total}) = i(\text{trans.}) + i(\text{steady})$$

$$i(\text{total}) = \left(I_0 e^{-t/\tau} \right) + \left(\frac{V_s}{R} (1 - e^{-t/\tau}) \right)$$