

Chapter # 09:

①

Sinusoids and Phasors

{ Examples and Practice Problems }

Example # 9.1:-

find amplitude, phase, period & frequency of sinusoid: $v(t) = 12 \cos(50t + 10^\circ)$

$$v(t) = 12 \cos(50t + 10^\circ) = V_m \angle \theta$$

So; $V_m = \text{amplitude} = 12$. $\therefore \omega = 50$

$$\theta = \text{phase} = 10^\circ$$

$$T = \text{period} = \frac{2\pi}{\omega}$$

$$T = \frac{2 \times 3.14}{50} = 0.12565$$

$$f = \frac{1}{T} = \frac{1}{0.1256} = 7.958 \text{ Hz}$$

Practice Problem 9.1:-

find amplitude, phase, angular frequency, period and frequency of: $v(t) = 30 \sin(4\pi t - 75^\circ)$

$$v(t) = 30 \sin(4\pi t - 75^\circ)$$

$$V_m = 30$$

$$\theta = -75^\circ$$

$$\omega = 4\pi = 12.56 \text{ rad/s}$$

$$T = \frac{2 \times 3.14}{12.56} = 0.5 \text{ s}$$

$$f = \frac{1}{T} = \frac{1}{0.5} = 2 \text{ Hz}$$

Example # 9.2:-

②

Calculate phase angle between V_1 & V_2 state which sinusoid is leading.

$$V_1 = -10 \cos(\omega t + 50^\circ)$$

$$V_2 = 12 \sin(\omega t - 10^\circ)$$

$$V_1 = -10 \cos(\omega t + 50^\circ) = 10 \cos(\omega t + 50 + 180^\circ)$$

$$\text{So, } V_1 = 10 \cos(\omega t + 230^\circ) \text{ or } V_1 = 10 \cos(\omega t - 130^\circ) \text{---(1)}$$

$$V_2 = 12 \cos(\omega t - 10^\circ - 90^\circ)$$

$$V_2 = 12 \cos(\omega t - 100^\circ) \text{---(2)}$$

from (1) & (2); we can see phase difference is 30° - we can write V_2 as:

$$V_2 = 12 \cos(\omega t - 130^\circ + 30^\circ) \text{ or } V_2 = 12 \cos(\omega t + 260^\circ) \text{---(3)}$$

comparing (1) & (3); we can say that V_2 is leading V_1 by 30° .

Practice problem # 9.2::


Find phase angle between $i_1 = 4 \sin(377t + 55^\circ)$ and $i_2 = 5 \cos(377t - 65^\circ)$ - which leads or lags?

$$i_1 = -4 \sin(377t + 55^\circ) = 4 \cos(377t + 55 + 90^\circ)$$

$$i_1 = 4 \cos(377t + 145^\circ) \text{---(1)}$$

$$i_2 = 5 \cos(377t - 65^\circ) \text{---(2)}$$

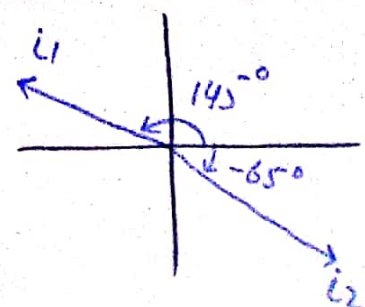comparing (1) & (2); we can say i_1 leads i_2 .



Example #9.3:-

Evaluate these complex numbers.

$$i) (40 \angle 50^\circ + 20 \angle -30^\circ)^{1/2}$$

$$= \sqrt{(40 \angle 50^\circ + 20 \angle -30^\circ)}$$

$$40 \angle 50^\circ = 40 [\cos 50^\circ + j \sin 50^\circ] = 25.71 + j30.64$$

$$20 \angle -30^\circ = 20 [\cos(-30^\circ) + j \sin(-30^\circ)] = 17.32 - j10.$$

Then adding:-

$$(25.71 + j30.64) + (17.32 - j10) = 43.02 + 20.64j$$

$$r = \sqrt{(43.02)^2 + (20.64)^2} \quad ; \quad \theta = \tan^{-1} \left(\frac{20.64}{43.02} \right)$$

$$r = \sqrt{2276.72} \quad ; \quad \theta = \tan^{-1} (0.479)$$

$$\boxed{r = 47.71}$$

$$\boxed{\theta = 25.63^\circ}$$

$$\begin{aligned} \rightarrow &= (47.71 \angle 25.63^\circ)^{1/2} \\ &= \sqrt{47.71} \angle 25.63/2 \\ &= \boxed{6.91 \angle 12.81^\circ} \text{ Ans.} \end{aligned}$$

$$ii) \frac{(10 \angle -30^\circ) + (3 - j4)}{(2 + j4)(3 - j5)^*}$$

$$= \frac{(8.66 - j5) + (3 - j4)}{(2 + j4)(3 + j5)}$$

$$= \frac{11.66 - j9}{-4 + j22} = \frac{14.73 \angle -37.66^\circ}{26.08 \angle 122.47^\circ}$$

$$= \boxed{0.565 \angle -160.13^\circ} \text{ Ans.}$$

Practice Problem # 9.3:-

Evaluate following complex numbers.

a) $[(5+j2)(-1+j4) - 5\angle 60^\circ]^*$

= $[(5+j2)(-1+j4) - (2.5 + j4.3)]^*$

= $[(-13+18j) - (2.5+j4.3)]^*$

= $[-15.5 + j13.7]^*$

= $\boxed{-15.5 - j13.7}$

b) $\frac{10 + j5 + 3\angle 40^\circ}{-3 + j4} + 10\angle 30^\circ + j5$

= $\frac{(10 + j5) + (2.29 + 1.9j)}{-3 + j4} + (8.66 + 5j) + j5$

= $(-0.37 - 2.79j) + (8.66 + j10)$

= $\boxed{0.28 + 7.2j}$

Example # 9.4:- Transform to phasors

a) $i = 6\cos(50t - 40^\circ) A$

$i = 6\cos(50t - 40^\circ) = \text{Im} \angle \theta$

$\boxed{i = 6\angle -40^\circ A}$

b) $v = -4\sin(30t + 50^\circ) V$

$v = -4\sin(30t + 50^\circ) = 4\cos(30t + 50^\circ + 90^\circ)$

$v = 4\cos(30t + 140^\circ) = \boxed{4\angle 140^\circ V}$

Practice Problem #9.4:-

5

Express sinusoids as phasors.

a) $v = 7 \cos(2t + 40^\circ) \text{ V}$

$$v = 7 \cos(2t + 40^\circ) = V_m \angle \theta$$

$$\boxed{V = 7 \angle 40^\circ \text{ V}}$$

b) $i = -4 \sin(10t + 10^\circ) \text{ A}$

$$i = 4 \cos(10t + 90^\circ + 10^\circ)$$

$$i = 4 \cos(10t + 100^\circ)$$

$$\boxed{I = 4 \angle 100^\circ}$$

Example #9.5:-

Find sinusoids from phasors.

a) $I = (-3 + j4) \text{ A}$

$$r = \sqrt{(-3)^2 + (4)^2} \quad ; \quad \theta = \tan^{-1}(4/-3)$$

$$r = \sqrt{25} = 5 \quad ; \quad \theta = -53.13^\circ$$

So, $\boxed{i(t) = 5 \cos(\omega t - 53.13^\circ)}$

b) $V = j8e^{-j20^\circ} \text{ V}$

since: $j = 1 \angle 90^\circ$

$$V = j8 \angle -20^\circ$$

$$= (1 \angle 90^\circ)(8 \angle -20^\circ)$$

$$= 8 \angle 90^\circ - 20^\circ$$

$$v(t) = 8 \angle 70^\circ$$

So, $\boxed{v(t) = 8 \cos(\omega t + 70^\circ) \text{ V}}$

Practice Problem #9.5:

find sinusoids from phasors.

a) $V = -10 \angle 30^\circ \text{ V}$

$$v(t) = -10 \cos(\omega t + 30^\circ) = 10 \cos(\omega t + 30^\circ + 180^\circ)$$

$$\boxed{v(t) = 10 \cos(\omega t + 210^\circ) \text{ V}}$$

b) $I = j(5 - 12j) \text{ A}$

$$I = 5j - 12j^2$$

$$I = 5j - 12(-1)$$

$$I = 12 + 5j$$

or: $r = \sqrt{(12)^2 + (5)^2}$; $\theta = \tan^{-1}(5/12)$

$$r = 13 \quad \theta = 67.3^\circ$$

$$\boxed{i(t) = 13 \cos(\omega t + 67.3^\circ) \text{ A}} \quad \text{Ans:}$$

Example #9.6:-

given: $i_1 = 4 \cos(\omega t + 30^\circ) \text{ A}$

$i_2 = 5 \sin(\omega t - 20^\circ) \text{ A}$; find sum.

$$i_1 = 4 \cos(\omega t + 30^\circ) = 4 \angle 30^\circ$$

$$i_2 = 5 \sin(\omega t - 20^\circ) = 5 \sin$$

$$= 5 \cos(\omega t - 110^\circ) = 5 \angle -110^\circ$$

$$i_1 = 4 [\cos 30^\circ + j \sin 30^\circ] = 3.46 + 2j$$

$$i_2 = 5 [\cos(-110^\circ) + j \sin(-110^\circ)] = -1.71 - 4.698j$$

$$i = i_1 + i_2 = (3.46 + 2j) + (-1.71 - 4.698j)$$

$$= 1.75 - 2.698j$$

or $\boxed{i = 3.218 \angle -57.03^\circ \text{ A}} \quad \text{Ans:}$

Practice Problem # 9.6:-

7

$$\text{If: } v_2 = +20 \cos(\omega t + 45^\circ)$$

$$v_1 = -10 \sin(\omega t - 30^\circ); \text{ find sum.}$$

$$v_1 = -10 \sin(\omega t - 30^\circ) = 10 \cos(\omega t + 60^\circ)$$

$$v_1 = 10 \angle 60^\circ$$

$$v_2 = 20 \cos(\omega t + 45^\circ) = 20 \angle 45^\circ$$

$$v = v_1 + v_2 = (10 \angle 60^\circ) + (20 \angle 45^\circ)$$

$$= 10[\cos 60^\circ + j \sin 60^\circ] + 20[\cos 45^\circ + j \sin 45^\circ]$$

$$= (5 + j8.66) + (14.14 + j14.14)$$

$$v = 19.14 + j22.8$$

$$\text{or } v = 29.77 \angle 49.98^\circ$$

$$\boxed{v(t) = 29.77 \cos(\omega t + 49.98^\circ) \text{ V}} \quad \text{Ans:}$$

Example # 9.7:-

Using phasor approach; find $i(t)$:

$$4i + 8 \int i dt - 3 \frac{di}{dt} = 50 \cos(2t + 75^\circ)$$

Here; $\omega = 2$

Transforming in phasors:-

$$4I + 8 \cdot \frac{I}{j\omega} - 3Ij\omega = 50 \angle 75^\circ$$

$$4I + 8 \cdot \frac{I}{j(2)} - 3Ij \times 2 = 50 \angle 75^\circ$$

$$4I + \frac{4I}{j} - 6jI = 50 \angle 75^\circ$$

$$4I + j\frac{4I}{j^2} - 6jI = 50 \angle 75^\circ$$

$$4I - j4I - 6jI = 50 \angle 75^\circ$$

$$4I - 10jI = 50 \angle 75^\circ$$

$$I = \frac{50 \angle 75^\circ}{(4 - j10)}$$

$$I = \frac{50 \angle 75^\circ}{10.77 \angle -68.2^\circ}$$

$$I = 4.64 \angle 143.2^\circ \text{ A}$$

or $i(t) = 4.64 \cos(2t + 143.2^\circ) \text{ A}$ Ans:

Practice Problem # 9.7:-

find $v(t) = ?$

$$2 \frac{dv}{dt} + 5v + 10 \int v dt = 50 \cos(5t - 30^\circ)$$

$\therefore \omega = 5$

$$2 \cdot j\omega V + 5V + 10 \cdot \frac{V}{j\omega} = 50 \angle -30^\circ$$

$$2j(5)V + 5V + 10 \frac{V}{j \times 5} = 50 \angle -30^\circ$$

$$10jV + 5V + \frac{10V}{8j} = 50 \angle -30^\circ$$

$$8jV + 5V = 50 \angle -30^\circ$$

$$V = \frac{50 \angle -30^\circ}{5 + j8}$$

$$V = \frac{50 \angle -30^\circ}{9.43 \angle 57.9^\circ}$$

$$V = 5.302 \angle -87.9^\circ$$

or $v(t) = 5.302 \cos(5t - 87.9^\circ) \text{ V}$ Ans:

Example # 9.8:-


Voltage $v = 12 \cos(60t + 45^\circ)$ is applied to 0.1 H inductor. Find steady state current through inductor.

$$V = L \frac{di}{dt} \Rightarrow V_m = L j \omega I$$

$$I = \frac{V}{j \omega L}$$

$$V = 12 \cos(60t + 45^\circ) = 12 \angle 45^\circ$$
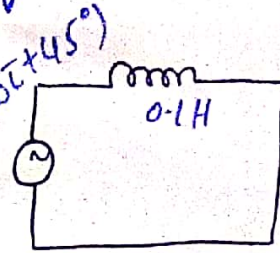
$$I = \frac{12 \angle 45^\circ}{(1 \angle 90^\circ)(60)(0.1)}$$



$$\because \omega = 60$$

$$\because j = 1 \angle 90^\circ$$

$$I = \frac{12 \angle 45^\circ}{1 \angle 90^\circ \times 0.6}$$

$$I = 2 \angle -45^\circ \text{ A}$$


or $i(t) = 2 \cos(60t - 45^\circ) \text{ A}$ Ans:

Practice Problem # 9.8:-

if voltage $v = 10 \cos(100t + 30^\circ)$ is applied to $50 \mu\text{F}$ capacitor - calculate $i(t)$.

$$V = 10 \cos(100t + 30^\circ) = 10 \angle 30^\circ$$
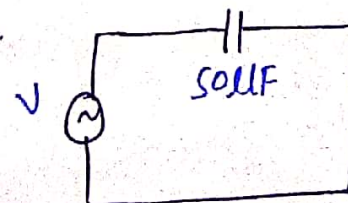
$$\omega = 100 ; C = 50 \times 10^{-6} \text{ F}$$



$$I = C j \omega V$$

$$I = (50 \times 10^{-6})(1 \angle 90^\circ)(100)(10 \angle 30^\circ)$$

$$I = (50 \times 10^{-6})(100)(10 \angle 120^\circ)$$

$$I = 50 \angle 120^\circ \text{ mA}$$

or $i(t) = 50 \cos(100t + 120^\circ) \text{ mA}$ Ans:

Example # 9.9:-

(10)


find $v_C(t)$ and $i_C(t)$ in circuit.

$$V_s = 10 \cos 4t \text{ V} = 10 \angle 0^\circ \text{ V}$$

impedance is:

$$Z = 5 + \frac{1}{j\omega C} = 5 + \frac{1}{j4 \times 0.1}$$

$$\boxed{Z = 5 - j2.5 \Omega}$$

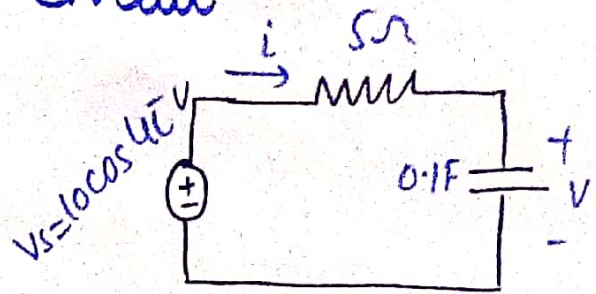

So, current \bar{i} ;

$$\bar{I} = \frac{V_s}{Z} = \frac{10 \angle 0^\circ}{(5 - j2.5)} = \frac{10(5 + j2.5)}{5^2 + 2.5^2}$$

$$\bar{I} = 1.6 + j0.8$$

or $\boxed{\bar{I} = 1.789 \angle 26.57^\circ \text{ A}}$

voltage across capacitor is:-

$$V = \bar{I} Z_C = \frac{\bar{I}}{j\omega C}$$

$$V = \frac{1.789 \angle 26.57^\circ}{j4 \times 0.1}$$

$$\because j = 1 \angle 90^\circ$$

$$V = \frac{1.789 \angle 26.57^\circ}{0.4 \angle 90^\circ}$$

$$\boxed{V = 4.47 \angle -63.43^\circ \text{ V}}$$

or

$$i_C(t) = 1.789 \cos(4t + 26.57^\circ) \text{ A}$$


$$v_C(t) = 4.47 \cos(4t - 63.43^\circ) \text{ V}$$

Practice Problem #9.9:-

Determine $v(t)$ and $i(t)$;

$$V_s = 20 \sin(10t + 30^\circ) \text{ V}$$
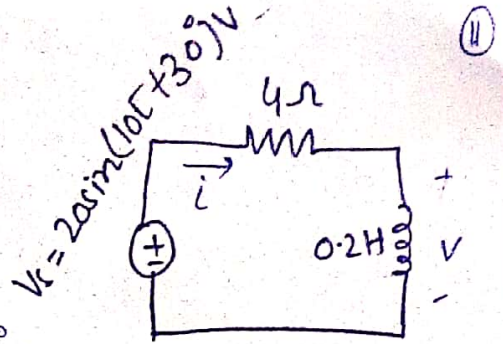
$$V_s = 20 \cos(10t - 60^\circ) \text{ V} = 20 \angle -60^\circ$$



$$i) \quad I = \frac{V_s}{Z} = ?$$

$$Z = R + j\omega L = 4 + j(10)(0.2)$$

$$Z = 4 + j2$$

$$\text{So, } I = \frac{20 \angle -60^\circ}{4 + j2} = \frac{20 \angle -60^\circ}{4.47 \angle 26.56^\circ}$$

$$I = 4.47 \angle -86.56^\circ \text{ A}$$

$$i(t) = 4.47 \cos(10t - 86.56^\circ) \text{ A}$$

$$ii) \quad V_L = I Z_L = I \times j\omega L \quad \because j = 1 \angle 90^\circ$$

$$V_L = (4.47 \angle -86.56^\circ) j(10)(0.2)$$

$$V_L = (4.47 \angle -86.56^\circ) (1 \angle 90^\circ) (2)$$



$$V_L = 8.94 \angle 3.43^\circ$$

$$\text{or } V_L = 8.94 \cos(10t + 3.43^\circ)$$

$$\text{or } V_L = 8.94 \sin(10t + 93.43^\circ) \text{ V}$$

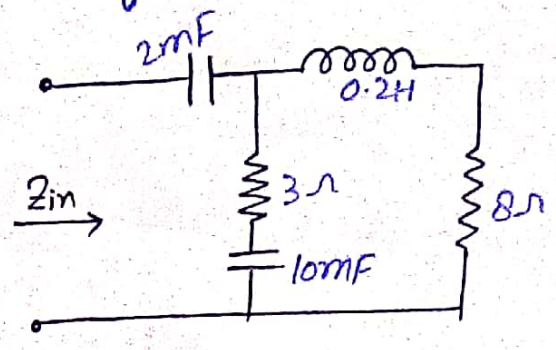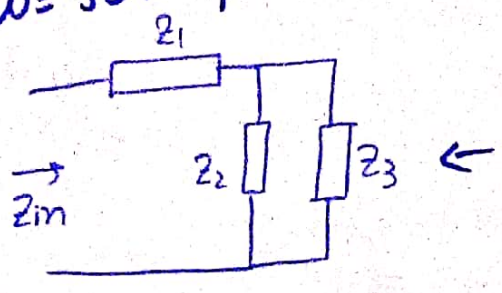Example #9.10:-

Find input impedance of circuit; while $\omega = 50 \text{ rad/s}$.



$$Z_1 = \frac{1}{j\omega C} = \frac{1}{j50 \times 2 \times 10^{-3}} = -j10 \Omega$$

$$Z_2 = 3 + \frac{1}{j\omega C} = 3 + \frac{1}{j50 \times 10 \times 10^{-3}} = (3 - j2) \Omega$$

$$Z_3 = 8 + j\omega L = 8 + j50 \times 0.2 = (8 + j10) \Omega$$

The input impedance is:-

$$Z_{in} = Z_1 + Z_2 \parallel Z_3$$



$$= (-j10) + \frac{(3 - j2)(8 + j10)}{(3 - j2) + (8 + j10)}$$

$$Z_{in} = -j10 + 3.22 - j1.07 \Omega$$

So, $Z_{in} = 3.22 - j11.07 \Omega$ Ans:

Practice Problem #9.10:-

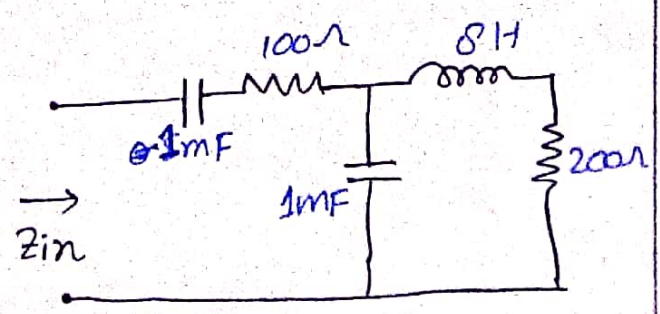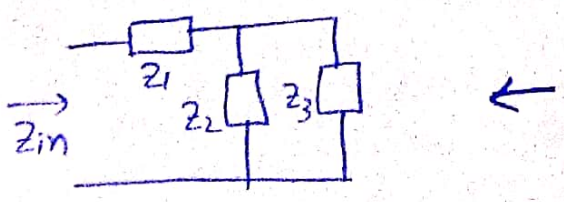$Z_{in} = ?$; $\omega = 10 \text{ rad/s}$.



$$Z_{in} = Z_1 + Z_2 \parallel Z_3$$

$$Z_1 = R + \frac{1}{j\omega C} = 100 + \frac{1}{j(10)(1 \times 10^{-3})}$$

$$Z_1 = 100 - j100 \Omega$$

$$Z_2 = \frac{1}{j\omega c} = \frac{1}{j \times 10 \times 10^{-3}} = -j100 \Omega$$

$$Z_3 = 200 + j(10)(8) = 200 + j80 \Omega$$



So,

$$Z_{in} = (100 - j100) + \frac{(-j100)(200 + j80)}{(-j100) + (200 + j80)}$$

$$Z_{in} = 149.5 - j195 \Omega \text{ Ans:}$$

Example # 9.11:-


Determine $V_o(t)$ in circuit.

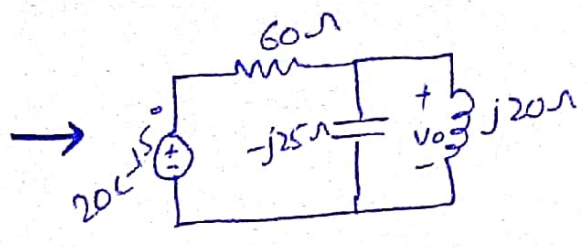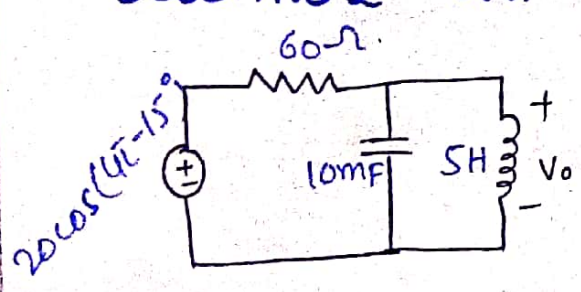

$$V_s = 20 \angle -15^\circ$$

$$10 \text{ mF} \Rightarrow \frac{1}{j\omega c} = \frac{1}{j4 \times 10 \times 10^{-3}} = -j25 \Omega$$
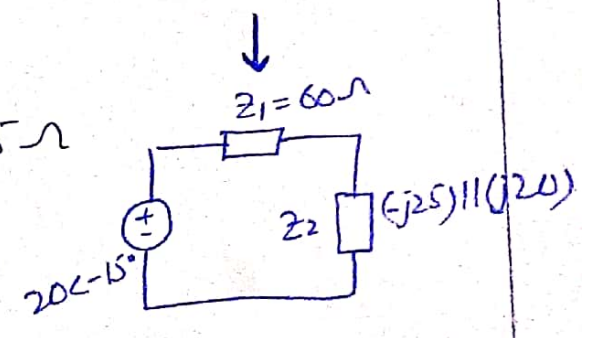
$$5 \text{ H} \Rightarrow j\omega L = j4 \times 5 = j20 \Omega$$



Hence;

$$Z_1 = 60 \Omega$$

$$Z_2 = -j25 \parallel j20 = \frac{-j25 \times j20}{-j25 + j20} = +j100 \Omega$$

So,

$$V_o = \frac{Z_2}{Z_1 + Z_2} V_s = \frac{j100}{60 + j100} \times (20 \angle -15^\circ)$$

$$V_o = (0.8975 \angle 30.96^\circ) (20 \angle -15^\circ)$$


$$V_o = 17.15 \angle 15.96^\circ \text{ V}$$

or converting to time domain:-

$$V_o(t) = 17.15 \cos(4t + 15.96^\circ) \text{ V} \text{ Ans:}$$

Practice Problem # 9.11:


calculate V_o in circuit:

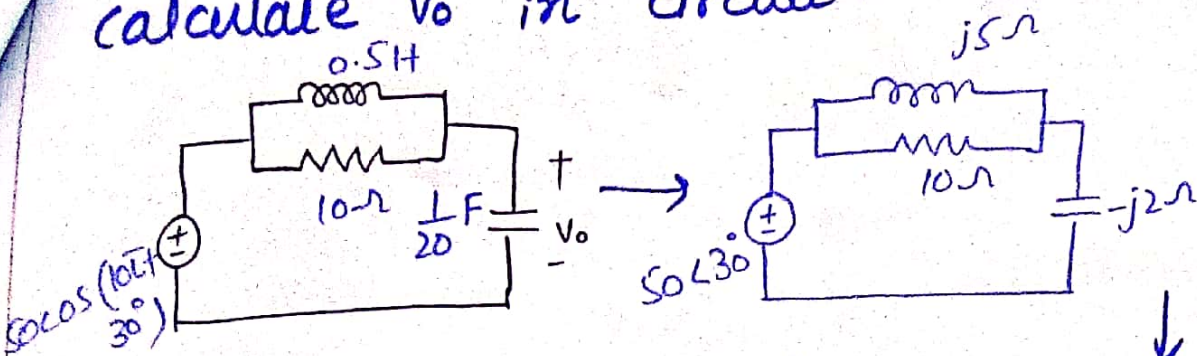

$$V_s = 50 \cos(10t + 30^\circ) = 50 \angle 30^\circ$$

$$0.5H \Rightarrow j\omega L = j10(0.5) = j5 \Omega$$
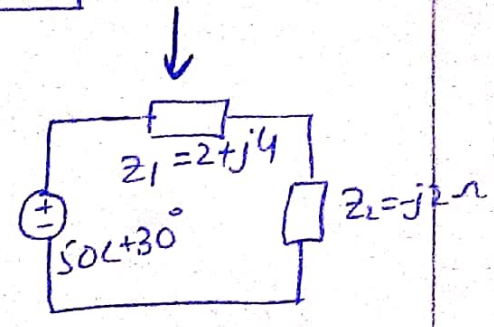
$$\frac{1}{20}F \Rightarrow \frac{1}{j\omega C} = \frac{1}{j10 \times \frac{1}{20}} = -j2 \Omega$$



$$Z_1 = j5 \parallel 10 = \frac{(j5)(10)}{j5 + 10} = 2 + j4$$

So,

$$V_{Z_2} = \frac{Z_2}{Z_1 + Z_2} (V_s)$$

$$Z_1 = 2 + j4 ; Z_2 = -j2$$


$$V_{Z_2} = \frac{-j2}{(2 + j4) + (-j2)} (50 \angle 30^\circ)$$

$$V_{Z_2} = 35.36 \angle -105^\circ$$

or $V_{oc}(t) = 35.36 \cos(10t - 105^\circ) V$ Ans:

Example # 9.12 :-


Find current I in circuit using Δ - Y .

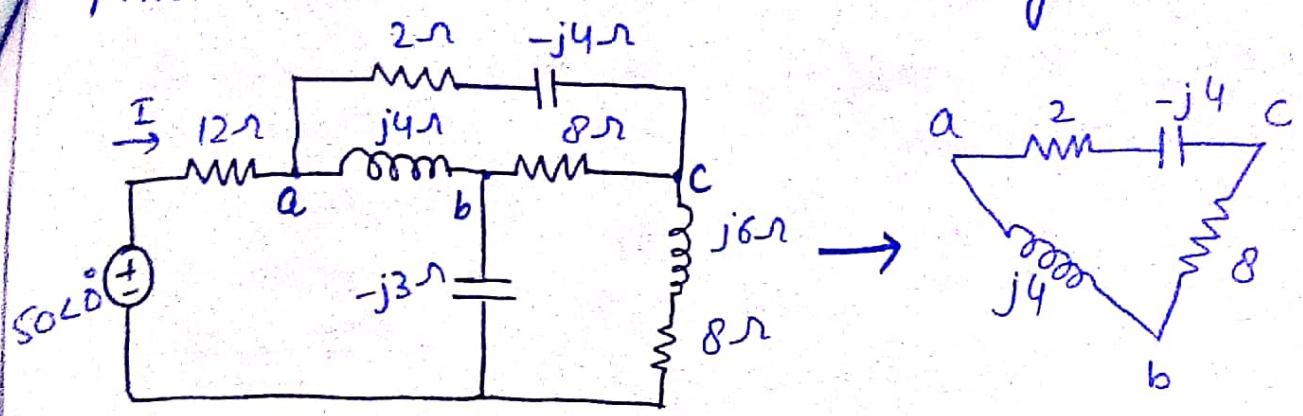

$$Z_{an} = Z_1 = \frac{(j4)(2-j4)}{(j4)+(2-j4)+(8)} = 1.6 + j0.8 \Omega$$

$$Z_{bn} = Z_2 = \frac{(j4)(8)}{(j4)+(2-j4)+(8)} = j3.2 \Omega$$

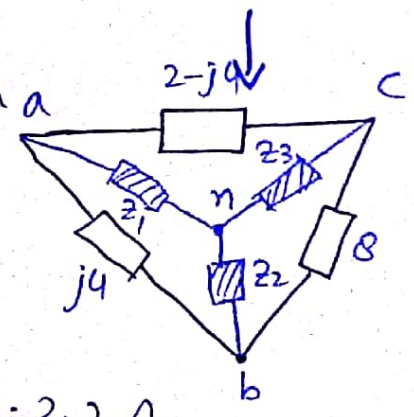
$$Z_{cn} = Z_3 = \frac{(2-j4)(8)}{(2-j4)+(8)+(j4)} = 1.6 - j3.2 \Omega$$



Now, transforming from $\Delta \rightarrow Y$:-

$$Z_{eq} = 12 + Z_1 + (Z_2 || Z_3)$$

$$Z_{eq} = 12 + Z_{an} + [(Z_{bn} - j3) || (Z_{cn} + j6 + 8)]$$

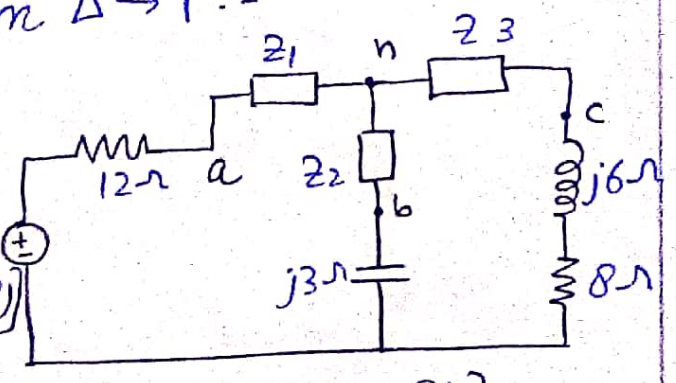

$$Z_{eq} = 12 + (1.6 + j0.8) + [(j3.2 - j3) || (1.6 - j3.2 + j6 + 8)]$$

$$Z_{eq} = (13.6 + j0.8) + \left[\frac{(j0.2)(9.6 + j2.8)}{(j0.2) + (9.6 + j2.8)} \right]$$

$$Z_{eq} = (13.6 + j0.8) + (3.79 + 0.19j) = 13.6 + 0.99j$$


$$Z_{eq} = 13.64 \angle 4.2^\circ \Omega$$

So,
$$I = \frac{V}{Z_{eq}} = \frac{50 \angle 0^\circ}{13.64 \angle 4.2^\circ}$$

$$I = 3.66 \angle -4.2^\circ \text{ A} \quad \text{Ans:}$$

Practice Problem #9.12:-

Find I in circuit:

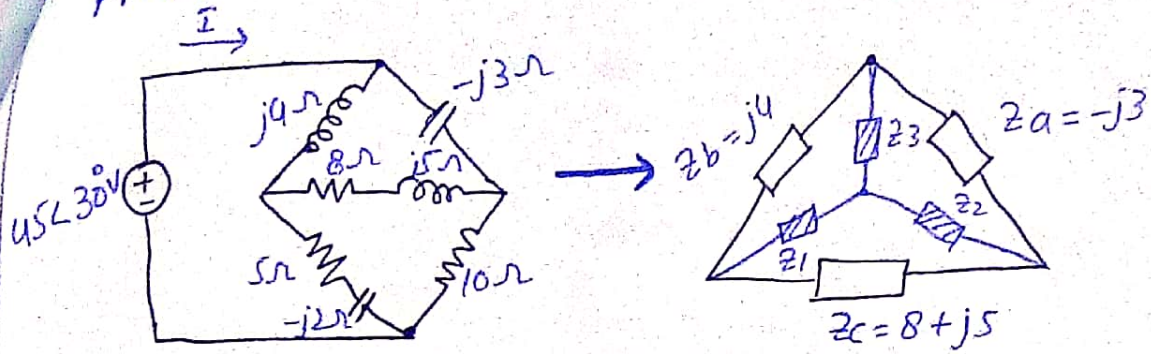

$$Z_1 = \frac{Z_c Z_b}{Z_a + Z_b + Z_c} = \frac{(8 + j5)(j4)}{(j4) + (8 + j5) + (-j3)} = 0.32 + j3.76 \Omega$$

$$Z_2 = \frac{Z_a Z_c}{Z_a + Z_b + Z_c} = \frac{(-j3)(8 + j5)}{(-j3) + (8 + j5) + (j4)} = -0.24 - j2.82 \Omega$$

$$Z_3 = \frac{Z_a Z_b}{Z_a + Z_b + Z_c} = \frac{(-j3)(j4)}{(-j3) + (j4) + (8 + j5)} = 0.96 - j0.72 \Omega$$

Then circuit will be:-

$$x = Z_1 + 5\Omega + (-j2)$$

$$x = (0.32 + j3.76) + 5 + (-j2)$$

$$x = 5.32 + j1.76$$

$$y = Z_2 + 10 = (-0.24 - j2.82) + 10$$

$$y = 9.76 - j2.82$$

$$Z = Z_3 = 0.96 - j0.72$$


$$Z_{eq} = x || y || Z$$

$$= \frac{(5.32 + j1.76)(9.76 - j2.82)(0.96 - j0.72)}{(5.32 + j1.76) + (9.76 - j2.82) + (0.96 - j0.72)}$$

$$Z_{eq} = 4.24 \angle -31^\circ \Omega$$

So, $I = \frac{V}{Z_{eq}} = \frac{30 \angle 0^\circ}{4.24 \angle -31^\circ}$

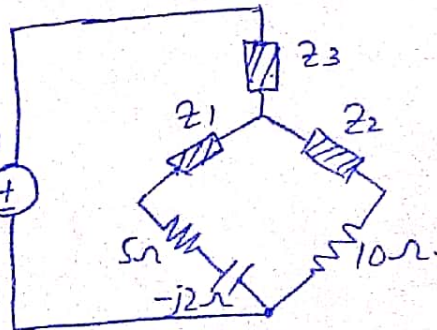
$$I = 7.07 \angle 31^\circ \text{ A} \quad \text{Ans:}$$



Δ -Y & Y- Δ Transformation:-

• $\Delta \rightarrow Y$:-

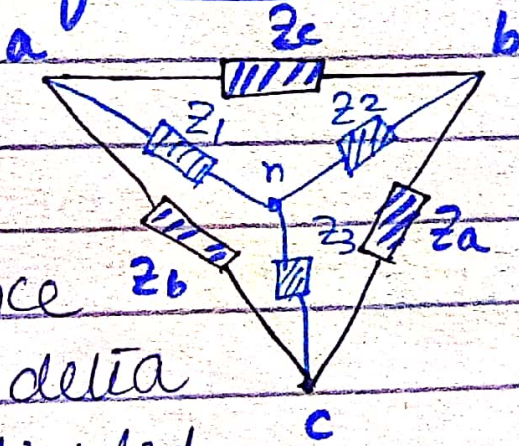"The impedance in Y-network is the product of impedance of two adjacent delta branches and divided by sum of all three delta branches."



$$\left. \begin{aligned} \bullet Z_1 &= \frac{Z_b Z_c}{Z_a + Z_b + Z_c} \\ \bullet Z_2 &= \frac{Z_a Z_c}{Z_a + Z_b + Z_c} \\ \bullet Z_3 &= \frac{Z_a Z_b}{Z_a + Z_b + Z_c} \end{aligned} \right\}$$

when $Z_a = Z_b = Z_c = Z$:-

$$Z_1 = Z_Y = \frac{Z^2}{3Z} = \frac{2Z}{3} = \frac{1}{3} Z \Rightarrow \boxed{1:3}$$

• $Y \rightarrow \Delta$:-

"Each impedance in delta(s) network is sum of all possible products of Y -impedences taken two at a time and divided by opposite impedences"

$$\bullet Z_a = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_1}$$

$$\bullet Z_b = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_2}$$

$$\bullet Z_c = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_3}$$

when $Z_1 = Z_2 = Z_3 = Z$:-

$$Z_a = \frac{3Z^2}{Z} = 3Z \Rightarrow \boxed{3:1}$$