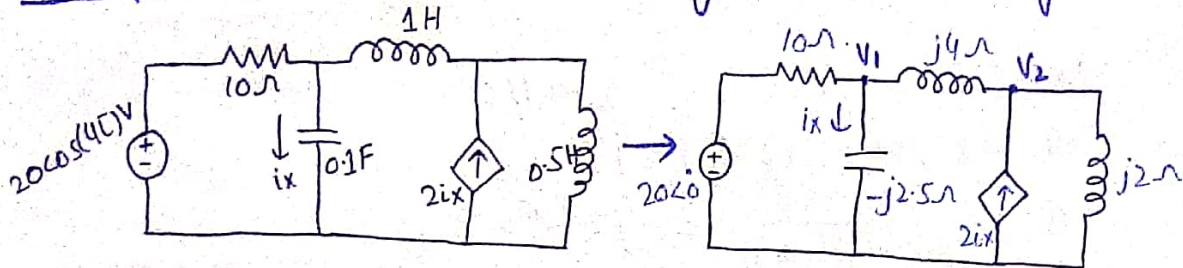


Chapter #10:-

Sinusoidal Steady State Analysis

→ Nodal Analysis:-

Example # 10.1:- find i_x using nodal analysis.



1) $V_s = 20 \cos 4t = 20 \angle 0^\circ \text{ V}$; $\omega = 4 \text{ rad/s}$.

• $0.1 \text{ F} \Rightarrow \frac{1}{j\omega C} = \frac{1}{j \times 4 \times 0.1} = -j2.5$

• $1 \text{ H} \Rightarrow j\omega L = j \times 4 \times 1 = j4$

• $0.5 \text{ H} \Rightarrow j\omega L = j \times 4 \times 0.5 = j2$

2) Nodal :-

at V_1 : $\frac{V_1 - 20}{10} = \frac{V_1}{-j2.5} + \frac{V_1 - V_2}{j4}$ / $\therefore I_x = \frac{V_1}{-j2.5}$

$$(1 + j1.5)V_1 + j2.5V_2 = 20 \quad \text{--- (1)}$$

at V_2 : $2I_x + \frac{V_1 - V_2}{j4} = \frac{V_2}{j2}$

$$11V_1 + 15V_2 = 0 \quad \text{--- (2)}$$

Cramer's rule:-

$$\begin{bmatrix} 1 + j1.5 & j2.5 \\ 11 & 15 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 20 \\ 0 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 1 + j1.5 & j2.5 \\ 11 & 15 \end{vmatrix} = 15 - j5$$

$$V_1 = \frac{\Delta_1}{\Delta} = \frac{300}{15 - j5} = 18.9 \angle 18.4^\circ$$

$$\Delta_1 = \begin{vmatrix} 20 & j2.5 \\ 0 & 15 \end{vmatrix} = 300$$

So,


$$I_x = \frac{V_1}{-j2.5} = \frac{18.9 \angle 18.4^\circ}{-j2.5}$$

$$\Delta_2 = \begin{vmatrix} 1 + j1.5 & 20 \\ 11 & 0 \end{vmatrix} = -220$$

$$I_x = 7.59 \angle 108.4^\circ \text{ A}$$

$$I_x = 7.5 \cos(4t + 108.4^\circ) \text{ A}$$

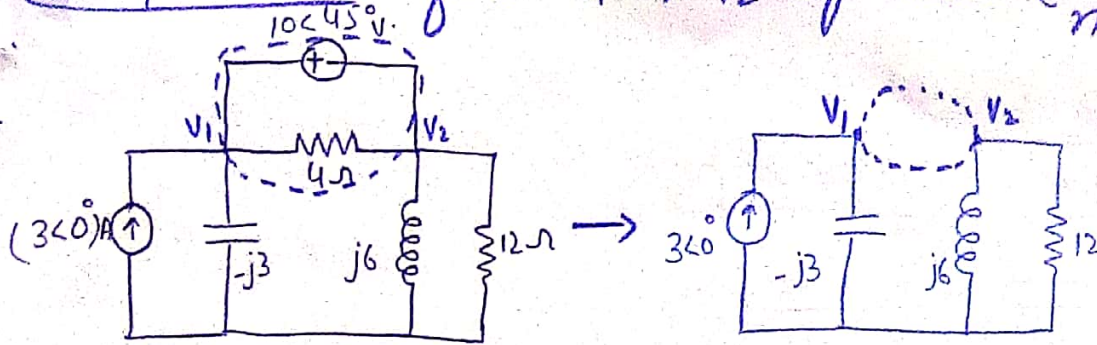
Example #10.2:- find V_1 & V_2 by nodal (super-node). (3)



super-node eqn. :-

$$V_1 - V_2 = 10\angle 45^\circ$$
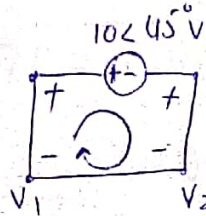
$$V_1 = V_2 + 10\angle 45^\circ \quad \text{--- (1)}$$



$$\rightarrow 3 = \frac{V_1}{-j3} + \frac{V_2}{j6} + \frac{V_2}{12}$$

$$36 = j4V_1 + (1-j2)V_2 \quad \text{--- (2)}$$

putting (1) in (2) :-

$$36 - j4(V_2 + 10\angle 45^\circ) = (1-j2)V_2$$

$$36 - 40\angle 135^\circ = (1+j2)V_2$$

$$V_2 = \frac{36 - 40\angle 135^\circ}{1+j2}$$


$$V_2 = 31.40\angle -87.18^\circ \text{ V} = 1.54 - j31.36 \text{ V}$$

put V_2 in (1) :-

$$V_1 = (31.40\angle -87.18^\circ) + (10\angle 45^\circ)$$

$$V_1 = 25.78\angle -70.48^\circ \text{ V}$$


Practice Problem #10.2:-

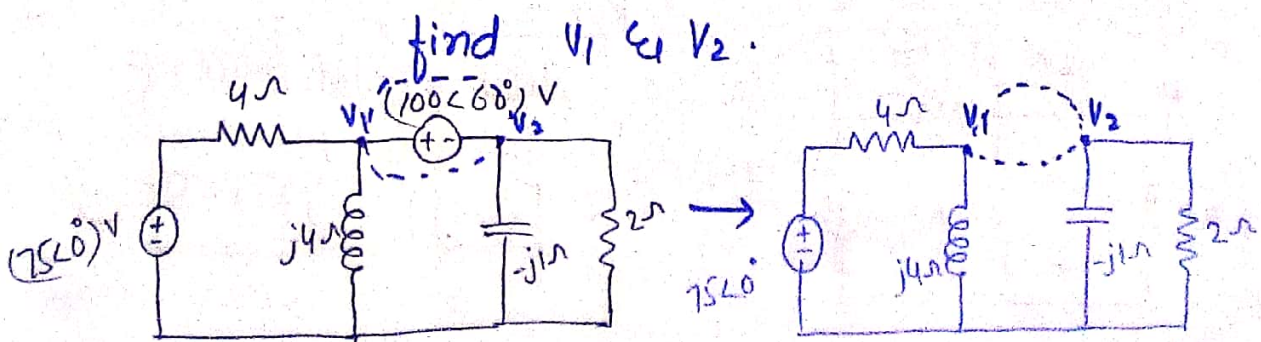

Super-node eqn :-

$$V_1 - V_2 = 100 \angle 60^\circ$$
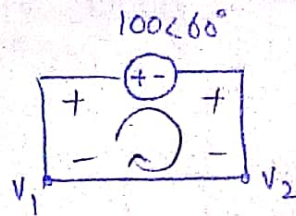
$$V_1 = V_2 + 100 \angle 60^\circ \quad \text{--- (1)}$$



$$\rightarrow \frac{V_1 - 75}{4} = \frac{V_1}{j4} + \frac{V_2}{-j1} + \frac{V_2}{2}$$

$$(1-j)V_1 + (2+j4)V_2 = 75 \quad \text{--- (2)}$$

put (1) in (2) :-

$$(1-j)(V_2 + 100 \angle 60^\circ) + (2+j4)V_2 = 75$$

$$V_2 - V_2 j + 2V_2 + 4jV_2 = 75 - (1-j)(50 + j86.66)$$

$$3V_2 + j3V_2 = 75 - (136.6 + j36.6)$$

$$V_2 = \frac{75 - (136.6 + j36.6)}{(3 + 3j)}$$

$$V_2 = \frac{-61.60 - j36.60}{3 + j3}$$


$$V_2 = 16.88 \angle 165.72^\circ \text{ V}$$

$$\text{(1)} \Rightarrow V_1 = (16.88 \angle 165.72^\circ) + (100 \angle 60^\circ)$$

$$V_1 = 96.8 \angle 69^\circ \text{ V}$$

Mesh Analysis :-

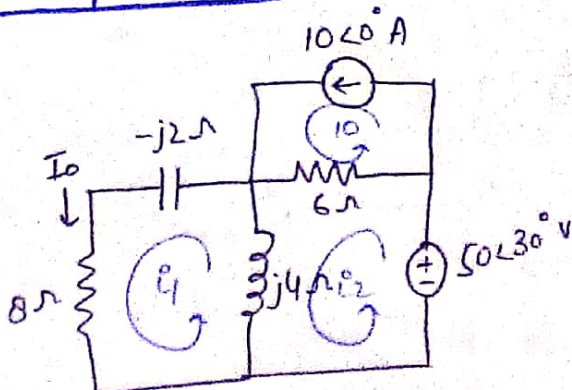P.P
Example # 10.3 :- Find I_0 by Mesh Analysis.



KVL at i1 :-

$$j4(i_1 - i_2) - j2i_1 + 8i_1 = 0$$

$$8i_1 + j2i_1 - j4i_2 = 0$$

$$\div \text{by } j \quad (4+j)i_1 - j2i_2 = 0 \quad \text{--- (1)}$$

KVL at i_2 :-

$$j4(i_2 - i_1) + 6(i_2 + 10) + 50 \angle 30^\circ = 0$$

$$-j4i_1 + j4i_2 + 6i_2 + 60 + (50 \angle 30^\circ) = 0$$

$$\boxed{j4i_1 - (6 + j4)i_2 = 103.3 + j25} \quad \text{--- (2)}$$

Cramer's rule:-

$$\begin{bmatrix} 4 + j & -j2 \\ j4 & -(6 + j4) \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 103.3 + j25 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 4 + j & -j2 \\ j4 & -(6 + j4) \end{vmatrix} = -28 - j22$$

$$\Delta_1 = \begin{vmatrix} 0 & -j2 \\ 103.3 + j25 & -(6 + j4) \end{vmatrix} = -50 + j206.6$$

$$i_1 = \frac{\Delta_1}{\Delta} = \frac{-50 + j206.6}{-28 - j22}$$

$$\boxed{i_1 = 5.96 \angle -164.5^\circ \text{ A}}$$


but: $I_0 = -i_1 = -5.96 \cos(\omega t - 164.5^\circ) \text{ A}$

so, $I_0 = 5.96 \cos(\omega t - 164.5^\circ + 180^\circ)$

$$\boxed{I_0 = 5.96 \angle 65.45^\circ \text{ A}}$$

Example # 10.3:-

find I_0 by mesh analysis.

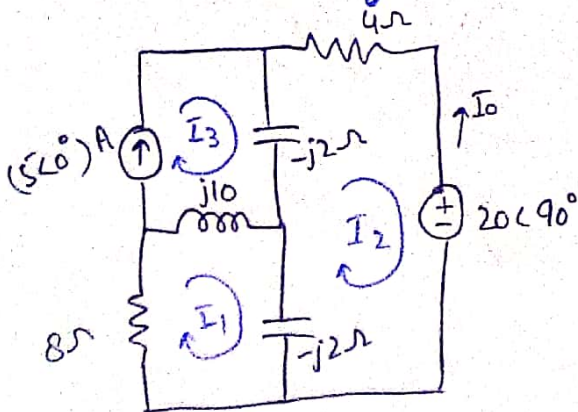

$$\therefore I_3 = 5 \text{ A}$$

KVL at I_1 :-

$$8I_1 + j10(I_1 - I_3) - j2(I_1 - I_2) = 0$$

$$\boxed{(8 + j8)I_1 + j2I_2 = j50} \quad \text{--- (1)}$$

KVL at I_2 :-

$$-j2(I_2 - I_3) + 4I_2 + 20 \angle 90^\circ - j2(I_2 - I_1) = 0$$

$$\boxed{j2I_1 + (4 - j4)I_2 = -j30} \quad \text{--- (2)}$$

using cramer's rule:-

$$\begin{bmatrix} 8+j8 & j2 \\ j2 & 4-j4 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} j50 \\ -j30 \end{bmatrix}$$

$\therefore I_0 = -I_2$

$$\Delta = \begin{vmatrix} 8+j8 & j8 \\ j2 & 4-j4 \end{vmatrix} = 68$$

$$\Delta_2 = \begin{vmatrix} 8+j8 & j50 \\ j2 & -j30 \end{vmatrix} = 340 - j240$$


$$I_2 = \frac{\Delta_2}{\Delta} = \frac{340 - j240}{68} = 6.2 \angle -35.21^\circ \text{ A}$$

Then:- $I_0 = -I_2 = 6.2 \cos(\omega t - 35.21 + 180^\circ) \text{ A}$

$$\boxed{I_0 = 6.2 \cos(\omega t + 144.78^\circ) \text{ A}} \text{ Ans:}$$

Example #10.4:-

Find V_0 by super-mesh.

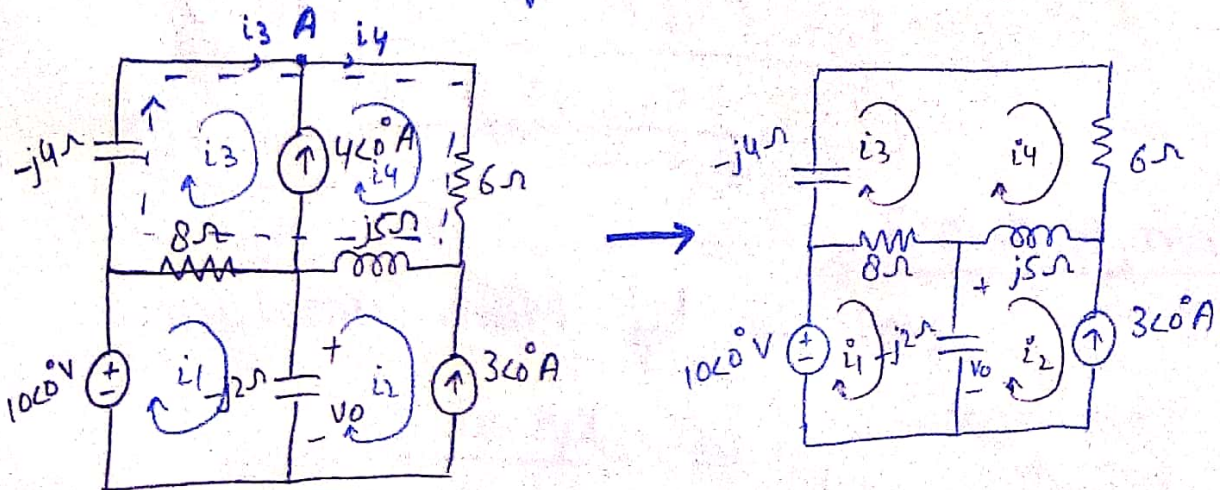

KCL at A:-

$$4 + i_3 = i_4$$

$$\boxed{i_3 = i_4 - 4} \text{ --- (a)}$$

KVL at mesh-2:-

$$\boxed{i_2 = -3 \text{ A}} \text{ --- (b)}$$

Mesh # 1:-

(7)

$$-10 \angle 0^\circ + 8(i_1 - i_3) - j2(i_1 - i_2) = 0$$

$$\therefore i_3 = i_4 - 4$$

$$8i_1 - 8i_3 - j2i_4 - j6 = 10$$

$$i_2 = -3A$$

$$(8-j2)i_1 - 8i_3 - j6 = 10$$

$$\boxed{(8-j2)i_1 - 8i_3 = 10 + j6} \quad \text{--- (1)}$$

Super-mesh:-

$$-j4i_3 + 6i_4 + j5(i_4 - i_2) + 8(i_3 - i_1) = 0$$

$$-j4i_3 + 6i_4 + j5i_4 + j15 + 8i_3 - 8i_1 = 0$$

$$-j4i_3 + 6(i_3 + 4) + j5(i_3 + 4) + 8i_3 - 8i_1 = -j15$$

$$-8i_1 + 8i_3 + 6i_3 - j4i_3 + j5i_3 + 24 + 20j = -15j$$

$$\boxed{-8i_1 + (14+j)i_3 = -24 - j35} \quad \text{--- (2)}$$

Cramer's rule:-

$$\Delta = \begin{vmatrix} (8-j2) & -8 \\ -8 & (14+j) \end{vmatrix} = 50 - j20$$

$$\Delta_1 = \begin{vmatrix} 10+j6 & -8 \\ -24-35j & 14+j \end{vmatrix} = -58 - j186$$

$$\Delta_3 = \begin{vmatrix} 8-j2 & (10+j6) \\ -8 & (-24-j35) \end{vmatrix} = -182 - j184$$

$$i_1 = \frac{\Delta_1}{\Delta} = \frac{-58 - j186}{50 - j20} = 3.61 \angle 274^\circ \text{ A}$$

$$i_3 = \frac{\Delta_3}{\Delta} = \frac{-182 - j184}{50 - j20} = 4.8 \angle -112^\circ \text{ A}$$


So,

$$V_o = -2j(i_1 - i_3)$$
$$= -2j(3.61 \angle 274^\circ - 4.8 \angle -112^\circ)$$

$$V_o = 9.746 \angle 222.2^\circ \text{ V}$$

$$\boxed{V_o = 9.746 \angle 222.2^\circ \text{ V}} \quad \text{Ans.}$$

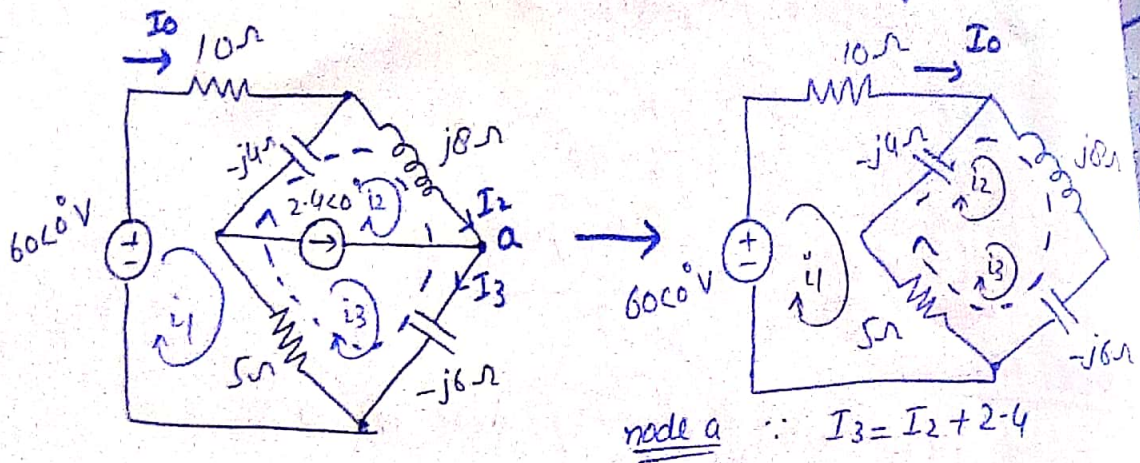Practice Problem # 10.4:- find I_o by mesh.



Mesh # 1:-

$$-60\angle 0^\circ + 10i_1 - j4(i_1 - i_2) + 5(i_1 - i_3) = 0$$

$$10i_1 - j4i_1 + j4i_2 + 5i_1 - 5i_3 = 60$$

$$(15 - j4)i_1 + j4i_2 - 5i_3 = 60$$

pulling $I_3 = I_2 + 2.4$:-

$$\boxed{(15 - j4)i_1 + (-5 + j4)i_2 = 72} \quad \text{--- (1)}$$

Super-mesh:-

$$-j4(i_2 - i_1) + j8i_2 - j6i_3 + 5(i_3 - i_1) = 0$$

$$-j4i_2 + j4i_1 + j8i_2 - j6(i_2 + 2.4) + 5(i_2 + 2.4) - 5i_1 = 0$$

$$(-5 + j4)i_1 + (-j4 + j8 - j6 + 5)i_2 = -12 + j14.4$$

$$\boxed{(-5 + j4)i_1 + (5 - j2)i_2 = -12 + j14.4} \quad \text{--- (2)}$$

Cramer's rule:-

$$\begin{bmatrix} 15 - j4 & -5 + j4 \\ -5 + j4 & 5 - j2 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 72 \\ -12 + j14.4 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 15 - j4 & -5 + j4 \\ -5 + j4 & 5 - j2 \end{vmatrix} = 58 - j10$$

$$\Delta_1 = \begin{vmatrix} 72 & -5 + j4 \\ -12 + j14.4 & 5 - j2 \end{vmatrix} = 357.6 - j24$$

$$I_o = I_1 = \frac{\Delta_1}{\Delta} = \frac{357.6 - j24}{58 - j10} = \boxed{6.08 \angle 5.94^\circ \text{ A}} \quad \text{Ans.}$$

Superposition Theorem:- (S.P.T)


→ When a circuit has more than one source (V & I) then, we have to solve all the sources independently - This principle is called S.P.T -

→ If a circuit has two or more independent source, one way to determine value of specific variable (V & I) is to use nodal, mesh analysis -

→ Another way to determine contribution of each independent source to variable x then add them up - (Steps from notes)

→ Super-position Theorem:-



Example #10.5:- find I_0 .

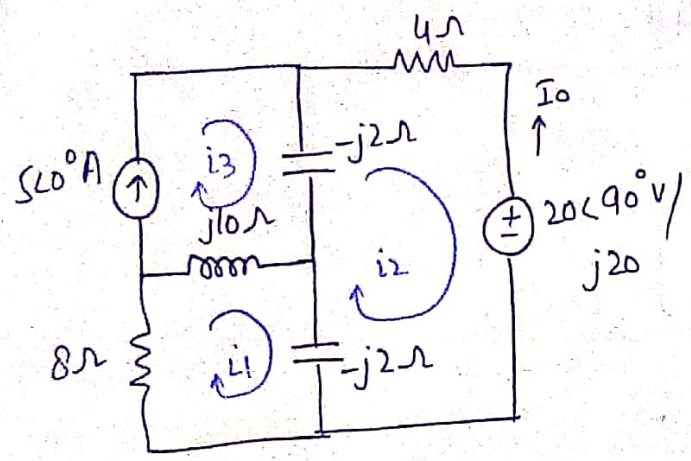

let $I_0 = I_0' + I_0''$

→ I_0' is due to voltage source & I_0'' is due to current source.

Due to voltage source:- (I_0')

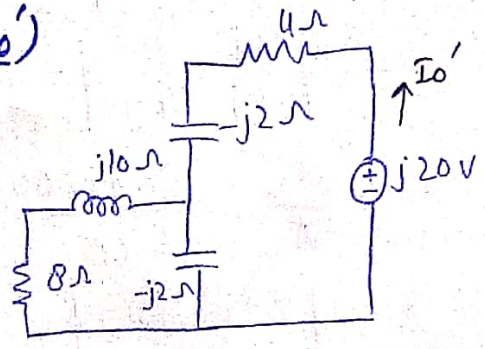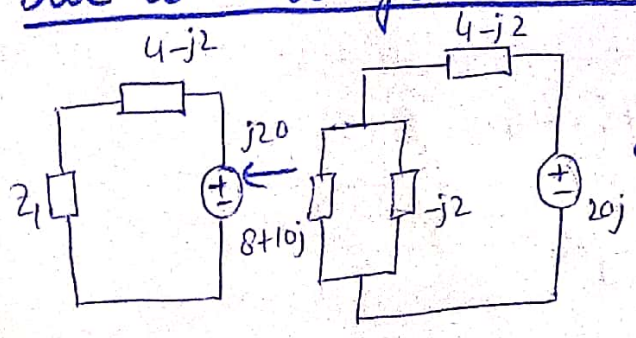

$Z_1 = (8+j10) \parallel (-j2)$

$Z_1 = 2.6 \angle 83.65^\circ$

So, $Z_{eq} = (4-j2) + (2.6 \angle 83.65^\circ)$

$Z_{eq} = 6.01 \angle -45^\circ \Omega$

So, $I_0' = \frac{V}{Z_{eq}} = \frac{20 \angle 90^\circ}{6.01 \angle -45^\circ}$

$I_0' = 3.32 \angle 135^\circ A$

Due to current source:- (I_0'')


$I_3 = 5A$

Mesh #1:-

$8i_1 + j10(i_1 - 5) - j2(i_1 - i_2) = 0$

$8i_1 + j10i_1 - j50 - j2i_1 + j2i_2 = 0$

$(8+j8)i_1 + j2i_2 = j50$

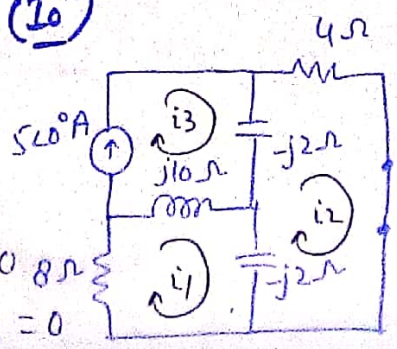

Mesh #2:-

$$-j2(i_2 - 5) + 4i_2 - j2(i_2 - i_1) = 0$$

$$-j2i_2 + 4i_2 - j2i_2 + j2i_1 = -j10$$

$$\boxed{j2i_1 + (4 - j4)i_2 = -j10}$$

Cramer's rule:-

$$\begin{bmatrix} 8+j8 & j2 \\ j2 & 4-j4 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} j50 \\ -j10 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 8+j8 & j2 \\ j2 & 4-j4 \end{vmatrix} = 68$$

$$\Delta_1 = \begin{vmatrix} j50 & j2 \\ -j10 & 4-j4 \end{vmatrix} = 180 + j200$$

$$i_1 = \frac{\Delta_1}{\Delta} = \frac{180 + j200}{68} = 3.95 \angle 48.01^\circ \text{ A}$$

$$\Delta_2 = \begin{vmatrix} 8+j8 & j50 \\ j2 & -j10 \end{vmatrix} = 180 - j80$$

$$i_2 = \frac{\Delta_2}{\Delta} = \frac{180 - j80}{68} = 2.89 \angle -23.96^\circ \text{ A} = 2.64 - j1.176$$

but: $I_0'' = -i_2 = -2.64 + j1.176 \text{ A}$

So,

$$I_0 = I_0' + I_0''$$


$$= (3.32 \angle 135^\circ) + (-2.64 + j1.176)$$

$$= (-2.34 + 2.34j) + (-2.64 + j1.176)$$

$$= -4.9 + j3.5 = \boxed{6.12 \angle 144.7^\circ \text{ A}} \text{ Ans:-}$$

Practice Problem #10.5:

Find I_0 using super-position Theorem.

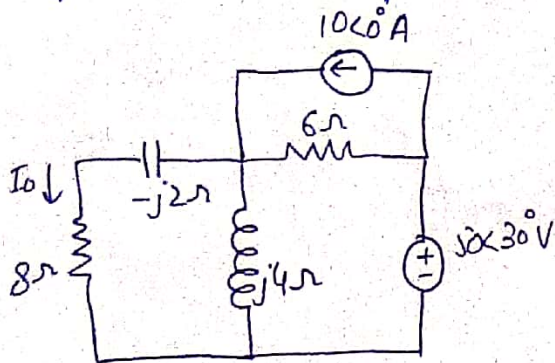

$$I_0 = I_0' + I_0''$$

Where I_0' is due to voltage source and I_0'' is due to current source.

Due to voltage source: (I_0')


$$\rightarrow 6i_1 + j4(i_1 - i_2) = 50\angle 30^\circ$$

$$\boxed{(6 + j4)i_1 - j4i_2 = 50\angle 30^\circ} \quad (1)$$

$$\rightarrow 8i_2 - j2i_2 + j4(i_2 - i_1) = 0$$

$$-j4i_1 + (8 + j2)i_2 = 0$$
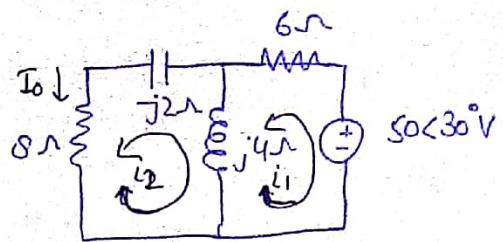
$$\div \text{by } j \quad \boxed{-j2i_1 + (4 + j)i_2 = 0} \quad (2)$$



By Cramer's rule:-

$$\begin{bmatrix} 6 + j4 & -j4 \\ -j2 & 4 + j \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 50\angle 30^\circ \\ 0 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 6 + j4 & -j4 \\ -j2 & 4 + j \end{vmatrix} = (6 + j4)(4 + j) - (-j2)(-j4)$$

$$\boxed{\Delta = 28 + j22}$$


$$\Delta_2 = \begin{vmatrix} 6 + j4 & 43.3 + j25 \\ -j2 & 0 \end{vmatrix} = -50 + j86.6$$

$$I_0' = i_2 = \frac{\Delta_2}{\Delta} = \frac{-50 + j86.6}{28 + j22} = \boxed{2.8\angle 81^\circ \text{ A}}$$

Due to current source:-

$$\rightarrow -j2i_1 + 8i_1 + j4(i_1 - i_2) = 0$$
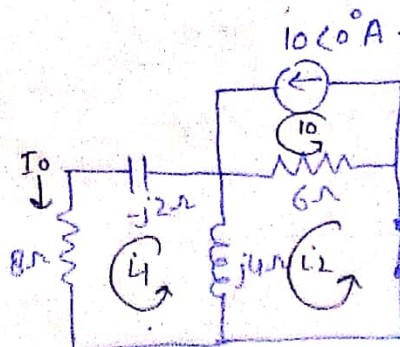
$$\boxed{(8 + j2)i_1 - j4i_2 = 0} \quad (1)$$



$$\rightarrow j4(i_2 - i_1) + j6(i_2 + 10) = 0$$

$$\boxed{-j4i_1 + (6 + j4)i_2 = 60} \quad \text{--- (2)}$$

Cramer's rule:-

$$\Delta = \begin{vmatrix} (8 + j2) & -j4 \\ -j4 & (6 + j4) \end{vmatrix} = 56 + j44$$

$$\Delta_1 = \begin{vmatrix} 0 & -j4 \\ 60 & (6 + j4) \end{vmatrix} = 0 - (-j4)(60) = j240$$

$$I_1 = I_0'' = \frac{\Delta_1}{\Delta} = \frac{j240}{56 + j44} = \boxed{3.36 \angle 51.84^\circ \text{ A}}$$


So,

$$\begin{aligned} I_0 &= I_0' + I_0'' \\ &= (2.8 \angle 81^\circ \text{ A}) + (3.36 \angle 51.84^\circ \text{ A}) \end{aligned}$$

$$\boxed{I_0 = 5.97 \angle 65^\circ \text{ A}}$$

Example #10.6:-

Find V_0 using S.P.T.

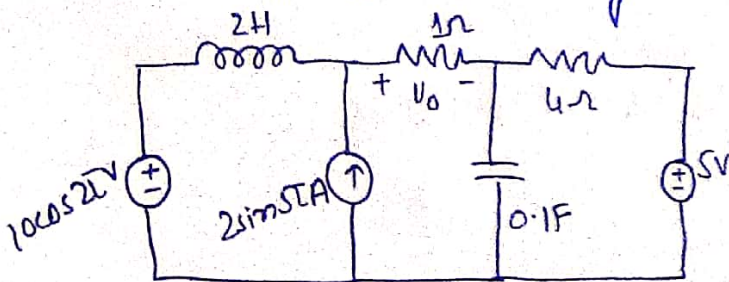

Here;

$$\boxed{V_0 = V_1 + V_2 + V_3}$$

V_1 is due to 5V;

V_2 is due to $10\cos 2t$ V;


V_3 is due to $2\sin 5t$ A.

For V_1 :-

$$-V_1 = \frac{1}{1+4} (5\text{V})$$

$$-V_1 = 8/8$$

$$\boxed{V_1 = -1\text{V}}$$


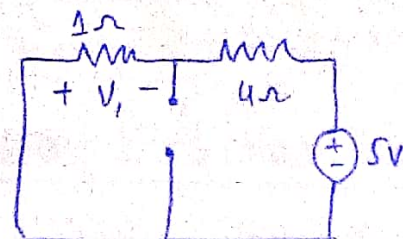


For V_2 :-

- $10\angle 0^\circ \text{V} \Rightarrow 10\angle 0^\circ; \omega = 2$
- $2\text{H} \Rightarrow j \times 2 \times 2 = 4j$
- $0.1\text{F} \Rightarrow \frac{1}{j \times 2 \times 0.1} = -j5\Omega$

$$Z = 4 \parallel -j5 = \frac{(4)(-j5)}{4 + (-j5)}$$

$$Z = 2.439 - j1.95 \Omega$$

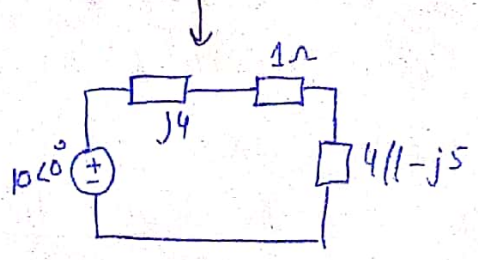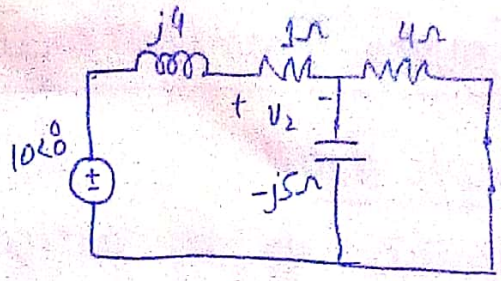

V.O.R:-



$$V_2 = \frac{1}{1 + j4 + Z} (10\angle 0^\circ) = \frac{1}{1 + j4 + 2.439 - j1.95} (10\angle 0^\circ)$$

$$V_2 = 2.498 \angle -30.79^\circ \text{V}$$

OR $V_2 = 2.498 \cos(2t - 30.79^\circ) \text{V}$

For V_3 :-

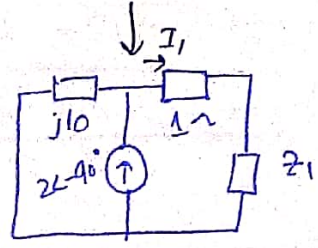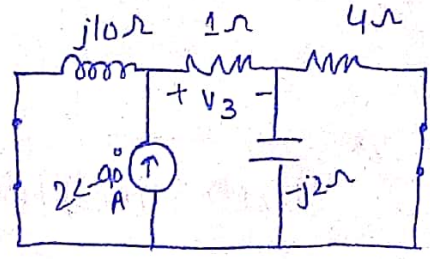- $2\sin 5t \text{V} \Rightarrow 2\angle -90^\circ \text{V}; \omega = 5$
- $2\text{H} \Rightarrow j \times 5 \times 2 = j10$
- $0.1\text{F} \Rightarrow \frac{1}{j \times 5 \times 0.1} = -j2\Omega$



$$Z_1 = (-j2) \parallel 4 = \frac{(-j2)(4)}{-j2 + 4} = 0.8 - j1.6$$

$$I_1 = \frac{j10}{j10 + 1 + Z_1} (2\angle -90^\circ)$$

So, $V_3 = I_1 R = \frac{j10}{(1 + j10) + 0.8 - 1.6j} (-j2) \times (1\Omega)$

$$V_3 = 0.48 - j2.27 \text{V} = 2.328 \angle -78^\circ \text{V} = 2.328 \cos(5t - 78^\circ)$$

OR $V_3 = 2.328 \sin(5t + 12^\circ) \text{V}$

$$V_0 = V_1 + V_2 + V_3$$

$$= -1 + 2.49 \cos(2t - 30.79^\circ) + 2.38 \sin(5t + 12^\circ) \text{ Ans:}$$

Source Transformation:-

A source transformation is the process of replacing a voltage source (V_s) with an impedance (Z) / Resistor (R) by a current source (I_s) in parallel with an impedance or vice versa.

$$V_s = Z_s I_s \Rightarrow I_s = \frac{V_s}{Z_s}$$

Steps:-

- 1) Replace all ^{voltage} sources which ~~are~~ is in series with that source to the current source that contain //al impedance.
- 2) Add all impedances.
- 3) Solve ckt.

→ Source Transformation :-

Example #10.7 :-



Calculate V_x by source transformation.

$$V_s = 20 \angle -90^\circ \text{ V}$$

$$Z_s = 5 \Omega$$

$$\text{So, } I_s = \frac{V_s}{Z_s} = \frac{20 \angle -90^\circ}{5}$$
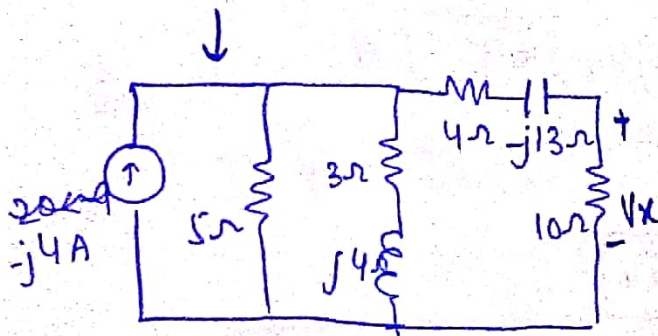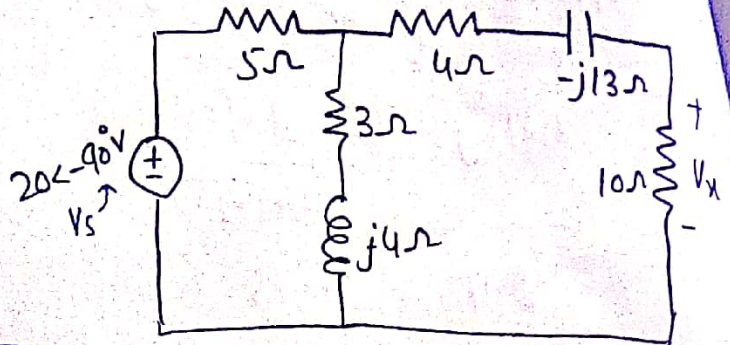
$$I_s = 4 \angle -90^\circ \text{ A} = -j4 \text{ A}$$




$$Z_{\text{eq}} = \frac{(5)(3+j4)}{5+3+j4} = 2.5 + j1.25$$

$$V_s = I_s Z_{\text{eq}}$$

$$V_s = (-j4)(2.5 + j1.25)$$

$$V_s = 5 - j10 \text{ V}$$

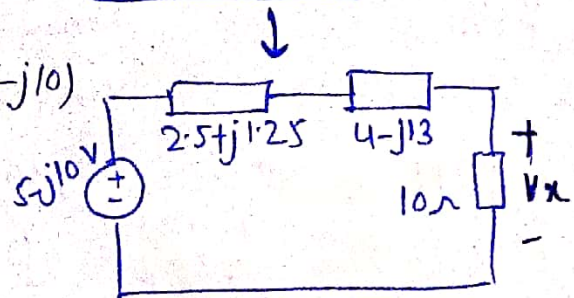

$$V_x = \frac{10}{(10) + (2.5 + j1.25) + (4 - j13)} \times (5 - j10)$$

$$V_x = 5.519 \angle -27.9^\circ \text{ V}$$

$$\text{or } V_x = 5.51 \angle -28^\circ \text{ V} \quad \text{Ans:-}$$


Practice Problem #10.7 :-


Find I_o using source transformation.

$$V_s = I_s Z_s$$

$$V_s = (j12)(4 - j3)$$

$$V_s = 36 + j48 \text{ V}$$

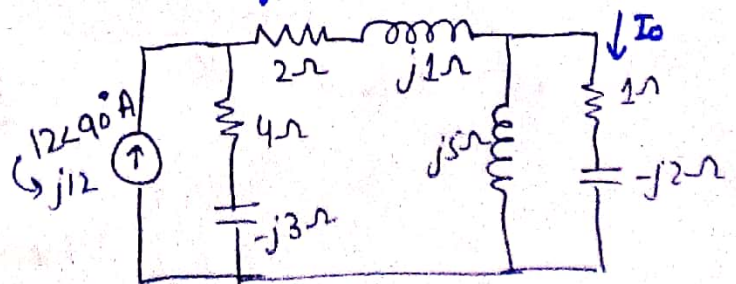

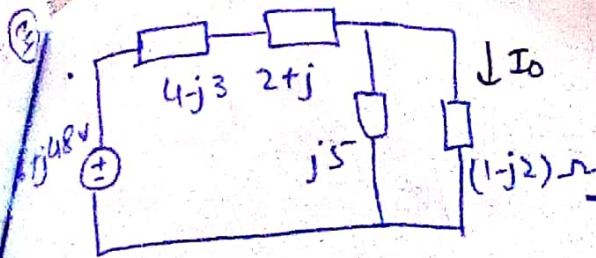



$$I_s = \frac{V_s}{Z_s}$$

$$Z_s = 4 - j3 + 2 + j$$

$$Z_s = 6 - j2$$

$$I_s = \frac{36 + j48}{6 - j2}$$

$$I_s = 3 + j9 \text{ A}$$

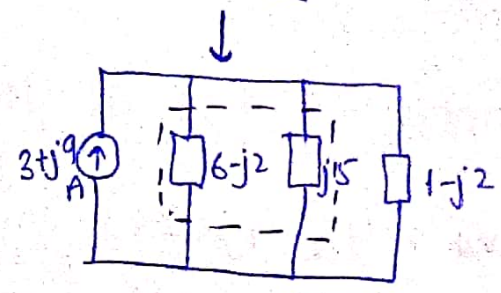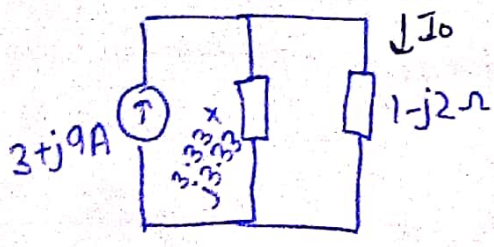

C.D.R.:-

$$I_0 = \frac{3.33 + j3.33}{3.33 + j3.33 + (1 - j2)} \times (3 + j9)$$



$$I_0 = 9.86 \angle 99.49^\circ \text{ A} \quad \text{Ans. :-}$$

→ Thevenin's Theorem:-

Example # 10.8:-

Obtain Thevenin's equivalent ckt. at terminal

a-b.

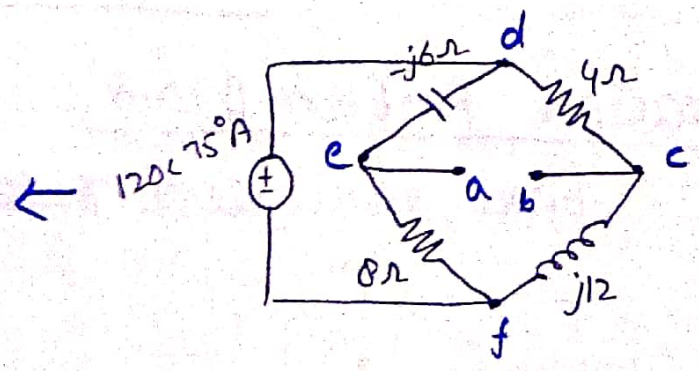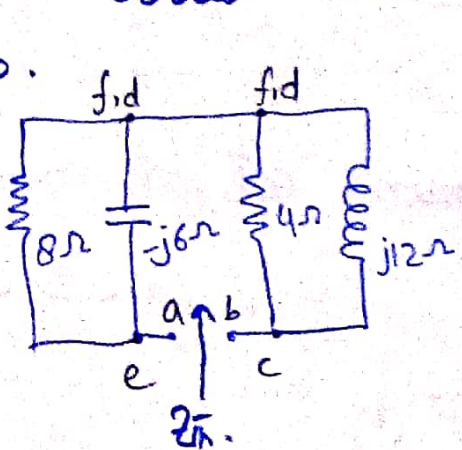


$$Z_1 = (8) \parallel (-j6) = 2.88 - j3.84 \Omega$$

$$Z_2 = (4) \parallel (j12) = 3.6 + j1.2 \Omega$$

$$Z_{th} = Z_1 + Z_2 = 6.4 - j2.64 \Omega$$

if ckt. is re-arranged:-

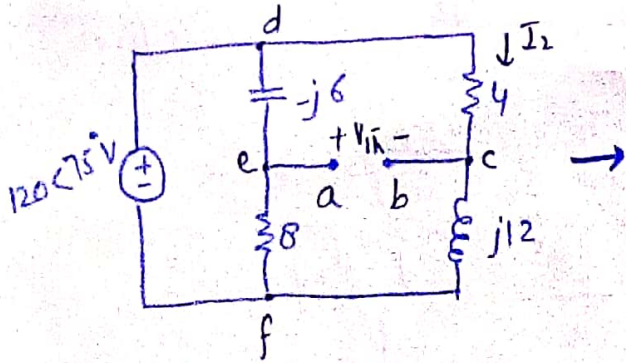

$$I_1 = \frac{120 \angle 75^\circ}{8 - j6}$$

$$I_2 = \frac{120 \angle 75^\circ}{4 + j12}$$

applying KVL at loop bcdeab:-


$$V_{th} = 4I_2 + j6I_1$$

$$= 4 \left[\frac{120 \angle 75^\circ}{4 + j12} \right] + j6 \left[\frac{120 \angle 75^\circ}{8 - j6} \right]$$

$$V_{th} = 37.94 \angle 3.43^\circ + 72 \angle -158^\circ$$



$$V_{th} = 37.95 \angle -139^\circ \text{ V} \quad \text{Ans.}$$

eq. cct. :-

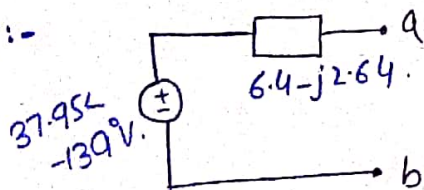

Practice Problem #10.8:-

Find equivalenti Thevenin's cct at a-b.

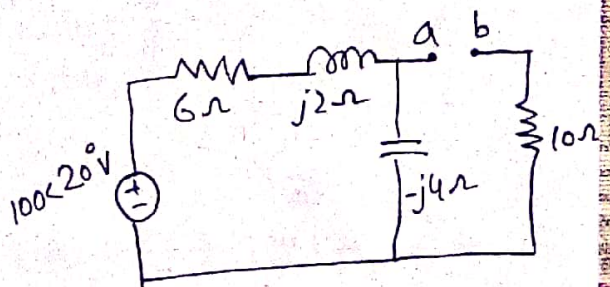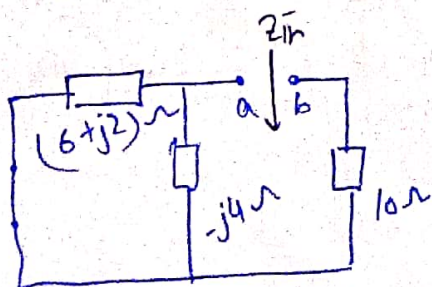

$$Z_{12} = (6 + j2) \parallel (-j4)$$

$$Z_{12} = 2.4 - j3.2 \Omega$$

So,

$$Z_{th} = (10) + (2.4 - j3.2)$$

$$Z_{th} = 12.4 - j3.2 \Omega$$


Q: V_{th} :-

voltage across $-j4 = V_{th}$


by VDR:-

$$V_{th} = \frac{(-j4)}{(-j4) + (6+j4)} (100 \angle 20^\circ)$$
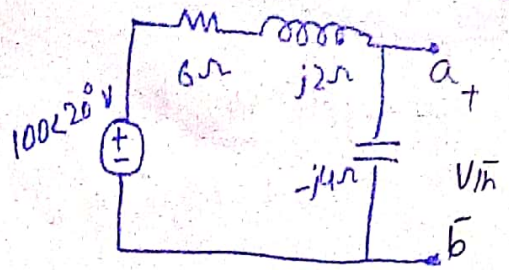
$$V_{th} = 63.24 \angle -51.56^\circ \text{ V Ans:-}$$




eqv. cct. :-

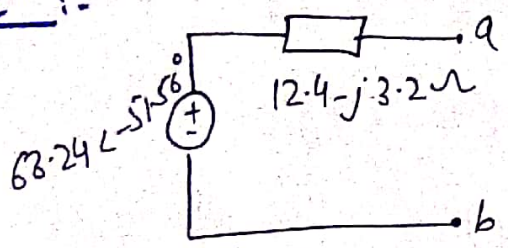

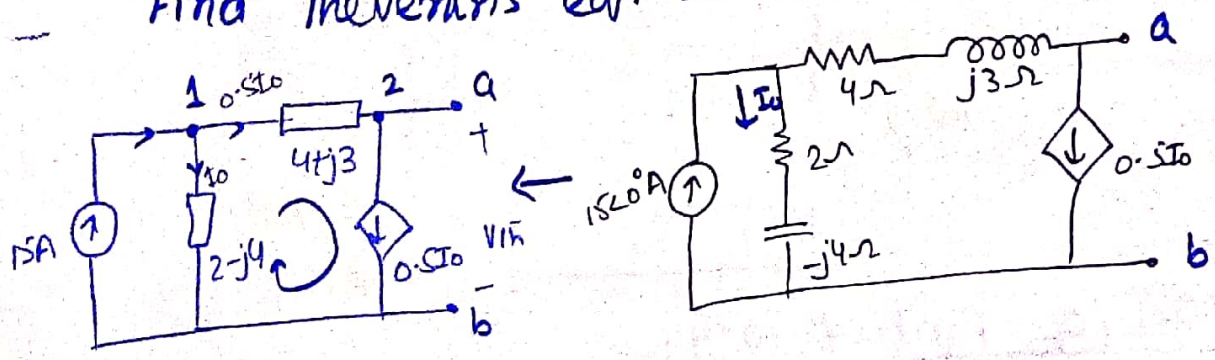Example #10.9:-

Find Thevenin's eq. cct. at terminal a-b.



KCL at node-1:-

$$15 = I_0 + 0.5I_0$$

$$I_0 = 10 \text{ A}$$

KVL at loop:-

$$-I_0(2-j4) + 0.5I_0(4+j3) + V_{th} = 0$$

$$V_{th} = 10(2-j4) - 5(4+j3)$$

$$V_{th} = -j55 \text{ V}$$

$$V_{th} = 55 \angle -90^\circ \text{ V}$$

For Z_{Th} :-

at node V_s ; KCL gives:-

$$\rightarrow 3 = I_o + 0.5 I_o$$

$$I_o = 2A$$

Applying KVL to outer loop:-

$$V_s = I_o(4 + j3 + 2 - j4)$$



$$V_s = 2(6 - j)$$

Thevenin's impedance (Z_{Th}) is:-

$$Z_{Th} = \frac{V_s}{I_s} = \frac{2(6 - j)}{3}$$

$$Z_{Th} = 4 - j0.6667 \Omega$$

eq. cct. :-

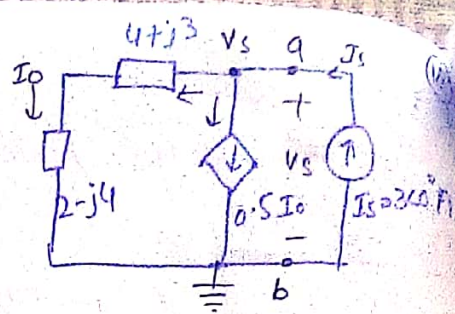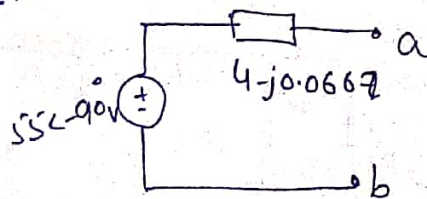

Practice Prob. # 10.9:-

Determine Thevenin's eq. cct. at a-b.

$$Z_1 = (4 - j2) \Omega$$


$$Z_2 = (8 + j4) \Omega$$

KCL at V_1 :-

$$\frac{V_1}{4 - j2} + \frac{V_1 - V_{Th}}{8 + j4} + 5 \angle 0^\circ = 0$$

$$V_1 \left(\frac{1}{4 - j2} \right) + V_1 \left(\frac{1}{8 + j4} \right) - V_{Th} \left(\frac{1}{8 + j4} \right) = -5$$
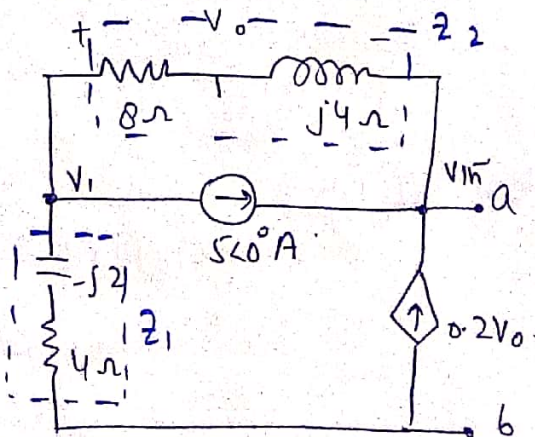
$$(0.3 + j0.05) V_1 - (0.1 - j0.05) V_{Th} = -5 \quad \text{--- (1)}$$



⑧ KCL at node V_1 :-

19

$$\frac{V_1 - V_{Th}}{8 + j4} + 0.2V_0 + 5 = 0$$

$$\text{or } \frac{V_{Th} - V_1}{8 + j4} - 0.2V_0 - 5 = 0 \quad \therefore V_0 = V_1 - V_{Th}$$

$$V_{Th} \left(\frac{1}{8 + j4} \right) - V_1 \left(\frac{1}{8 + j4} \right) - 0.2(V_1 - V_{Th}) - 5 = 0$$

$$(0.1 - j0.05)V_{Th} - (0.1 - j0.05)V_1 - 0.2V_1 + 0.2V_{Th} = 5$$

$$\text{or } \boxed{(-0.3 + j0.05)V_1 + (0.3 - j0.05)V_{Th} = 5} \quad \text{--- (2)}$$

from eq (1) :-

$$(0.3 + j0.05)V_1 = -5 + [(0.1) - j0.05]V_{Th}$$

$$V_1 = \left[\frac{0.1 - j0.05}{0.3 + j0.05} \right] V_{Th} - \frac{5}{0.3 + j0.05}$$

$$\boxed{V_1 = (0.297 - j0.216)V_{Th} - (16.216 - j2.7)}$$

put in (2)

$$\text{(2)} \Rightarrow (-0.3 + j0.05)[(0.297 - j0.216)V_{Th} - (16.216 - j2.7)] + (0.3 - j0.05)V_{Th} = 5$$


$$(0.2217 + j0.02965)V_{Th} = 5 - 4.7298 + j1.62$$

$$V_{Th} = \frac{5 - 4.7298 + j1.62}{0.2217 + j0.02965}$$

$$V_{Th} = 2.156 + j7.01V$$

$$\text{or } \boxed{V_{Th} = 7.34 \angle 72.92^\circ V}$$

for Z_{Th} :-

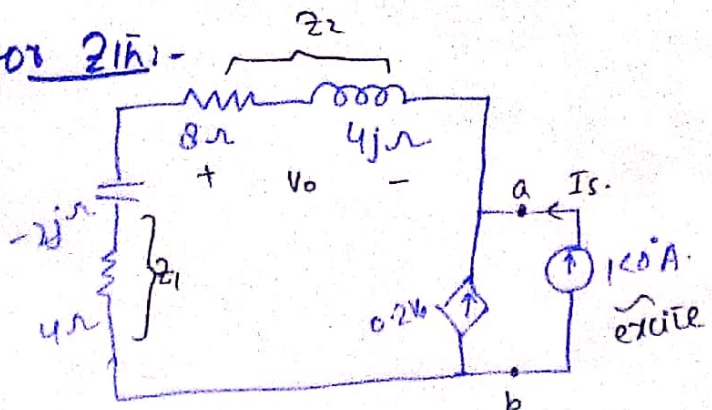

$$\text{as: } Z_1 = 4 - j2$$

$$Z_2 = 8 + j4$$

So,

$$V_0 = -V_s \left(\frac{Z_2}{Z_1 + Z_2} \right)$$

KCL at V_s :-

$$\frac{V_s}{z_1 + z_2} - 0.2[V_s] - 1 = 0.$$

put value of V_o :-

$$\frac{V_s}{z_1 + z_2} - 0.2 \left[-V_s \left(\frac{z_2}{z_1 + z_2} \right) \right] = 1$$

$$V_s [1 + 0.2 z_2] = z_1 + z_2$$

$$V_s = \frac{12 + j2}{2.6 + j0.8}$$


$$V_s = 4.473 \angle -7.64^\circ \text{ V}$$

So, $Z_{in} = \frac{V_s}{I_s}$

$$Z_{in} = \frac{4.473 \angle -7.64^\circ \text{ V}}{1 \angle 0^\circ \text{ A}}$$

$$Z_{in} = 4.473 \angle -7.64^\circ \Omega$$

eq. cct. :-

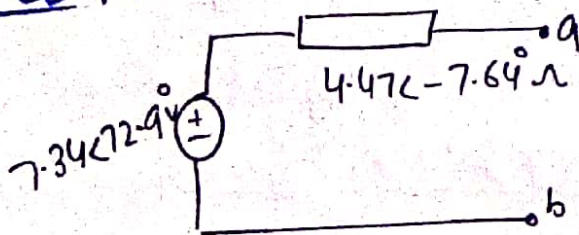

Thevenin's Theorem:-


- 1) find R_{th} / Z_{th} by turn off all sources ($V \rightarrow \text{short}$, $I \rightarrow \text{open}$)
- 2) for V_{th} ; find V_{th} using any C.D.R, V.D.R etc.
- 3) Remove ~~the~~ load R_L for V_{th} .
- 4) Excite any of arbitrary source if there is any independent source.

20) Norton's Theorem:-


(21)

Example # 10.10:-

Find I_o using Norton's Theorem.

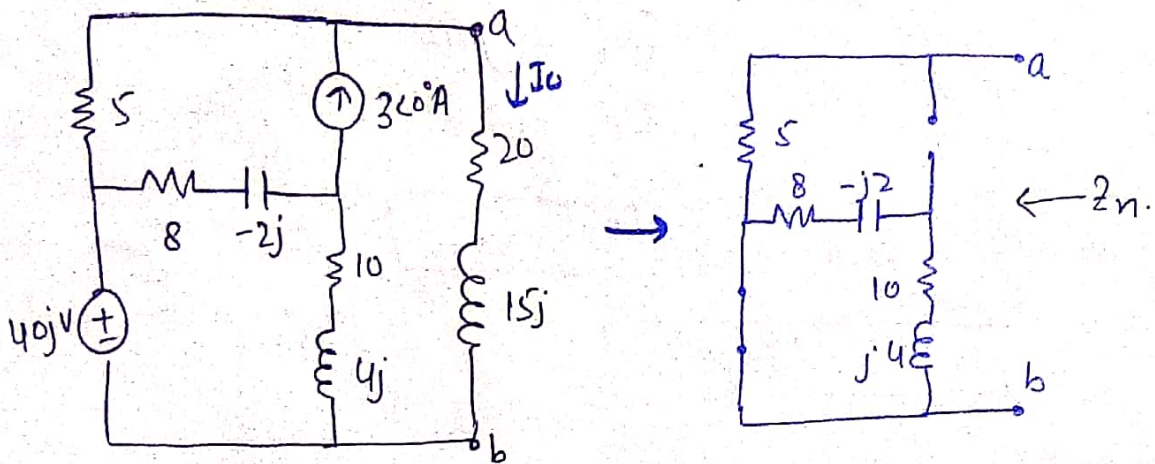

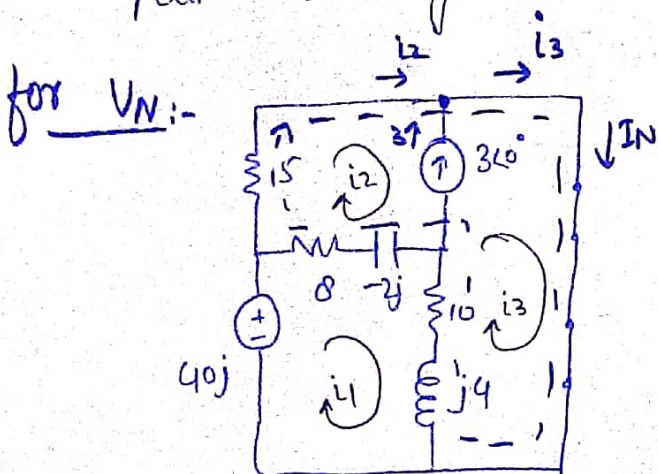current pass through short-wired / easiest path through 5Ω so; $Z_N = 5 \Omega$



KCL at node:-

$$I_N = I_2 + 3$$

Mesh # 1:-

$$-40j + (8-j2)(i_1 - i_2) + (10+j4)(i_1 - i_3) = 0$$

$$(8-j2)i_1 + (10+j4)i_1 + (8-j2)(-i_2) + (10+j4)(i_2+3) = 40j$$

$$\boxed{(18+j2)i_1 + (-18-j2)i_2 = 30+j52} \quad \text{--- (1)}$$

Super-mesh:-

$$(10+j4)(i_3 - i_1) + (8-j2)(i_2 - i_1) + 5i_2 = 0$$

$$10i_2 + 30 - 10i_1 + 4ji_2 + 12j - 4ji_1 + 8i_2 - 8i_1 - j2i_2 + j2i_1 + 5i_2 = 0$$

$$\boxed{(-18-j2)i_1 + (23+j2)i_2 = -30-j12} \quad \text{--- (2)}$$

adding ① & ② :-

$$\begin{aligned} (18+j2)i_1 + (-18-j2)i_2 &= 30+j52 \\ + (-18-j2)i_1 + (23-j2)i_2 &= -30-j12 \end{aligned}$$

$$5i_2 = j40$$


$$i_2 = j8$$

So,

$$i_3 = i_2 + 3 \Rightarrow i_3 = 3+j8$$

&

$$I_N = I_3 = (3+j8)A$$

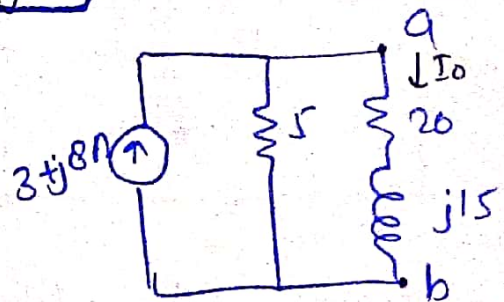

C.D.R.:-

$$I_0 = \frac{5}{5+(20+j15)} (3+j8)$$

$$I_0 = 1.465 \angle 38.48^\circ A \quad \text{Ans:-}$$