

### Chapter # 13:-

## Magnetically Coupled Circuits

Def:- (mutual inductance)

"When 2-coils are placed close to each other, the magnetic flux caused by current in one coil links with other coil, so inducing Emf/V in second."


→ for  $V = L di/dt$ .

Faraday's law →  $V = N d\phi/dt$  — (1)

(1) x 1:-  $V = N d\phi/dt \times di/dt$  ∴  $1 \approx di/dt$

$$V = L \frac{di}{dt}$$

$$\therefore L = \frac{Nd\phi}{di}$$

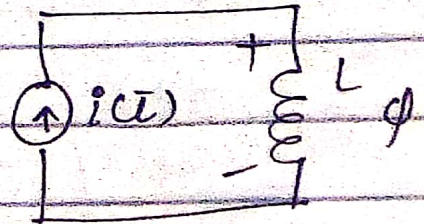

## Diff. b/w Self & Mutual Inductance:-

### → Self-inductance:-

Let we have one coil and  $\vec{i}$  current is flowing through it. Rate of change of current produces emf/voltages within same coil. This phenomenon is self-inductance.

$$V \propto \frac{di}{dt} \Rightarrow V = -L \frac{di}{dt}$$

\* -ve sign is due to Lenz's law.

Lenz's law:- According to Lenz's law, generated emf opposes rate of change of current through which it is generated. (cause)

### → Mutual inductance:-



If rate of change of current through one coil produces emf/voltages in another coil placed near it, it is called mutual inductance.

→ coils are physically separated.  $L_1$   $L_2$

coil #1

$$\Phi_1 = \Phi_{11} + \Phi_{12}$$
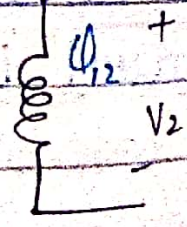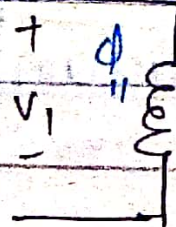
$$V_1 = N_1 \frac{d\Phi}{dt}, \quad V_2 = N_2 \frac{d\Phi}{dt}$$



$$V_1 = N_1 \frac{d\Phi}{dt} \times \frac{di_1}{dt}, \quad V_2 = N_2 \frac{d\Phi}{dt} \times \frac{di_1}{dt}$$

$$V_1 = L_1 \frac{di_1}{dt}$$

$$V_2 = M_{21} \frac{di_1}{dt}$$

coil #2 :-

$$\phi_2 = \phi_{21} + \phi_{22}$$

$$V_2 = N_2 \frac{d\phi_2}{dt} \times \frac{di_2}{dt} \quad ; \quad V_1 = N_1 \frac{d\phi_{21}}{dt} \times \frac{di_2}{dt}$$

$$V_2 = N_1 \frac{d\phi_2}{di_2} \times \frac{di_2}{dt}$$

$$V_1 = N_1 \frac{d\phi_{21}}{di_2} \times \frac{di_2}{dt}$$

$$V_2 = L_2 \frac{di_2}{dt}$$

$$V_1 = M_{12} \frac{di_2}{dt}$$


in coil  $L_2$

in coil  $L_1$

$M_{12} = M_{21} = M \rightarrow$  mutual inductance.

EX# 13.1 :-

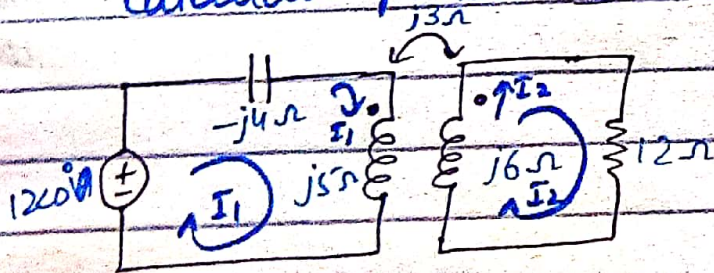calculate phasor currents  $I_1$  &  $I_2$  in ca :-



KVL at loop #  $I_1$  :-

$$-12 - j4I_1 + j5I_1 - j3I_2 = 0$$

due to opposite convention (leaving & entering currents)

$$jI_1 - j3I_2 = 12 \quad \text{--- (1)}$$

KVL at loop #  $I_2$  :-

$$-j3I_1 + (12 + j6)I_2 = 0$$

$$I_1 = \frac{(12 + j6)I_2}{j3} = \frac{(2 - j4)I_2}{j} \rightarrow \text{put in (1)}$$

$$j(2 - j4)I_2 - j3I_2 = 12$$

$$(j2 + 4 - j3)I_2 = 12 \Rightarrow (4 - j)I_2 = 12$$

$$I_2 = \frac{12}{4 - j}$$

$$I_2 = 2.91 \angle 14.04^\circ \text{ A}$$

for  $I_1$  :-

$$I_1 = (2-j4)I_2$$

$$I_1 = (2-j4)(2.91 \angle 14.04^\circ)$$

$$I_1 = (4.47 \angle -63.43^\circ)(2.91 \angle 14.04^\circ)$$

$$I_1 = 13.01 \angle -49.39^\circ \text{ A}$$

Monday  
06-04-2022

PP#13.1:- Find  $V_o$  in following.

KVL at  $I_1$  :-

$$-120 \angle 45^\circ + 4I_1 + j8I_1 + j1I_2 = 0 \quad 120 \angle 45^\circ \text{ V}$$

$$(4+j8)I_1 + j1I_2 = 120 \angle 45^\circ \quad \text{--- (1)}$$

KVL at  $I_2$  :-

$$j5I_2 + 10I_2 + j1I_1 = 0$$

$$j1I_1 + (10+j5)I_2 = 0$$

$$\text{or } I_1 = \frac{(10+j5)}{j1} I_2$$

$I_1$  &  $I_2$  both enters in dotted terminals. (addition of mutual inductive voltages i.e.  $-j1I_1$ )

$$I_1 = (-5+j10)I_2 \rightarrow \text{put in (1)}$$

$$\text{(1)} \Rightarrow (4+j8)(-5+j10)I_2 + j1I_2 = 120 \angle 45^\circ$$

$$-100I_2 + jI_2 = 120 \angle 45^\circ$$

$$I_2 = \frac{120 \angle 45^\circ}{(-100+j)}$$

$$I_2 = 1.199 \angle -134.43^\circ \text{ A}$$

$$\rightarrow V_o = I_2 \times 10$$

$$= (1.199 \angle -134.43^\circ)(10)$$

$$V_o = 12 \angle -134.4^\circ \text{ V}$$

EX#13.2 calculate mesh currents in following:


$\therefore I_1$  enters in coil # 1 (dotted)

$I_2$  leaves in coil # 2 (dotted end)


KVL at loop # 1 :-

$$-100 + 4I_1 - j3I_1 + j6(I_1 - I_2) - j2I_2 = 0$$
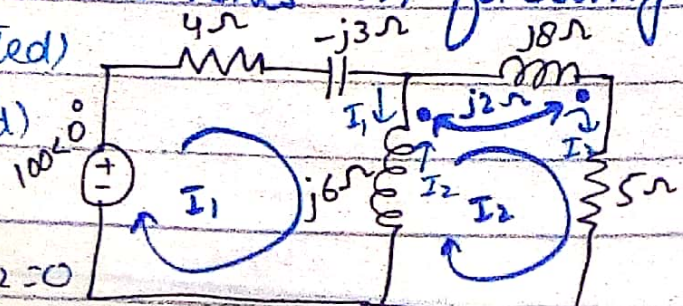
$$(4+j3)I_1 - j8I_2 = 100 \quad \text{--- (1)}$$



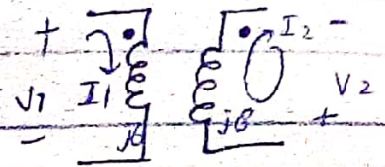for mesh #2 - We see  $I_2$  in both coil in series.  $I_2$  is leaving from dotted terminals in both coils; so.  
 $L = L_1 + L_2 + 2M$ . → use here.



$$V_1 = -j2I_2$$

$$V_2 = -j2I_1$$

KVL at mesh #2: →  $j6(I_2 - I_1)$

$$-j2I_1 - j6I_1 + (L_1 + L_2 + 2M + 5)I_2 = 0$$

$$-j2I_1 - j6I_1 + (j6 + j8 + 2(j2) + 5)I_2 = 0$$

$$\boxed{-j8I_1 + (5 + j18)I_2 = 0} \quad \text{--- (2)}$$

$$\begin{cases} L = L_1 + L_2 + 2M \\ L = L_1 + L_2 - 2M \end{cases}$$

Cramer's rule:-

$$\Delta = \begin{vmatrix} (4+j3) & -j8 \\ -j8 & (5+j18) \end{vmatrix} = (4+j3)(5+j18) - (-j8)(-j8) = \boxed{30 + j87}$$

$$\Delta_1 = \begin{vmatrix} 100 & -j8 \\ 0 & 5+j18 \end{vmatrix} = 500 + j1800$$

$$\Delta_2 = \begin{vmatrix} 4+j3 & 100 \\ -j8 & 0 \end{vmatrix} = j800$$


$$I_1 = \frac{\Delta_1}{\Delta} = \frac{500 + j1800}{30 + j87} = \boxed{20.3 \angle 3.5^\circ \text{ A}}$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{j800}{30 + j87} = \boxed{8.69 \angle 19.025^\circ \text{ A}}$$

PP#13.2 :- Find  $I_1$  &  $I_2$  in fig.


KVL at mesh #1:-

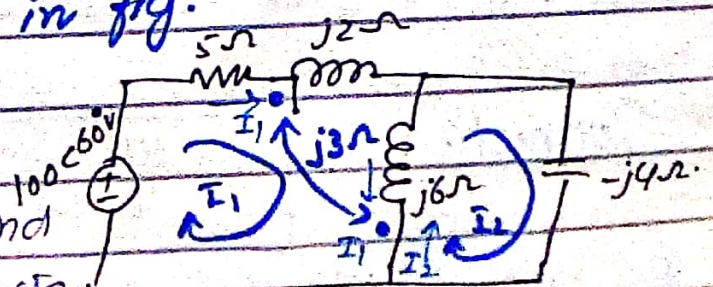$I_1$  &  $I_2$  enters at dotted terminals → +ve mutual inductance.



$$-100\angle 60 + 5I_1 + j2I_1 + j6(I_1 - I_2) + j3I_1 = 0$$
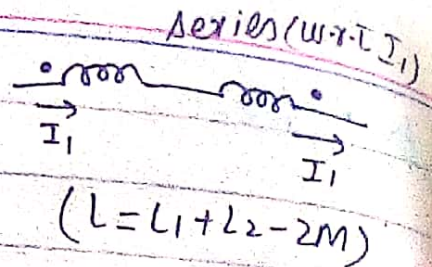
$$-100 \angle 60^\circ + 5 I_1 + (j8 + j6 - 2(j3)) I_1 - j6 I_2 + j3 I_2 = 0$$



$$(5 + j2) I_1 - j3 I_2 = 100 \angle 60^\circ \quad \text{--- (1)}$$

Mesh #2:-

$$j6(I_2 - I_1) - j4 I_2 + j3 I_1 = 0$$

$$-j3 I_1 + j2 I_2 = 0$$

$$-j3 I_1 = -j2 I_2$$

$$I_2 = \frac{3}{2} I_1 \quad \text{or}$$

$$I_2 = 1.5 I_1 \quad \rightarrow \text{put in (1)}$$

$$(5 + j2) I_1 - j3(1.5 I_1) = 100 \angle 60^\circ$$

$$5 I_1 + j2 I_1 - j4.5 I_1 = 100 \angle 60^\circ$$

$$I_1 = \frac{100 \angle 60^\circ}{5 - j2.5}$$

$$I_1 = 17.88 \angle 86.56^\circ \text{ A}$$

$$I_2 = (1.5)(17.88 \angle 86.56^\circ)$$

$$I_2 = 26.83 \angle 86.57^\circ \text{ A}$$

### Q-factor:- (Quality factor)

"It is ratio of inductor 'L' to Resistor 'R' of a coil at given frequency  $\omega$  defines efficiency of an inductor."

→ The higher Q-factor of inductor, closer inductor to ideal without losses.

Formula:-

$$Q = \frac{\omega L}{R} = \frac{2\pi f L}{R}$$

$$\because \omega = 2\pi f$$

Q bandwidth  $\propto \frac{1}{Q}$  ;  $\uparrow L \propto \uparrow Q$  ;  $\downarrow R \propto \frac{1}{Q}$

Normally / generally:  $0 \leq Q \leq 100$ .

## Q-factor of series Resonating ckt (RLC) :-

→ in resonating ckt, Q-factor is ratio of voltage across inductor ( $V_L$ ) / ( $V_C$ ) capacitor to applied voltage.

i.e. :-  $Q = \frac{V_L}{V_{\text{Applied}}}$

$Q = \frac{V_C}{V_{\text{Applied}}}$

for inductor :-

$$Q = \frac{I X_L}{I R}$$

$$Q = \frac{X_L}{R} = \frac{\omega L}{R}$$

for capacitor :-

$$Q = \frac{I X_C}{I R}$$

$$Q = \frac{X_C}{R} = \frac{\frac{1}{\omega C}}{R} = \frac{1}{\omega C R}$$

at fr

$$X_C = X_L$$

$$\frac{1}{\omega C} = \omega L$$

$$\omega = \frac{1}{\sqrt{LC}}$$

put  $\omega = \frac{1}{\sqrt{LC}}$  in both :-

$$Q = \frac{1}{\sqrt{LC}} \cdot \frac{L}{R} = \frac{\sqrt{L} \times \sqrt{L}}{\sqrt{L} \times \sqrt{C} \cdot R}$$

$$Q = \frac{1}{\frac{1}{\sqrt{LC}} \cdot C R} = \frac{\sqrt{L} \times \sqrt{L}}{\sqrt{L} \times \sqrt{C} \cdot R}$$

$$Q = \frac{\sqrt{L} \cdot 1}{\sqrt{C} \cdot R}$$

$$Q = \frac{\sqrt{L} \cdot 1}{\sqrt{C} \cdot R}$$

→ same for both L & C.


$$Q = \frac{\omega}{\text{B.W (bandwidth)}}$$

→ less bandwidth, better quality-factor

b.w =  $f_c = \text{higher freq.} - \text{Lower freq.}$   $\omega_2 - \omega_1$
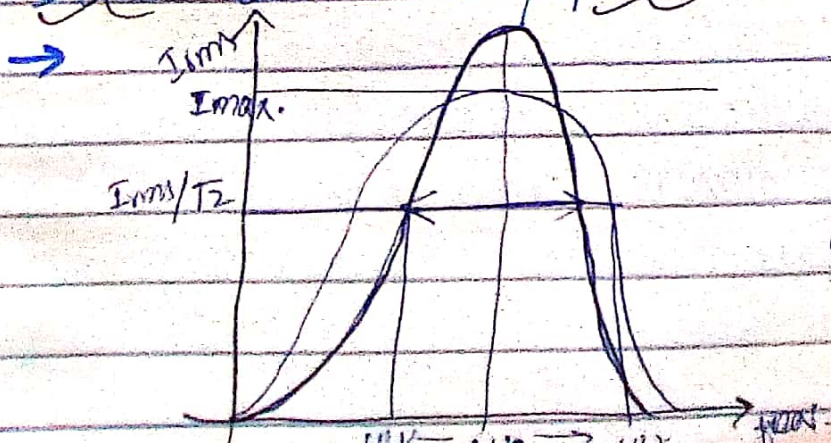
## → Sound Quality (sharpness of tuning) :-

→ Q-factor is physical quantity which tells us better sound quality / at which value of current sound will better / power will better. (I ↑, P ↑, sound quality ↑)



$$\therefore P = I^2 R_{\text{max}}$$

$$\omega_0 = \text{bandwidth} = \text{B.W}$$



B.W ↓, sound ↑ (better)

if  $\omega > \omega_0$   $I_L$ ,  $P_L$ ,  $\cos \phi > 1$ ,  $P_f I \uparrow$ ,  $P_f$ .

→ Q-factor decides how sharp resonance curve / determine sharpness of resonance curve.

→ if  $R \downarrow$ , sharpness  $\uparrow$ . ( $0 \rightarrow 100$  (value of Q-factor))

RLC-circuit:

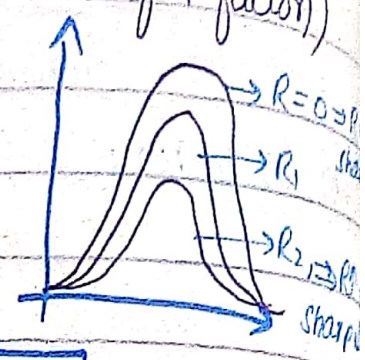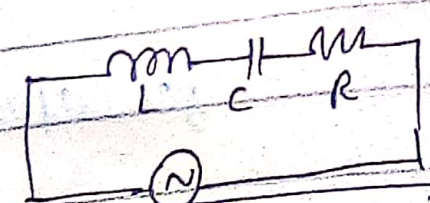

When  $I$  is max. in ckt,  $\therefore Z = \sqrt{R^2 + (X_L - X_C)^2}$


This condition is called resonance. at  $X_L = X_C$ ;  $Z = R$  → purely resistive ckt.

13.4 Linear Transformers:- | Air-Core TIF:- Wednesday  
08-04-2020

"A transformer is generally a four terminal device comprising two magnetically coupled coils."

→ In fig, coil  $L_1$ , is directly coupled to voltage source, is called "primary winding/coil".

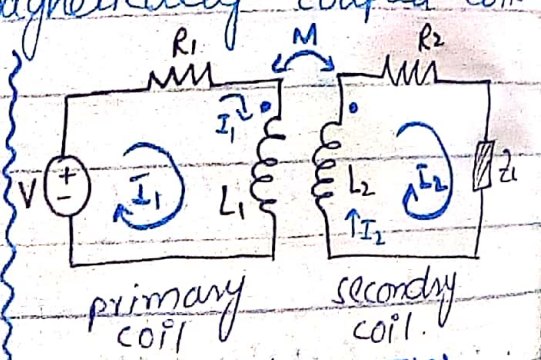→ The coil connected to load  $P_s$  called "secondary coil".



(A linear TIF)

- Resistances  $R_1$  &  $R_2$  are included to account for losses (power dissipation) in coil.
- Transformer is said to be linear; if coils are wound on magnetically linear material.
- A material for which magnetic permeability  $\mu$  is const. e.g.:- air, plastic, wood etc.
- linear magnetic materials are characterized by a linear relation b/w magnetization & magnetic field.



→ Permeability is measure of reactance-material against formation of magnetic field.

→ Linear transformers are sometimes called Air-core transformers. They are used in radio & TV.

⇒ We would like to obtain input impedance  $Z_{in}$  as seen from source, bcz  $Z_{in}$  control behaviour of primary coil.

Applying KVL to both meshes (in fig) :-

**Mesh #1** :-  $-V + I_1 R_1 + L_1 \frac{di_1}{dt} - M \frac{di_2}{dt} = 0$ .

or:  $-V + I_1 R_1 + j\omega L_1 I_1 - j\omega M I_2 = 0$ .

$(R_1 + j\omega L_1) I_1 - j\omega M I_2 = V$  — (1)

**Mesh #2** :-  $I_2 R_2 + I_2 Z_L + j\omega L_2 I_2 - j\omega M I_1 = 0$ .

$(R_2 + Z_L + j\omega L_2) I_2 - j\omega M I_1 = 0$  — (2)

or  $I_2 = \frac{j\omega M I_1}{R_2 + Z_L + j\omega L_2}$  — (3) → put in (1)

(1) ⇒  $(R_1 + j\omega L_1) I_1 - j\omega M \left[ \frac{j\omega M I_1}{R_2 + Z_L + j\omega L_2} \right] = V$   $\because j^2 = -1$

$I_1 \left[ (R_1 + j\omega L_1) - \frac{j^2 \omega^2 M^2}{R_2 + Z_L + j\omega L_2} \right] = V$   $\because \frac{V}{I_1} = Z_{in}$

or  $R_1 + j\omega L_1 + \frac{\omega^2 M^2}{R_2 + Z_L + j\omega L_2} = \frac{V}{I_1} = Z_{in}$

So,

$Z_{in} = R_1 + j\omega L_1 + \frac{\omega^2 M^2}{R_2 + Z_L + j\omega L_2}$  — (4)

1st term is primary impedance

2nd term due to coupling b/w pri. & sec. coils.


→ Notice  $Z_{in}$  consists of 2-terms - However, this impedance is reflected to primary, thus it is known as Reflected Impedance ( $Z_R$ ) or coupled impedance ( $Z_c$ ).

$$\text{i.e.:- } Z_R = \frac{\omega^2 M^2}{R_2 + j\omega L_2 + Z_L} \quad \text{--- (5)}$$

→ It should be noted from results in (4) & (5); they are not affected by location of dots on T/F, bcz same result is produced in (4) & (5) if  $M$  is replaced with  $(-M)$  → bcz of square of  $M (M^2)$

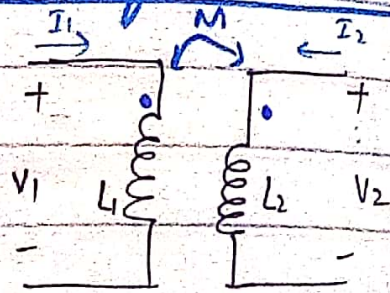
### Determining the equivalent ckt. of a linear T/F:-

For Analysis:- It is sometime convenient to replace a magnetically coupled ckt. by an equivalent ckt. with no



magnetic coupling. We want to fig # 13-21 replace linear T/F in 13-21 by an  $T(Y)$  or  $\bar{\pi}(D)$  ckt. which would have no mutual inductance

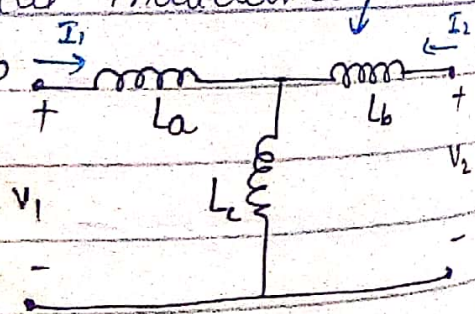→ voltage-current relationship for primary & sec. coil given by applying KVL on both loops for fig # 13-21.



loop #1 :-

$$-V_1 + j\omega L_1 I_1 + j\omega M I_2 = 0$$

$$j\omega L_1 I_1 + j\omega M I_2 = V_1 \quad \text{--- (1)}$$

loop #2 :-

$$-V_2 + j\omega L_2 I_2 + j\omega M I_1 = 0$$

$$j\omega L_2 I_2 + j\omega M I_1 = V_2 \Rightarrow j\omega M I_1 + j\omega L_2 I_2 = V_2$$

Putting these 2 eqn's in matrix form:-

$$\underbrace{\begin{bmatrix} j\omega L_1 & j\omega M \\ j\omega M & j\omega L_2 \end{bmatrix}}_A \underbrace{\begin{bmatrix} I_1 \\ I_2 \end{bmatrix}}_X = \underbrace{\begin{bmatrix} V_1 \\ V_2 \end{bmatrix}}_B \quad \text{--- (6)}$$

$$AX = B$$

$$X = A^{-1}B$$

for  $A^{-1}$ , we change sign of  $\swarrow$  &  $\searrow$  position of  $\downarrow$  (diagonal) divided by det

By matrix inversion:-

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \frac{1}{j^2\omega^2 L_1 L_2 - j^2\omega^2 M^2} \begin{bmatrix} j\omega L_2 & -j\omega M \\ -j\omega M & j\omega L_1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \frac{1}{j^2\omega^2 L_1 L_2 - j^2\omega^2 M^2} \begin{bmatrix} j\omega L_2 & -j\omega M \\ -j\omega M & j\omega L_1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \rightarrow \text{simplify}$$

Taking  $j^2\omega^2$  common.

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} \frac{j\omega L_2}{j^2\omega^2(L_1 L_2 - M^2)} & \frac{-j\omega M}{j^2\omega^2(L_1 L_2 - M^2)} \\ \frac{-j\omega M}{j^2\omega^2(L_1 L_2 - M^2)} & \frac{j\omega L_1}{j^2\omega^2(L_1 L_2 - M^2)} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$


$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} \frac{L_2}{j\omega(L_1 L_2 - M^2)} & \frac{-M}{j\omega(L_1 L_2 - M^2)} \\ \frac{-M}{j\omega(L_1 L_2 - M^2)} & \frac{L_1}{j\omega(L_1 L_2 - M^2)} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \quad \text{--- (7)}$$

→ our main objective is to match eqn (6) & (7) with corresponding eqn for T & π networks -

loop #1:-

$$-V_1 + j\omega L_a I_1 + j\omega L_c (I_1 + I_2) = 0$$
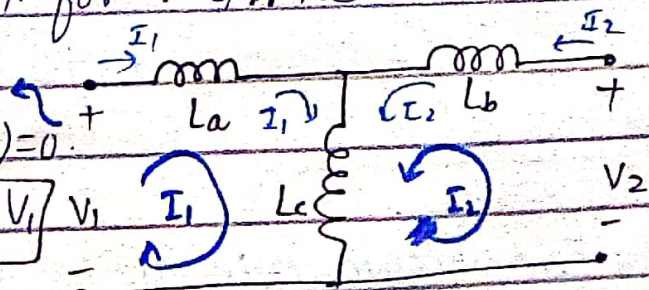
$$\textcircled{2} \quad j\omega (L_a + L_c) I_1 + j\omega L_c I_2 = V_1$$



loop #2:-

$$-V_2 + j\omega L_b I_2 + j\omega L_c (I_2 + I_1) = 0$$

$$j\omega (L_b + L_c) I_2 + j\omega L_c I_1 = V_2$$

$$\text{or } j\omega L_c I_1 + j\omega (L_b + L_c) I_2 = V_2 \quad \text{--- (9)}$$

→ For T/Y network of above fig., mesh analysis provides terminal equations as under in matrix; for (considering eq. (8) & (9)):-

$$\begin{bmatrix} j\omega(L_a + L_c) & j\omega L_c \\ j\omega L_c & j\omega(L_b + L_c) \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \quad (10)$$

If circuits in fig# 13.21 & 13.22 are equivalent in value, then eq. (8) & (10) should be identical.

$$(8) \Rightarrow \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} j\omega L_1 & j\omega M \\ j\omega M & j\omega L_2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$(10) \Rightarrow \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} j\omega(L_a + L_c) & j\omega L_c \\ j\omega L_c & j\omega(L_b + L_c) \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

→ Consider/Evaluating terms in impedance matrices of eq. (8) & (10):-

$$j\omega L_1 = j\omega(L_a + L_c) \quad \& \quad j\omega M = j\omega L_c$$

$L_1 = L_a + L_c \leftarrow \begin{matrix} \text{put in} \\ \leftarrow \end{matrix} \boxed{M = L_c}$   
 So,  $L_1 = L_a + M \rightarrow \boxed{L_a = L_1 - M}$


Similarly:-

$$j\omega M = j\omega L_c \quad \& \quad j\omega L_2 = j\omega(L_b + L_c)$$

$\boxed{M = L_c} \xrightarrow{\text{put in}} \& \quad L_2 = L_b + L_c$   
 $L_2 = L_b + M \rightarrow \boxed{L_b = L_2 - M} \quad \& \quad \boxed{L_c = M}$

→ For  $\pi/\pi$  network in fig# 13.23; we apply nodal analysis:-

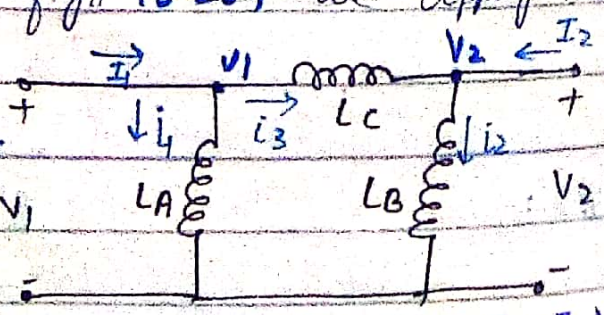By inspection method:-  
at node:  $V_1$ :-



$$I_1 = I_4 + I_3$$

$$I_1 = \frac{V_1 - 0}{X_A} + \frac{V_1 - V_2}{X_C}$$

$$I_1 = \frac{X_C V_1 + X_A (V_1 - V_2)}{X_A X_C}$$

Fig# 13.23 (eq.  $\pi$  net.)

$$I_1 = \frac{V_1(X_C + X_A) - X_A V_2}{X_A X_C} = V_1 \left( \frac{X_C + X_A}{X_A X_C} \right) - \frac{X_A V_2}{X_A X_C}$$

$$I_1 = \left( \frac{1}{X_A} + \frac{1}{X_C} \right) V_1 - \frac{1}{X_C} V_2 \quad \text{--- (a)}$$

or

$$I_1 = \left( \frac{1}{j\omega L_A} + \frac{1}{j\omega L_C} \right) V_1 - \frac{1}{j\omega L_C} V_2 \quad \text{--- (b)}$$

Relat node:  $V_2$  :-

$$I_2 + I_3 = I_2$$

$$I_2 = I_2 - I_3$$

$$I_2 = \left( \frac{V_2 - 0}{X_B} \right) - \left( \frac{V_1 - V_2}{X_C} \right)$$

or

$$I_2 = \frac{X_C V_2 - X_B (V_1 - V_2)}{X_B X_C} = \frac{X_C V_2 - X_B V_1 + X_B V_2}{X_B X_C}$$

$$I_2 = \left( \frac{X_C + X_B}{X_B X_C} \right) V_2 - \frac{X_B V_1}{X_B X_C}$$

$$I_2 = \left( \frac{1}{X_B} + \frac{1}{X_C} \right) V_2 - \frac{V_1}{X_C} = \left( \frac{1}{j\omega L_B} + \frac{1}{j\omega L_C} \right) V_2 - \frac{1}{j\omega L_C} V_1$$

or

$$I_2 = -\frac{1}{j\omega L_C} V_1 + \left( \frac{1}{j\omega L_B} + \frac{1}{j\omega L_C} \right) V_2 \quad \text{--- (c)}$$

re-arrange eqn. (b) & (c) in matrix form.

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} \frac{1}{j\omega L_A} + \frac{1}{j\omega L_C} & -\frac{1}{j\omega L_C} \\ -\frac{1}{j\omega L_C} & \frac{1}{j\omega L_B} + \frac{1}{j\omega L_C} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \quad \text{--- (ii)}$$

Evaluating Terms in Admittance matrices of (i) & (ii) :-

eqn (i) becomes

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} \frac{L_2}{j\omega(L_1 L_2 - M^2)} & \frac{-M}{j\omega(L_1 L_2 - M^2)} \\ \frac{-M}{j\omega(L_1 L_2 - M^2)} & \frac{L_1}{j\omega(L_1 L_2 - M^2)} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \quad \text{--- (i)}$$

## Evaluating Terms:-

$$\frac{L_2}{j\omega(L_1L_2 - M^2)} = \frac{1}{j\omega L_A} + \frac{1}{j\omega L_C} \quad \text{Eq 1} \quad \frac{+M}{j\omega(L_1L_2 - M^2)} = \frac{+1}{j\omega L_C}$$

$$\frac{L_2}{j\omega(L_1L_2 - M^2)} = \frac{1}{j\omega} \left( \frac{1}{L_A} + \frac{1}{L_C} \right) \quad \frac{M}{L_1L_2 - M^2} = \frac{1}{L_C} \quad \text{--- (13) put in (12)}$$

$$\frac{L_2}{L_1L_2 - M^2} - \frac{1}{L_C} = \frac{1}{L_A} \quad \text{--- (12)}$$

$$\frac{L_2}{L_1L_2 - M^2} - \frac{M}{L_1L_2 - M^2} = \frac{1}{L_A} \Rightarrow \frac{L_2 - M}{L_1L_2 - M^2} = \frac{1}{L_A}$$


$$\boxed{L_A = \frac{L_1L_2 - M^2}{L_2 - M}} \quad \text{Eq 1} \quad \boxed{L_C = \frac{L_1L_2 - M^2}{M}}$$

Similarly:-  $\boxed{L_B = \frac{L_1L_2 - M^2}{L_1 - M}}$

Analysis:- Note in fig# 13.22 & 13.23; The inductors are not magnetically coupled & also note that changing location of dots in (13.21) can cause M to become -M.

→ Therefore, eq. model is still mathematically valid

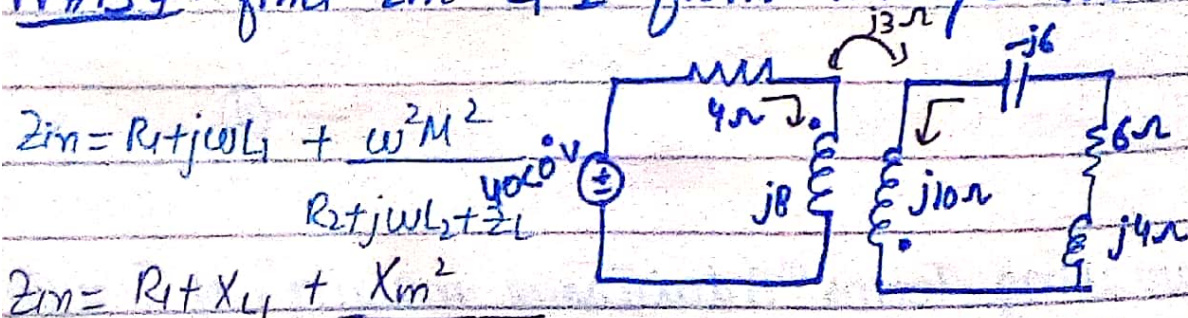PP#13.4:- find  $Z_{in}$  &  $I$  from voltage source.



$$Z_{in} = R_1 + X_{L1} + \frac{X_m^2}{R_2 + j\omega L_2 + Z_L}$$

$$= 4 + j8 + \frac{(3)^2}{j10 - j6 + 6 + j4}$$


$$\therefore \omega = 1 \text{ rad/s}$$

$$X_m^2 = j^2 (3)^2$$

$$Z_{in} = 4 + j8 + 0.54 - j0.72 = 4.57 + j7.28$$

$$\boxed{Z_{in} = 8.58 \angle 58.05^\circ \Omega} \rightarrow I = \frac{40 \angle 0^\circ}{8.58 \angle 58.05^\circ} = \boxed{4.66 \angle -58^\circ}$$

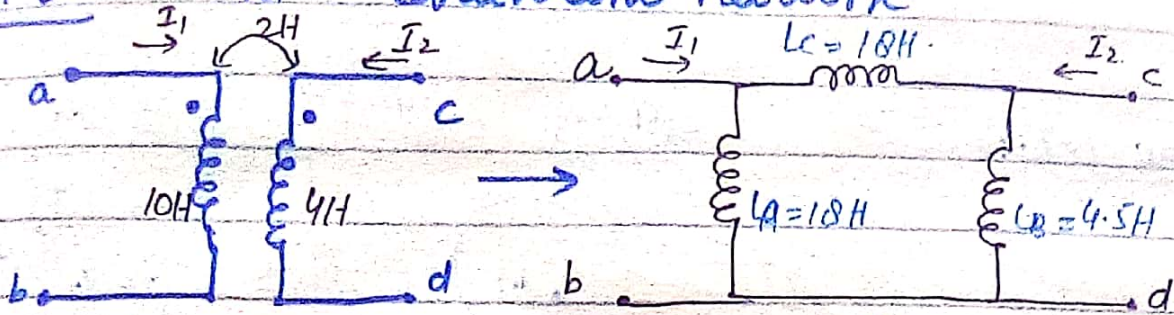PP#13.5:- Find  $\pi$  equivalent network.



Here,  $L_1 = 10H$ ,  $L_2 = 4H$ ,  $M = 2H$ .

( $\pi$ -eq. ckt.)

So,  $L_A = L_1 L_2 - M^2 = (10)(4) - (2)^2 = 18H$

$L_2 - M = 4 - 2$

$L_B = \frac{L_1 L_2 - M^2}{L_1 - M} = \frac{(10)(4) - (2)^2}{10 - 2} = 4.5H$

$L_C = \frac{L_1 L_2 - M^2}{2} = \frac{(10)(4) - (2)^2}{2} = 18H$

for T-eq. ckt.:-

$L_a = L_1 - M$

$L_b = L_2 - M$


$L_c = M$

Ex# 13.6:-  $\xrightarrow{\text{imp}}$  Solve for  $I_1, I_2, V_o$  using T-eq. ckt.



for linear T/F. (Same as PP#13-1)

for T-eq. ckt, we have

To change magnetically coupled coil with

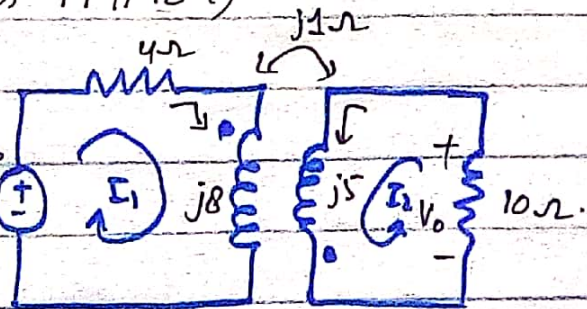

T-ckt. So,

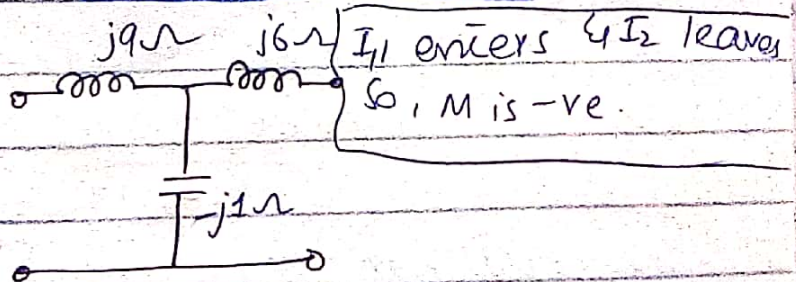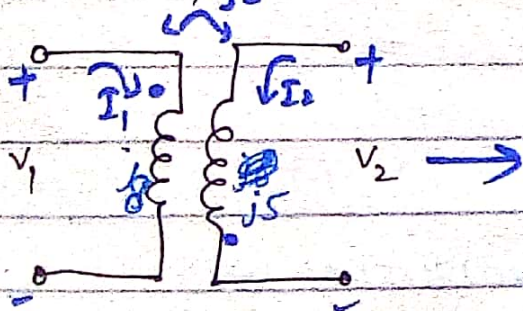

$I_1$  enters &  $I_2$  leaves  
So,  $M$  is -ve.

$L_a = L_1 - M = j8 - (-j1) = j9$

$L_b = L_2 - M = j5 - (-j1) = j6$


$L_c = M = -j1$

for capacitor's capacitance, so we placed capacitor in T-model.

$X_c = \frac{1}{j\omega c} = -j\omega c$

→ Inserting T-eq c.c. in fig 13-29 (given c.c.)  
 then solving using nodal/mesh.

Now, c.c. :-

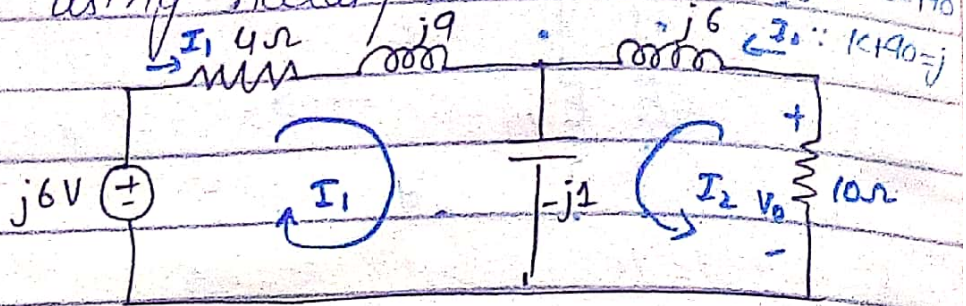

Mesh Analysis :-

Loop#1 :-

$$-j6 + 4I_1 + j9I_1 - j1(I_1 + I_2) = 0$$

$$\boxed{(4 + j8)I_1 + (-j1)I_2 = j6} \quad \text{--- (1)}$$

Loop#2 :-

$$10I_2 + j6I_2 - j1(I_2 + I_1) = 0$$

$$\boxed{(10 + j5)I_2 + (-j1)I_1 = 0} \quad \text{--- (2)}$$

$$-j1I_1 = -(10 + j5)I_2$$

$$I_1 = \frac{(10 + j5)I_2}{j}$$

$$\boxed{I_1 = (5 - j10)I_2} \quad \text{--- (3)}$$

Put (3) in (1) :-

$$j6 = (4 + j8)(5 - j10)I_2 - j1I_2$$

$$(20 - j40 + j40 - j^280)I_2 - j1I_2 = j6$$

$$(20 + 80)I_2 - j1I_2 = j6$$

$$\boxed{(100 - j1)I_2 = j6} \quad \text{--- (4)}$$

100 → real part ; -1 → imaginary part.

So,  $(100 \gg 1) \Rightarrow$  so  $100 - j \approx 100$

$$100I_2 = j6$$

$$I_2 = \frac{j6}{100} = \frac{6 \angle 90^\circ}{100}$$

$$\boxed{I_2 = 0.06 \angle 90^\circ \text{ A}}$$



putting value of  $I_2$  in eq(3):-

$$I_1 = (5 - j10) (0.06 \angle 90^\circ)$$

$$I_1 = (5 - j10) (j0.06)$$

$$I_1 = 0.6 + j0.3 \text{ A}$$

$$\rightarrow V_0 = I_2 R_{\text{load}}$$

$$V_0 = -10 I_2$$


$$V_0 = (-10)(j0.06) = -j0.6$$

$$V_0 = 0.6 \angle -90^\circ \text{ V}$$


$I_2 \rightarrow$  opposite direction  
so -ve.
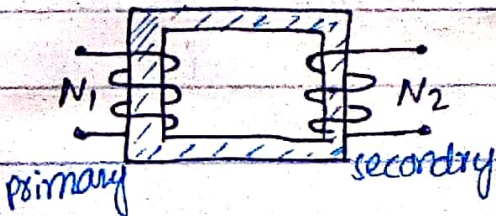
### 13.5 Ideal Transformer:-

"An ideal transformer is a unity-coupled, lossless transformer, in which primary & secondary coils have infinite self-inductance."



ideal T/F

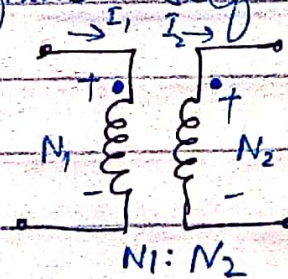

cc: symbol.

Ac only  
 $n=1$

$\rightarrow$  if  $V_2 > V_1 \rightarrow$  step-up T/F

$\rightarrow$  if  $V_2 < V_1 \rightarrow$  step-down T/F

Application:-


\* T/F as an isolation

device to isolate dc b/w two amplifier stages (ac-only)  
 $n=1$

\* T/F as matching device using ideal T/F  
to match speaker to amplifier.

$$\left. \begin{aligned} I_1 &= \frac{V_2}{V_1} = \frac{N_2}{N_1} = n \text{ (turn-ratio)} \\ I_2 &= \frac{V_1}{V_2} = \frac{N_1}{N_2} = \frac{1}{n} \end{aligned} \right\}$$
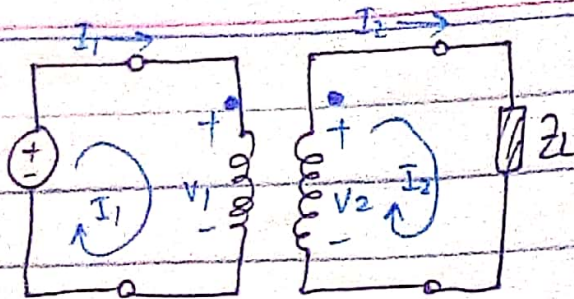
$$\frac{E_2}{I_1} = \frac{N_1}{N_2} = \frac{V_1}{V_2} = \frac{1}{n}$$



$$k = \frac{M}{\sqrt{L_1 L_2}}$$

$$M = k \sqrt{L_1 L_2}$$

$$\left\{ \begin{array}{l} k < 0.5 \\ k = 1 \\ k > 0.5 \end{array} \right\}$$

579(13.31) Relating pri & sec coils quantities is ideal I/F

By KVL:-

$$V_1 = j\omega L_1 I_1 + j\omega M I_2 \quad \text{--- 13.49(a)}$$

$$V_2 = j\omega M I_1 + j\omega L_2 I_2 \rightarrow 13.49(b)$$

$$V_1 - j\omega M I_2 = j\omega L_1 I_1$$

$$I_1 = \frac{V_1 - j\omega M I_2}{j\omega L_1} \quad \text{--- 13.49(c)} \quad \therefore V_L = L \frac{di}{dt}$$

→ put  $I_1$  in 13.49(b) :-

$$V_2 = j\omega M \left( \frac{V_1 - j\omega M I_2}{j\omega L_1} \right) + j\omega L_2 I_2 \quad \therefore \frac{dM}{dt} = M \frac{di_2}{dt} = j\omega M I_2$$

$$V_2 = \frac{M V_1}{L_1} - \frac{j\omega M^2 I_2}{L_1} + j\omega L_2 I_2$$

re-arrange:-

$$V_2 = j\omega L_2 I_2 + \frac{M V_1}{L_1} - \frac{j\omega M^2 I_2}{L_1}$$


BUT  $M = \sqrt{L_1 L_2}$  for perfect coupling ( $k=1$ ) ;

$$V_2 = j\omega L_2 I_2 + \frac{\sqrt{L_1 L_2} \times V_1}{\sqrt{L_1} \cdot \sqrt{L_1}} - j\omega \frac{(\sqrt{L_1 L_2})^2}{L_1} I_2$$

$$V_2 = j\omega L_2 I_2 + \sqrt{\frac{L_2}{L_1}} V_1 - j\omega L_2 I_2$$

$$\boxed{V_2 = \sqrt{\frac{L_2}{L_1}} V_1}$$

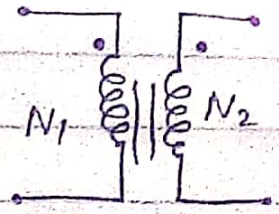
→ Vertical lines b/w coils indicates an iron core as distinct from air core used in linear transformer.



- Primary winding has  $N_1$ -turns.
- Secondary winding has  $N_2$ -turns.

→ in fig# 13.31:-

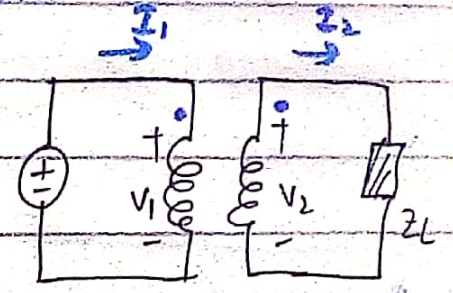when sinusoidal voltage is applied to primary winding, same flux ( $\phi$ ) goes through both winding.



\* Acc. to Faraday's law; voltage across primary;

$$V_1 = N_1 \frac{d\phi_1}{dt} \quad \text{--- 13.50(a)}$$

$$\therefore \phi_1 = \phi_2 = \phi$$

\* Voltage across secondary :-

$$V_2 = N_2 \frac{d\phi_2}{dt} \quad \text{--- 13.50(b)}$$

13.50 (b)  $\div$  by 13.50(a) :-

$$\frac{V_2}{V_1} = \frac{N_2}{N_1} \frac{d\phi/dt}{d\phi/dt}$$

$$\frac{V_2}{V_1} = \frac{N_2}{N_1} = n \quad \text{--- 13.52}$$

$\therefore n$  is turns ratio of transformer ratio.

→ For power conservation, energy supplied to primary must equal to secondary's absorbed power. Since; no losses in ideal T/F:-

$$P_1 = P_2$$

$$\therefore \frac{V_2}{V_1} = n = \frac{N_2}{N_1}$$

$$V_1 I_1 = V_2 I_2 \quad / \quad V_1 I_1 = V_2 I_2 \quad \text{--- 13.53}$$

$$\boxed{\frac{I_1}{I_2} = \frac{V_2}{V_1} = \frac{N_2}{N_1} = n} \quad \text{--- 13.54}$$

→ Similarly, pri & sec currents are related to turn ratio, in inverse manner of voltage

$$\frac{I_2}{I_1} = \frac{N_1}{N_2} = \frac{1}{n} \quad \text{--- 13.55}$$

Note:-

\* when  $n > 1$ , we have step-up T/F, as in.   
 step-up T/F, sec. V > pri. V ( $V_2 > V_1$ ) /  $N_2 > N_1$

\* when  $n = 1$ , T/F is generally named as isolation T/F.

\* when  $n < 1$ , transformer is step-down ( $V_2 < V_1$ )   
 ( $N_2 < N_1$ )

↳ Ratings of T/F are usually specified as  $V_1/V_2 =$



→ Proper polarity of voltage & current Direction:-


Rules:-

1) If  $V_1$  &  $V_2$  both are +ve / both -ve at dotted end, use  $n \rightarrow +ve$ , other-wise (for different conventions of  $V_1, V_2$ ) use  $n \rightarrow -ve$ .


2) If  $I_1$  &  $I_2$  both enter into / both leave from dotted ends, use  $n \rightarrow -ve$ , otherwise (for same convention of  $I_1, I_2$ , both enter dot / leave dot) use  $n \rightarrow +ve$ .

e.g:-

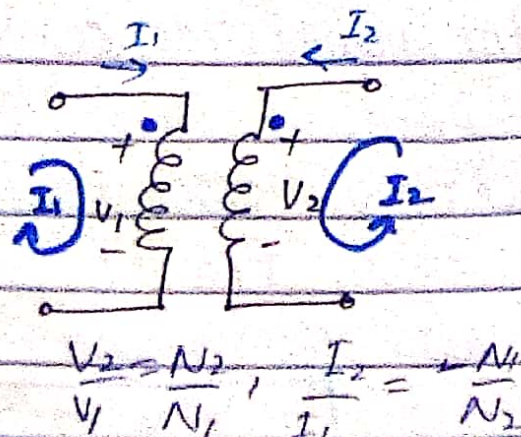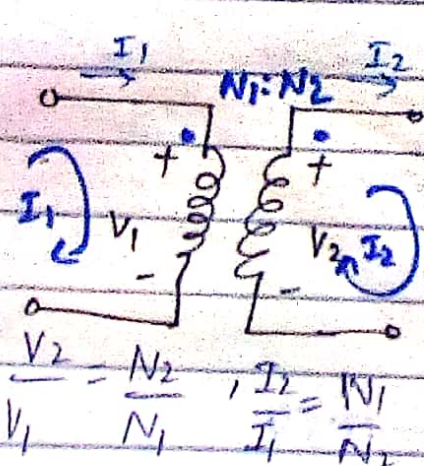

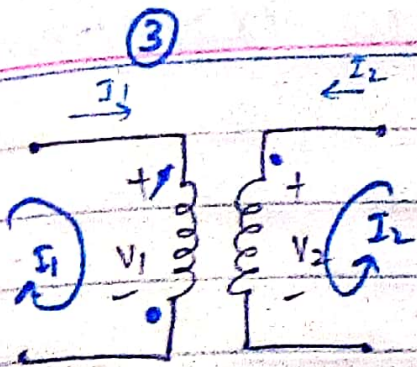
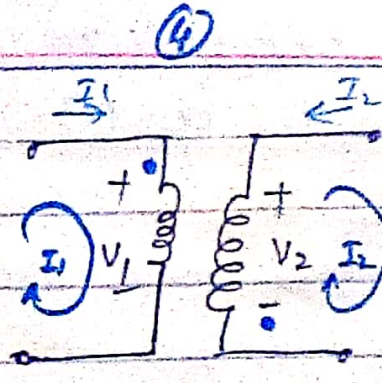
$$\frac{V_2}{V_1} = -\frac{N_2}{N_1}, \quad \frac{I_2}{I_1} = \frac{N_1}{N_2}$$



$$\frac{V_2}{V_1} = -\frac{N_2}{N_1}, \quad \frac{I_2}{I_1} = -\frac{N_1}{N_2}$$

$$\rightarrow \frac{V_2}{V_1} = n$$

$$\rightarrow \frac{I_2}{I_1} = \frac{1}{n}$$

$$V_2 = nV_1, \quad \boxed{V_1 = \frac{1}{n} \cdot V_2} \quad (13.56)$$

$$\boxed{I_2 = \frac{I_1}{n}; \quad I_1 = nI_2} \quad (13.57)$$

→ Complex power in Primary winding :-

$$S_1 = V_1 I_1$$

$$\because V_1 = \frac{V_2}{n} \quad \& \quad I_1 = nI_2$$

So,  $S_1 = \frac{V_2 \times I_2}{n}$

$$S_1 = V_2 \times I_2$$

$$\boxed{S_1 = S_2}$$

→ show complex power supplied to primary is delivered to sec. without any loss. T/F (ideal) absorbs no-power.

$$\because V_1 = V_2/n$$

$$I_1 = nI_2$$

$$\rightarrow Z_{in} = \frac{V_1}{I_1}$$

$$\because \frac{V_2}{I_2} = Z_L$$

So,  $Z_{in} = \frac{V_2 \cdot 1}{n \cdot nI_2}$

$$\boxed{Z_{in} = \frac{Z_L}{n^2}}$$

→ input / reflected impedance.

→ This ability of T/F to transform given impedance into another impedance means us "impedance matching."