

# Chapter 19

## Two-Port Networks.

### Introduction:

What is Port?

"A Pair of terminals through a current may enter or leave a network is known as a Port". "OR"


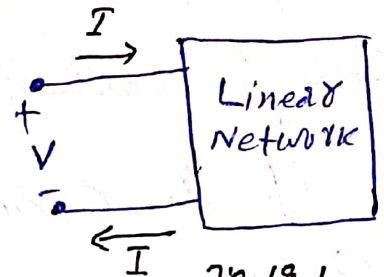
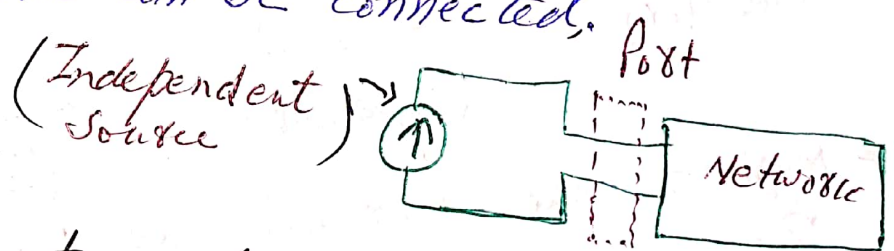


Fig 19.1  
(one-port n/w)

Port: "It is a pair of terminals which connects the electrical circuits or networks to the external circuits."

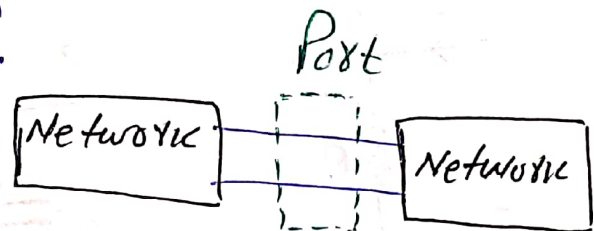So, through this port, any external network or any independent source can be connected to the existing network




**But**

Any two terminals can not be called as a port, and for that, they need to satisfy the port condition.

Port condition :- "If the current ( $I$ ) enter through the one terminal of the port, then the same current ( $I$ )


Should leave through the second terminal of the port.

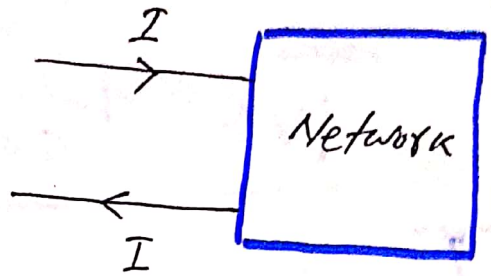So, if the pair of terminal satisfy this condition then they can be called as a Port.




So, if the circuit or the electrical network contains one such port then it called the one-port network

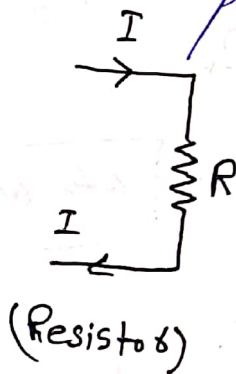
Note All the basic elements like the Resistor, the Capacitor, and the Inductor are the example of one-port n/w.



(Resistor)

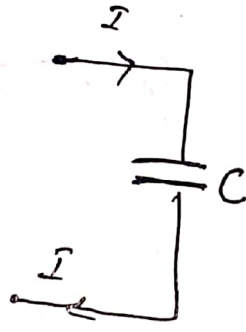

(Capacitor)

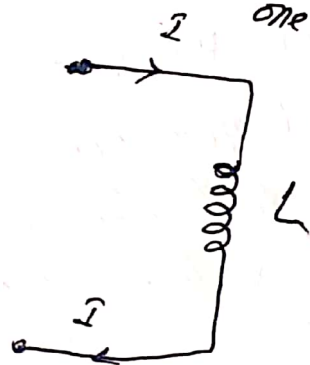

(Inductor)


⇒ Most of the circuits we have dealt with so far are two-terminal or one-port circuits.

⇒ We have also studied four-terminal or two-port circuits involving, Transformers, OP-Amp & transistors & (Diodes),

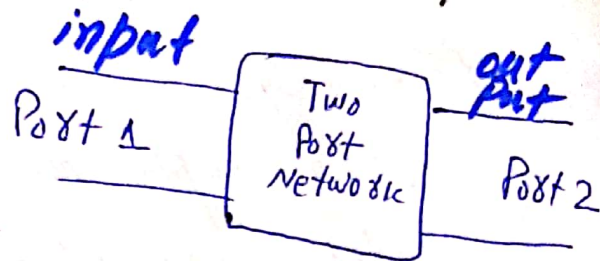
# Definition of Two-Port Network

" A two-port network is an electrical network with two separate ports for input and output.

if the electrical circuit <sup>OR</sup> or the network, <sup>which</sup> contains two ports, then it is called the two-port network."



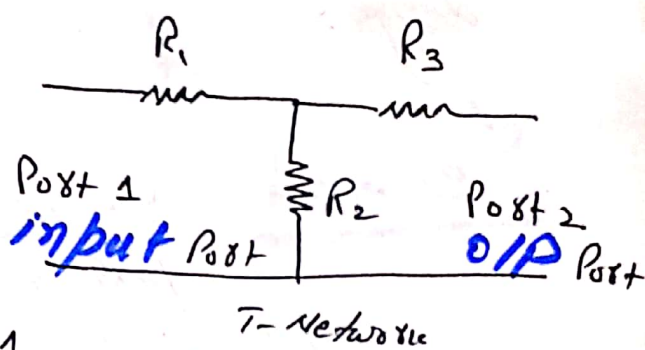
Example. This simple T-network is an example of two-port network.



⇒ In the two-port network, Port 1 is often considered as the **input** port, while the second port (Port 2) is considered as the **output** port.

by using the two-port network model, we can isolate the portion of larger circuits, so, here basically this two-port network is

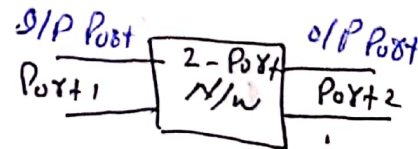regarded as the black box, and the property of this network is specified by some parameters.



## 'Black Box'

A bunch of components, we ~~to~~ don't know what is inside

Note

Our study of two-port network is for at least two seasons.

4

First Such networks are useful in Communication (Signal & system), Control system (Linear Control System), Power system, and Electronics (EDC / ECD).

For example they are used in electronics to model transistor and to facilitate cascaded design.

Second, Knowing the parameters of a two-port network enables us to treat as a "black box", when embedded with in a larger network.

"This allows the response of the network to the signal applied to the ports to be calculated easily, without solving for all the internal voltage & currents in the network"

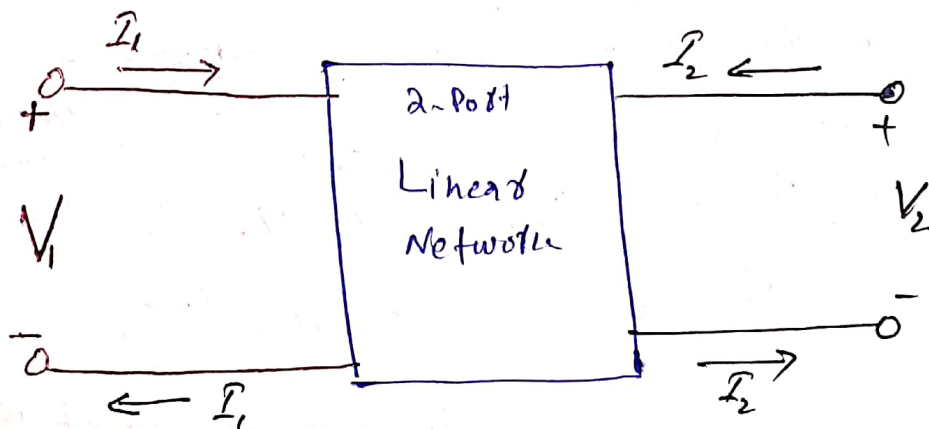


Fig. 19.1 (two-port network)  
Fig. 19.1 (b)

LTI system (Linear Time Invariant)

To characterize a two-port network requires that we relate the terminal quantities  $V_1, V_2, I_1$  &  $I_2$  in fig 19.1 (b), out of which two are independent.\* The various terms that relates these voltages & currents are called Parameters.

We will assume that the two-port circuit contains no independent source, although they can contain dependent sources.

The analysis method, we will discuss require the following condition be met

1. Linearity

2. No independent source inside the network

3. No energy stored inside the network (Zero initial condition)

4.  $I_{1 \text{ entering}} = I_{1 \text{ leaving}}$  &  $I_{2 \text{ entering}} = I_{2 \text{ leaving}}$  (Satisfies the port condition).

⇒ Generally, the n/w is analyzed in s-domain

Independent Variables

⇒  $V_1 = f(I_1, I_2)$  ⇒  $V_1$  &  $V_2$  can be expressed in term of independent variable  $I_1$   
 $V_2 = f(I_1, I_2)$   
 ⇒ BCD ⇒  $V_1 = f(I_1, V_2)$   $V_2$  &  $I_1$  indep  
 $I_2 = f(I_1, V_2)$   $V_1$  &  $I_2$  depen

and based on which variables are independent variables, (6)  
the six different models or the six different  
parameters can be defined for this two-port n/w.

1. Z-Parameters or Impedance Parameters
2. Y-Parameters or Admittance Parameters
3. h-Parameters or Hybrid Parameters
4. ABCD Parameters or Transmission Parameters
5. Inverse Hybrid Parameters
6. Inverse Transmission Parameters.



## 19.2 1 Impedance Parameters OR Z-Parameters

Impedance & admittance parameters are commonly used in the synthesis of filter. (Combination of components)

They are also useful in the design & analysis of impedance-matching networks & power distribution networks.

# Z-Parameters

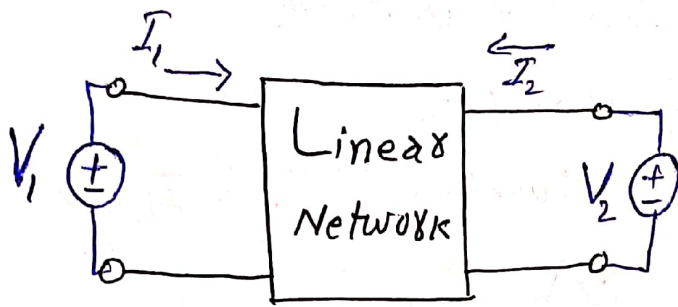


Fig (19.2) (a)

The Linear two-port Network  
(a) driven by voltage source

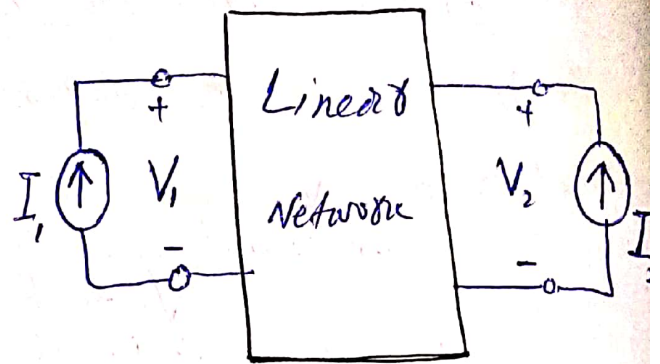


Fig 19.2 (b)

(b) Driven by current source

From either Fig. 19.2 (a) or (b), the terminal voltage can be related to the terminal current as

$$\left. \begin{aligned} V_1 &= Z_{11} I_1 + Z_{12} I_2 \\ V_2 &= Z_{21} I_1 + Z_{22} I_2 \end{aligned} \right\} \rightarrow 19.1$$

$$V = Z I$$

$$Z = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix}$$

or in Matrix form as

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} \Rightarrow V = Z I$$

$$[V] = [Z] [I] \rightarrow 19.2$$

where the Z-term are called the impedance parameters or simply Z-Parameters.

- ⇒ We have four variables  $V_1, V_2, I_1$  &  $I_2$ ,
- ⇒  $V_1$  &  $I_1$  for the Port 1 while
- ⇒  $V_2$  &  $I_2$  for the Port 2
- ⇒ Out of the four variables, the two variables are independent variables, while the remaining two are the

dependent variables, So, for the Z-Parameter the  $I_1$  &  $I_2$  are the independent variables, while the  $V_1$  &  $V_2$  are the dependent variables,

That means  $V_1$  &  $V_2$  are the function of  $I_1$  &  $I_2$  &

$$V_1 = f(I_1, I_2)$$

$$V_2 = f(I_1, I_2)$$

They can be expressed in term of the  $I_1$  &  $I_2$ .  
Be, Remember, two-port network contains only linear elements (i.e) that means the relation of this  $V_1$  &  $V_2$  with  $I_1$  &  $I_2$  is also linear.

So for Z-Parameter

by KVL


$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

This current controlled voltage source depends on current ( $I_2$ ).

$I_2$ . It is current controlled voltage source whose voltage depends on  $I_2$ .

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

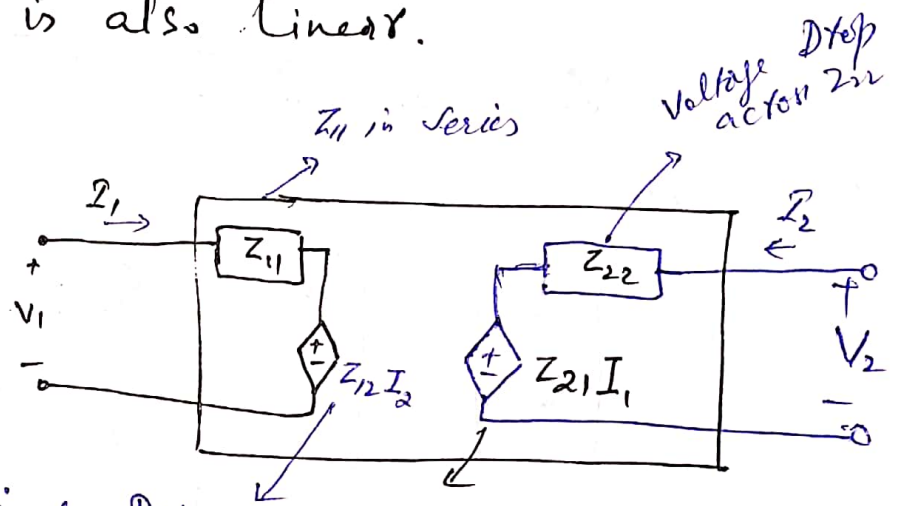Depends on another source (This is dependent voltage source), (Equivalent circuit)



→ This voltage source is depend on  $I_1$

where  $Z_{11}$ ,  $Z_{12}$ ,  $Z_{21}$  &  $Z_{22}$  are Proportionality constants of known as the Z-Parameters.

→  $Z_{21} \times I_1$  is the current-controlled voltage source, So this is the Equivalent circuit of the 2-port network in term of Z-Parameters.



where  $V$  is the matrix of the dependent variables.  $[V] = [Z][I]$  where  $Z$  is the matrix of the independent variables.  $Z$  is the matrix of this Z-Parameters.

So now, we let's see, how we can find the individual Z-Parameters

$$V_1 = Z_{11} I_1 + Z_{12} I_2 \rightarrow 19.1 (a)$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \rightarrow 19.1 (b)$$

So, the individual Z Parameters can be found by setting one of the port currents to zero.

(1) When  $I_2 = 0$  that mean the Port 2 is o.c (open circuit)

So in this condition the Eq 19.1 (a) become


$$V_1 = Z_{11} I_1 + 0$$

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0}$$

Similarly when  $I_2 = 0$ , the Eq 19.1 (b)  $\Rightarrow$  2nd expression

$$V_2 = Z_{21} I_1 + 0$$

$$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0}$$

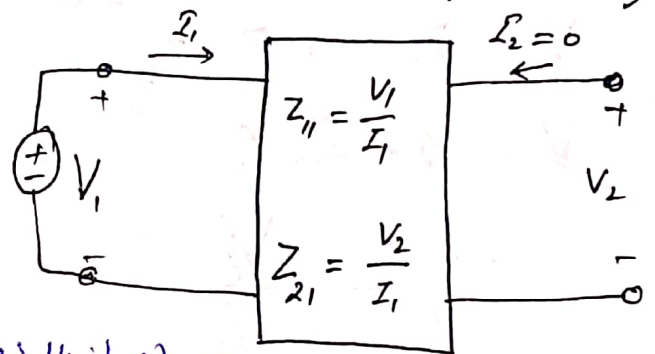

It has unit of Impedance & in fact that is, why it is represented by the symbol  $Z$ , here  $V_1$  in the numerator, the Voltage is on the Port-1, while in the denominator the current on the Port-1 side. & in fact that's why the subscript is  $Z_{11}$  for finding  $Z_{11}$ , the port is open circuit, so, this parameter is known as the open circuit driving point impedance. / I/P Impedance.

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

$\therefore Z_{21}$  is open circuit transfer impedance from Port 2 to Port 1.

So, here in  $Z_{21}$ , the voltage is the Numerator is on the output side or from the Port 2, while the current is in the denominator is on the Port 1 side. So, this parameter is known as the open circuit forward transfer impedance, because it relates the voltage on the output side with the current on the input side.

Similarly

$$\boxed{I_1=0}$$

$\Rightarrow$  When the Port 1 is open circuit (o.c) or  $\boxed{I_1=0}$

By 19.1 (a) becomes

$$I_1=0$$

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_1 = 0 + Z_{12} I_2$$

$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0}$$

(o.c Port 1)

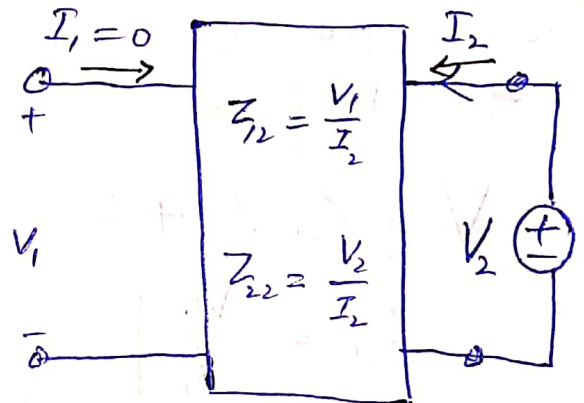


Fig 19.3 (b)

$Z_{12}$  is open circuit transfer impedance from Port 1 to Port 2.

So, this ( $Z_{12}$ ) parameter relates the input voltage with the output current, when port 1 is open-circuited, so this parameter is known as the open circuit reverse transfer impedance.

Now Consider By 19.1 (b),  $I_1=0$ ,

19.1 (b)  $\Rightarrow$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$V_2 = 0 + Z_{22} I_2$$

$$\boxed{I_1=0}$$

$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0} \quad \text{When } I_1=0$$

So ( $Z_{22}$ ) Parameter relates the output voltage with the output current, when port 1 is open-circuited, so, it is known as the open circuit driving point impedance or simply it is known as the output impedance of the two-port network when the port-1 is open-circuited.

All four Parameters

$$\left. \begin{array}{ll} Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0} & Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0} \\ Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0} & Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0} \end{array} \right\} \rightarrow 19.3$$

Since the Z-Parameters are obtained by open-circuiting the in the input or output port, they are also called the open-circuit impedance parameters. Specifically

$Z_{11}$  = open-circuit input Impedance

$Z_{12}$  = open-circuit transfer impedance from port 1 to port 2

$Z_{21}$  = open-circuit transfer impedance from port 2 to port 1

$Z_{22}$  = open-circuit output Impedance.

# Properties of 2-Port N/W.


- (i)  $Z_{11} = Z_{22}$  Symmetrical
- (ii)  $Z_{12} = Z_{21}$  Reciprocal.

Now, there are certain Properties of the two-port network, which frequently also occur in the practical networks, and using these Properties the network can be analyzed quite easily. These Properties are Reciprocity and Symmetry

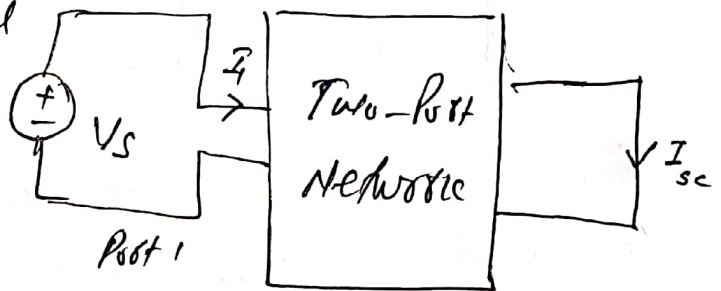
## Reciprocal

" what is Reciprocal Network "

Let us have applied the supplied voltage  $V_s$  at Port 1 & we are measuring the short circuit current at the Port 2. Now, if the N/W is reciprocal then we should get the same short circuit current at Port 1, when the supply voltage  $V_s$  at the Port 2.



or in other words

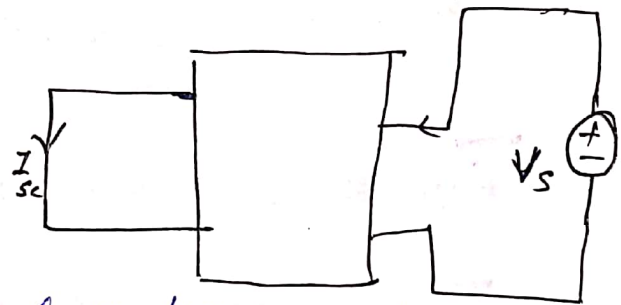

A Two-Port network is said to be a Reciprocal network, if the ratio of excitation at one Port to the response at other port is same, if the excitation and the response are interchanged.

Condition for Reciprocity

if  $Z_{12} = Z_{21}$

So, The two-port network is said to be reciprocal if  $Z_{12}$  is equal to  $Z_{21}$ , so if we know the Z-Parameters of any network & if this condition gets satisfied then we can say that the given two-port network is the reciprocal network.

So Now, Lets Prove this condition (For understanding).

Let say we have applied the supply the voltage  $V_s$  at Port 1 we are measuring the short circuit current at the Port 2

Here  $V_1 = V_s$   
 $I_2 = -I_2'$  ,  $V_2 = 0$

So Port 2 is short-circuited, so the voltage  $V_2 = 0$

Eq 19.1  $\Rightarrow$

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_s = Z_{11} I_1 - Z_{12} I_2'$$

Similarly  $V_2 = Z_{21} I_1 + Z_{22} I_2 \rightarrow 1^{st}$   
 $V_2 = 0 = Z_{21} I_1 - Z_{22} I_2' \rightarrow 2^{nd}$

we are interested to find the ratio of  $V_s$  &  $I_2'$ . That means the ratio of excitation ( $V_s$ ) to the response, so, let find the value of  $I_1$  in term of  $I_2'$ , consider the 2nd expression

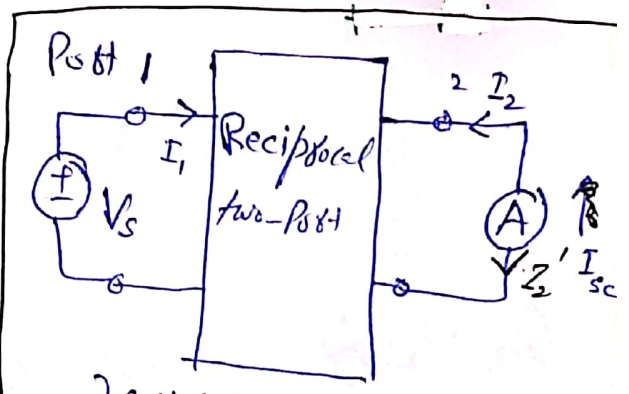


Fig 19.4 (a)

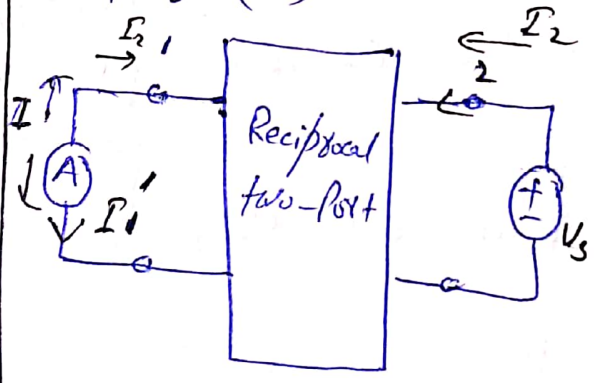


Fig 19.4 (Interchanging a voltage source at one port with an ideal Ammeter at the other port produces the same reading in a Reciprocal 2-port)

$$Z_{21} I_1 - Z_{22} I_2' = 0$$

$$Z_{21} I_1 = Z_{22} I_2'$$

$$I_1 = \left( \frac{Z_{22}}{Z_{21}} \right) \cdot I_2'$$

Now we will put the value of  $I_1$  in 1st Expression

$$V_s = Z_{11} I_1 - Z_{12} I_2'$$

$$V_s = Z_{11} \left( \frac{Z_{22}}{Z_{21}} \right) \cdot I_2' - Z_{12} I_2'$$

LCM

$$V_s = \left( \frac{Z_{11} Z_{22} - Z_{12} Z_{21}}{Z_{21}} \right) \cdot I_2'$$

$$\frac{V_s}{I_2'} = \frac{Z_{11} Z_{22} - Z_{12} Z_{21}}{Z_{21}} \rightarrow \textcircled{1}$$

### Similarly

Consider the fig 19.4 (b)  $\Rightarrow$  Port 1 /  $I_1$  is s.c  
& Excitation applied to Port 2

In this condition:  $V_1 = 0$  due to  $I_1'$  short circuit

Putting all these values in Eq 19.1  $\Rightarrow$   
 $V_2 = V_s$  &  $I_1 = -I_1'$

$$V_1 = Z_{11} I_1 + Z_{12} I_2 \Rightarrow 0 = -Z_{11} I_1' + Z_{12} I_2 \rightarrow \textcircled{2}$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \Rightarrow V_s = -Z_{21} I_1' + Z_{22} I_2 \rightarrow \textcircled{3}$$

Now once again here we are interested to finding the ratio of Voltage ( $V_s$ ) &  $I_1'$ , i.e. the ratio of Excitation to the Response

First we will find the value of  $I_2$  from Eq (1) (15)

$$\text{Eq (1)} \Rightarrow Z_{11} I_1' = Z_{12} I_2$$

$$I_2 = \left( \frac{Z_{11}}{Z_{12}} \right) I_1' \rightarrow (4)$$

Putting the value of  $I_2$  in Eq (2) to get  $\left( \frac{V_s}{I_1'} \right)$ .

$$\text{Eq (2)} \Rightarrow V_s = -Z_{21} I_1' + Z_{22} I_2$$

$$V_s = -Z_{21} I_1' + Z_{22} \times \left( \frac{Z_{11}}{Z_{12}} \right) I_1'$$

$$V_s = \left( \frac{-Z_{12} Z_{21} + Z_{11} Z_{22}}{Z_{12}} \right) I_1'$$

$$V_s = \left( \frac{Z_{11} Z_{22} - Z_{12} Z_{21}}{Z_{12}} \right) I_1'$$

The ratio

$$\frac{V_s}{I_1'} = \frac{Z_{11} Z_{22} - Z_{12} Z_{21}}{Z_{12}} \rightarrow (5)$$

So if the two-port network is reciprocal

then these two ratios of the Eq no. (1) & Eq (5) should be equal.

$$\Rightarrow \frac{V_s}{I_1'} = \frac{V_s}{I_2'}$$

Putting Values

$$\frac{Z_{11} Z_{22} - Z_{12} Z_{21}}{Z_{12}} = \frac{Z_{11} Z_{22} - Z_{12} Z_{21}}{Z_{21}}$$

if  $Z_{12} = Z_{21}$

$$Z_{12} = Z_{21}$$

that means if this condition gets satisfied then we can say the network is Reciprocal

# 2) Symmetrical Network

When  $Z_{11} = Z_{22}$ , the two port network is said to be symmetrical. This implies that the network has mirror like symmetry about some center line; that is a line can be found that divides the network into two similar halves.



## Detail Symmetrical Network <sup>"OR"</sup>

"A two-port network is said to be symmetrical network, if the ratio of voltage to the current at one port is same as the ratio of the voltage to the current at the other port, with one of the port open circuited."

∴

$$\frac{V_1}{I_1} \Big|_{I_2=0} = \frac{V_2}{I_2} \Big|_{I_1=0}$$



Input Impedance = O/P Impedance

$$Z_{11} = Z_{22}$$

Proof

$$V_1 = Z_{11} I_1 + Z_{12} I_2 \Rightarrow \frac{V_1}{I_1} = Z_{11} \Big|_{I_2=0}$$

Let Assume  $I_2 = 0$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \Rightarrow I_1 = 0 \quad Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0}$$

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0} = \frac{V_2}{I_2} \Big|_{I_1=0} = Z_{22}$$

both Ratio should be equal


$$\boxed{Z_{11} = Z_{22}}$$


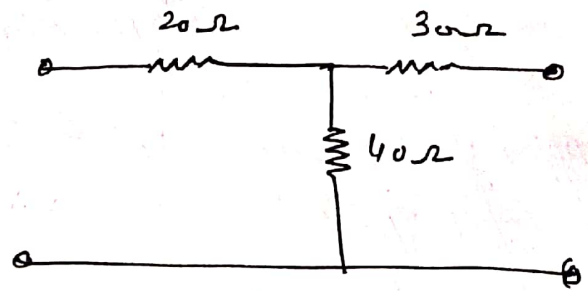
# Example 19.1

(F6)  
(17)

Determine the Z Parameter for the circuit in Fig 19.7



To determine  $Z_{11}$  &  $Z_{21}$ , we apply a voltage source  $V_1$  to the input port and leave the output port open as Fig 19.8(a)

then

$$Z_{11} = \frac{V_1}{I_1} =$$

$$Z_{11} = \frac{(20 + 40) I_1}{I_1}$$

$$Z_{11} = 60 \Omega$$

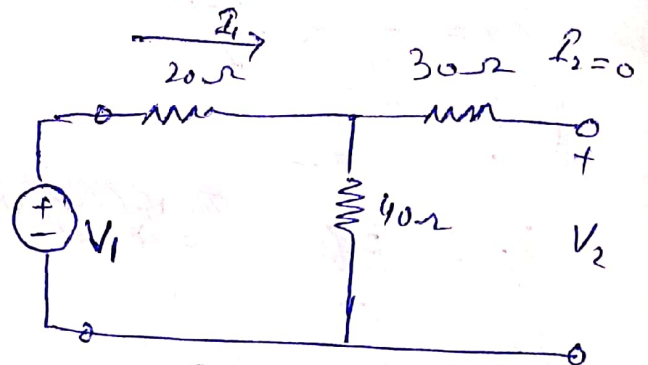


Fig 19.8(a)

i.e.  $Z_{11}$  is the input impedance at port 1.

$$Z_{21} = \frac{V_2}{I_1} = \frac{40 I_1}{I_1} \rightarrow \text{voltage across } 40 \Omega \text{ resistor}$$

$$Z_{21} = 40 \Omega$$

check

To find  $Z_{12}$  &  $Z_{22}$ , we apply a voltage  $V_2$  to the output port and leave the input port as open. Fig 19.8(b)

$$Z_{12} = \frac{V_1}{I_2} = \frac{40 I_2}{I_2} = 40 \Omega$$

$$Z_{12} = 40 \Omega$$

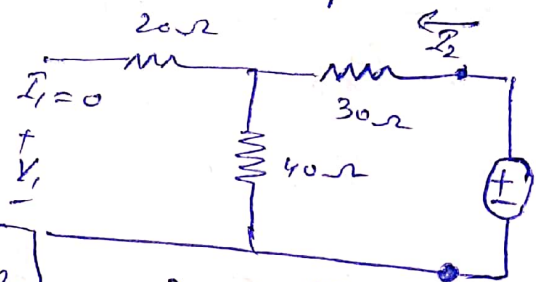


Fig 19.8(b)

$$Z_{22} = \frac{V_2}{I_2} = \frac{(30 + 40) I_2}{I_2}$$

$$Z_{22} = 70 \Omega$$


$$Z_{21} = Z_{12}$$

Reciprocal

$$\Rightarrow [Z] = \begin{bmatrix} 60 \Omega & 40 \Omega \\ 40 \Omega & 70 \Omega \end{bmatrix}$$

P.P 19.1 Find the Z-Parameters of (10)

The two-port Network in Fig. 19.9

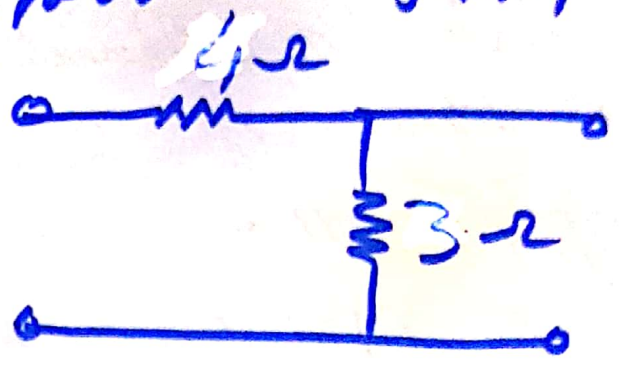

Similar fashion as Example 19.1  
 $I_2 = 0$   
 Apply Voltage source  $V_1$  to the input port

$$V_1 = (4 + 3)I_1$$


$$Z_{11} = \frac{V_1}{I_1} = \frac{7I_1}{I_1}$$

$$Z_{11} = 7 \Omega$$


The voltage  $V_2$

$$Z_{21} = \frac{3I_1}{I_1}$$

$$Z_{21} = 3 \Omega$$

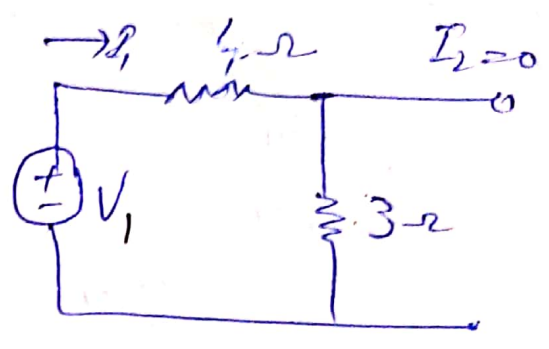

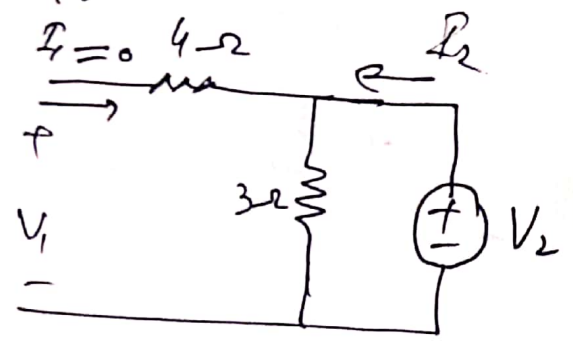To determine  $Z_{12}$  &  $Z_{22}$  apply  $V_2$  to the OP & leave the input port as open. The



$$V_2 = 3I_2$$

$$Z_{22} = \frac{V_2}{I_2} = \frac{3I_2}{I_2}$$

$$Z_{22} = 3 \Omega$$

The voltage  $V_1$  is

$$V_1 = 3I_2$$

$$Z_{12} = \frac{V_1}{I_2} = \frac{3I_2}{I_2}$$

$$Z_{12} = 3 \Omega$$


Ex. 19.1 SAME

The Z-parameter for the two-port N/w is

$$Z = \begin{bmatrix} 7 \Omega & 3 \Omega \\ 3 \Omega & 3 \Omega \end{bmatrix}$$

# Example 19.2 Find $I_1$ & $I_2$ (19)

in the circuit in Fig 19.10

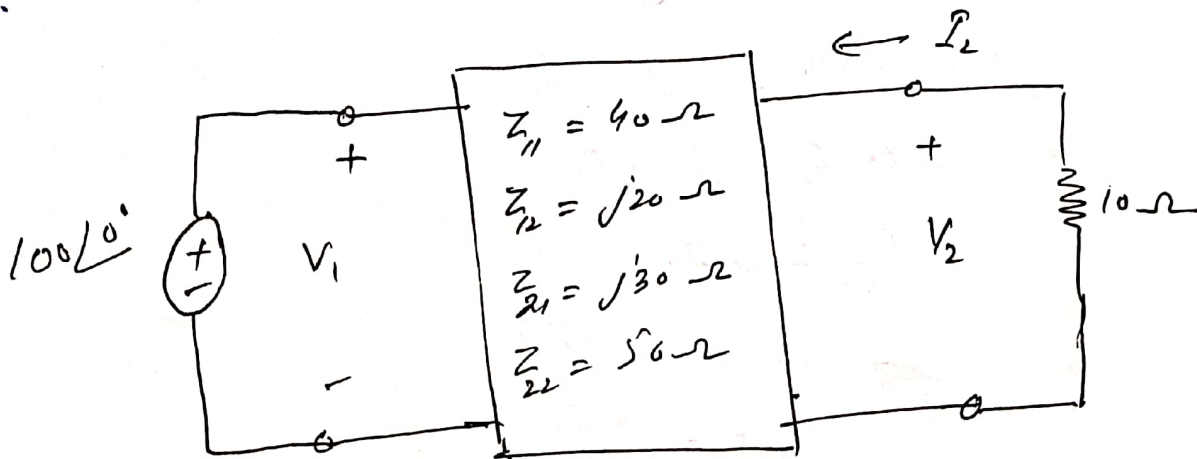


Solution

This is not a reciprocal network because  $Z_{12} \neq Z_{21}$ .  
we may use the equivalent circuit in Fig 19.5 (b)

$$\text{Eq (19.1)} \Rightarrow \begin{aligned} V_1 &= Z_{11} I_1 + Z_{12} I_2 \quad \rightarrow \textcircled{1} \\ V_2 &= Z_{21} I_1 + Z_{22} I_2 \quad \rightarrow \textcircled{2} \end{aligned}$$

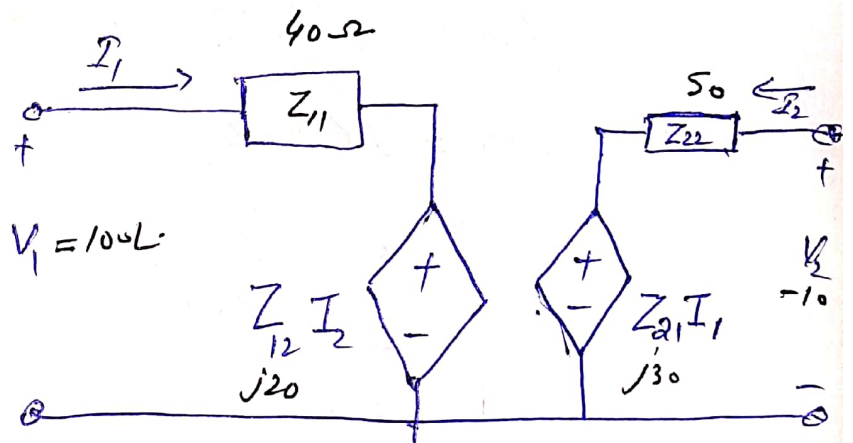Substituting the given Z-parameters in Eq No. (1) & (2) respectively



$$\Rightarrow \begin{aligned} V_1 &= 40 I_1 + j20 I_2 \quad \rightarrow \textcircled{3} \\ V_2 &= j30 I_1 + 50 I_2 \quad \rightarrow \textcircled{4} \end{aligned}$$

Since we are looking for  $I_1$  &  $I_2$ , we substitute

$$V_1 = 100 \angle 0^\circ \quad \& \quad V_2 = -10 I_2$$

Substitute the value of  $V_1$  &  $V_2$  in Eq (3) & (4).

→ Devices that deliver power have negative power values

Eq (3)  $\Rightarrow$

$$100 = 40 I_1 + j20 I_2 \rightarrow (5)$$

Eq (4)  $\Rightarrow$

$$-10 I_2 = j30 I_1 + 50 I_2$$

$$-10 I_2 - 50 I_2 = j30 I_1$$

$$-60 I_2 = j30 I_1$$

$$-\frac{60}{30} I_2 = j I_1$$

$$j I_1 = -2 I_2$$

$$I_1 = -\frac{2 I_2}{j} \times \frac{j}{j}$$

$$I_1 = j^2 I_2 \rightarrow (6)$$

Putting the value of  $I_1$  in Eq (5)

Eq (5)  $\Rightarrow$

$$100 = 40 (j^2 I_2) + j20 I_2$$

$$100 = j^2 80 I_2 + j20 I_2$$

$$100 = j^2 100 I_2$$

$$I_2 = \frac{100}{j^2 100} = -j$$

$$I_2 = -j$$

From Eq (6)  $\Rightarrow I_1 = j^2 (I_2)$

Putting the value of  $I_2$

$$I_1 = j^2 (-j)$$

$$I_1 = -j^2 2$$

$$I_1 = 2$$

$$I_1 = 2 \angle 0^\circ$$

$$I_2 = 1 \angle 90^\circ$$

A

# Practice Problem B.2


(Example 19.2 Do Your self)  
Easy & self  
Same as PP18.2

24

Calculate  $I_1$  &  $I_2$  in the two-Port of given circuit

Solution

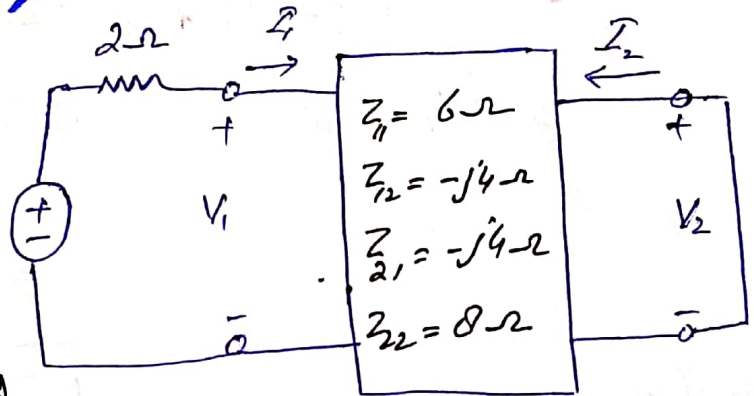The given network is a Reciprocal network  
(thus, T-equivalent ckt)



$$V_1 = Z_{11} I_1 + Z_{12} I_2 + 2I_1 \quad \& \quad V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$2\angle 30^\circ = 6I_1 - j^4 I_2 \rightarrow (1)$$

$$0 = -j^4 I_1 + 8I_2 \rightarrow (2)$$

Eq (2) becomes

$$8I_2 = j^4 I_1$$

$$I_2 = \frac{j^4}{8} I_1 \Rightarrow \frac{j}{2} I_1$$

$$I_2 = \frac{j}{2} I_1$$

Putting the value of  $I_2$  in Eq (1)

$$2\angle 30^\circ = 6I_1 - j^4 \left( \frac{j}{2} I_1 \right) + 2I_1$$

$$2\angle 30^\circ = 6I_1 - j^2 \frac{4}{2} I_1 + 2I_1$$

$$2\angle 30^\circ = 6I_1 + 2I_1 + 2I_1$$

$$2\angle 30^\circ = 8I_1 + 2I_1$$

$$I_1 = \frac{2\angle 30^\circ}{10}$$

$$I_1 = 0.2\angle 30^\circ$$

$$\Rightarrow I_1 = 200\angle 30^\circ$$

Similarly short  $V_1$  & use  $V_2$  as source.

$$\boxed{V_1 = 0}$$

$$\boxed{V_2 = V_s}$$

242

$$V_1 = Z_{11} I_1 + Z_{12} I_2 + 2 I_1$$

$$0 = 6 I_1 + (-j4) I_2 + 2 I_1$$

$$0 = 8 I_1 - j4 I_2$$

$$8 I_1 = j4 I_2$$

$$I_1 = \frac{j4}{8} I_2$$

$$I_1 = j \frac{1}{2} I_2$$

$$\boxed{I_1 = \frac{j}{2} I_2}$$

IV.

and by

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$V_2 = -j4 I_1 + 8 I_2$$

$$V_2 = -j4 \left( \frac{j}{2} I_2 \right) + 8 I_2$$

$$V_2 = -j^2 2 I_2 + 8 I_2$$

$$V_2 = 2 I_2 + 8 I_2$$

Putting  $I_1 = \frac{j}{2} I_2$

Suppose  $\boxed{V_2 = 1 \text{ V}}$

$1 \angle 120^\circ \text{ V}$

$$1 \angle 120^\circ = 10 I_2 =$$

$$I_2 = \frac{1}{10} \angle 120^\circ$$

$$I_2 = 0.1 \angle 120^\circ$$

$$\Rightarrow \boxed{I_2 = 100 \text{ mA}}$$

19.3

# Admittance Parameters (23)

In either 19.12 (a) / b, the terminal currents can be expressed in term of the terminal voltage as

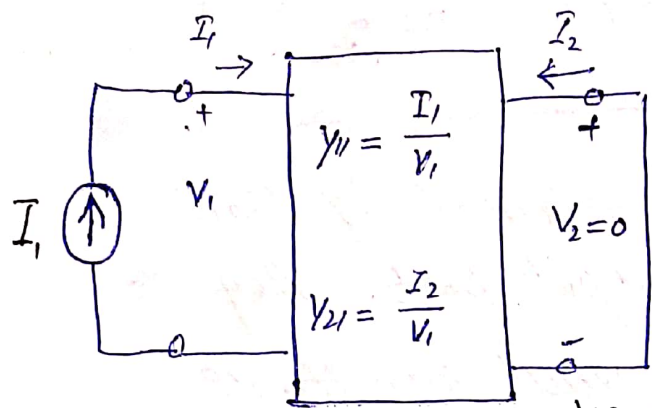


Fig 19.12 (a)  
Finding  $Y_{11}$  &  $Y_{21}$

Port 2 is short circuit

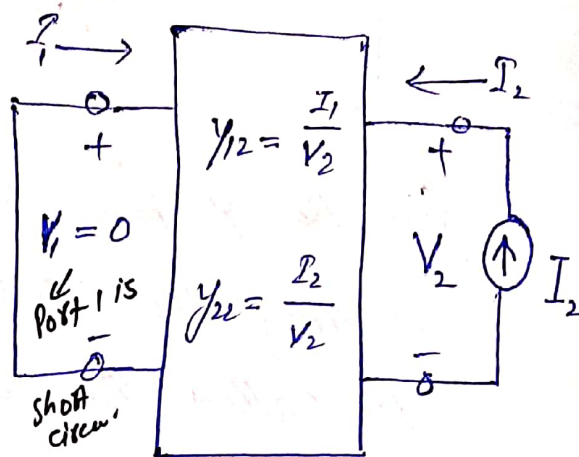


Fig 19.12 (b) Finding  $Y_{12}$  &  $Y_{22}$

$$\begin{cases} I_1 = Y_{11} V_1 + Y_{12} V_2 \\ I_2 = Y_{21} V_1 + Y_{22} V_2 \end{cases} \rightarrow (19.8)$$

or in matrix form

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$[I] = [Y][V] \rightarrow 19.9$$

The  $Y$  term are known as the admittance parameter or simply  $Y$ -parameters & have unit of Siemens.

The values of the parameter can be determine by setting  $V_1 = 0$  input port short-circuited.

or  $V_2 = 0$  (output port short-circuited). Page 24

Then

$$\begin{aligned}
 Y_{11} &= \frac{I_1}{V_1} \Big|_{V_2=0} & Y_{12} &= \frac{I_1}{V_2} \Big|_{V_1=0} \\
 Y_{21} &= \frac{I_2}{V_1} \Big|_{V_2=0} & Y_{22} &= \frac{I_2}{V_2} \Big|_{V_1=0}
 \end{aligned}$$

→ 19.10

Since the  $Y$ -Parameter are obtained by short-circuiting the input or output port, they are also called the "short-circuit admittance parameters", specifically.

(short-circuit driving point admittance, or)

- $Y_{11}$  = Short-circuit Input Admittance
- $Y_{12}$  = Short-circuit transfer admittance from Port 2 to Port 1
- $Y_{21}$  = Short-circuit transfer admittance from Port 1 to Port 2
- $Y_{22}$  = Short-circuit output admittance.

Equivalent circuit

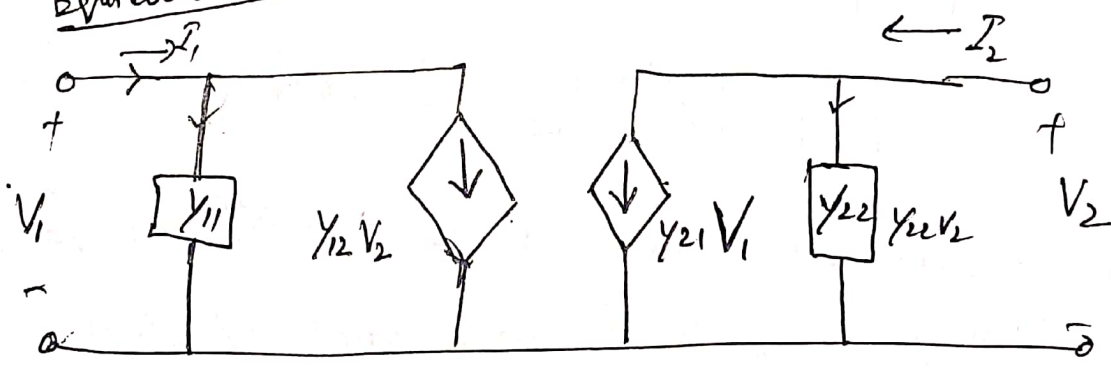


Fig. 19.13 (General Equivalent Circuit)




Extra

# Detail of Y-Parameter

(25)

In two port N/w there are four variables

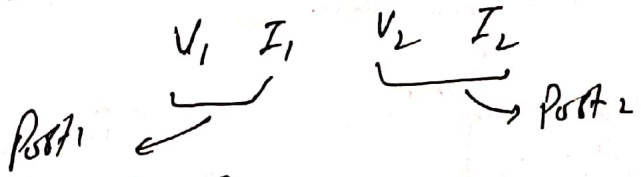

2 - are Independent  
2 - are dependent

For Y-parameter the voltage  $V_1$  &  $V_2$  are the Independent Variable, while  $I_1$  &  $I_2$  are the dependent variable

$$I_1 = f(V_1, V_2)$$

$$I_2 = f(V_1, V_2)$$

that mean  $I_1$  &  $I_2$  are the function of  $V_1$  &  $V_2$ .

incoming current  $\leftarrow I_1 = Y_{11} V_1 + Y_{12} V_2$  &  $I_2 = Y_{21} V_1 + Y_{22} V_2$

It is Voltage Controlled Current Source


So, here  $Y_{12} \cdot V_2$ , it is dependent

source & to be precise it is

Voltage-Controlled Current Source (VCCS) in this source, the value of the current depends on the voltage at port 2.

Reciprocal Network  $Y_{12} = Y_{21}$  Same current

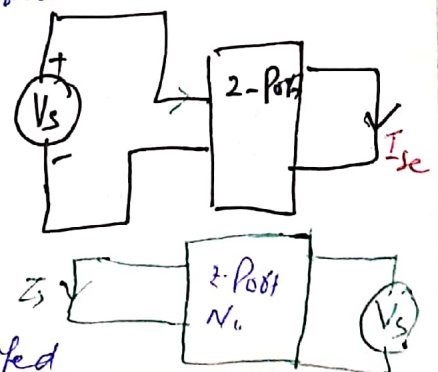"A network is said to be a Reciprocal network, if the ratio of excitation at one port to the response at another port is same, if the excitation and the response are interchanged."



# Example 19.3

obtain the  $Y$ -Parameter for the  $\pi$  network shown in Fig 19.14 (26)

Solution

To find  $Y_{11}$  &  $Y_{21}$ , short-circuit the output port and connect

a current source  $I_1$  to the input port as Fig 19.15(a)

Since  $8\Omega$  resistor is short-circuited, the  $2\Omega$  resistor is in parallel with  $4\Omega$  resistor.

$$2 \parallel 4 = \frac{2 \times 4}{6} = \frac{8}{6} = \frac{4}{3}$$

$$V_1 = I_1 (4 \parallel 2)$$

$$V_1 = \frac{4}{3} I_1$$

$$Y_{11} = \frac{I_1}{V_1} = \frac{\frac{I_1}{\frac{4}{3} I_1}}{\frac{4}{3} I_1} = \frac{3}{4} \text{ S} \rightarrow \text{Siemens (Unit)}$$

$$\boxed{Y_{11} = \frac{3}{4} \text{ S}}$$

$$\Rightarrow \boxed{Y_{11} = 0.75 \text{ S}}$$

By C.D.R

$$-I_2 = \frac{4}{4+2} \times I_1$$

$$\boxed{-I_2 = \frac{2}{3} I_1}$$

$$\Rightarrow \boxed{I_2 = -\frac{2}{3} I_1}$$

$$Y_{21} = \frac{I_2}{V_1} = \frac{-\frac{2}{3} I_1}{\frac{4}{3} I_1} = -\frac{2}{4} = -\frac{1}{2} = -0.5 \text{ S}$$

$$\boxed{Y_{21} = -0.5 \text{ S}}$$

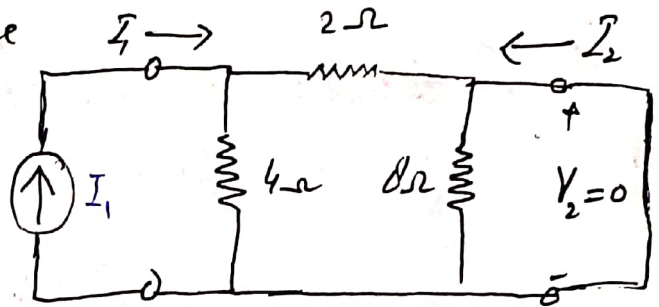
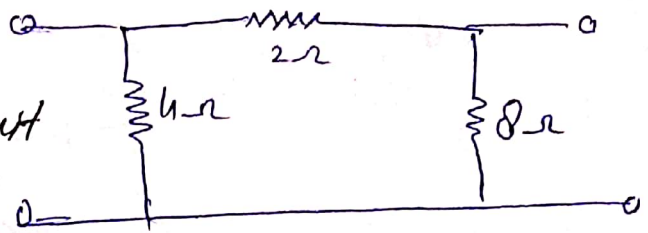


Fig 19.15 (finding  $Y_{11}$  &  $Y_{21}$ )

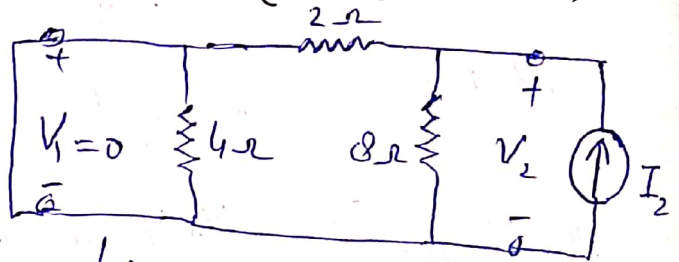


Fig 19.5 b (finding  $Y_{12}$  &  $Y_{22}$ )

# Example 19.3

obtain the  $Y$ -Parameter for the  $\pi$  network shown in Fig 19.14

(20)

Solution

To find  $Y_{11}$  &  $Y_{21}$ , short-circuit the output port and connect

a current source  $I_1$  to the input port as Fig 19.15(a)

Since  $8\Omega$  resistor is short-circuited, the

$2\Omega$  resistor is in parallel with  $4\Omega$  resistor.

$$2 \parallel 4 = \frac{2 \times 4}{6} = \frac{8}{6} = \frac{4}{3}$$

$$V_1 = I_1 (4 \parallel 2)$$

$$V_1 = \frac{4}{3} I_1$$

$$Y_{11} = \frac{I_1}{V_1} = \frac{I_1}{\frac{4}{3} I_1} = \frac{3}{4} \text{ S} \rightarrow \text{Siemens (unit)}$$

$$\boxed{Y_{11} = \frac{3}{4} \text{ S}}$$

$$\Rightarrow \boxed{Y_{11} = 0.75 \text{ S}}$$

By C.D.R

$$-I_2 = \frac{4}{4+2} \times I_1$$

$$\boxed{-I_2 = \frac{2}{3} I_1}$$

$$\Rightarrow \boxed{I_2 = -\frac{2}{3} I_1}$$

$$Y_{21} = \frac{I_2}{V_1} = \frac{-\frac{2}{3} I_1}{\frac{4}{3} I_1} = -\frac{2}{4} = -\frac{1}{2} = -0.5 \text{ S}$$

$$\boxed{Y_{21} = -0.5 \text{ S}}$$

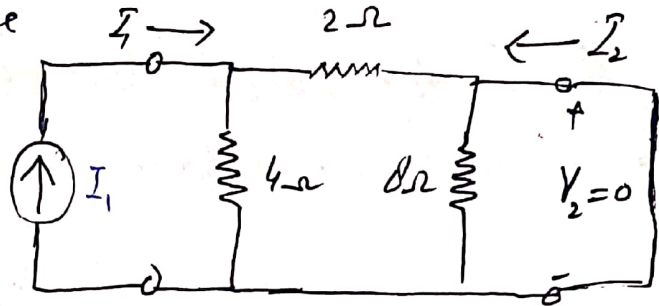
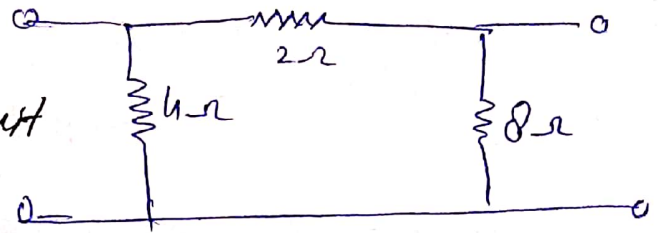


Fig 19.15 (finding  $Y_{11}$  &  $Y_{21}$ )

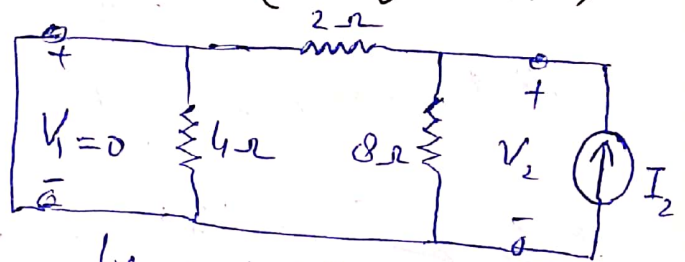


Fig 19.15 b (finding  $Y_{12}$  &  $Y_{22}$ )

To get  $Y_{12}$  &  $Y_{22}$ , short circuit the input port and connect a current source  $I_2$  to the output port as Fig 19.15(b).

The  $4\Omega$  resistor is short-circuited so that the  $2\Omega$  &  $8\Omega$  are in parallel.

$$8 \parallel 2 = \frac{8 \times 2}{8 + 2} = \frac{16}{10} = \frac{8}{5}$$

$$V_2 = I_2 (8 \parallel 2)$$

$$V_2 = \frac{8}{5} I_2 \Rightarrow Y_{22} = \frac{I_2}{V_2} = \frac{I_2}{\frac{8}{5} I_2} = \frac{5}{8}$$

$$\boxed{Y_{22} = 0.625 S}$$

By C.D.R

$$-I_1 = \frac{8}{8+2} \times I_2$$

$$-I_1 = \frac{8}{10} I_2$$

$$\boxed{I_1 = -\frac{4}{5} I_2}$$

$$\Rightarrow Y_{12} = \frac{I_1}{V_2} = \frac{-\frac{4}{5} I_2}{\frac{8}{5} I_2} = -0.5 S$$

$$\boxed{Y_{12} = -0.5 S}$$

$Y_{21}$


$\Rightarrow$  Analysis

$$Y_{21} = Y_{12} \\ -0.5 S = -0.5 S$$

The circuit is reciprocal.
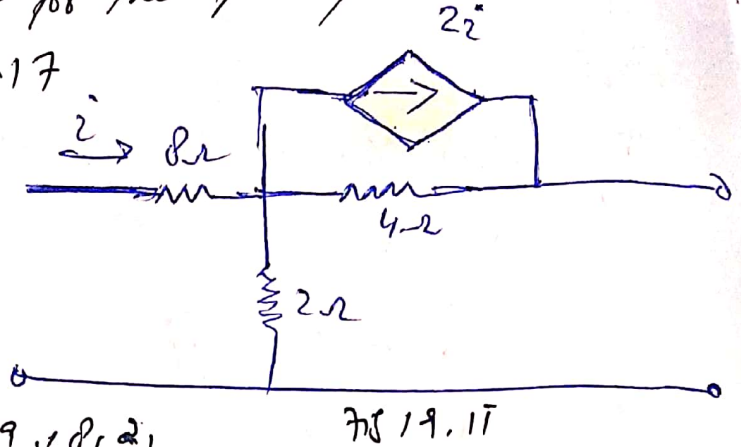
# Example 19.4

Determine the  $Y$ -Parameter for the two-port network shown in figure 19.17




Same procedure as we did in previous examples.

To get  $Y_{11}$  &  $Y_{21}$ , we

use the circuit in fig 19.18(a) in which port 2 is short circuited & current source is applied to port 1.

At Node 1

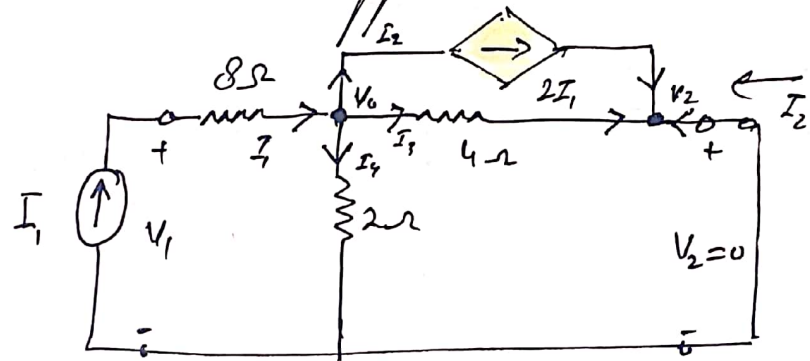

$$I_1 = I_2 + I_3 + I_4$$

$$\frac{V_1 - V_0}{8} = 2I_1 + \frac{V_0}{2} + \frac{V_0 - 0}{4}$$

But  $I_1 = \frac{V_1 - V_0}{8}$

$$I_1 = 2I_1 + \frac{V_0}{2} + \frac{V_0}{4}$$

$$0 = 2I_1 - I_1 + \frac{3V_0}{4}$$

$$0 = I_1 + \frac{3V_0}{4}$$

$$0 = \left( \frac{V_1 - V_0}{8} \right) + \frac{3V_0}{4}$$

$$0 = \frac{V_1 - V_0 + 6V_0}{8}$$

$$V_1 - V_0 + 6V_0 = 0$$

$$V_1 + 5V_0 = 0$$

$$\boxed{V_1 = -5V_0} \rightarrow \textcircled{1}$$

taking Lcm

$$\frac{2V_0 + V_0}{4} = \frac{3V_0}{4}$$

As we know that  $I_1 = \frac{V_1 - V_0}{8}$

$$V_1 = -5V_0$$

$$I_1 = \frac{-5V_0 - V_0}{8} = -\frac{6V_0}{8}$$

$$I_1 = -0.75V_0$$

$$Y_{11} = \frac{I_1}{V_1} = \frac{-0.75V_0}{-5V_0}$$

$$Y_{11} = 0.15 \text{ S}$$

At node #2  
for 19.10(a)

$$\frac{V_0 - 0}{4} + 2I_1 + I_2 = 0$$

$$-I_2 = 2(-0.75V_0) - \left(\frac{1V_0}{4}\right) \quad \text{for 19.10 (finding } y_{21} \text{ \& } y_{22})$$


$$-I_2 = -1.5V_0 - 0.25V_0$$

$$I_2 = 1.25V_0$$

$$I_2 = 1.25V_0$$

$$Y_{21} = \frac{I_2}{V_1} = \frac{1.25V_0}{-5V_0} = -0.25 \text{ S}$$

$$Y_{21} = -0.25 \text{ S}$$

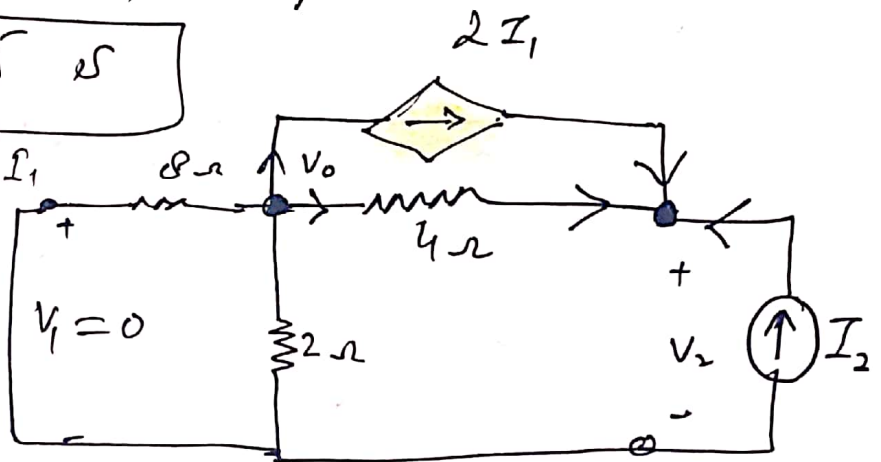

Similarly, we get  $y_{12}$  &  $y_{22}$  using Fig 19.18 (b) (30)  
at node 1

$V_1 = 0$

$$0 - \frac{V_0}{8} = 2I_1 + \frac{V_0}{2} + \frac{V_0 - V_2}{4}$$

But =  
 $I_1 = \frac{0 - V_0}{8}$

$$0 \Rightarrow I_1 = -\frac{V_0}{8}$$

$$0 = -\frac{V_0}{8} + \frac{V_0}{2} + \frac{V_0 - V_2}{4}$$

$$0 = \frac{-V_0 + 4V_0 + V_0 - 2V_2}{8} \quad \text{LCM}$$

$$+5V_0 - 2V_2 = 0$$

$$+2V_2 = +5V_0$$

~~$$V_2 = \frac{5V_0}{2}$$~~

$$V_2 = \frac{5}{2}$$

$$V_2 = 2.5V_0$$

Here

$$y_{12} = \frac{I_1}{V_2} = \frac{-V_0/8}{2.5V_0} = -0.05 \text{ S}$$

$$y_{12} = -0.05 \text{ S}$$

at node 2

$$\frac{V_0 - V_2}{4} + 2I_1 + I_2 = 0$$

$$-I_2 = 0.25V_0 - \frac{1}{4}(2.5V_0) - 2\left(\frac{V_0}{8}\right)$$

$$I_2 = -0.625V_0$$

$$y_{22} = \frac{I_2}{V_2} = \frac{0.625V_0}{2.5V_0} = 0.25 \text{ S}$$

$$y_{12} \neq y_{21}$$

19.4

# Hybrid Parameter or h-Parameters (3)

→ The Z & Y Parameters of two-port network do not always exist. So there is need for developing another set of parameters.

Thus the third set of parameter is based on making  $V_1$  &  $I_2$  the dependent variable &  $I_1$  &  $V_2$  are independent variables.

H-Parameter have mixed dimension, so they are called hybrid parameter

$$V_1 = f(V_2, I_1)$$


$$I_2 = g(V_2, I_1)$$

- Input Impedance
- output Impedance
- Voltage Gain
- Current Gain

The hybrid parameter are generally used to determine amplifier characteristic parameters such as voltage gain, input resistance / input impedance, output resistance / output impedance etc. Thus


$$V_1 = h_{11} I_1 + h_{12} V_2 \rightarrow (V/V)$$
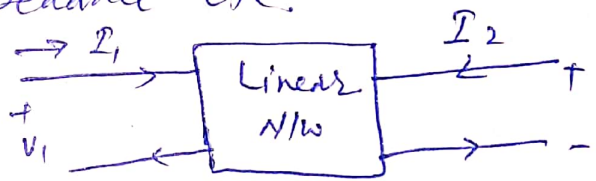
$$I_2 = h_{21} I_1 + h_{22} V_2 \rightarrow (C/C)$$



The h-parameter equivalent network of a two port N/w

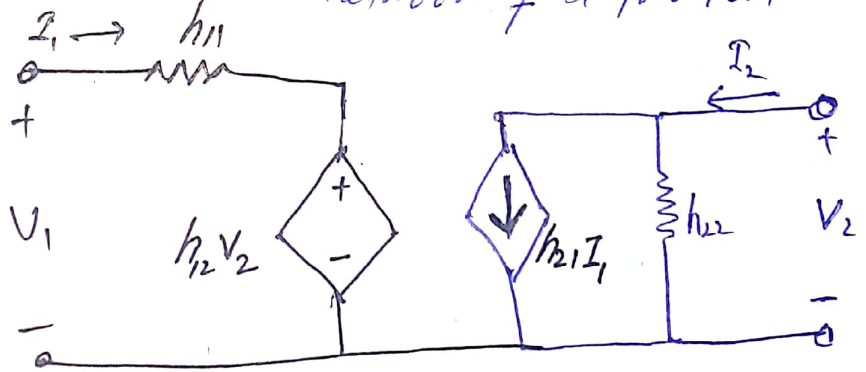$h_{11} I_1$  is voltage drop across  $h_{11}$  &  $h_{12} V_2$  is the VCVS (Voltage Controlled Voltage Source)



The value of this voltage source depend on voltage at ports (V1).

Fig. 19.20




# Determination of h-Parameters

(4)  $\Rightarrow$  The parameter  $h_{11}$  &  $h_{21}$  may be determined by short circuiting the output terminals of given circuit.

While on the other hand,  $h_{12}$  &  $h_{22}$  may be determined by open circuiting the input terminal.

## Determination of $h_{11}$ & $h_{21}$

①  $V_2 = 0$

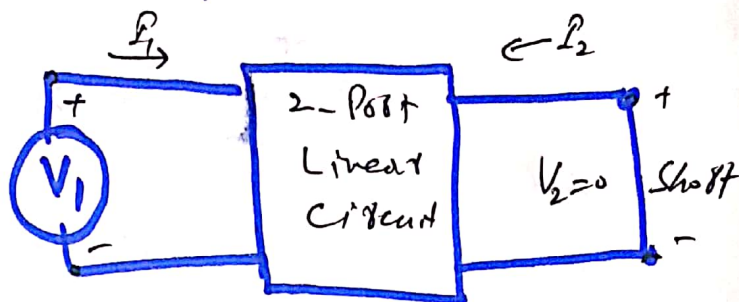

Considering the Equation

$$V_1 = h_{11} \cdot I_1 + h_{12} V_2 \xrightarrow{V_2=0}$$

$$V_1 = h_{11} I_1 + 0$$

Fig (Output Short Circuited)

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0}$$

$\therefore h_{11}$  is ratio of voltage to current (I/P side) & it has unit of  $\Omega$  (ohm)

$h_{11}$  is called input resistance or short-circuit input impedance

Similarly

$$I_2 = h_{21} I_1 + h_{22} V_2 \xrightarrow{V_2=0}$$

$$I_2 = h_{21} I_1 \Rightarrow h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0}$$


$h_{21}$  is the ratio of o/p current to input current. It has no unit.

$\therefore h_{21}$  is known as short circuit forward current gain (unitless)

The  $h_{21}$  is called the forward current gain with output short-circuited.
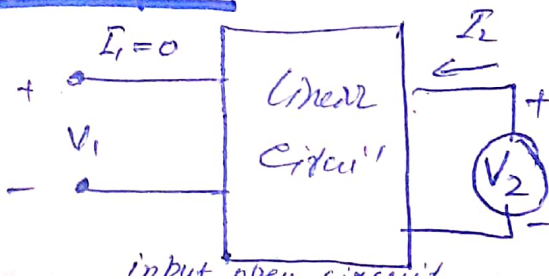
## Determination of $h_{12}$ & $h_{22}$

$\Rightarrow$  These are determined by open circuiting the input terminal  $I_1 = 0$



$$V_1 = 0 + h_{12} V_2$$

$$h_{12} = \frac{V_1}{V_2} \Big|_{I_1 = 0}$$

o/p port is o.c,  $h_{12}$  is ratio of o/p voltage to i/p voltage, it is called reverse voltage gain (it's unitless parameter)

$$h_{22} = \frac{I_2}{V_2} \Big|_{I_1 = 0 \text{ (o.c.p.)}} \Rightarrow \text{It has unit of Admittance (open circuit o/p admittance)}$$

All h-h Parameters

$$h_{11} = \frac{V_1}{I_1} \Big|_{V_2 = 0}$$

$$h_{12} = \frac{V_1}{V_2} \Big|_{I_1 = 0}$$

$$h_{21} = \frac{I_2}{I_1} \Big|_{V_2 = 0}$$

$$h_{22} = \frac{I_2}{V_2} \Big|_{I_1 = 0}$$

Summary

- $h_{11}$  = short-circuit input Impedance
- $h_{12}$  = open-circuit reverse voltage gain
- $h_{21}$  = short-circuit forward current gain
- $h_{22}$  = open-circuit output Admittance.

In BJT:

$h_i = h_{11}$
$h_r = h_{12}$
$h_f = h_{21}$
$h_o = h_{22}$

Condition for Reciprocity

$$h_{12} = -h_{21}$$

Condition for Symmetry


$$h_{11} h_{22} - h_{12} h_{21} = 1$$

# (34)
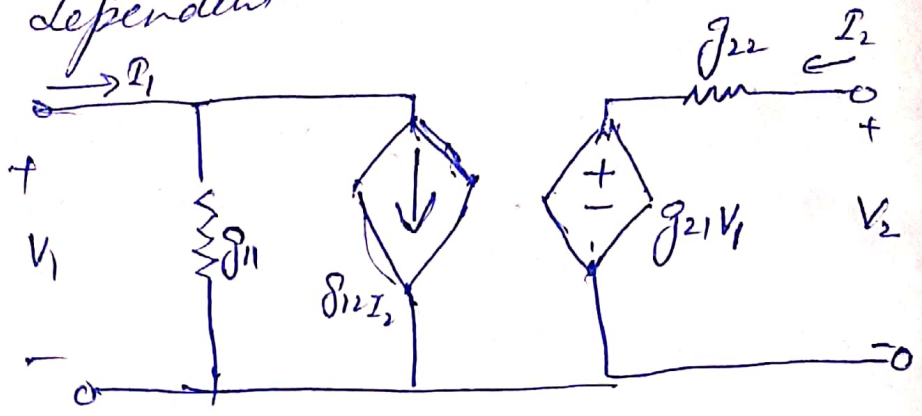
# g-Parameter / Inverse h-Parameters

$V_1$  &  $I_2$  are independent variables  
 $I_1$  &  $V_2$  are dependent variables

A set of parameters closely related to the h-parameter are the g-parameters, or Inverse-hybrid parameters. These are used to describe the terminal voltage & current -



$$I_1 = g_{11} V_1 + g_{12} I_2$$

$$V_2 = g_{21} V_1 + g_{22} I_2$$

$$\begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ I_2 \end{bmatrix}$$

$$\begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = [g] \begin{bmatrix} V_1 \\ I_2 \end{bmatrix}$$

The g-parameters are frequently used to model the field-effect transistor (FET).

The value of g-parameters  $V_1 = 0$  s.c

$$g_{11} = \frac{I_1}{V_1} \Big|_{I_2=0}$$

$g_{11}$  = open circuit I/P admittance

$$g_{12} = \frac{I_1}{I_2} \Big|_{V_1=0}$$

$g_{12}$  = short-circuit reverse gain


$$g_{21} = \frac{V_2}{V_1} \Big|_{I_2=0}$$

$g_{21}$  = open circuit forward gain

$$g_{22} = \frac{V_2}{I_2} \Big|_{V_1=0}$$

$g_{22}$  = short circuit O/P impedance

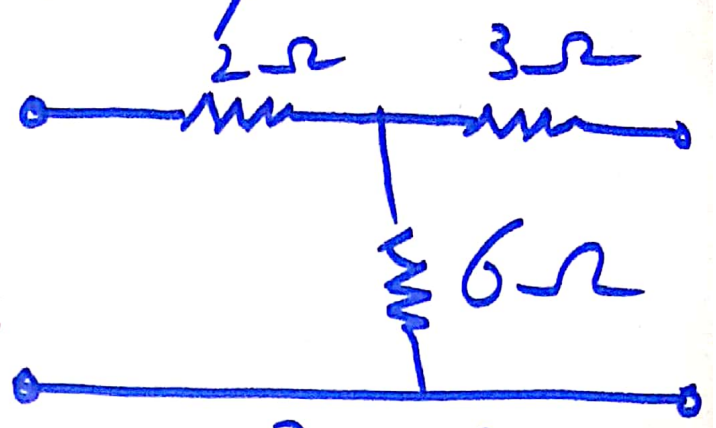Example 19.5 Find the hybrid parameter for the two-port network of fig 19.22. (35)



Solution To find  $h_{11}$  &  $h_{21}$ , we short-circuit the output port and connect a current source  $I_1$  to the input port as shown

fig. 19.22

in fig. 19.23 (c)  
 $R_2 || R_3$   
 $3 || 6$   
 $\Rightarrow \frac{3 \times 6}{3+6} = \frac{18}{9} = 2\Omega$

Voltage across  $4\Omega$  Resistor.

$V_1 = 4I_1$


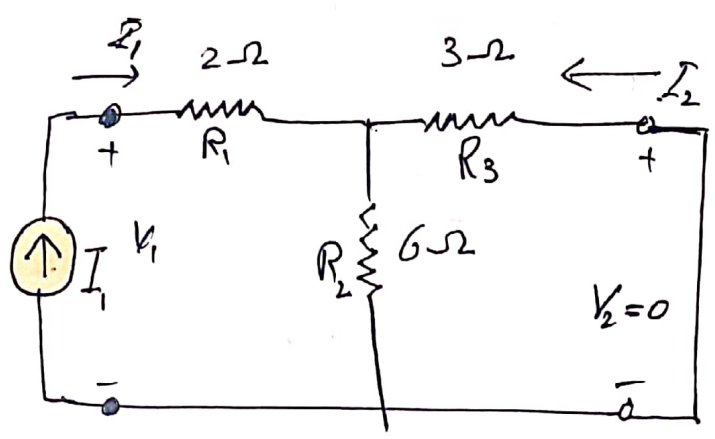


Fig 19.23 (c) Computing  $h_{11}$  &  $h_{21}$

Hence  
 $h_{11} = \frac{V_1}{I_1} = \frac{4I_1}{I_1}$

$h_{11} = 4\Omega$

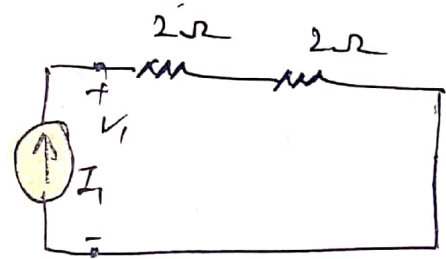

4Ω


Also, from fig 19.23 (a), we obtain by CDR (Current Division Rule)

$h_{21} = \frac{I_2}{I_1}$

$-I_2 = \frac{6}{6+3} \times I_1$

$-I_2 = \frac{6}{9} I_1$

$+I_2 = -\frac{2}{3} I_1$

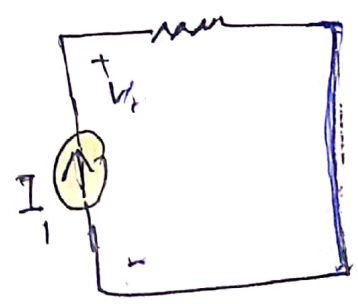

Here  $h_{21} = \frac{I_2}{I_1} = \frac{-\frac{2}{3} I_1}{I_1}$

$h_{21} = -\frac{2}{3}$

To obtain  $h_{12}$  &  $h_{22}$ , we open-circuit the input port and connect a voltage source  $V_2$  to the output as in Fig 18.23(b), By VDR (Voltage Division Rule)

$h_{12} = \frac{V_1}{V_2}$

$V_1$  is the voltage across  $6\Omega$  resistor

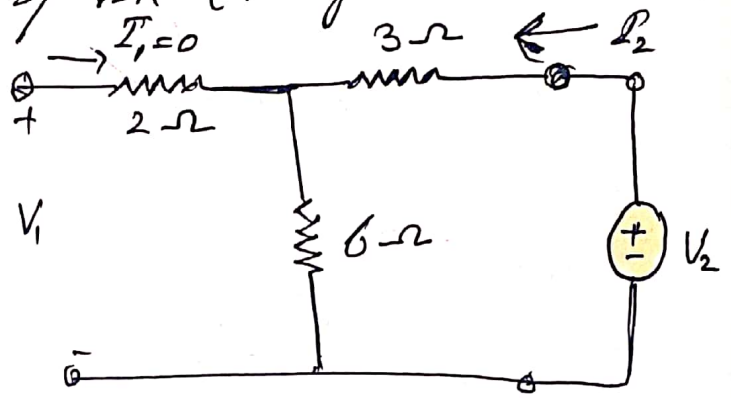


FIG. 18.23(b)  
Computing  $h_{12}$  &  $h_{22}$

$V_1 = \frac{6}{6+3} \times V_2$

$V_1 = \frac{6}{9} V_2 \Rightarrow V_1 = \frac{2}{3} V_2$

$\rightarrow h_{12} = \frac{\frac{2}{3} V_2}{V_2} \Rightarrow h_{12} = \frac{2}{3}$

&  $h_{22} = \frac{I_2}{V_2}$  for  $V_2$  Apply KVL.

$V_2 = (3+6) I_2$   
 $V_2 = 9 I_2$

$h_{22} = \frac{I_2}{V_2} = \frac{I_2}{9 I_2} = \frac{1}{9} S \Rightarrow h_{22} = \frac{1}{9} S$

$[h] = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} = \begin{bmatrix} 4 & \frac{2}{3} \\ -\frac{2}{3} & \frac{1}{9} \end{bmatrix}$

# Practice Problem 19.6


Find the impedance at the input port of the circuit in Fig B.27

$$h_{11} = 2 \text{ k}\Omega = 2 \times 10^3 \Omega$$

$$h_{12} = 10^{-4}$$

$$h_{21} = 100$$

$$h_{22} = 10^{-5} \text{ S}$$

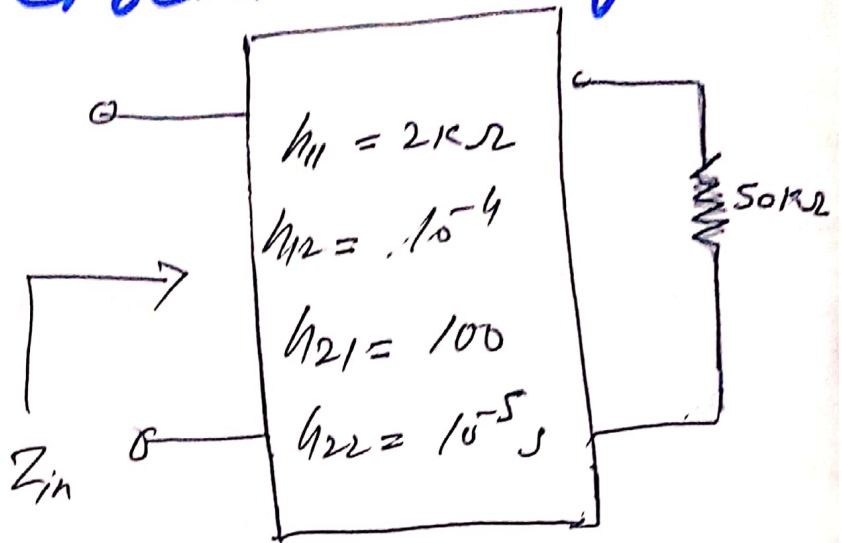

Solution

The hybrid parameter based on  $V_1$  &  $I_2$  the dependent variables, thus

$$V_1 = h_{11} I_1 + h_{12} V_2 \quad \text{--- (1)}$$

$$I_2 = h_{21} I_1 + h_{22} V_2 \quad \text{--- (2)}$$

Substituting the hybrid parameter, we obtain,

$$\text{Eq (1)} \Rightarrow V_1 = 2000 I_1 + 10^{-4} V_2 \quad \text{--- (3)}$$

$$I_2 = 100 I_1 + 10^{-5} V_2 \quad \text{--- (4)}$$

Since from the circuit, the output voltage at output port

$$V_2 = -50,000 I_2$$

Putting the value of  $V_2$  in Eq (4)

$$\text{By (4)} \Rightarrow I_2 = 100 I_1 + 10^{-5} (-50,000) I_2$$

(38)

$$I_2 (1 + 0.5) = 100 I_1$$

$$I_2 = \frac{100}{1.5} I_1$$

Substituting the values of  $V_2$  &  $I_2$  in Eq  
①, we get

$$V_1 = 2000 I_1 + 10^{-4} (-50,000) I_2$$

$$V_1 = 2000 I_1 + (-5) \left( \frac{1000}{1.5} \right) I_1$$

$$V_1 = I_1 \left[ 2000 - \frac{1000}{3} \right]$$

$$\frac{V_1}{I_1} = \frac{6000 - 1000}{3}$$

$$\frac{V_1}{I_1} = \frac{5000}{3} = \frac{5}{3} (1000)$$

Thus the ~~the~~ Impedance at the input  
Port of the circuit  $| Z_{in} = 1.667 \text{ k}\Omega$

# Example 19.7: Find the $g$ -Parameters as function

of  $s$  for the circuit in Fig 19.28

$$g = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix}$$

$$g_{11} = \frac{I_1}{V_1} \Big|_{I_2=0}, \quad g_{21} = \frac{V_2}{V_1} \Big|_{I_2=0} \text{ (o.c.)}$$

$$g_{12} = \frac{I_1}{I_2} \Big|_{V_2=0}, \quad g_{22} = \frac{V_2}{I_2} \Big|_{V_2=0} \text{ (s.c.)}$$

Solution In the  $s$ -Domain

1H Inductor  $\Rightarrow sL = s \times 1 = s$

1F Capacitor  $\Rightarrow \frac{1}{sC} = \frac{1}{s \times 1} = \frac{1}{s}$

1- $\Omega$  Resistor  $\Rightarrow$  1- $\Omega$  Remains same

To get  $g_{11}$  &  $g_{21}$ , we open-circuit the output port and connect a voltage source  $V_1$  to the input port as in Fig 19.29(a), from the fig.

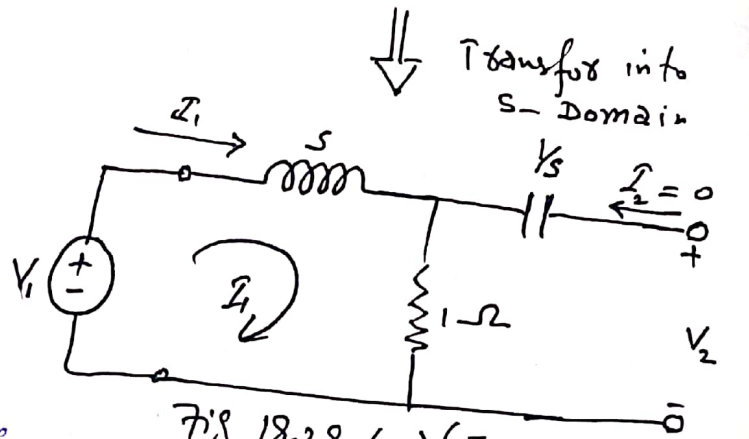
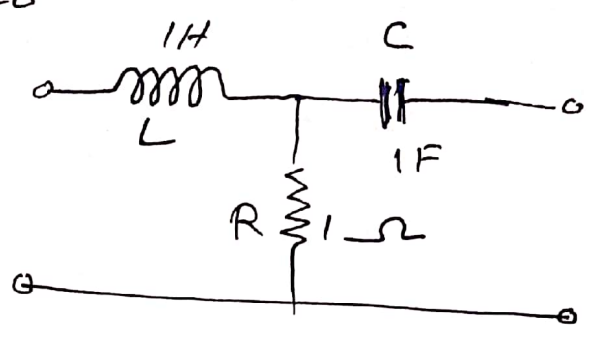


Fig 19.29 (a) ( $I_2=0$ ) o.s (o/p)

$$g_{11} = \frac{I_1}{V_1} \quad \text{for } I_1 = \frac{V_1}{s+1} \quad (\text{by KVL})$$

$$g_{11} = \frac{V_1 / (s+1)}{V_1} \Rightarrow g_{11} = \frac{1}{s+1}$$

For  $g_{21} = \frac{V_2}{V_1}$

for  $V_2$  we apply V.D.R. (Voltage Divisn) we will find voltage across 1- $\Omega$  resist

$$g_{21} = \frac{V_1 / (s+1)}{V_1}$$

$$V_2 = \frac{1}{s+1} \times V_1$$

$$V_2 = \frac{V_1}{s+1}$$

$$g_{21} = \frac{1}{s+1}$$



To obtain  $G_{12}$  &  $G_{22}$ , we short-circuit the input port and connect a current source  $I_2$  to the output port as Fig 19.29 (b).

By CDR (current Dividing Rule)

$$-I_1 = \frac{1}{s+1} \times I_2$$

$$I_1 = -\frac{1}{s+1} \times I_2$$

$$G_{12} = \frac{I_1}{I_2} = \frac{-\frac{1}{s+1} \times I_2}{I_2}$$

$$G_{12} = -\frac{1}{s+1}$$

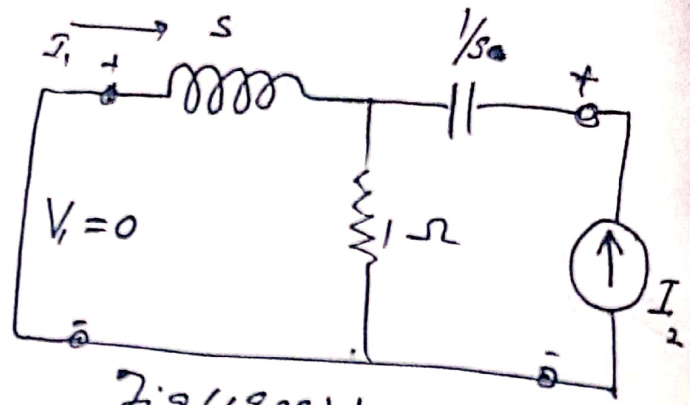


Fig (19.29) b

&  $G_{22} = \frac{V_2}{I_2}$   $\therefore$  for  $V_2 = I_2 \left( \frac{1}{s} + s/1 \right)$

$$G_{22} = \frac{I_2 \left( \frac{s^2 + s + 1}{s(s+1)} \right)}{I_2} \quad \left| \quad \begin{aligned} V_2 &= I_2 \left( \frac{1}{s} + \frac{s}{s+1} \right) & \frac{s \times 1}{s+1} &= \frac{s}{s+1} \\ V_2 &= I_2 \left( \frac{s+1 + s^2}{s(s+1)} \right) \\ V_2 &= I_2 \left( \frac{s^2 + s + 1}{s(s+1)} \right) \end{aligned} \right.$$

$$G_{22} = \frac{s^2 + s + 1}{s(s+1)}$$

$$[G] = \begin{bmatrix} \frac{1}{s+1} & -\frac{1}{s+1} \\ \frac{1}{s+1} & \frac{s^2 + s + 1}{s(s+1)} \end{bmatrix}$$

# Transmission Parameters

OR ABCD Parameters or T-Parameter or Cascade Parameter or Chain Parameters

$V_1 = V_S =$  Sending Voltage

$V_2 = V_R =$  Receiving Voltage

$I_1 = I_S$

$-I_2 = I_R$  (opposite sign) Leaving

$V_2$  &  $I_R \Rightarrow$  Independent Variable

$V_S$  &  $I_S \Rightarrow$  dependent variable.



Fig 19.31

$-I_2$  is used rather than  $I_2$ , because the current is considered to be leaving the network.

Reason (why  $I_2$  -ve)

(i) When cascade two-port (output to Input) of Transmission Line

Practical use of T-Parameter

- $\Rightarrow$  used in Telephone system
- $\Rightarrow$  used in Microwave Network
- $\Rightarrow$  used in Radar system

T-Parameter is also known as Cascade or chain Parameters because one two or more system are cascaded then for analysis of cascaded system these ABCD Parameters are useful

$$V_1 = AV_2 - BI_2$$


$$I_1 = CV_2 - DI_2$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = [T] \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

$$T = \begin{bmatrix} A & B \\ C & D \end{bmatrix}$$

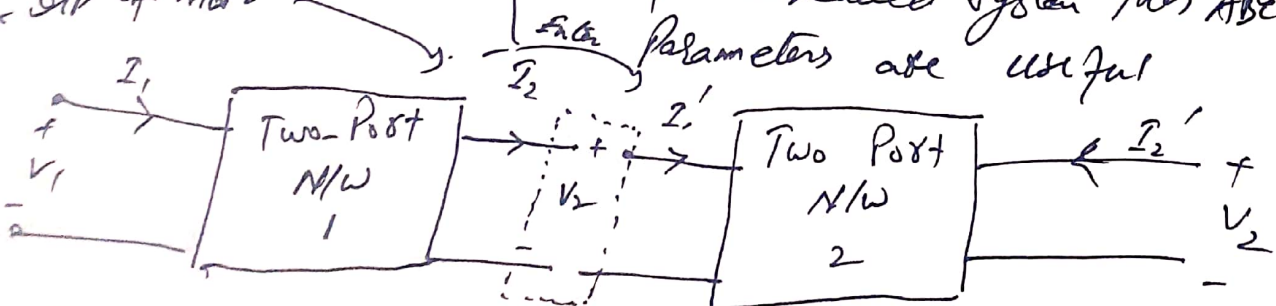The  $I_2$  current is o/p of NW1 & o/p of NW2



To find A & C, let us assume that  $I_2 = 0$

(42)

$$V_1 = AV_2 - BI_2 \rightarrow 0$$

$$A = \frac{V_1}{V_2} \Big|_{I_2 = 0}$$

Similarly  $I_1 = CV_2 - 0 \Rightarrow C = \frac{I_1}{V_2} \Big|_{I_2 = 0}$

To find B & D, let  $V_2 = 0$  short circuit

$$V_1 = AV_2 - BI_2$$

$$V_1 = -BI_2 \Rightarrow B = -\frac{V_1}{I_2} \Big|_{V_2 = 0}$$

Similarly

$$I_1 = CI_2 - DI_2$$

$$I_1 = -DI_2 \Rightarrow D = -\frac{I_1}{I_2} \Big|_{V_2 = 0}$$

A = open circuit voltage ratio

B = Negative short circuit transfer Impedance

C = open circuit transfer Admittance

D = Negative short-circuit current ratio

where A & D are Dimensionless (Unit less)

B is in  $\Omega$  (ohm) where


C is in Siemens (S)

Example 19.8 :- (Find the Transmission Parameters) (43)

For the two-port network in Fig 19.32

Solution

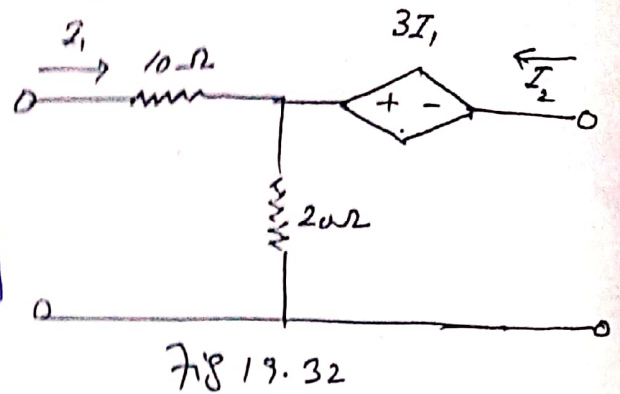To determine A & C, we leave the output port open circuit as in fig. 33(a), so that  $I_2 = 0$  and place a voltage source  $V_1$  at the input port. we have




$$V_1 = (10 + 20)I_1$$

$$V_1 = 30I_1$$

Dependent Source

$$V_2 = 20I_1 - 3I_1$$

$$V_2 = 17I_1$$

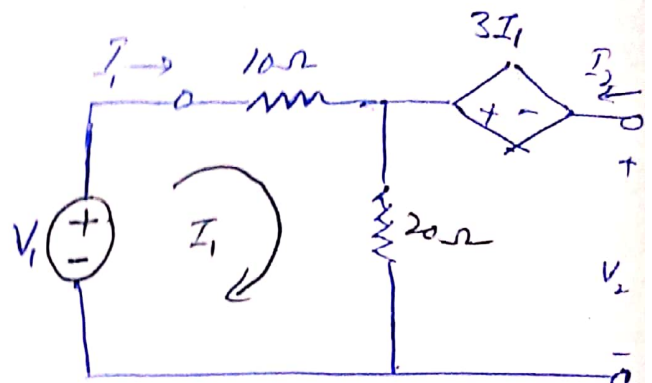

$$A = \frac{V_1}{V_2} \bigg|_{I_2=0} = \frac{30I_1}{17I_1} = \frac{30}{17}$$

$$A = 1.765$$

&

$$C = \frac{I_1}{V_2} = \frac{I_1}{17I_1} = \frac{1}{17} \Rightarrow C = 0.0588 S$$

To obtain B & D, we short-circuit the output port, so that  $V_2 = 0$  as shown in fig 19.33(b) on next page & place a voltage source  $V_1$  at the input port.


Apply KCL at Node A

$$I_1 - I_3 + I_2 = 0 \rightarrow (1)$$

$$\frac{V_1 - V_A}{10} - \frac{V_A}{20} + I_2 = 0 \rightarrow (2)$$

But  $V_A = 3I_1$

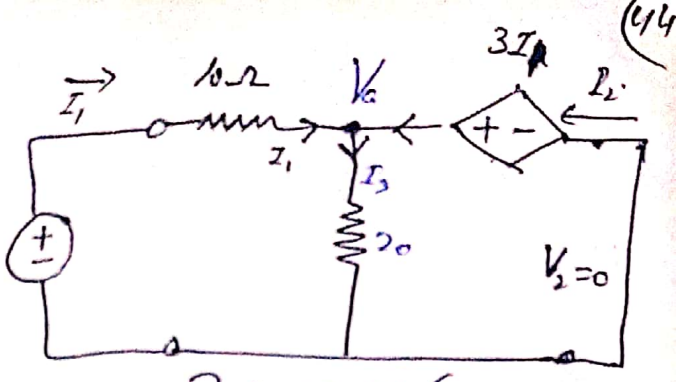&  $I_1 = \left( \frac{V_1 - V_A}{10} \right), I_3 = \frac{V_A}{20}$



7/8 19.33 (5)  
finding B & D.

from (1)  $I_1 - \frac{3I_1}{20} + I_2 = 0$

$$I_1 - \frac{3I_1}{20} = -I_2$$

Let  $\frac{20I_1 - 3I_1}{20} = -I_2$

$$\frac{17}{20} I_1 = -I_2 \Rightarrow$$

Therefore  $D = -\frac{I_1}{I_2} = \frac{I_1}{\left(\frac{17}{20}\right) I_1}$

$$\boxed{D = \frac{20}{17}} \Rightarrow \boxed{D = 1.176}$$

from (2)  $V_A = 3I_1$  &  $I_1 = \frac{V_1 - V_A}{10}$

$$I_1 = \frac{V_1 - 3I_1}{10} \Rightarrow 10I_1 = V_1 - 3I_1$$

$$\Rightarrow V_1 = 10I_1 + 3I_1$$

$$\boxed{V_1 = 13I_1}$$

$$\Rightarrow B = -\frac{V_1}{I_2}$$

$$B = \frac{13I_1}{\left(\frac{17}{20}\right) I_1}$$

$$B = \frac{20 \times 13}{17} = \frac{260}{17} \Rightarrow \boxed{B = 15.29 \Omega}$$