

## EXPERIMENT NO. 4

### DEMONSTRATION OF KIRCHHOFF'S VOLTAGE AND KIRCHHOFF'S CURRENT LAWS

#### OBJECTIVE:

To verify the following circuit using KCL & KVL

- a) Express I as a function of V and R.
- b) Express V as a function of I and R.
- c) Demonstration of KVL
- d) Demonstration of KCL

#### EQUIPMENTS REQUIRED:

- Variable DC power supply
- DMM (Digital Multi Meter)
- Resistors with different Resistances
- Breadboard

#### THEORY:

### KIRCHHOFF'S VOLTAGE LAW

According to Kirchhoff's Voltage Law

*“The sum of all voltages in a closed loop is equal to zero”*

Mathematically,

$$\sum V_{All} = 0 \quad (i)$$

Alternatively, in a closed loop the sum of all voltage rises is equal to the sum of all voltage drops

$$\sum V_{Rise} = \sum V_{Drop} \quad (ii)$$

We can also say that voltage drops across each resistor in a close loop must be equal to the applied voltages.

### CIRCUIT DIAGRAM

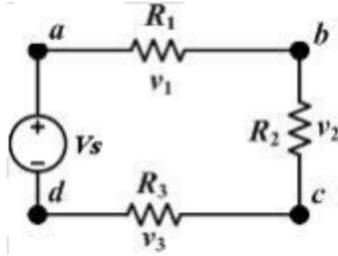


Figure 3.4 ( Circuit for Kirchhoff's Voltage Law)

Applying KVL to the circuit above

$$\begin{aligned}
 -V_s + V_1 + V_2 + V_3 &= 0 \\
 V_s &= IR_1 + IR_2 + IR_3 \\
 I &= V_s / R_{eq}
 \end{aligned}$$

## PROCEDURE

Measure the values of given Resistors and fill in the corresponding columns of Table. 4.1  
 Connect the circuit as shown in Figure above and set  $V_s$  to 5 V  
 Calculate the values with the formulas provided in theory section of this experiment and fill the corresponding row in Table 7.2  
 Measure  $V_1$  ,  $V_2$  and  $V_3$  and fill in corresponding Column in Table 7.2

## RESULTS & CALCULATIONS

Table 4.3

R ( Nominal)	R1 =      k $\Omega$	R2 =      k $\Omega$	R3=      k $\Omega$
R (Actual)			

Table 4.4

Value	$V_1$	$V_2$	$V_3$	$V_1 + V_2 + V_3$	$V_s$
Measured					
Calculated					

## KIRCHHOFF CURRENT LAW

According to Kirchhoff's current law

*“The algebraic sum of all currents entering a node is equal to the sum of all the currents leaving a node”*

Mathematically,

$$\sum I_{Enter} = \sum I_{Leave} \quad (iii)$$

Alternatively, the sum of all currents in a junction is equal to zero

Mathematically,

$$\sum I_{All} = 0 \quad (iv)$$

## CIRCUIT DIAGRAM

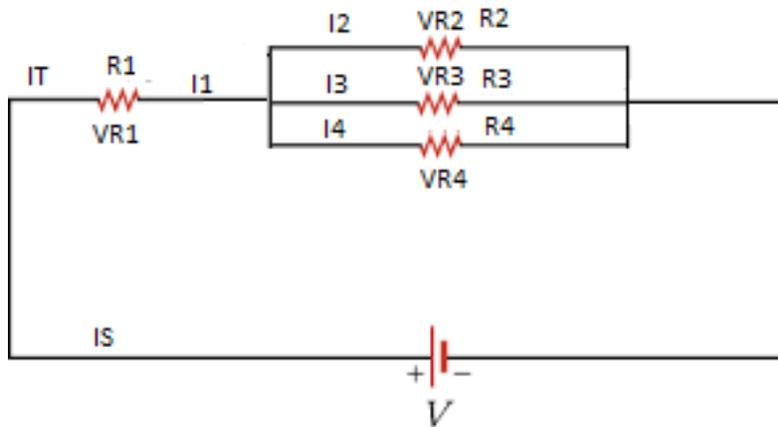


Figure 3.4 ( Circuit for Kirchhoff's Current Law)

**Select::** R1 = \_\_\_\_\_ k $\Omega$ , R2 = \_\_\_\_\_ k $\Omega$  and R3 = \_\_\_\_\_ k $\Omega$  R4 = \_\_\_\_\_ k $\Omega$

In the Figure 3.4 , the sum of current IR2, IR3 and IR4 is equal to the IR1 or total supply current Iin or IS OR IT.

## PROCEDURE

1. On the breadboard connect the resistors in parallel configuration as shown in Figure 4.4
2. Connect the positive lead (Red wire) of the power supply to the open terminal of the one of the resistors.
3. Connect the negative lead (Black wire) of the power supply to the second terminal of the same resistor.
4. Switch on the power supply and set the supply voltage at 5 volts.
5. Use the D.C. Ammeter mode of the multi-meter with appropriate range as preset.
6. Connect Ammeter in such a way that it forms a series connection with the resistor and measure the current flowing through the resistor.
7. Record the observation accordingly in the table 4.4
8. Rearrange the circuit to measure the currents in table 4.4



## Evaluation Chart

	Total Marks	Obtained Marks
Participation in the Lab	3	
Accuracy of Results Obtained	4	
Viva	3	
<b>Total</b>	10	

**Comments from Lab Instructor:**

---

---

---

---

---

Date

---

Instructor's Signature