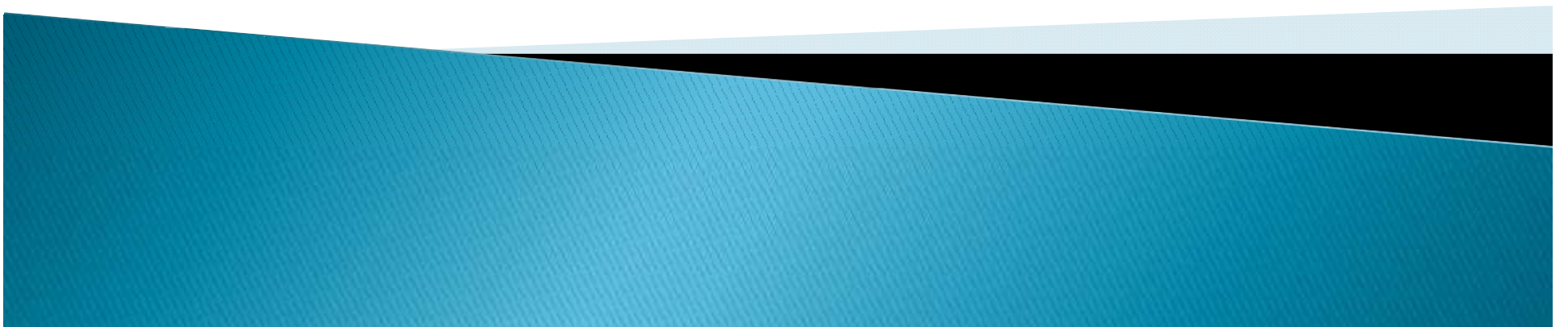



Power Systems Analysis

ET-321




References

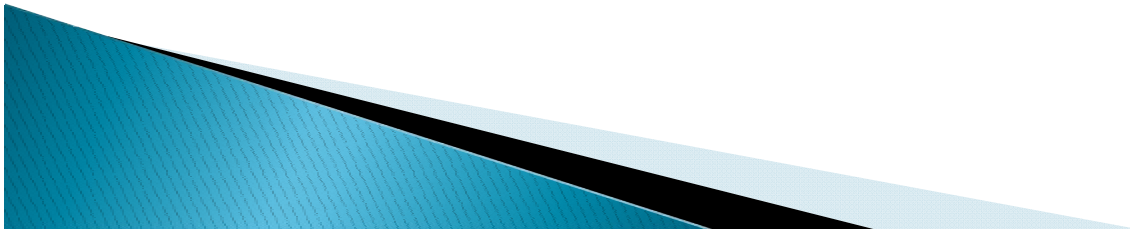- **Elements of power system analysis**
(**William Stevenson**)
- **Power system analysis**
(**Hadi Sadaat**)




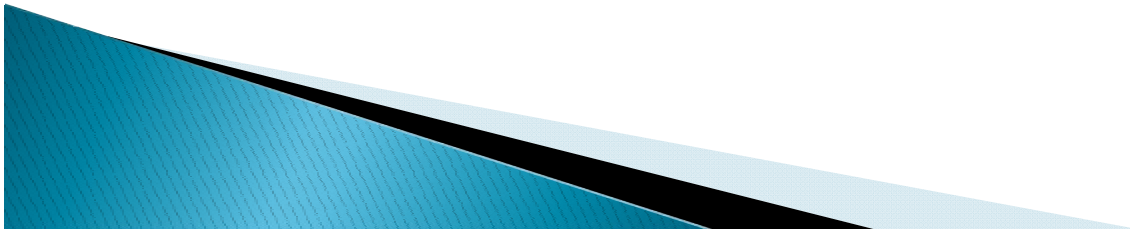Current and Voltage
Relations on a
Transmission line



Short Transmission line

- ▶ In the case of a short transmission line the capacitance and conductance to earth may be neglected.
- ▶ Leaving only the series resistance and inductance to be taken into consideration.
- ▶ The current entering the line at the sending-end termination is equal to the current leaving at the receiving-end, and this same current flows through all the line sections.
- ▶ The R and L parameters may therefore be regarded as 'lumped'.

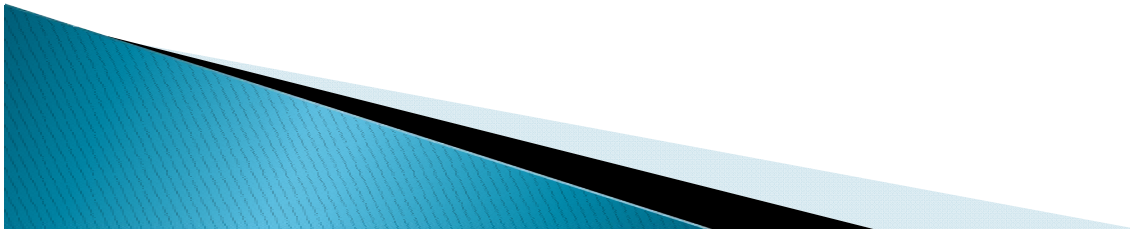

- ▶ The equivalent circuit diagram and the vector diagram for a short line are shown in fig.(6.1) in which:

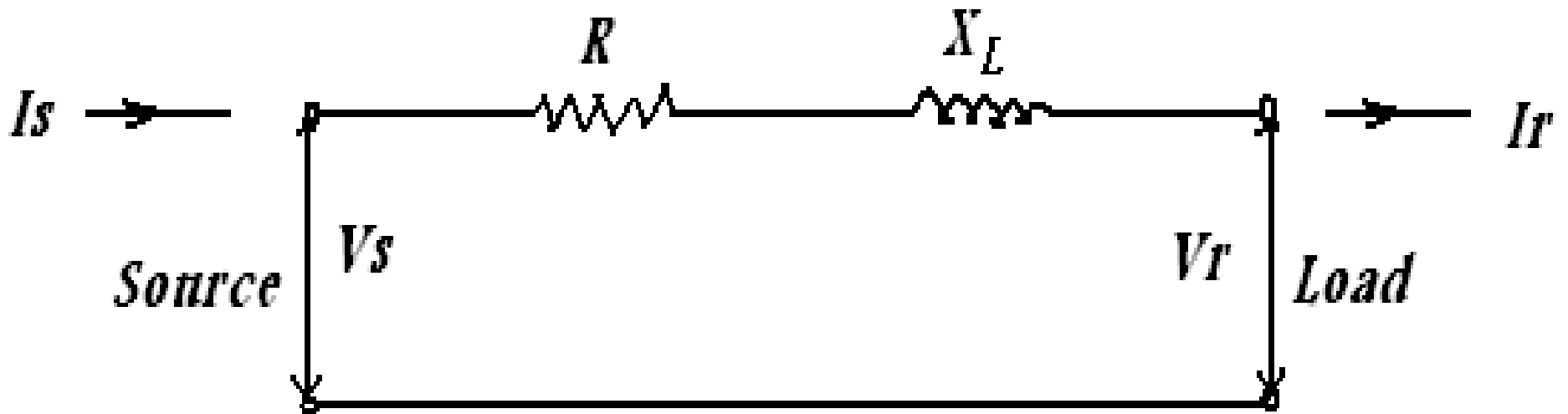


Fig.(6.1 a): Equivalent circuit for a short transmission line

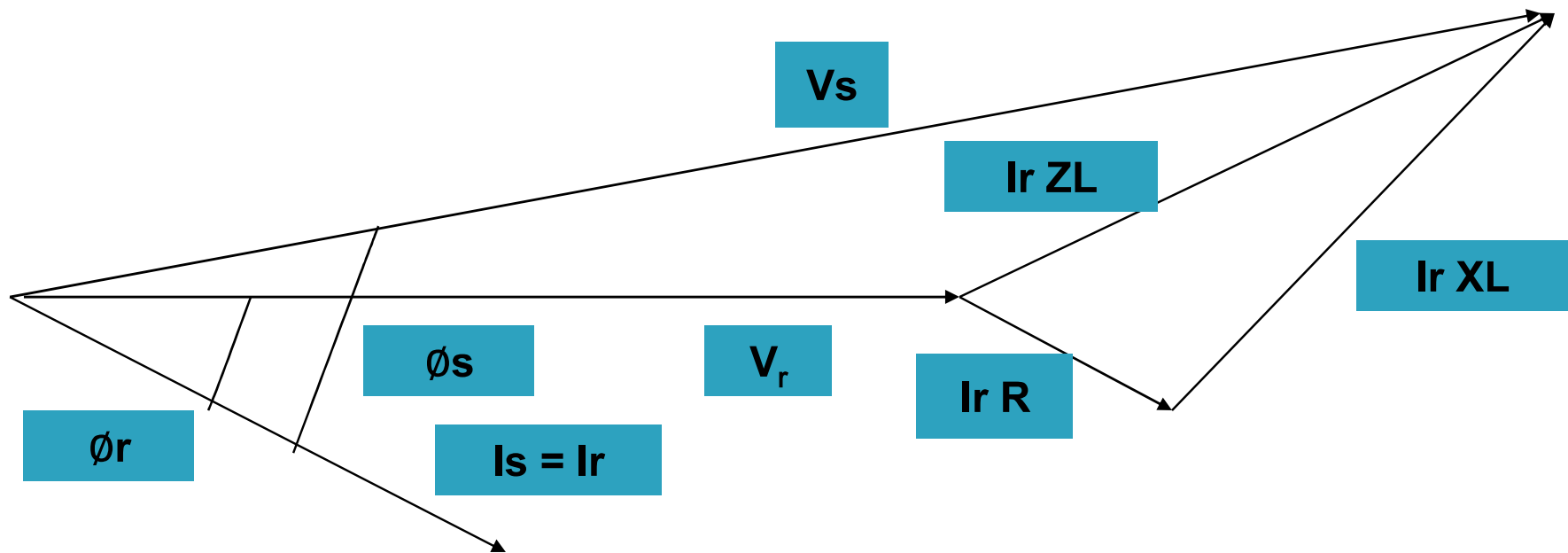


Fig.(6.1 b): Vector diagram for a short transmission line .

V_S : phase voltage at sending-end .

V_R : phase voltage at receiving-end

I_S : phase current at sending-end .

I_R : phase current at receiving-end


$\cos \phi_S$: power factor at sending-end .

$\cos \phi_R$: power factor at receiving-end .

R : resistance per phase of circuit .

X_L : inductive reactance per phase of circuit .

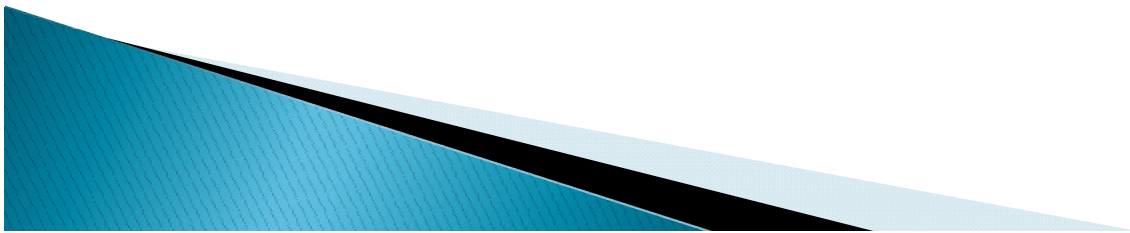- ▶ The currents I_S and I_R will be equal in magnitude but not in phase.
- ▶ R is obtained from a knowledge of the line length ,the size of conductor and the specific resistance of the conductor material ,
- ▶ while X_L is calculated from the conductor spacing and radius .




- ▶ Referring to the equivalent circuit :

$$I_S = I_R \quad (6.1a)$$

$$V_S = V_R + (R + jX_L)I_R \quad (6.1b)$$

$$= V_R + Z I_R$$

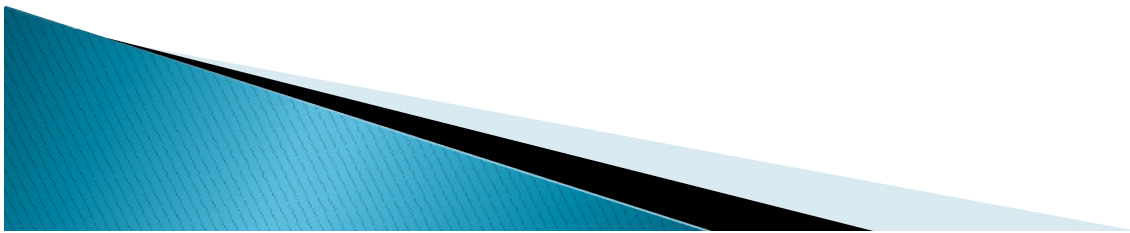
- ▶ Hence, if the receiving-end conditions are known the necessary sending-end voltage may be calculated .



- ▶ It will be noted that (6.1a) and (6.1b) are phasor equations , a more approximate method involving scalar quantities is as follows: Referring to the vector diagram,

$$V_{SX} = V_R + I_R R \cos \phi_R + I_R X_L \sin \phi_R$$


$$V_{SY} = I_R X_L \cos \phi_R - I_R R \sin \phi_R$$

$$\therefore V_S = [(V_R + I_R R \cos \phi_R + I_R X_L \sin \phi_R)^2 + (I_R X_L \cos \phi_R - I_R R \sin \phi_R)^2]^{1/2}$$


- ▶ However $(I_R X_L)$ and $(I_R R)$ are very much less than V_R and the small voltage is in quadrate with the much larger V_{SX} ,

- $\therefore V_S \cong V_{SX} \cong V_R + I_R R \cos \phi_R + I_R X_L \sin \phi_R.$
- ▶ The voltage regulation of the line is given by the rise in voltage when full loads is removed , or :
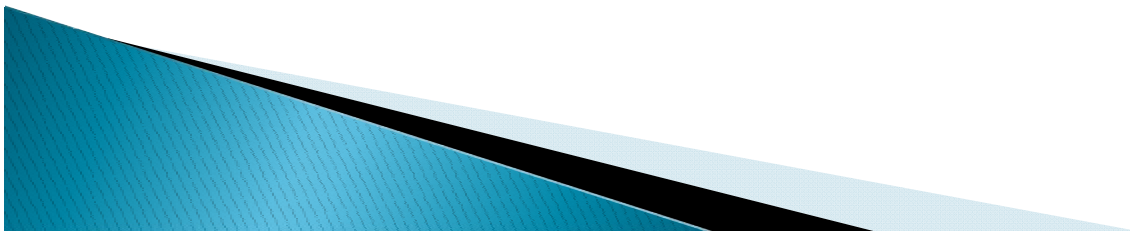
$$\%age \text{ voltage regulation} = \frac{V_S - V_R}{V_R} \cong I_R \frac{(R \cos \phi_R + X_L \sin \phi_R)}{V_R}$$



Example

A three-phase line delivers 3 MW at 11 KV for a distance of 15 Km . Line loss is 10 % of power delivered , load power factor is 0.8 lagging . frequency is 50 Hz , 1.7 m equilateral spacing of conductors . Calculate the sending-end voltage and regulation .

Solution

$$\text{Receiving-end phase voltage} = \frac{11,000}{\sqrt{3}} = 6.360 = V_R$$

Line current = phase current (assuming a star connection)


$$= \frac{3,000 \times 10^3}{\sqrt{3} \times 11 \times 10^3 \times 0.8} = 197 \text{ A}$$

Total line loss = $3 I^2 R$ (in three conductors)

$$= \frac{10}{100} \times 3,000 \times 10^3$$

$$\begin{aligned} \therefore R &= \frac{300 \times 10^3}{3 \times 197^2} \\ &= 2.58 \quad \text{ohms} \end{aligned}$$

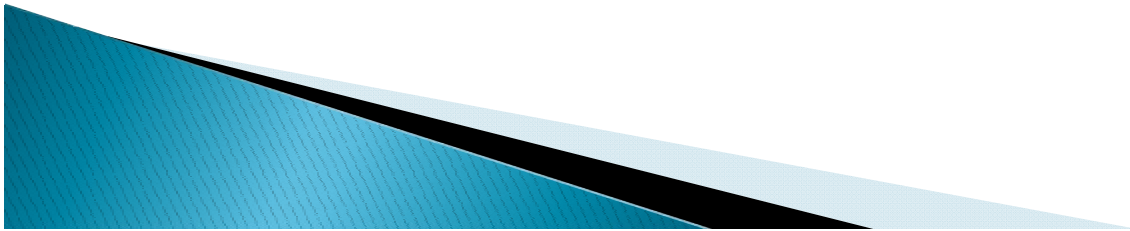- ▶ Assuming that the conductors are manufactured from copper having a resistance of 0.0137 ohms per meter for a cross-sectional area of 1 mm², the conductor cross-section is 80 mm² corresponding to a radius of 5 mm.




$$\text{Inductance} = L = \frac{1}{2} (1 + 4 \log_c \frac{d}{r}) \times 10^{-7} \quad H / \text{metre}$$


$$\therefore X_L = \omega L \times \text{length}$$

$$= 314 \times \frac{1}{2} (1 + 4 \log_c \frac{1.7 \times 10^{-3}}{5}) \times 10^{-7} \times 15 \times 10^3$$

$$= 5.75 \quad \text{ohms}$$

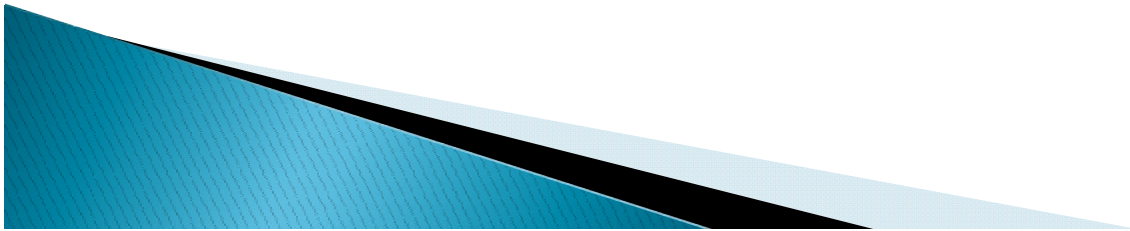


$$\begin{aligned}
\therefore V_S &\cong V_R + I_R R \cos \phi_R + I_R X_L \sin \phi_R \\
&= 6,350 + (197 \times 2.58 \times 0.8) + (197 \times 5.75 \times 0.6) \\
&= 6,350 + 1057 \\
&= 7,407 \quad \text{V per phase} \\
&= 12,780 \quad \text{V line}
\end{aligned}$$

$$\begin{aligned}
\text{Regulation} &= I_R \frac{(R \cos \phi_R + X_L \sin \phi_R)}{V_R} = \frac{V_S - V_R}{V_R} \\
&= \frac{1,057}{6,350} = 16.7 \%
\end{aligned}$$


Medium Transmission line

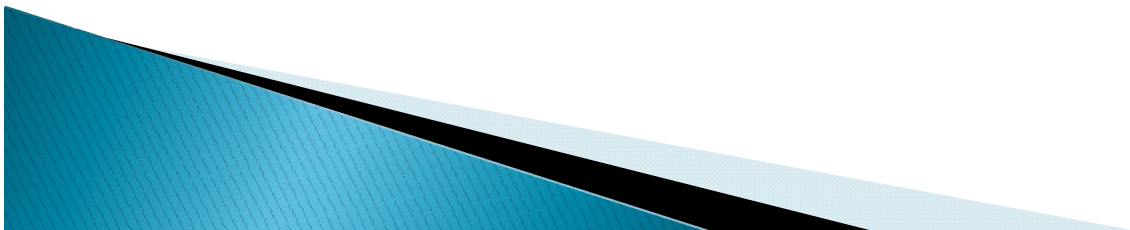- ▶ It has been mentioned in section 6.2 that the capacitance of medium length lines is significant.
- ▶ When the effect of capacitance is not negligible , it may be assumed to be concentrated at one or more definite points along the line.
- ▶ A number of localized capacitance methods have been used to make approximate line performance calculations.




- ▶ The following methods are more commonly used :

a) Nominal T method .

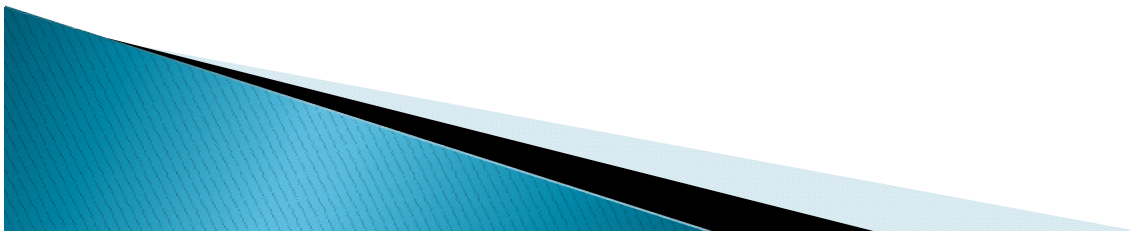b) Nominal π method .

- ▶ These methods of calculation give reasonably accurate results for the solution of most transmission-line problems .




Nominal T method .

- ▶ In a nominal T method the total line capacitance is assumed to be concentrated at the middle point of the line . The T representation of a line is shown in fig.(6.12).

Series impedance of the line $\bar{Z} = R + jX$

Shunt admittance $\bar{Y} = j\omega C$

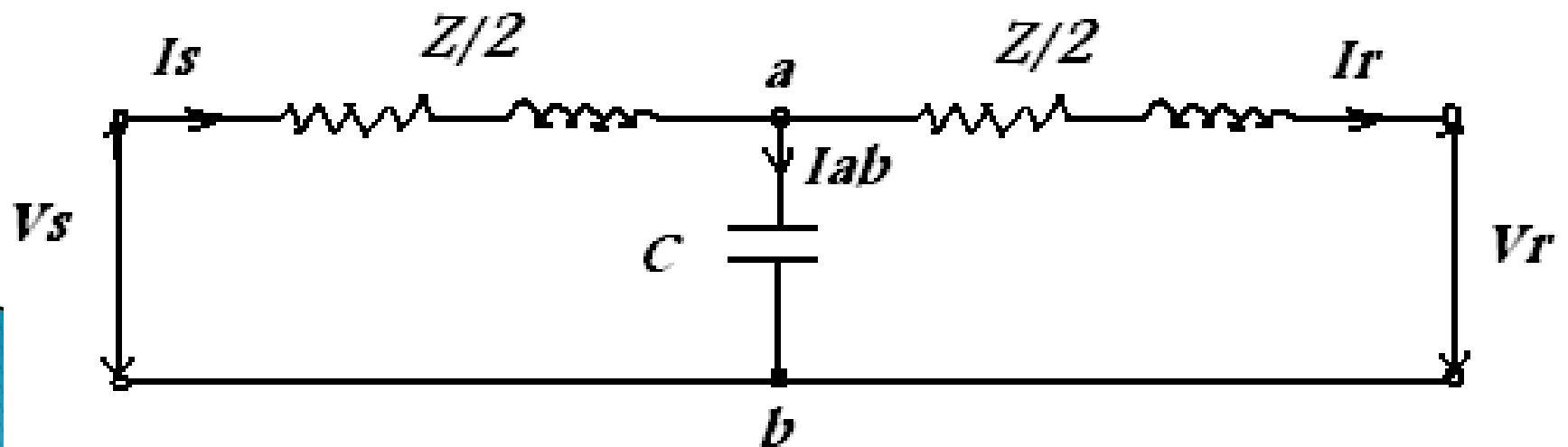

- ▶ With the usual meanings of the quantities given in fig.(2) ,
- ▶ Voltage at the mid-point of the line .

$$\bar{V}_{ab} = \bar{V}_r + \bar{I}_r \frac{\bar{Z}}{2}$$

- ▶ Current in the capacitor ,

- ▶ Sending-end current ,

$$\bar{I}_{ab} = \bar{V}_{ab} \bar{Y}$$


$$\begin{aligned} \bar{I}_s &= \bar{I}_r + \bar{I}_{ab} \\ &= \bar{I}_r + \bar{V}_{ab} \bar{Y} \\ &= \bar{I}_r + \left(\bar{V}_r + \bar{I}_r \frac{\bar{Z}}{2} \right) \bar{Y} \end{aligned}$$

$$\bar{I}_s = \bar{I}_r \left(1 + \frac{\bar{Z} \bar{Y}}{2} \right) + \bar{Y} \bar{V}_r \quad (6.13.1)$$

- ▶ Sending-end voltage ,


$$\begin{aligned}
 \bar{V}_s &= \bar{V}_{ab} + \bar{I}_s \frac{\bar{Z}}{2} \\
 &= \bar{V}_r + \bar{I}_r \frac{\bar{Z}}{2} + [\bar{I}_r (1 + \frac{\bar{Z} \bar{Y}}{2} + \bar{Y} \bar{V}_r)] \frac{\bar{Z}}{2} \\
 \bar{V}_s &= \bar{V}_r (1 + \frac{\bar{Z} \bar{Y}}{2}) + \bar{I}_r (\bar{Z} + \frac{\bar{Z} \bar{Y}}{4}) \quad (6.13.2)
 \end{aligned}$$

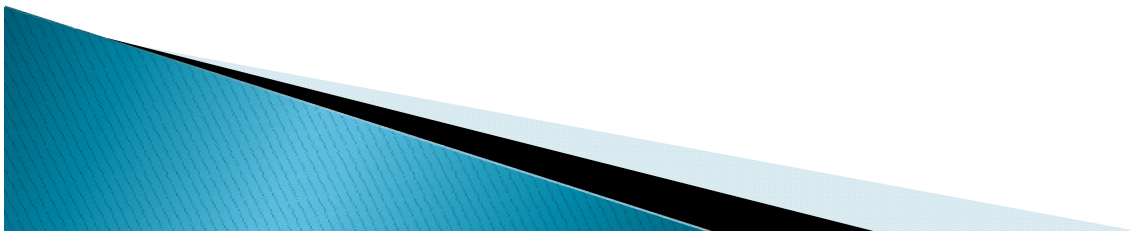- ▶ Equations (6.13.1) and (6.13.2) give the sending-end current and sending-end voltage respectively.
- ▶ Other quantities , such as phase shift, power input, efficiency, regulation, etc, can be determined in the usual manner .



Phasor diagram

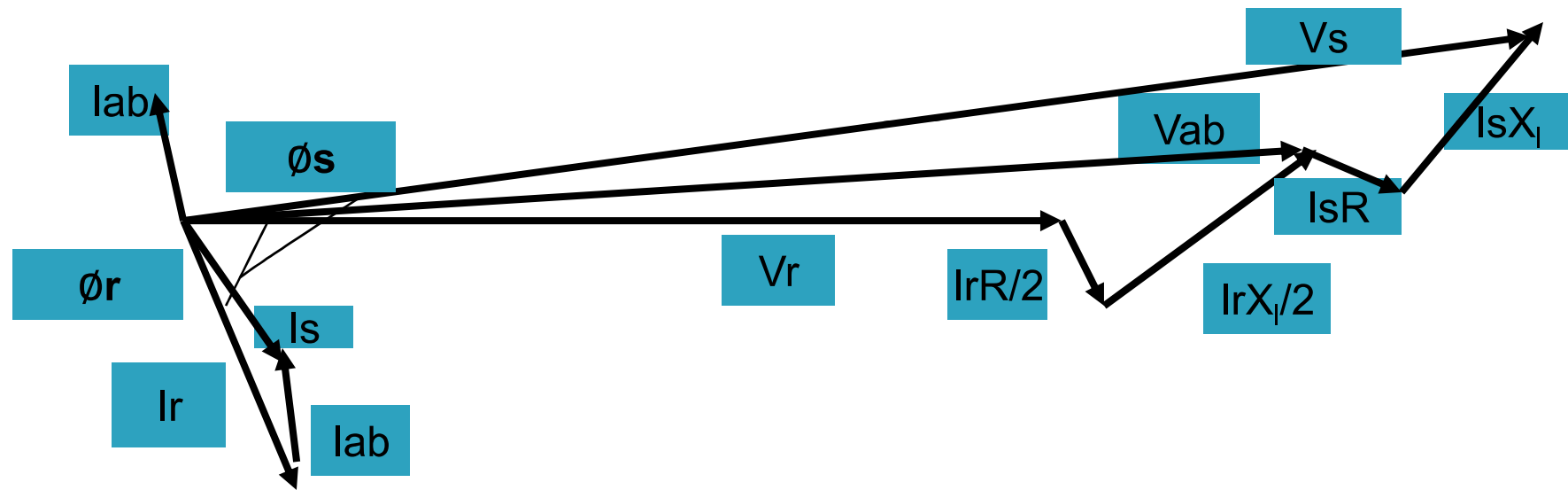- ▶ The phasor diagram of the nominal T circuit can be drawn for a lagging power factor as :



Phasor diagram of a nominal T network

► In the phasor diagram :


$OA = \bar{V}_r$: receiving-end voltage to neutral . It is taken as a reference phasor .

$OB = \bar{I}_r$: load current lagging behind \bar{V}_r by an angle ϕ_r , $\cos \phi_r$ is the power factor of the load .

$AC = I_r \frac{R}{2}$: voltage drop in the resistance of the right-hand half of the line . It is parallel to \bar{I}_r .

$CD_1 = I_r \frac{X}{2}$: voltage drop in the reactance of the right-hand half of the line . It is perpendicular to OB , i.e. , \bar{I}_r .

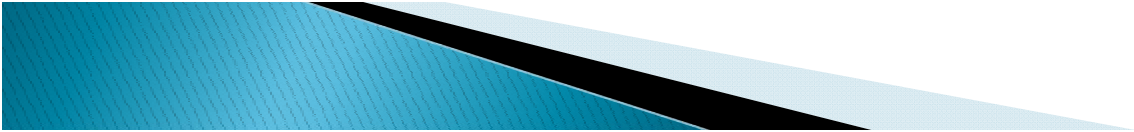$OD_1 = \bar{V}_{ab}$: voltage at the mid-point of the line across the capacitance C .



$BE = \bar{I}_{ab}$: current in the capacitor . It leads the voltage \bar{V}_{ab} by 90° .


$OE = \bar{I}_s$: sending-end current , the phasor sum of load current and capacitor current .

$D_1C_1 = I_s \frac{R}{2}$: voltage drop in the resistance in the left-hand side of the line . It is drawn parallel to \bar{I}_s .

$C_1D = I_s \frac{X}{2}$: voltage drop in the reactance in the left-hand half of the line . It is perpendicular to \bar{I}_s .


$OD = \bar{V}$: sending-end voltage . It is the phasor sum of \bar{V}_{ab} and the impedance drop in the left-hand half of the line .

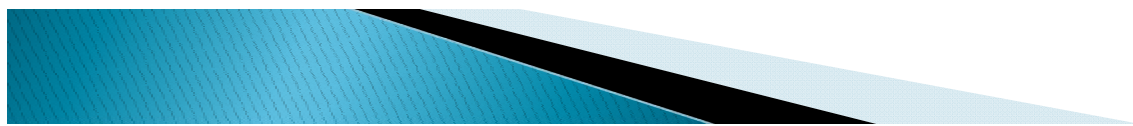ϕ_s : phase angle at the sending-end , $\cos \phi_s$ is the power factor at the sending end .



Nominal π method .

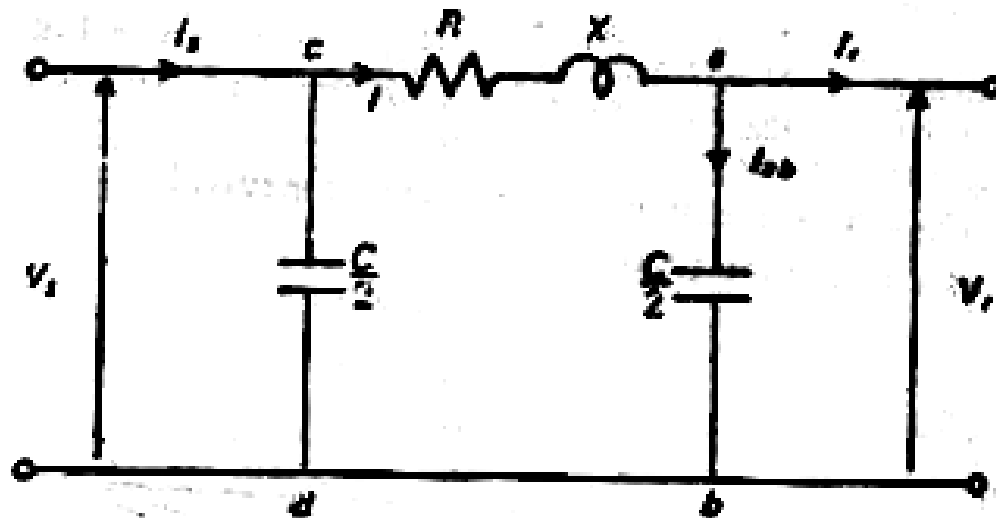- ▶ This method assumed that one-half of the total line capacitance is concentrated at each end of the line and the total resistance and inductive reactance are concentrated at the center .
- ▶ Fig.(6.14) shows the nominal π representation of the line.



- ▶ From fig.(6.14),

$$\bar{I}_{ab} = \bar{V}_r \frac{\bar{Y}}{2}$$

$$\bar{I} = \bar{I}_r + \bar{I}_{ab} = \bar{I}_r + \bar{V}_r \frac{\bar{Y}}{2}$$

- ▶ Voltage at the sending-end ,

$$\bar{V}_s = \bar{V}_r + \bar{I} \bar{Z}$$

$$= \bar{V}_r + (\bar{I}_r + \bar{V}_r \frac{\bar{Y}}{2}) \bar{Z}$$

$$= (1 + \frac{\bar{Z} \bar{Y}}{2}) \bar{V}_r + \bar{Z} \bar{I}_r$$

(6.14.1)

$$\begin{aligned}\bar{I}_{cd} &= \bar{V}_s \frac{\bar{Y}}{2} \\ &= \left[\left(1 + \frac{\bar{Z} \bar{Y}}{2} \right) \bar{V}_r + \bar{Z} \bar{I}_r \right] \frac{\bar{Y}}{2}\end{aligned}$$

- ▶ Sending-end current,


$$\bar{I}_s = \bar{I} + \bar{I}_{cd}$$

$$\begin{aligned}\bar{I}_s &= \bar{I}_r + \bar{V}_r \frac{\bar{Y}}{2} + \left[\left(1 + \frac{\bar{Z} \bar{Y}}{2} \right) \bar{V}_r + \bar{Z} \bar{I}_r \right] \frac{\bar{Y}}{2} \\ &= \left(\bar{Y} + \frac{\bar{Z} \bar{Y}^2}{4} \right) \bar{V}_r + \left(1 + \frac{\bar{Z} \bar{Y}}{2} \right) \bar{I}_r\end{aligned}\quad (6.14.2)$$

- ▶ Equations (6.14.1) and (6.14.2) give the sending-end voltage and current respectively . The other calculations can be made in the usual manner.

Phasor diagram

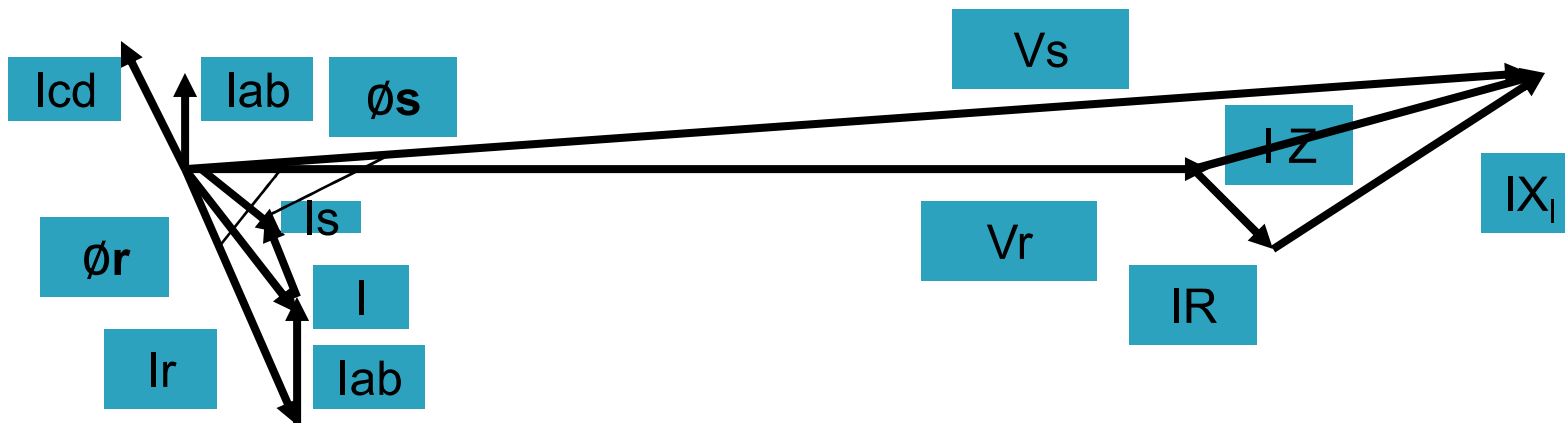- ▶ The phasor diagram of a nominal π circuit is can be drawn for a lagging power factor of the load as :



Phasor diagram of a nominal π network

Example

A three-phase, 50 Hz, transmission line, 40 km long delivers 36 Mw at 0.8 power factor lagging at 60 kv (phase). The line constants per conductor are ,

$$R = 2.5 \Omega , L = 0.1 H , C = 0.25 \mu F$$

Shunt leakage may be neglected. Find the sending-end voltage , current , phase angle, and the efficiency . Use (a) nominal **T** method, (b) nominal **π** method.

Solution

Phase voltage at the receiving-end

$$V_r = 60 \text{ kv} = 60 \times 10^3 \text{ v}$$

$$\text{Power per phase} = \frac{1}{3} \times 36 \text{ Mw} = 12 \times 10^6 \text{ w}$$

- ▶ Therefore, the receiving-end current ,

$$I_r = \frac{12 \times 10^6}{60 \times 10^3 \times 0.8} = 250 \quad \text{A}$$

- ▶ Taking \bar{V}_r as the reference phasor,

$$\bar{V}_r = V_r + jQ$$

$$\cos \phi_r = 0.8 \quad , \quad \sin \phi_r = 0.6$$

$$\begin{aligned} \bar{I}_r &= I_r \cos \phi_r - j I_r \sin \phi_r \\ &= 250 \times 0.8 - j 250 \times 0.6 = 200 - j 150 \end{aligned}$$

- ▶ Reference per phase,

$$R = 2.5 \quad \Omega$$


- ▶ Inductive reactance per phase ,

$$X = 2 \pi f L = 2 \times 3.14 \times 50 \times 0.1 = 31.4 \quad \Omega$$


- ▶ Series impedance per phase,

$$\begin{aligned} \bar{Z} &= R + jX = 2.5 + j 31.4 = 31.4 \angle \tan^{-1} 12.56 \\ &= 31.4 \angle 85.4^\circ \quad \Omega \end{aligned}$$

- ▶ Shunt admittance per phase

$$\begin{aligned} Y &= 2 \pi f C = 2 \times 3.14 \times 50 \times 0.25 \times 10^{-6} \\ &= 78.5 \times 10^{-6} \quad \text{siemens} \end{aligned}$$
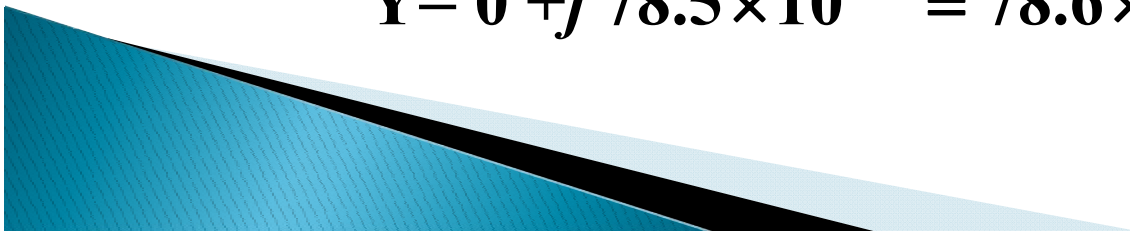
$$Y = 0 + j 78.5 \times 10^{-6} = 78.6 \times 10^{-6} \angle 90^\circ$$



Calculation by nominal T method

- ▶ The nominal T circuit for the line is shown in Fig.(6.1).

$$\begin{aligned}\bar{V}_{ab} &= \bar{V}_r + \bar{I}_r \frac{\bar{Z}}{2} \\ &= V_r + j 0 + (I_r \cos \phi_r - j I_r \sin \phi_r) \left(\frac{R}{2} + j \frac{X}{2} \right) \\ &= 60 \times 10^3 + (200 - j 150)(1.25 + j 15.7) \\ &= 60 \times 10^3 + 2.605 + j 2959 \\ &= (62.605 - j 2.959) \times 10^3 \quad \text{v}\end{aligned}$$

- ▶ The current in the capacitor ,

$$\begin{aligned}\bar{I}_{ab} &= \bar{Y} \bar{V}_{ab} \\ &= j 78.6 \times 10^{-6} (62.605 - j 2.959) \times 10^3 \\ &= -0.2315 + j 4.903\end{aligned}$$

- ▶ The current at the sending-end ,

$$\begin{aligned}\bar{I}_s &= \bar{I}_r + \bar{I}_{ab} \\ &= (200 - j 150) + (-0.2315 + j 4.903) \\ &= 199.8 - j 145 \\ &= [(199.8)^2 + (145)^2]^{1/2} \angle \tan^{-1}(-145/199.8) \\ &= 247 \angle -\tan^{-1} 0.7257 \\ &= 247 \angle -35^\circ 57'\end{aligned}$$

- ▶ Voltage drop in the left-hand half of the line ,

$$\begin{aligned}&= \bar{I}_s \frac{\bar{Z}}{2} = (199.8 - j 145)(1.25 + j 15.7) \\ &= 2527 + j 2959\end{aligned}$$



- ▶ Voltage at the sending-end ,

$$\begin{aligned}
 \bar{V}_s &= \bar{V}_{ab} + \bar{I}_s \frac{\bar{Z}}{2} \\
 &= 62.605 + j 2959 + 2527 + j 2959 \\
 &= 65132 + j 5918 \\
 &= [(65132)^2 + (5918)^2]^{1/2} \angle \tan^{-1}(5918/65132) \\
 &= 65450 \angle \tan^{-1} 0.09077 \\
 &= 65450 \angle 5^\circ 11' \quad \text{v/phase}
 \end{aligned}$$

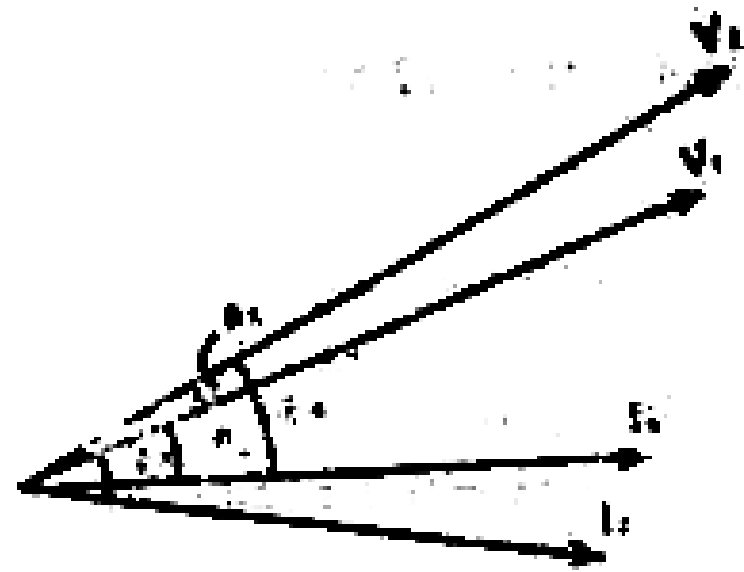


Fig.(6.16):Phasor diagram

- ▶ Sending-end line voltage ,

$$=65450\sqrt{3} = 113400 \quad \text{v}$$

$$=113.4 \quad \text{kv}$$


- ▶ Phase difference between \bar{V}_s and \bar{I}_s ,

$$\phi_s = 5^\circ 11' - (-35^\circ 57')$$

$$= 41^\circ 8'$$

- ▶ Sending-end power factor ,
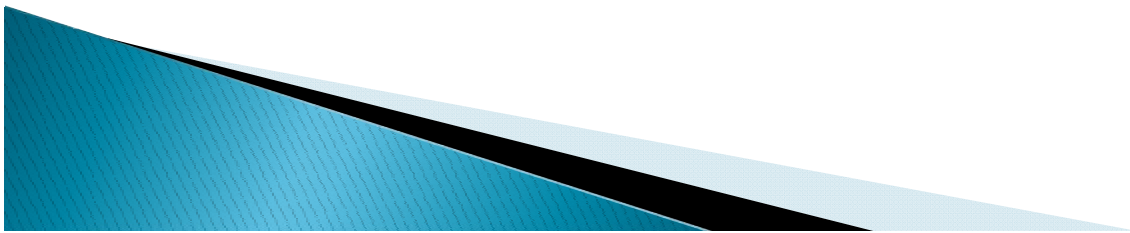
$$\cos \phi_s = \cos 41^\circ 8' = 0.7532$$



- ▶ Power loss in the line ,


$$\begin{aligned} &= 3I_r^2 \frac{R}{2} + 3I_s^2 \frac{R}{2} \\ &= 3 \times (250)^2 \times 1.25 + 3 \times (247)^2 \times 1.25 \\ &= 463.2 \times 10^3 \quad \text{W} \end{aligned}$$

- ▶ Transmission efficiency ,

$$\begin{aligned} \eta_T &= \frac{\text{Power output}}{\text{Power output} + \text{Power loss}} \\ &= \frac{36 \times 10^6}{36 \times 10^6 + 463.2 \times 10^3} \\ &= 0.9872 \quad \text{or} \quad 98.72 \text{ per cent} \end{aligned}$$

- ▶ Alternatively , transmission efficiency may be calculated as follows :
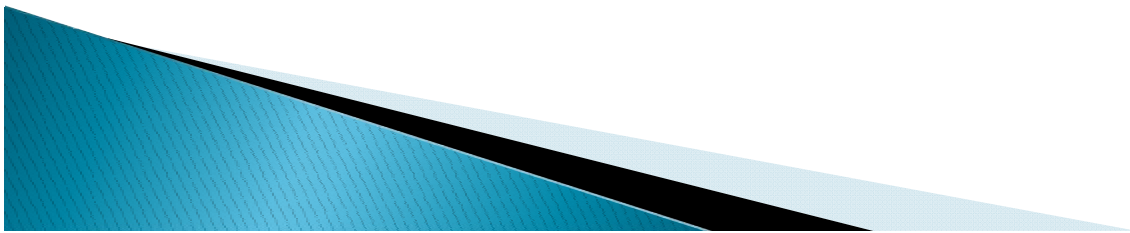
$$\begin{aligned}\eta_T &= \frac{3V_r I_r \cos\phi_r}{3V_s I_s \cos\phi_s} \\ &= \frac{36 \times 10^6}{3 \times 65450 \times 247 \times 0.7532} \\ &= 0.986 \quad \text{or} \quad 98.6 \text{ per cent}\end{aligned}$$



Calculation by nominal π method

- ▶ The nominal circuit for the line is shown in Fig.(6.14)

$$\begin{aligned}\bar{I}_{ab} &= \frac{\bar{Y}}{2} \bar{V}_r \\ &= j 39.3 \times 10^{-6} \times 60 \times 10^3 = j 2.35\end{aligned}$$

$$\begin{aligned}\bar{I} &= \bar{I}_r + \bar{I}_{ab} \\ &= (200 - j 150) + j 2.35 \\ &= 200 - j 147.65 \\ &= [(200)^2 + (147.65)^2]^{1/2} \angle \tan^{-1}(-147.65/200) \\ &= 245.6 \angle -36^\circ 26'\end{aligned}$$

- ▶ Voltage drop per phase ,

$$\begin{aligned} &= \bar{I} \bar{Z} = (200 - j 147.65)(2.5 + j 31.4) \\ &= 5136 + j 5910 \end{aligned}$$

- ▶ Voltage at the sending-end per phase ,

$$\begin{aligned} \bar{V}_s &= \bar{V}_{ab} + \bar{I} \bar{Z} \\ &= 60 \times 10^3 + 5136 + j 5910 \\ &= 65136 + j 5910 \\ &= [(65136)^2 + (5910)^2]^{1/2} \angle \tan^{-1}(5910/65136) \\ &= 65390 \angle 5^\circ 11' \quad \text{v/phase} \end{aligned}$$


▶ Sending-end line voltage ,

$$= 65390\sqrt{3} = 113.2 \quad \text{kV}$$

$$\bar{I}_{cd} = \frac{\bar{Y}}{2} \bar{V}_s$$

$$= j 39.3 \times 10^{-6} (65136 + j 5190)$$


$$= -0.232 + j 2.557$$

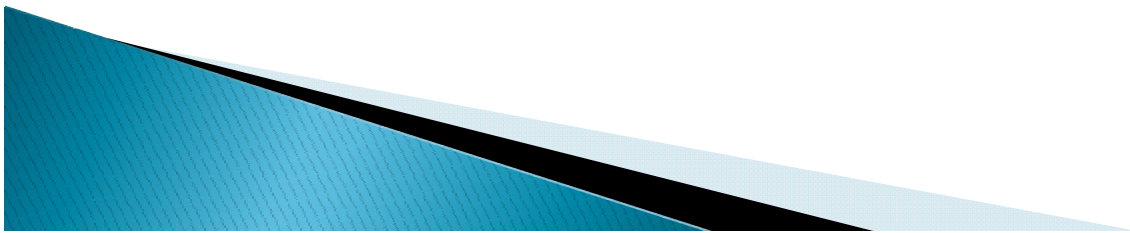

Sending-end current ,

$$\begin{aligned}\bar{I}_s &= \bar{I}_r + \bar{I}_{cd} \\ &= (200 - j 150) + -0.232 + j 2.557 \\ &= 199.8 - j 145 \\ &= [(199.8)^2 + (145)^2]^{1/2} \angle \tan^{-1}(-145/199.8) \\ &= 247 \angle -35^\circ 57' \quad \text{A}\end{aligned}$$

Phase difference between \bar{V}_s and \bar{I}_s ,
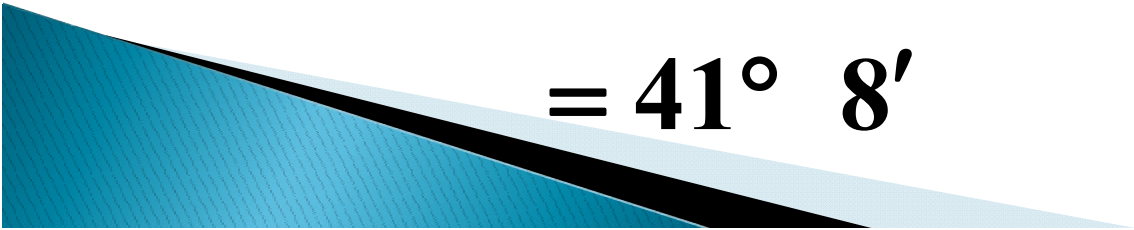
$$\begin{aligned}\phi_s &= 5^\circ 11' - (-35^\circ 57') \\ &= 41^\circ 8'\end{aligned}$$


- ▶ Sending-end power factor ,

$$\cos\phi_s = \cos 41^\circ 8' = 0.7532$$

- ▶ Power loss in the line ,

$$= 3 I^2 R$$

$$= 3 \times (248.6)^2 \times 2.5$$

$$= 463.6 \text{ Kw}$$

- ▶ Transmission efficiency ,

$$\eta_T = \frac{36 \times 10^6}{36 \times 10^6 + 463.6 \times 10^3}$$
$$= 0.9873 \text{ or } 98.73 \text{ per cent}$$

Example

- A three-phase , 50 Hz , 150 km line operates at 110 Kv between the lines at the sending-end. The total inductance and capacitance per phase are (0.2 H) and (1.5 μF) . Neglecting losses calculate the value of receiving-end load having a power factor of unity for which the voltage at the receiving-end will be the same as that at the sending-end . Assume one-half of the total capacitance of the line to be concentrated at each end .

Solution

- The circuit for the given line is shown in fig.(6.17) . It is a nominal representation .

$$V_r = V_s = \frac{110 \times 1000}{\sqrt{3}} = 63510 \quad v$$

- ▶ Inductive reactance per phase ,


$$X_L = 2 \pi f L = 2 \times 3.14 \times 50 \times 0.2 = 62.8 \quad \Omega$$

- ▶ Series impedance per phase ,

$$\bar{Z} = j X_L = j 62.8 \quad \Omega$$


- ▶ Shunt admittance per phase ,

$$\begin{aligned} Y &= 2 \pi f C = 2 \times 3.14 \times 50 \times 1.5 \times 10^{-6} \\ &= 4.71 \times 10^{-4} \quad \text{siemens} \end{aligned}$$

$$\bar{Y} = j 4.71 \times 10^{-4}$$


Taking \bar{V}_r as the reference phasor ,

$$\bar{V}_r = V_r + j 0$$

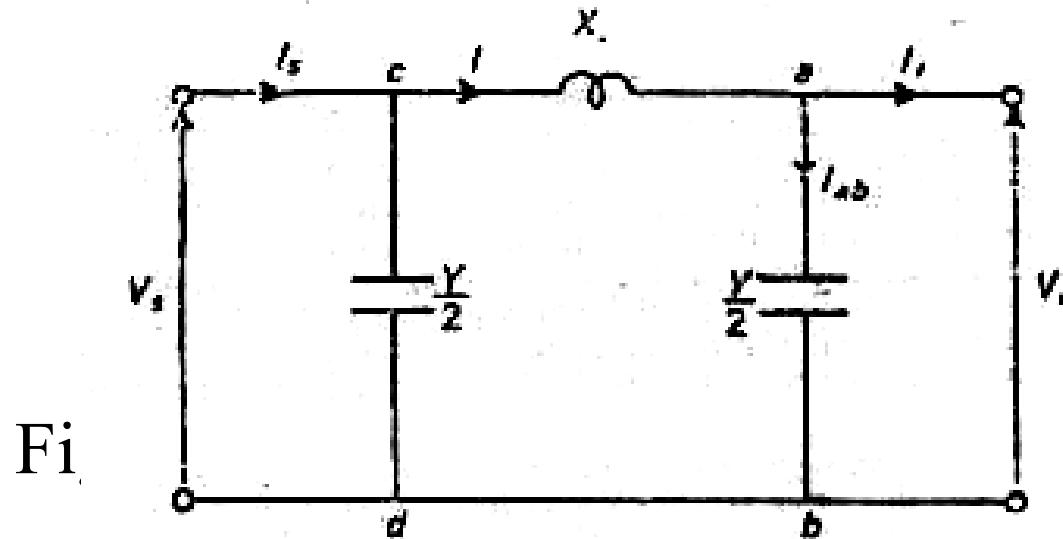

- ▶ Current in the load-end capacitor ,


$$\bar{I}_{ab} = \frac{\bar{Y}}{2} \bar{V}_r = j \frac{4.71}{2} \times 10^{-4} \times 63510 = j 14.96 \quad A$$

- ▶ Let the load current be I_r . Since the load power factor is unity ,

$$\bar{I}_r = I_s \angle 0^\circ = I_s + j 0$$

- ▶ Current through the inductive reactance ,
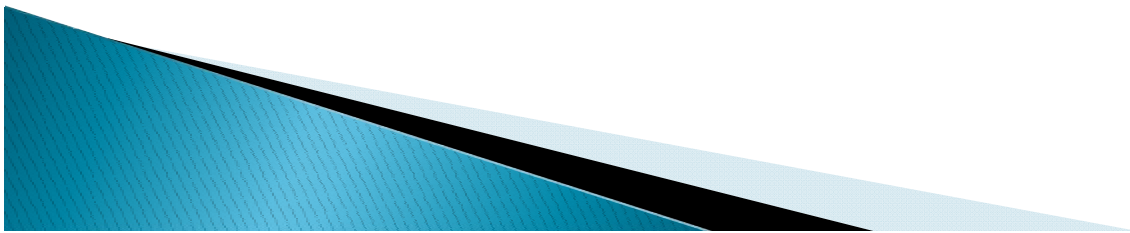
$$\begin{aligned} \bar{I} &= \bar{I}_r + \bar{I}_{ab} \\ &= \bar{I}_r + j 14.96 \end{aligned}$$



► Sending-end voltage ,

$$\begin{aligned}\bar{V}_s &= \bar{V}_r + \bar{I} \bar{Z} \\ &= V_r + j 0 + (\bar{I}_r + j 14.96)(j 62.8) \\ &= (V_r - 939.5) + j 62.8 I_r\end{aligned}$$

$$\begin{aligned}V_s^2 &= (V_r - 939.5)^2 + (62.8 I_r)^2 \\ (63510)^2 &= (63510 - 939.5)^2 + (62.8 I_r)^2 \\ (62.8 I_r)^2 &= 118 \times 10^6\end{aligned}$$

$$\therefore I_r = \frac{10862}{62.8} = 173 \quad A$$

