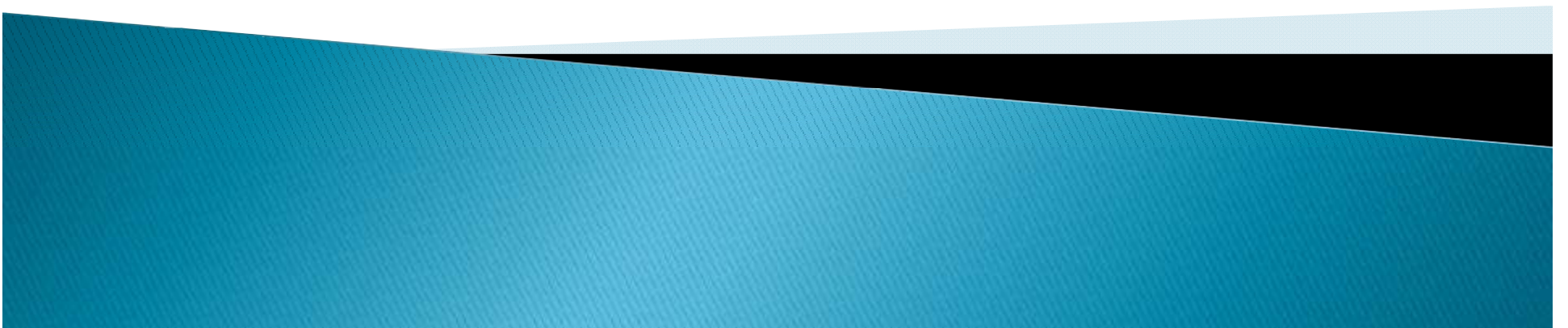



# Power Systems Analysis

## ET-321



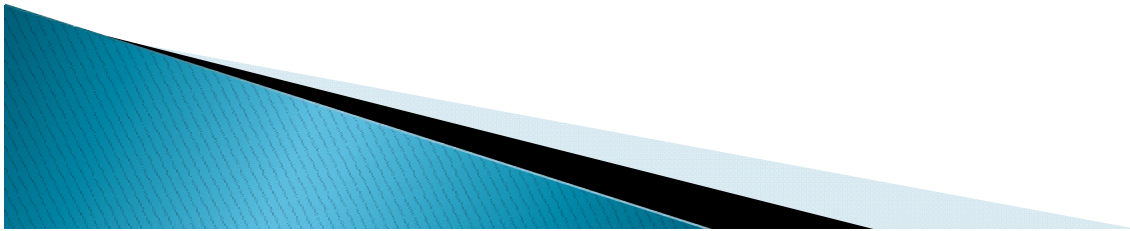
# References

- **Elements of power system analysis**  
( **William Stevenson** )
- **Power system analysis**  
( **Hadi Sadaat** )



# *General Network* *Constants*

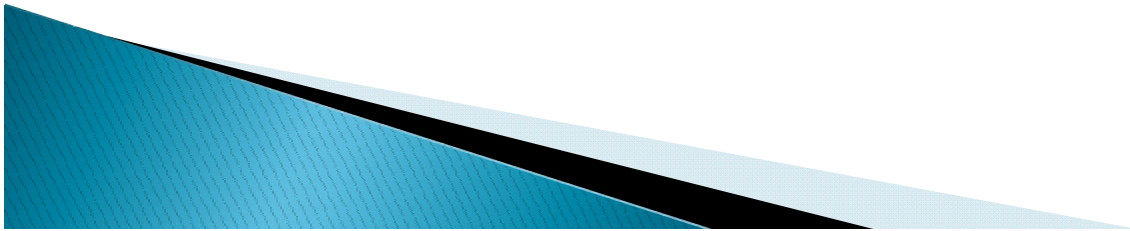

# Introduction

- ▶ A network having two input and two output terminals is known as a two-port network . It may also be called a two-terminal-pair network or quadruple network . In fig.(1 . a,b) represent the input pair terminals and ( c,d ) the output pair terminals . The two pairs of terminals are usually shown to be enclosed in a box .


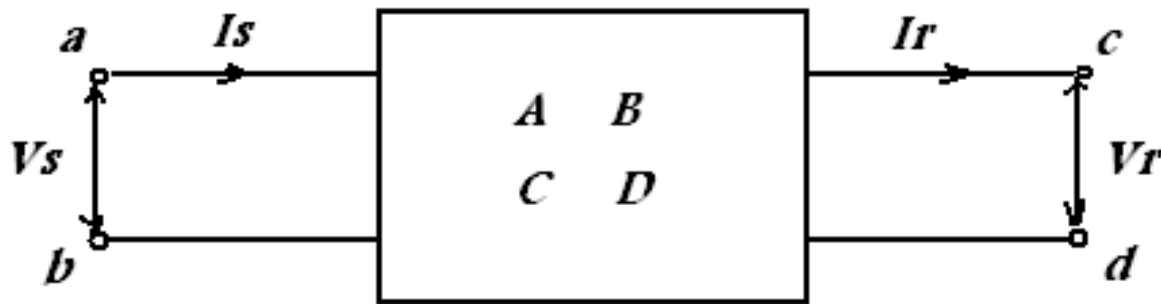


Fig.( 1 ) :Two-port network .

- ▶ A circuit consisting of any arrangement of its components is connected to these terminals .

$$\left. \begin{aligned} V_s &= AV_r + BI_r \\ I_s &= CV_r + DI_r \end{aligned} \right\} \quad (1.1)$$

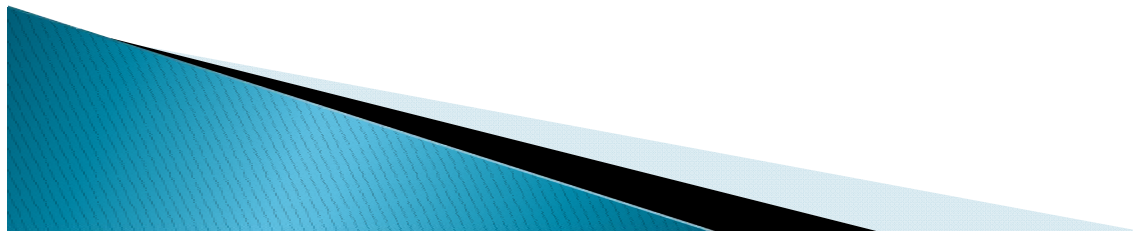
- ▶ Where  $A$  ,  $B$  ,  $C$  ,  $D$  are called the general network constants of the system . These constants are known by other names like transmission parameters , chain parameters and auxiliary network constants .



- ▶ Equation (1) can be put in the matrix form as :

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_r \\ I_r \end{bmatrix} \quad (1.2)$$

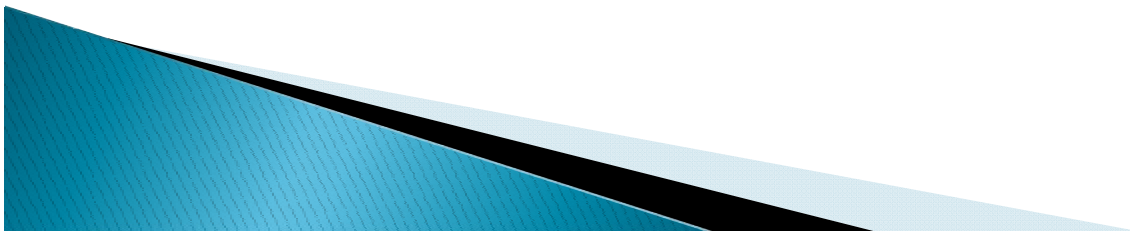- ▶ The matrix  $\begin{bmatrix} A & B \\ C & D \end{bmatrix}$  is called the transfer matrix or transmission matrix of the network



# Cascaded network

- ▶ The overall **A** , **B** , **C** , **D** constants for several 2-port networks connected in cascade ( or chain arrangement ) can be found out easily . Fig.( 2 ) shows two cascaded networks , and one that is the equivalent of both . The constants of the two component networks are **A**<sub>1</sub> , **B**<sub>1</sub> , **C**<sub>1</sub> , **D**<sub>1</sub> and **A**<sub>2</sub> , **B**<sub>2</sub> , **C**<sub>2</sub> , **D**<sub>2</sub> . Let the constants for the equivalent network be **A**<sub>0</sub> , **B**<sub>0</sub> , **C**<sub>0</sub> , **D**<sub>0</sub> .

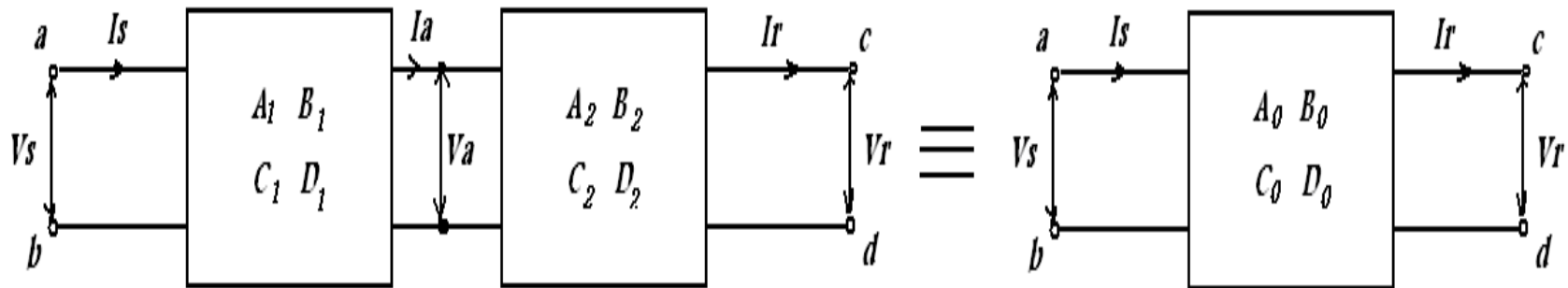



Fig.( 2 ) : Two cascaded networks and their equivalents.

- ▶ Let  $V_a$  and  $I_a$  be the voltage and current respectively at the junction (a) of the two networks.

$$\left. \begin{aligned} V_a &= A_2 V_r + B_2 I_r \\ I_a &= C_2 V_r + D_2 I_r \end{aligned} \right\} \quad (2.1)$$

- ▶ For the network ( 1 ),
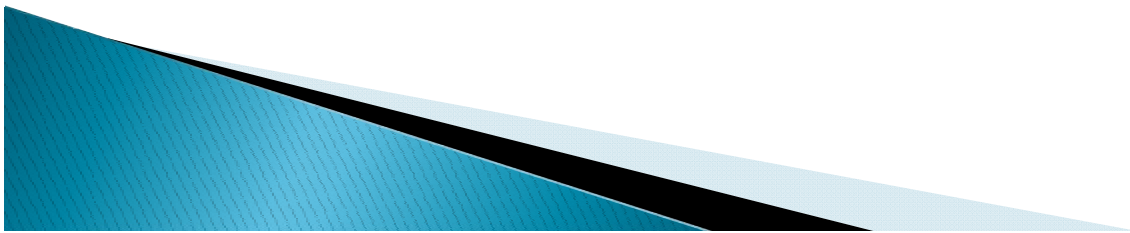
$$\left. \begin{aligned} V_s &= A_1 V_a + B_1 I_a \\ I_s &= C_1 V_a + D_1 I_a \end{aligned} \right\} \quad (2.2)$$






- ▶ Substituting the values of  $V_a$  and  $I_a$  from the first set of equations in the second set, we have :

$$\begin{aligned} V_s &= A_1 (A_2 V_r + B_2 I_r) + B_1 (C_2 V_r + D_2 I_r) \\ &= (A_1 A_2 + B_1 C_2) V_r + (A_1 B_2 + B_1 D_2) I_r \end{aligned} \quad (2.3)$$
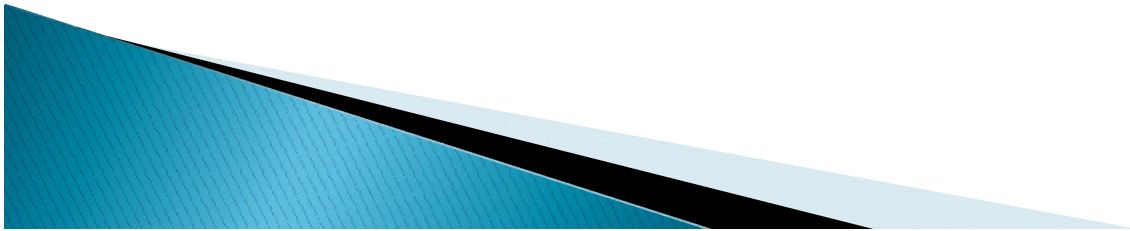
$$\begin{aligned} I_s &= C_1 (A_2 V_r + B_2 I_r) + D_1 (C_2 V_r + D_2 I_r) \\ &= (C_1 A_2 + D_1 C_2) V_r + (C_1 B_2 + D_1 D_2) I_r \end{aligned} \quad (2.4)$$



- ▶ The sending-end voltage and current for the equivalent network with constants  $A_0, B_0, C_0, D_0$  are given by :

- ▶ Equating the constants of  $V_s$  and  $I_s$ , the overall constants for the two networks in cascade are :
 
$$\left. \begin{aligned} V_s &= A_0 V_a + B_0 I_a \\ I_s &= C_0 V_a + D_0 I_a \end{aligned} \right\} \quad (2.5)$$


$$\left. \begin{aligned} A_0 &= A_1 A_2 + B_1 C_2 \\ B_0 &= A_1 B_2 + B_1 D_2 \\ C_0 &= C_1 A_2 + D_1 C_2 \\ D_0 &= C_1 B_2 + D_1 D_2 \end{aligned} \right\} \quad (2.6)$$

- ▶ Matrix method . For the first network ,

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} V_a \\ I_a \end{bmatrix} \quad (2.7)$$

- ▶ But  $V_a$  and  $I_a$  are the input voltage and current respectively of the second network , so that :
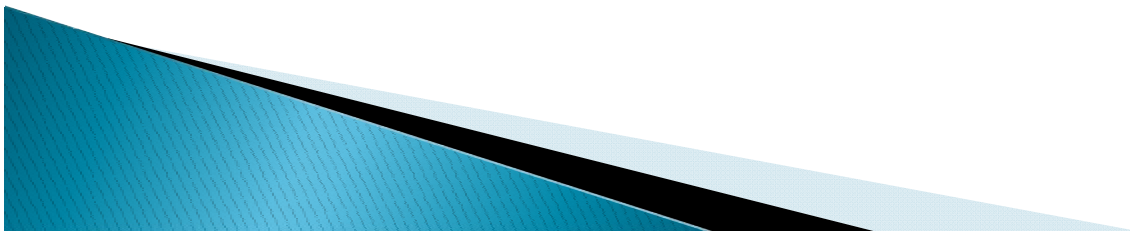
$$\begin{bmatrix} V_a \\ I_a \end{bmatrix} = \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} V_r \\ I_r \end{bmatrix} \quad (2.8)$$



- ▶ Combining these equations ,

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} V_r \\ I_r \end{bmatrix} \quad (2.9)$$

- ▶ For the equivalent network ,

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} A_0 & B_0 \\ C_0 & D_0 \end{bmatrix} \begin{bmatrix} V_r \\ I_r \end{bmatrix} \quad (2.10)$$

- ▶ Comparing equations (2.9) and (2.10) we get ,


$$\begin{bmatrix} A_0 & B_0 \\ C_0 & D_0 \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \quad (2.11)$$

## Relations between $A, B, C, D$ constants

- ▶ The relations between  $A, B, C, D$  constants of a passive, linear and bilateral network can be found with the help of reciprocity theorem. First a voltage  $V$  is applied to the input terminals keeping the output terminals short circuited fig.( 3 ,a ). Since under short circuit  $V_r = 0$ , equations ( 1.1 ) give :

$$V = B I_{rs} \quad (3.1)$$


$$I_{ss} = D I_{rs} \quad (3.2)$$

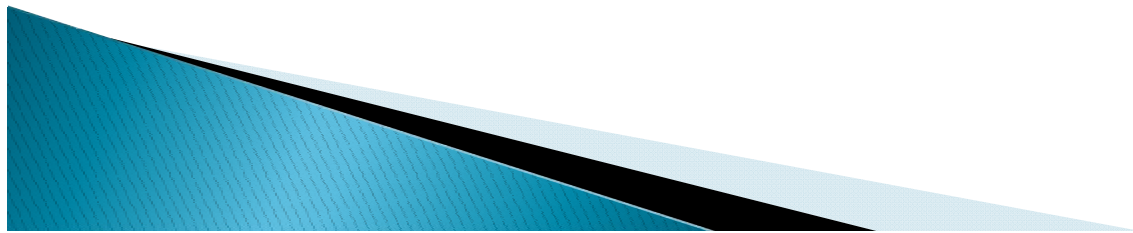

- ▶ Now , the voltage  $V$  is applied to the output terminals and the input terminals are short circuited fig.( 3 ,b ) . The directions of flow of currents at the input and output terminals are reversed and the sending-end voltage  $V_s$  becomes zero. Equation ( 1.1 ) become :

$$\mathbf{0 = AV - BI'_r}$$

$$\mathbf{I'_r = \frac{AV}{B}} \quad \mathbf{(3.3)}$$
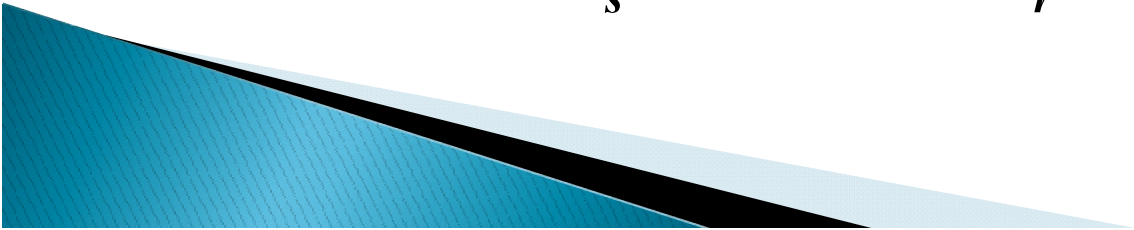
$$\mathbf{-I'_s = CV - DI'_r} \quad \mathbf{(3.4)}$$


- ▶ Since the network is passive , by the reciprocity theorem ,

$$I'_s = I_{rs} \quad (3.5)$$

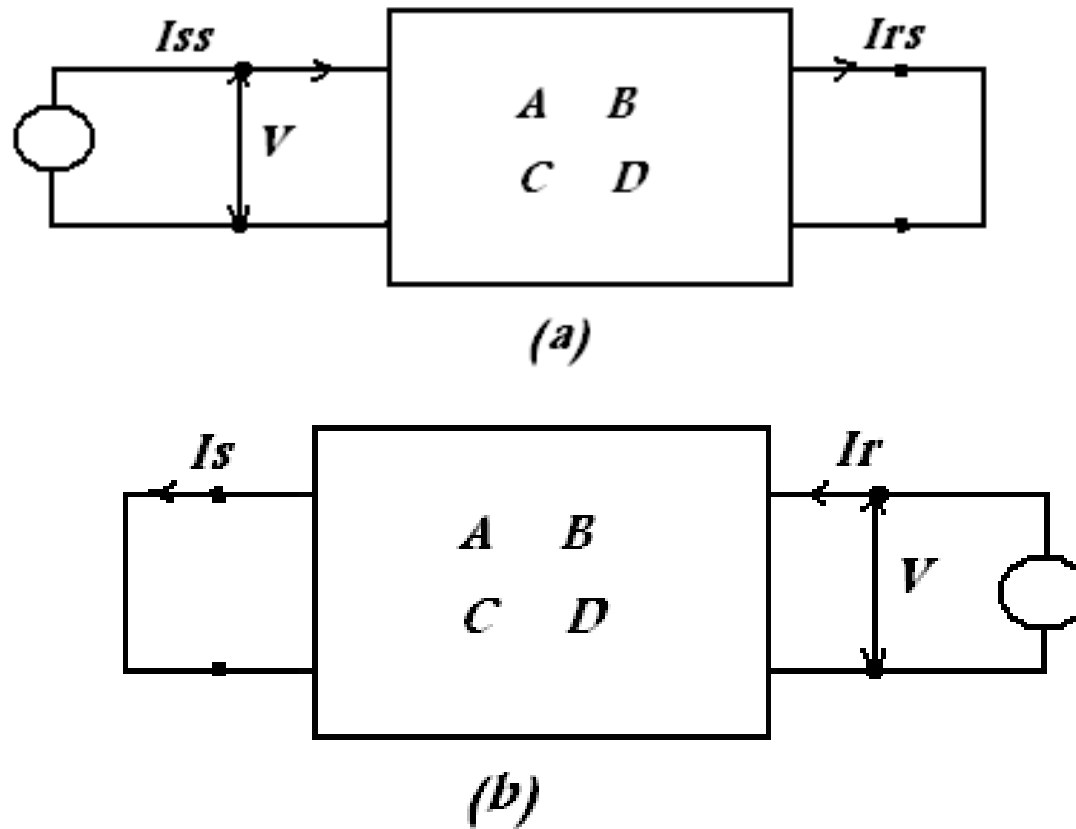


Fig.( 3 )

- ▶ Combining equations ( 3.1 ), ( 3.3 ), ( 3.4 ) and ( 3.5 ) we get ,

$$-I_{rs} = CV - \frac{DAV}{B}$$

$$-\frac{V}{B} = CV - \frac{DAV}{B}$$

- ▶ Dividing both the sides of the above equation by  $-V/B$  we get ,

$$AD - BC = 1 \quad (3.6)$$

- ▶ Equation ( 3.6 ) is of one of the required relations between the network constants. This relation may also be put in the determinant form as :

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = 1$$



# Series impedance circuit

- ▶ A circuit having a series impedance  $Z$  is shown in fig.(4) . Such a case is found in a short transmission line where the line capacitance is negligible and the shunt admittance  $Y$  is zero . A transformer with magnetizing current neglected can also be represented by such a circuit .

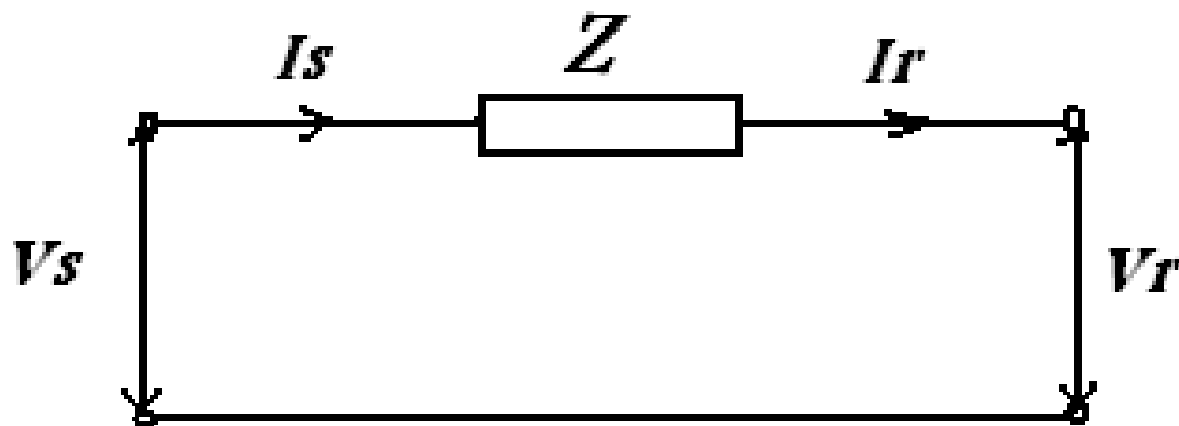


Fig.( 4 ) :Series impedance circuit .

- ▶ For the network shown in fig.( 4 ) we may write :


$$\left. \begin{aligned} V_s &= V_r + Z I_r \\ I_s &= I_r \end{aligned} \right\} \quad (4.1)$$

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix} \begin{bmatrix} V_r \\ I_r \end{bmatrix} \quad (4.2)$$

- ▶ By comparing these equations with the general equations (1.1) and (1.2) the general constants for the series impedance network can be written as :

$$\left. \begin{aligned} A &= 1 & B &= Z \\ C &= 0 & D &= 1 \end{aligned} \right\} \quad (4.3)$$

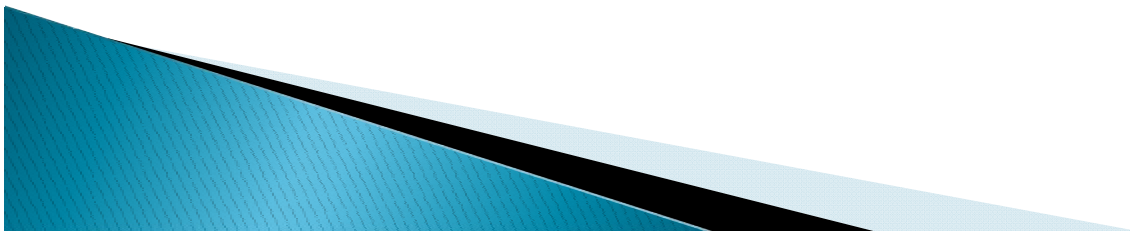- ▶ The transfer matrix for the network is  $\begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix}$



# Shunt admittance circuit

- ▶ Fig.( 5 ) , shows a transmission network with a shunt admittance  $Y$  . Such a network may represent the magnetizing current circuit of a transformer or a shunt capacitor .


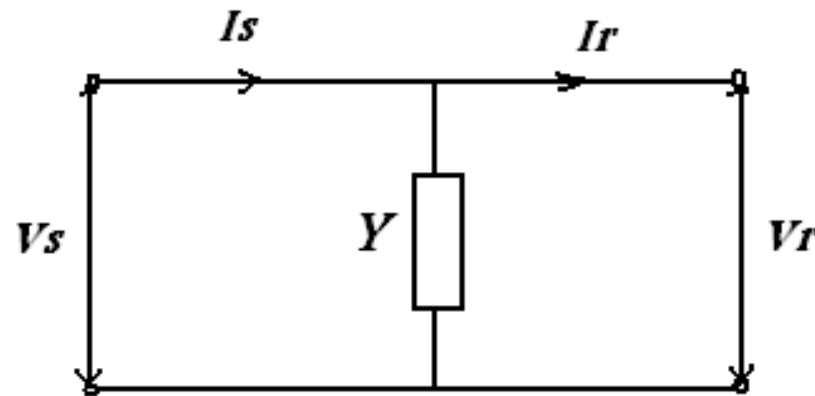


Fig.( 5 ) : Shunt admittance circuit

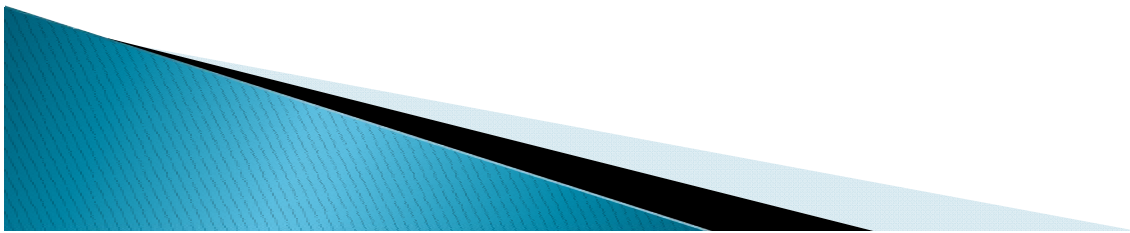


- ▶ For the network shown in fig.( 5 ) we may write :

$$\left. \begin{aligned} V_s &= V_r \\ I_s &= Y V_r + I_r \end{aligned} \right\} \quad (5.1)$$

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix} \begin{bmatrix} V_r \\ I_r \end{bmatrix} \quad (5.2)$$

- ▶ Hence,
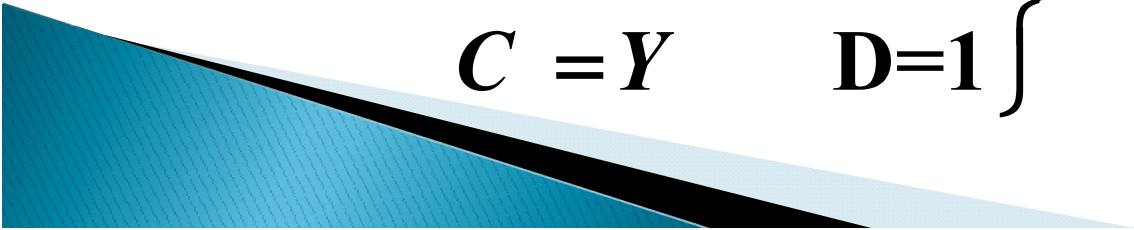
$$\left. \begin{aligned} A &= 1 & B &= 0 \\ C &= Y & D &= 1 \end{aligned} \right\} \quad (5.3)$$


# Half - T network

- ▶ A half - T network is shown in fig.( 6 ) .

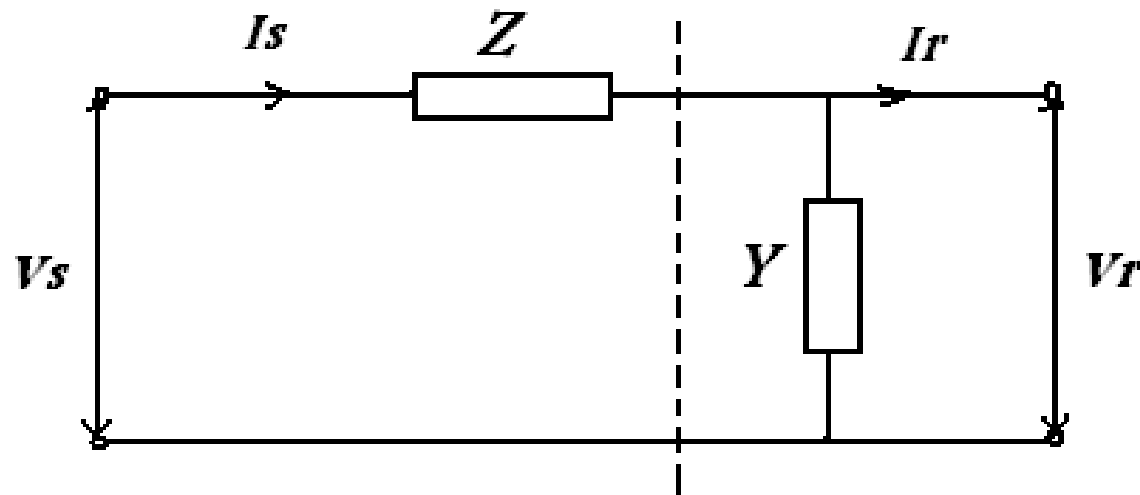



Fig.( 6 ): Half-T network .

$$\begin{aligned}
 V_s &= V_r + Z I_r \\
 &= V_r + (Y V_r + I_r) Z \\
 &= (1 + Z Y) V_r + Z I_r
 \end{aligned}$$

▶ Hence, 
$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} (1 + Z Y) & Z \\ Y & 1 \end{bmatrix} \begin{bmatrix} V_r \\ I_r \end{bmatrix} \tag{6.1}$$

$$\left. \begin{aligned}
 A &= 1 + Z Y & B &= Z \\
 C &= Y & D &= 1
 \end{aligned} \right\} \tag{6.2}$$


- ▶ Matrix method , The half –  $T$  network can be considered as the cascade connection of two sections . One section is a series impedance  $Z$  and the other a shunt admittance  $Y$  . The overall constants are obtained from the matrix product of the transfer matrices of each section in the correct order.

$$\begin{aligned} \begin{bmatrix} V_s \\ I_s \end{bmatrix} &= \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix} \begin{bmatrix} V_r \\ I_r \end{bmatrix} \\ &= \begin{bmatrix} (1+ZY) & Z \\ Y & 1 \end{bmatrix} \begin{bmatrix} V_r \\ I_r \end{bmatrix} \end{aligned}$$

