

# LAB SESSION 6

## MODELING COMMON PROBLEMS OF CONTROL SYSTEMS

### OBJECTIVE

- To explore the use of LTIView in control systems simulation.

### EQUIPMENT

- MATLAB / SIMULINK

### PROCEDURE

#### LTIView:

'LTIVIEW' is used to create several plots to a Linear Time Invariant (LTI) system. The syntax for LTIVIEW is

$$\text{ltiview}(\text{sys})$$

where 'sys' is a system model.

Various plots can be selected for viewing by right clicking on the current plot and then selecting 'plot type' and then clicking on the desired plot.

Find the transfer function ( $V_L / V$ ) of the following circuit using symbolic toolbox.

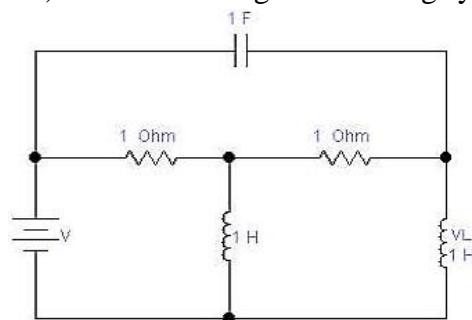


Figure 6.1: An Electrical Circuit

Once transfer function is determined, name it 'Gs'.

Following commands will convert symbolic object to transfer function object.

```
[numga,denga]=numden(Gs);
```

```
numga=sym2poly(numga);
```

```
denga=sym2poly(denga);
```

```
VL=tf(numga,denga)
```

Having found transfer function, enter

```
ltiview (VL)
```

The resulting window will show the step response considering output across inductor.

### Step Response


Find.

1. Settling time
2. Rise time
3. Peak time
4. Steady State value.

Does the steady-state value match the expected value? \_\_\_\_\_

How impulse response can be found from the same command?

Explore LTI view.





### Step Response


### Impulse response


Let's find state-space model for the following circuit. Here, notice that there are two outputs, one capacitor voltage and other inductor voltage.

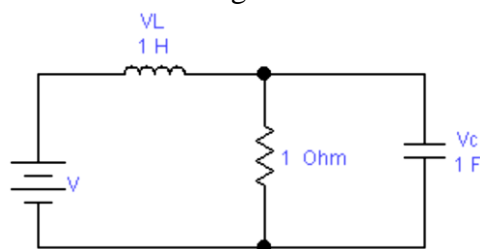


Figure 6.2: An Electrical Circuit with two outputs

Here are required matrices.

$$\mathbf{A} = \begin{bmatrix} 0 & -1 \\ 1 & -1 \end{bmatrix};$$

$$\mathbf{B} = \begin{bmatrix} 1 \\ 0 \end{bmatrix};$$

$$\mathbf{C} = \begin{bmatrix} 0 & -1 \\ 0 & 1 \end{bmatrix};$$

**D= [1 ; 0];**

State-space model 'sys' is

**sys=ss(A,B,C,D);**

**ltiview(sys)**



**Outputs Vc and VL**

Find

1. Settling time
2. Rise time
3. Peak time
4. Steady State value

Also Settling Time is set for 2% definition. Can you change it for 10%? [Hint: right click on graph and explore properties.]

Compare settling time for 2% and 10% values. Write your comments

.....  
 .....  
 .....  
 .....


Similarly, by default, Rise Time definition is set for 10% to 90%. Change it to 5% to 95% and compare results.

.....  
 .....  
 .....  
 .....  
 .....  
 .....

There are many more features are provided by LTI view, which you need to explore by yourself.

**Modeling Multiple Output Systems**

Consider the following electrical circuit. If the output is taken across R1, find the state space representation.

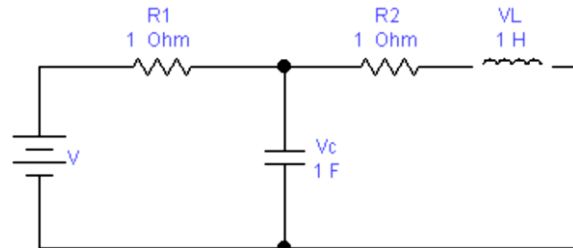

**Figure 6.3: An Electrical Circuit**

Required Matrices are:

**A = [-1 -1; 1 -1];**

**B = [1; 0];**

**C = [-1 0];**

**D = [1];**

Use the following model to analyze step response of the above state-space model:


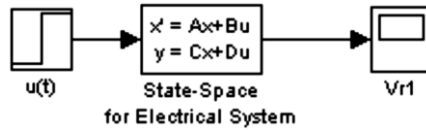


Figure 6.4: Model to analyze step response of the above state-space model

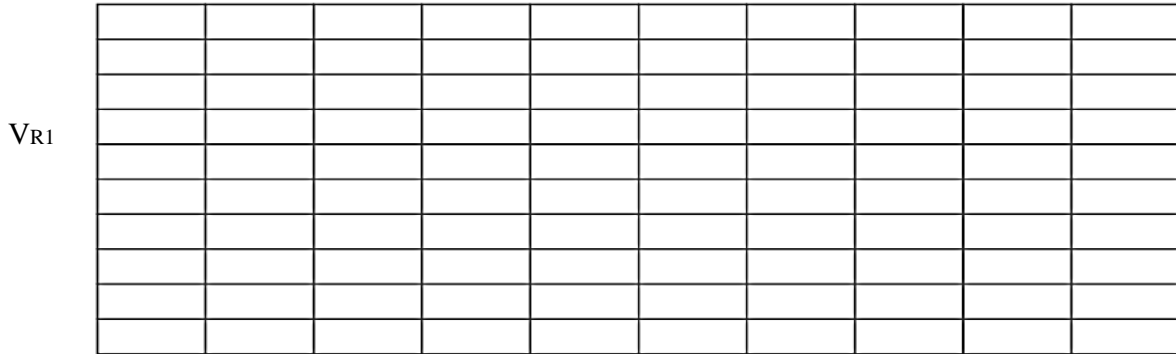

Now, if we want four outputs, voltage across every component. Required C and D matrices as below.

**C = [-1 0; 0 1; 1 0; 1 -1];**

**D = [1; 0; 0; 0];**

Verify these matrices from calculations. Will A and B matrices change? Why or Why not?

Model becomes

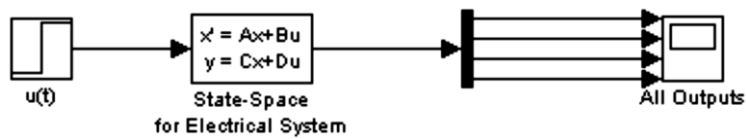


Figure 6.5: A model for four outputs

Identify each output (V<sub>C</sub>, V<sub>L</sub>, V<sub>R1</sub>, V<sub>R2</sub>) and sketch them below.



