

University of Wisconsin - Madison

ECE/Comp Sci 352 Digital Systems Fundamentals

Charles R. Kime

Section 2 – Fall 2001

Logic and Computer Design Fundamentals

Chapter 2 – Combinational Logic Circuits – Part 7

Charles Kime & Thomas Kaminski

© 2001 Prentice Hall, Inc


NAND and NOR Implementation

- We found that we could implement general Boolean equations with these three primitives:
 - AND
 - OR
 - NOT
- In this section we will find that either of two gates, the NAND gate or the NOR gate can be used to implement arbitrary logic functions.
- We use the Positive Logic Convention (where all signals are active high) and a small circle to on a symbol to represent NOT or invert.

NAND Gates

- The basic positive logic NAND gate is denoted by the following symbol:

- AND-Invert (NAND)

 


- NAND comes from NOT AND, I. e., the AND function with a NOT applied. We call this symbol for a NAND gate an AND-Invert. The small circle represents the invert function.
- If we apply DeMorgan's Law we get:

$$\overline{X \cdot Y \cdot Z} = \overline{X} + \overline{Y} + \overline{Z}$$

NAND Gates (Cont.)

- Applying DeMorgan's Law gives:


- Invert-OR (NAND)

 

- We call this symbol for a NAND gate the Invert - OR since all inputs are inverted, followed by the OR function.
- Both symbols represent the NAND gate - it is sometimes more logically descriptive to use one form over the other.
- A NAND gate with one input degenerates to an inverter.

NAND Function Implementation

 - **NAND gates can implement a simplified Sum-of-Products form. Constructing two level NAND-NAND gate circuit:**




- **The first level is two 2-input NAND gates using AND-Invert. The second level is one 2-input NAND gate using Invert-OR. Using the NAND relationship, we have:**

$$\begin{aligned} G(A, B, C, D) &= \overline{\overline{A \cdot B} \cdot \overline{C \cdot D}} \\ &= \overline{\overline{A \cdot B}} + \overline{\overline{C \cdot D}} \\ &= A \cdot B + C \cdot D \end{aligned}$$

NAND Implementation (Cont.)

In the implementation, note that the bubbles are on opposite ends of the same line.


Thus, they can be combined and deleted:

 

This form of the implementation is the Sum-of-Products form.

NAND Implementation (Cont.)

 
- In the implementation, the bubbles are on opposite ends of the same line.
- By $X = \overline{\overline{X}}$, they can be combined and deleted:




- A sum-of-products (SOP) form results
- To implement an equation like: $F(A,B,C) = A + BC$, the NAND for A degenerates to a NOT since there is only one input

Degenerate AND Term

 - The degenerate NAND becomes an inverter:



 - To implement the complement of F using NAND gates, add an inverter to the output:



NAND-NAND Example

- Implement: $F(w,x,y,z) = \overline{y}z + \overline{w}x + \overline{x}y + \overline{w}z$

	y				
	1 ₀	1 ₁	1 ₃	1 ₂	
	1 ₄	0 ₅	0 ₇	1 ₆	x
	1 ₁₂	0 ₁₃	0 ₁₅	0 ₁₄	
w	1 ₈	1 ₉	0 ₁₁	0 ₁₀	
	z				
	F(w,x,y,z)				

	y				
	1 ₀	1 ₁	1 ₃	1 ₂	
	1 ₄	0 ₅	0 ₇	1 ₆	x
	1 ₁₂	0 ₁₃	0 ₁₅	0 ₁₄	
w	1 ₈	1 ₉	0 ₁₁	0 ₁₀	
	z				
	F'(w,x,y,z)				

Summary: Two-Level NAND Circuits


- Find minimum literal SOP form for F and F
- Select SOP form with smallest literal count
- Convert selected form to NAND circuit using AND-invert (inverters for single literal AND terms) and invert-OR symbols
- If SOP form for F used, add inverter to circuit output.

NOR Gates

The basic positive logic NOR gate (Not-OR) is denoted by the following symbol:



 This is called the OR-Invert, since it is logically an OR function followed by an invert. By DeMorgan's Law we have the following Invert-AND symbol for a NOR gate:




A single-input NOR gate is an inverter, too.

NOR Gates

▪ The basic positive logic NOR gate is denoted by the following symbol:

- OR-Invert (NOR)

 

▪ NOR comes from NOT OR, I. e., the OR function with a NOT applied. We call this symbol for a NOR gate an OR-Invert. The small circle represents the invert function.


▪ If we apply DeMorgan's Law we get:

$$\overline{X+Y+Z} = \overline{X} \overline{Y} \overline{Z}$$

NOR Gates (Cont.)

- Applying DeMorgan's Law gives:


- Invert-AND (NOR)

 

- We call this symbol for a NOR gate the Invert-AND since all inputs are inverted, followed by the AND function.
- Both symbols represent the NOR gate - it is sometimes more logically descriptive to use one form over the other.
- A NOR gate with one input degenerates to an inverter.

NOR Function Implementation

 - NAND gates can implement a simplified Sum-of-Products form. Constructing two-level NOR-NOR circuit:



- The first level is two 2-input NOR gates using OR-Invert. The second level is one 2-input NOR gate using Invert-AND.
- Using the NOR relationship, we have:

$$\begin{aligned} G(A, B, C, D) &= \overline{\overline{(A+B)} + \overline{(C+D)}} \\ &= \overline{(A+B) (C+D)} \\ &= (A+B) (C+D) \end{aligned}$$

Useful Transformations

From Involution (i.e. $(A')' = A$) and DeMorgan's Law, we get the following useful equivalences:

$$(A \bullet B) = ((A \bullet B)')' \Leftrightarrow (A' + B')'$$

$$(A + B) = \Leftrightarrow (A' \bullet B')'$$

$$((A + B)')'$$

$$(A \bullet B)' \Leftrightarrow (A' + B')$$

$$(A + B)' \Leftrightarrow (A' \bullet B')$$

These simple transformations can be used to manipulate a two level network.

Graphical Transformations

The relations from the previous slide lead to the following transformations:





$$(A \bullet B) = ((A \bullet B)')' \Leftrightarrow (A' + B')'$$

$$(A + B) = \Leftrightarrow (A' \bullet B')'$$

$$((A + B)')'$$

$$(A \bullet B)' \Leftrightarrow (A' + B')$$
    
$$(A + B)' \Leftrightarrow (A' \bullet B')$$



Recall that two bubbles in series can be removed from the circuit

General Two-level Implementations

We need to consider whether the form of a two-level implementation is to be:

1. **SOP** (AND-OR) or
2. **POS** (OR-AND).

Complemented output functions (i.e. AND-NOR or OR-NAND) can be handled by complementing the function.

Given a function F expressed as a Karnaugh Map, we can use the same general procedures we have used before to minimize the function and express it in SOP or POS form.

General Implementations (Cont.)

Given a two level implementation desired, use the previous transformations to get it into one of the below forms. Then follow the steps to transform the function to the desired form:

For Type:	Use:
AND-OR (SOP Form)	Circle 1's in the K-Map and minimize (Also use for NAND-NAND)
AND-NOR (SOP complemented)	Circle 0's in the K-Map and minimize
OR-AND (POS Form)	Circle 0's in the K-Map and minimize SOP. Use DeMorgan's to transform to POS. (Also use for NOR-NOR)
OR-NAND (POS complemented)	Circle 1's in the K-Map and minimize SOP. Use DeMorgan's to transform to POS.

Implementation Example 1

			B	
	1	1	0	1
A	1	1	0	0
			C	

Implement the function in NOR-OR.

We can remove the "Inverter" and replace it with the complement of the input variable

Implementation Example 2

			B	
	1	1	0	1
A	1	1	0	0


Implement the function in AND-NOR.

Multi-level NAND Implementations

- Add inverters in two-level implementation into the cost picture
- Attempt to “combine” inverters to reduce the term count
- Attempt to reduce literal + term count by factoring expression into POSOP or SOPOS

Multi-level NAND Example 1

 - $F = A B' + A C' + B A' + B C'$ 15 inputs and 8 gates*
 $= A A' + A B' + A C' + B A' + B B' + B C'$
 $= A (A' + B' + C') + B (A' + B' + C')$



* Counting inverters (NOTS) as 1 input and 1 gate

Multilevel NAND Example 2

- $F = AB + AD' + BC + CD'$