

# ECE 331 – Digital System Design

## Multiplexers, Decoders and Encoders

(Lecture #16)



The slides included herein were taken from the materials accompanying *Fundamentals of Logic Design, 6<sup>th</sup> Edition*, by Roth and Kinney, and were used with permission from Cengage Learning.

# Multiplexers

# Multiplexers


- A multiplexer has
  - $2^n$  data inputs
  - $n$  control inputs
  - 1 output
- A multiplexer routes (or connects) the selected data input to the output.
  - The value of the control inputs determines the data input that is selected.

# Multiplexers

 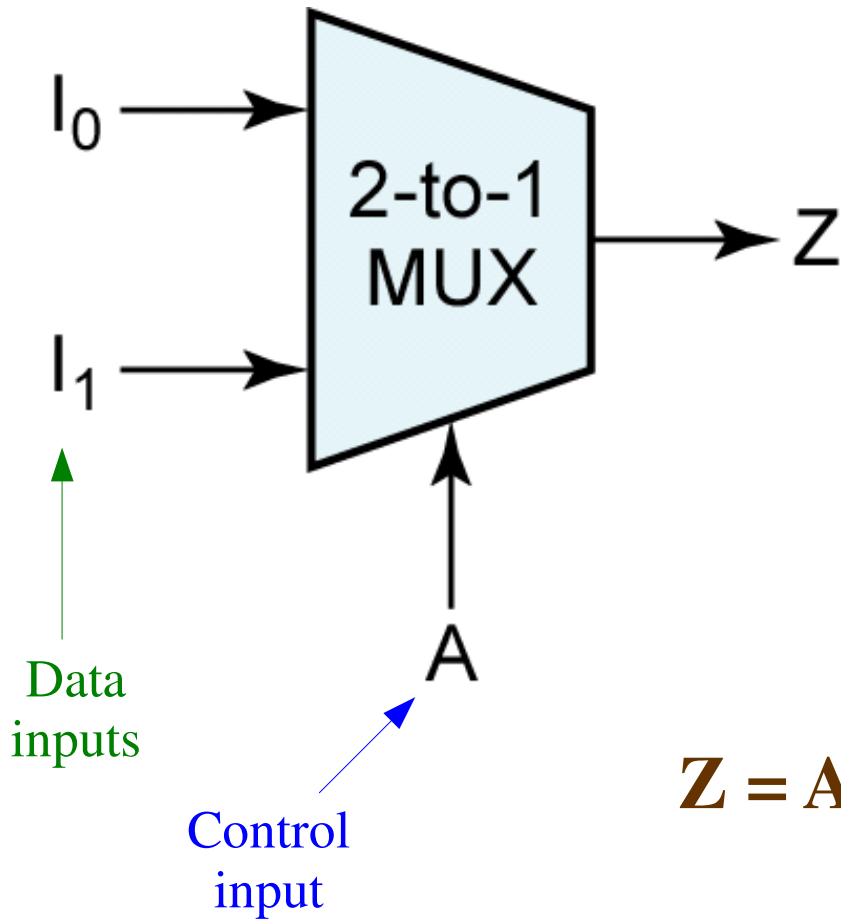

$$Z = A'.I_0 + A.I_1$$

# Multiplexers

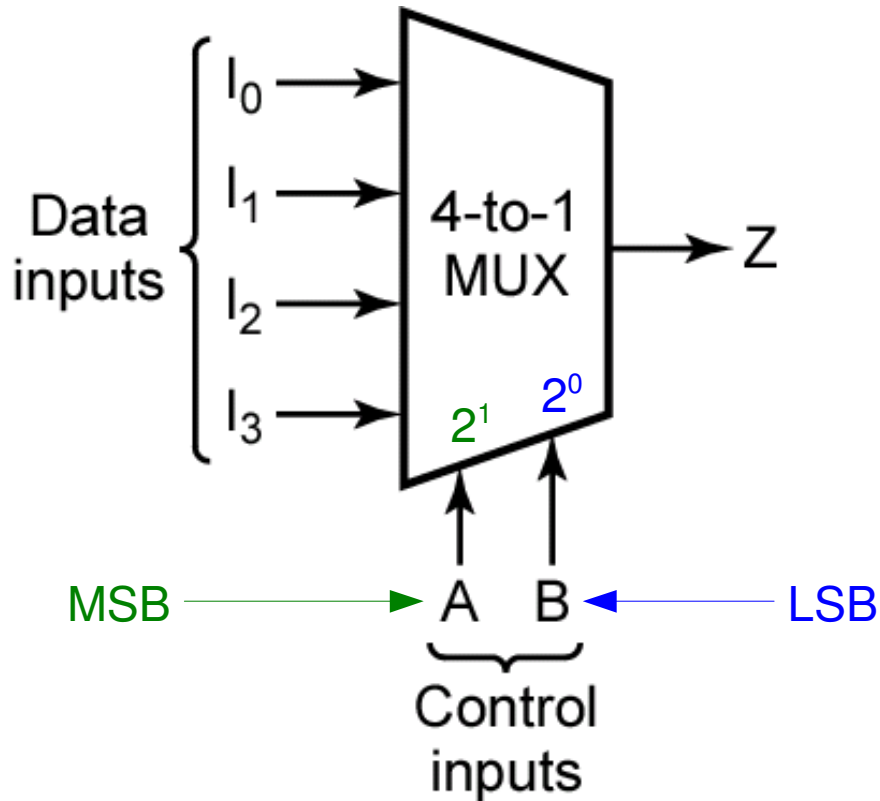

| <b>A</b> | <b>B</b> | <b>Z</b> |
|----------|----------|----------|
| 0        | 0        | $I_0$    |
| 0        | 1        | $I_1$    |
| 1        | 0        | $I_2$    |
| 1        | 1        | $I_3$    |

$$m_0 = A'.B'$$


$$m_1 = A'.B$$

$$m_2 = A.B'$$

$$m_3 = A.B$$

$$Z = A'.B'.I_0 + A'.B.I_1 + A.B'.I_2 + A.B.I_3$$


# Multiplexers

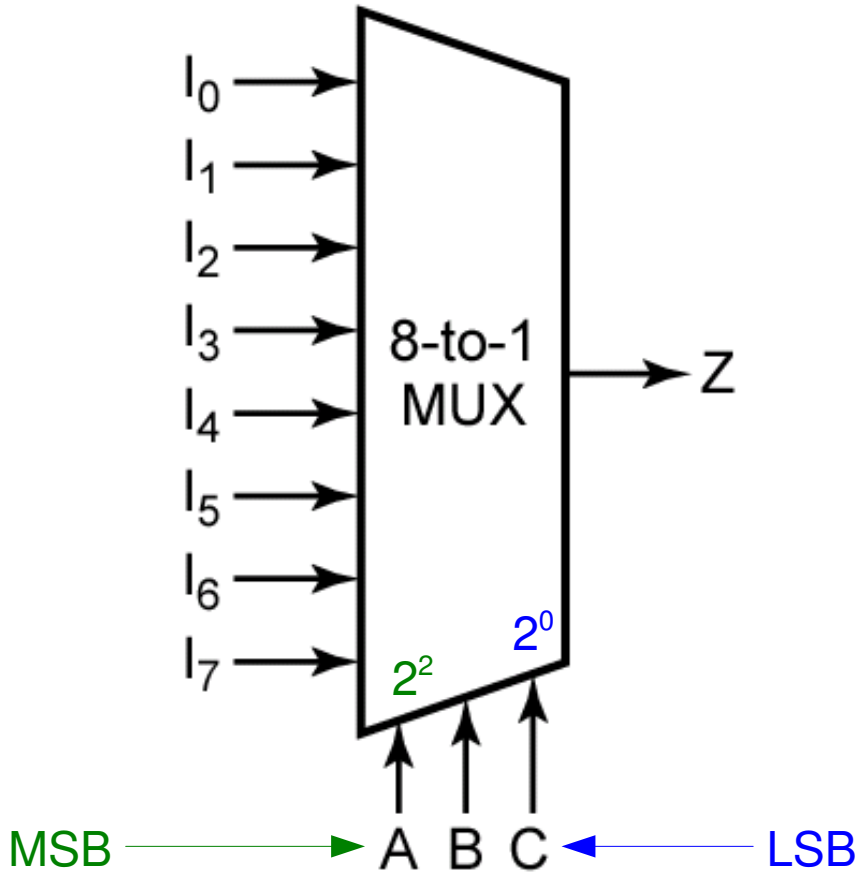

| A | B | C | Z              |                |
|---|---|---|----------------|----------------|
| 0 | 0 | 0 | I <sub>0</sub> | m <sub>0</sub> |
| 0 | 0 | 1 | I <sub>1</sub> | m <sub>1</sub> |
| 0 | 1 | 0 | I <sub>2</sub> | m <sub>2</sub> |
| 0 | 1 | 1 | I <sub>3</sub> | m <sub>3</sub> |
| 1 | 0 | 0 | I <sub>4</sub> | m <sub>4</sub> |
| 1 | 0 | 1 | I <sub>5</sub> | m <sub>5</sub> |
| 1 | 1 | 0 | I <sub>6</sub> | m <sub>6</sub> |
| 1 | 1 | 1 | I <sub>7</sub> | m <sub>7</sub> |

$$Z = A'.B'.C'.I_0 + A'.B'.C.I_1 + A'.B.C'.I_2 + A'.B.C.I_3 + A.B'.C'.I_4 + A.B'.C.I_5 + A'.B.C'.I_6 + A.B.C.I_7$$

# Multiplexers

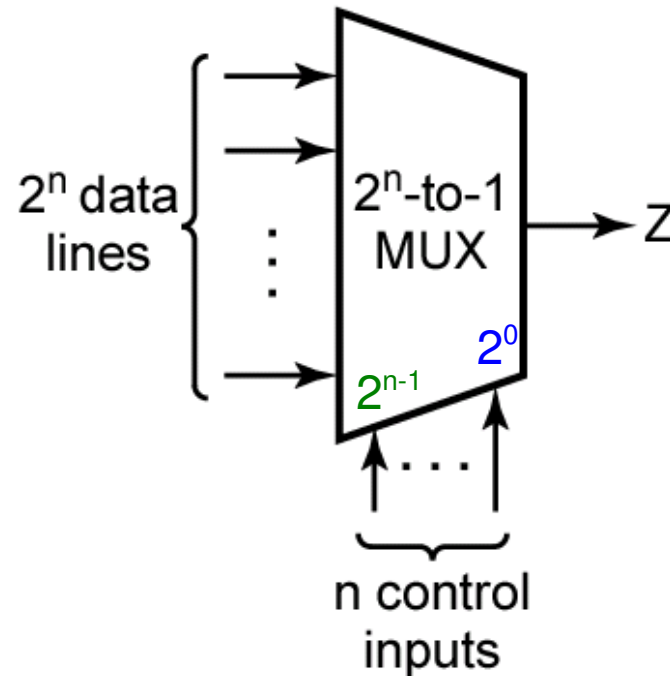

$$Z = \sum m_i \cdot I_i$$

# Multiplexers in VHDL



# 8-to-1 Multiplexer

```
entity Multiplexer_8to1 is
    Port ( I : in  STD_LOGIC_VECTOR (7 downto 0);
          sel : in  STD_LOGIC_VECTOR (2 downto 0);
          Z : out  STD_LOGIC);
end Multiplexer_8to1;

architecture Bool_Exp of Multiplexer_8to1 is

begin

    Z <= ( not(sel(2)) and not(sel(1)) and not(sel(0)) and I(0) ) or
        ( not(sel(2)) and not(sel(1)) and sel(0) and I(1) ) or
        ( not(sel(2)) and sel(1) and not(sel(0)) and I(2) ) or
        ( not(sel(2)) and sel(1) and sel(0) and I(3) ) or
        ( sel(2) and not(sel(1)) and not(sel(0)) and I(4) ) or
        ( sel(2) and not(sel(1)) and sel(0) and I(5) ) or
        ( sel(2) and sel(1) and not(sel(0)) and I(6) ) or
        ( sel(2) and sel(1) and sel(0) and I(7) );

end Bool_Exp;
```

# 8-to-1 Multiplexer

```
entity Multiplexer_8to1_2 is
    Port ( I : in  STD_LOGIC_VECTOR (7 downto 0);
          sel : in  STD_LOGIC_VECTOR (2 downto 0);
          Z : out  STD_LOGIC);
end Multiplexer_8to1_2;

architecture Truth_Table of Multiplexer_8to1_2 is

begin

    with sel select

        Z <=  I(7)  when "111",
              I(6)  when "110",
              I(5)  when "101",
              I(4)  when "100",
              I(3)  when "011",
              I(2)  when "010",
              I(1)  when "001",
              I(0)  when "000",
              I(0)  when others;

end Truth_Table;
```


# Decoders

# Decoders

- A decoder has
  - $n$  inputs
  - $2^n$  outputs
- A decoder selects one of  $2^n$  outputs by decoding the binary value on the  $n$  inputs.
- The decoder generates all of the minterms of the  $n$  input variables.
  - Exactly one output will be active for each combination of the inputs.


What does “active” mean?

# Decoders

 

| A | B | Z <sub>0</sub> | Z <sub>1</sub> | Z <sub>2</sub> | Z <sub>3</sub> |                |
|---|---|----------------|----------------|----------------|----------------|----------------|
| 0 | 0 | 1              | 0              | 0              | 0              | m <sub>0</sub> |
| 0 | 1 | 0              | 1              | 0              | 0              | m <sub>1</sub> |
| 1 | 0 | 0              | 0              | 1              | 0              | m <sub>2</sub> |
| 1 | 1 | 0              | 0              | 0              | 1              | m <sub>3</sub> |


# Decoders

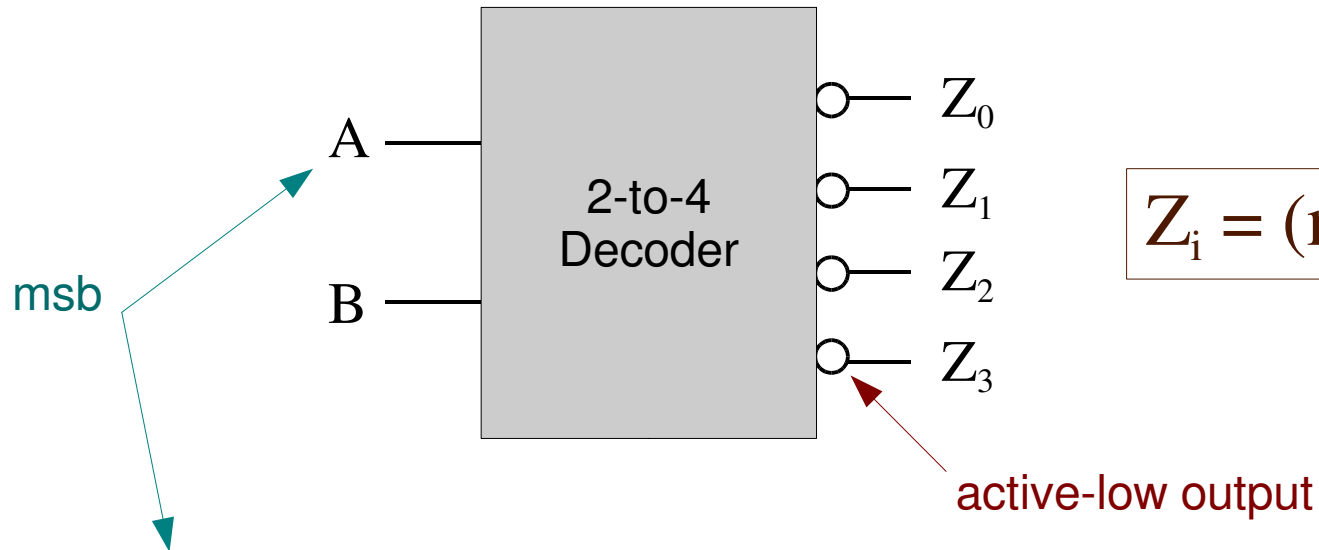

| A | B | $Z_0$ | $Z_1$ | $Z_2$ | $Z_3$ |       |
|---|---|-------|-------|-------|-------|-------|
| 0 | 0 | 0     | 1     | 1     | 1     | $M_0$ |
| 0 | 1 | 1     | 0     | 1     | 1     | $M_1$ |
| 1 | 0 | 1     | 1     | 0     | 1     | $M_2$ |
| 1 | 1 | 1     | 1     | 1     | 0     | $M_3$ |




# Decoder with Enable

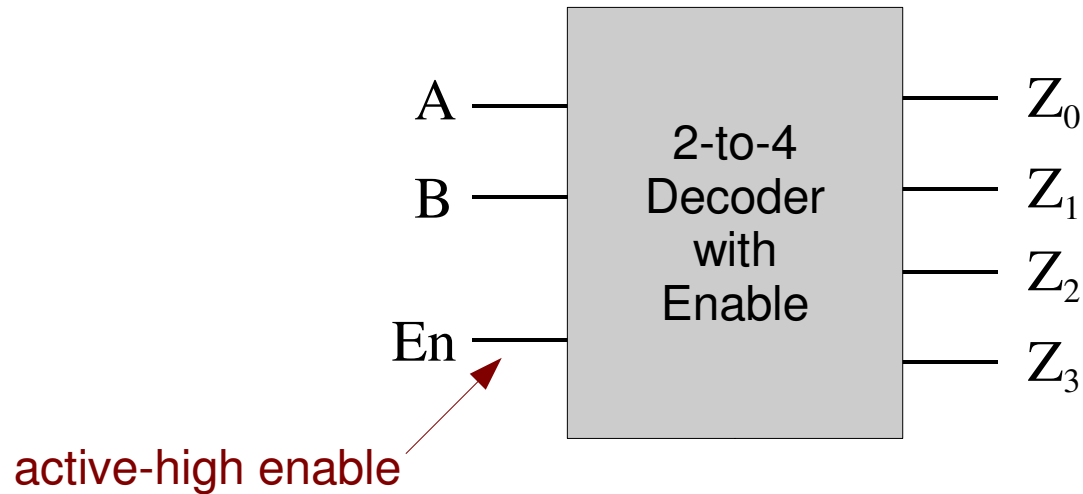

|          | En | A | B | Z <sub>0</sub> | Z <sub>1</sub> | Z <sub>2</sub> | Z <sub>3</sub> |
|----------|----|---|---|----------------|----------------|----------------|----------------|
| enabled  | 1  | 0 | 0 | 1              | 0              | 0              | 0              |
|          | 1  | 0 | 1 | 0              | 1              | 0              | 0              |
|          | 1  | 1 | 0 | 0              | 0              | 1              | 0              |
|          | 1  | 1 | 1 | 0              | 0              | 0              | 1              |
| disabled | 0  | x | x | 0              | 0              | 0              | 0              |



# Decoder with Enable

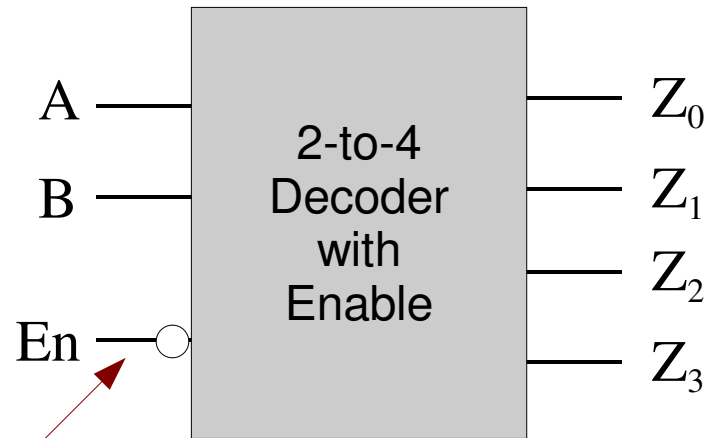

active-low enable

enabled

disabled

| En | A | B | Z <sub>0</sub> | Z <sub>1</sub> | Z <sub>2</sub> | Z <sub>3</sub> |
|----|---|---|----------------|----------------|----------------|----------------|
| 0  | 0 | 0 | 1              | 0              | 0              | 0              |
| 0  | 0 | 1 | 0              | 1              | 0              | 0              |
| 0  | 1 | 0 | 0              | 0              | 1              | 0              |
| 0  | 1 | 1 | 0              | 0              | 0              | 1              |
| 1  | x | x | 0              | 0              | 0              | 0              |

# Decoders in VHDL

# 3-to-8 Decoder

```
entity Decoder_3to8_1 is
    Port ( I : in  STD_LOGIC_VECTOR (2 downto 0);
          Z : out  STD_LOGIC_VECTOR (7 downto 0) );
end Decoder_3to8_1;

architecture Boolean_Expression of Decoder_3to8_1 is

begin

    Z(0) <= ( not(I(2)) and not(I(1)) and not(I(0)) );
    Z(1) <= ( not(I(2)) and not(I(1)) and I(0) );
    Z(2) <= ( not(I(2)) and I(1) and not(I(0)) );
    Z(3) <= ( not(I(2)) and I(1) and I(0) );
    Z(4) <= ( I(2) and not(I(1)) and not(I(0)) );
    Z(5) <= ( I(2) and not(I(1)) and I(0) );
    Z(6) <= ( I(2) and I(1) and not(I(0)) );
    Z(7) <= ( I(2) and I(1) and I(0) );

end Boolean_Expression;
```

# 3-to-8 Decoder

```
entity Decoder_3to8_2 is
    Port ( I : in  STD_LOGIC_VECTOR (2 downto 0);
          Z : out  STD_LOGIC_VECTOR (7 downto 0));
end Decoder_3to8_2;

architecture Truth_Table of Decoder_3to8_2 is

begin

    with I select

        Z <=  "10000000"  when "111",
              "01000000"  when "110",
              "00100000"  when "101",
              "00010000"  when "100",
              "00001000"  when "011",
              "00000100"  when "010",
              "00000010"  when "001",
              "00000001"  when "000",
              "00000000"  when others;

end Truth_Table;
```

# 2-to-4 Decoder with Enable

```
entity Decoder_2to4_withEN is
    Port ( I : in  STD_LOGIC_VECTOR (1 downto 0);
          Z : out  STD_LOGIC_VECTOR (3 downto 0);
          En : in  STD_LOGIC);
end Decoder_2to4_withEN;

architecture Truth_Table of Decoder_2to4_withEN is
    signal EnabledInput : STD_LOGIC_VECTOR (2 downto 0);

begin

    EnabledInput <= En & I;      -- concatenate the En signal
                                -- with the data inputs (I)

    with EnabledInput select

        Z <=  "1000"  when "111",
              "0100"  when "110",
              "0010"  when "101",
              "0001"  when "100",
              "0000"  when "000",
              "0000"  when others;


end Truth_Table;
```

# Encoders

# Encoders

- An encoder has
  - $2^n$  inputs
  - $n$  outputs
- Outputs the binary value of the selected (or active) input.
- Performs the inverse operation of a decoder.
- Issues
  - What if more than one input is active?
  - What if no inputs are active?

# Encoders

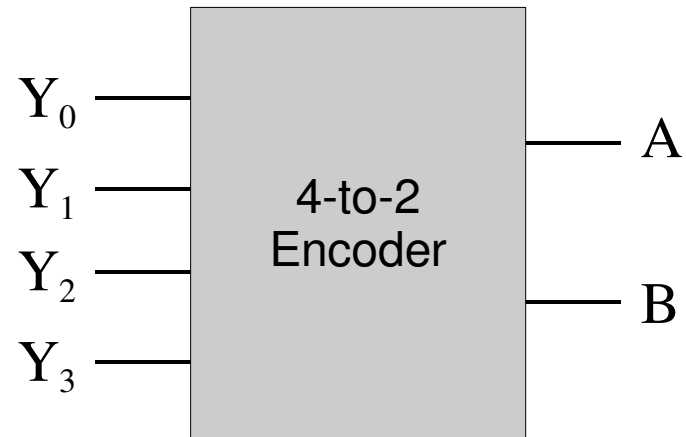

| $Y_0$ | $Y_1$ | $Y_2$ | $Y_3$ | A | B |
|-------|-------|-------|-------|---|---|
| 1     | 0     | 0     | 0     | 0 | 0 |
| 0     | 1     | 0     | 0     | 0 | 1 |
| 0     | 0     | 1     | 0     | 1 | 0 |
| 0     | 0     | 0     | 1     | 1 | 1 |




# Priority Encoders

- If more than one input is active, the higher-order input has priority over the lower-order input.
  - The higher value is encoded on the output
- A valid indicator,  $d$ , is included to indicate whether or not the output is valid.
  - Output is invalid when no inputs are active
    - $d = 0$
  - Output is valid when at least one input is active
    - $d = 1$

Why is the valid indicator needed?

# Priority Encoders

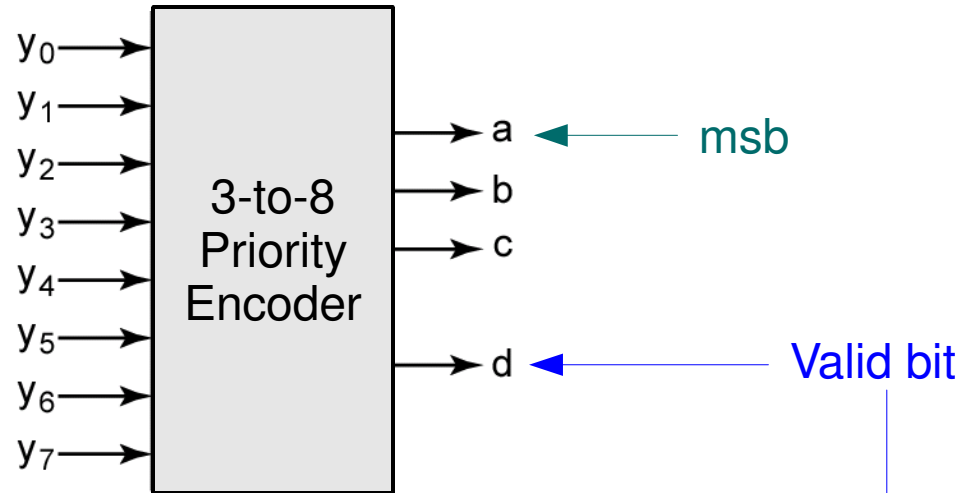

| $y_0$ | $y_1$ | $y_2$ | $y_3$ | $y_4$ | $y_5$ | $y_6$ | $y_7$ | $a$ | $b$ | $c$ | $d$ |
|-------|-------|-------|-------|-------|-------|-------|-------|-----|-----|-----|-----|
| 0     | 0     | 0     | 0     | 0     | 0     | 0     | 0     | 0   | 0   | 0   | 0   |
| 1     | 0     | 0     | 0     | 0     | 0     | 0     | 0     | 0   | 0   | 0   | 1   |
| X     | 1     | 0     | 0     | 0     | 0     | 0     | 0     | 0   | 0   | 1   | 1   |
| X     | X     | 1     | 0     | 0     | 0     | 0     | 0     | 0   | 1   | 0   | 1   |
| X     | X     | X     | 1     | 0     | 0     | 0     | 0     | 0   | 1   | 1   | 1   |
| X     | X     | X     | X     | 1     | 0     | 0     | 0     | 1   | 0   | 0   | 1   |
| X     | X     | X     | X     | X     | 1     | 0     | 0     | 1   | 0   | 1   | 1   |
| X     | X     | X     | X     | X     | X     | 1     | 0     | 1   | 1   | 0   | 1   |
| X     | X     | X     | X     | X     | X     | X     | 1     | 1   | 1   | 1   | 1   |

# Encoders in VHDL

# 4-to-2 Priority Encoder

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;
```

```
ENTITY priority IS  
    PORT ( w   : IN      STD_LOGIC_VECTOR(3 DOWNTO 0) ;  
          y   : OUT     STD_LOGIC_VECTOR(1 DOWNTO 0) ;  
          z   : OUT     STD_LOGIC ) ;
```

```
END priority ;
```

valid indicator

```
ARCHITECTURE Behavior OF priority IS  
BEGIN
```

```
    y <= "11" WHEN w(3) = '1' ELSE  
        "10" WHEN w(2) = '1' ELSE  
        "01" WHEN w(1) = '1' ELSE  
        "00" ;
```

```
    z <= '0' WHEN w = "0000" ELSE '1' ;
```

```
END Behavior ;
```

4 input bits



2 output bits

Active-high  
inputs and outputs

# Circuit Design using Multiplexers

# Using a $2^n$ -input Multiplexer

- Use a  $2^n$ -input multiplexer to realize a logic circuit for a function with  $2^n$  minterms.
  - $n = \#$  of control inputs =  $\#$  of variables in the function
- Each minterm of the function can be mapped to a data input of the multiplexer.
- For each row in the truth table, for the function, where the output is 1, set the corresponding data input of the multiplexer to 1.
  - That is, for each minterm in the minterm expansion of the function, set the corresponding input of the multiplexer to 1.
- Set the remaining inputs of the multiplexer to 0.

# Using an $2^n$ -input Mux

Example:

Using an 8-to-1 multiplexer, design a logic circuit to realize the following Boolean function

$$F(A,B,C) = \Sigma m(2, 3, 5, 6, 7)$$

# Using an $2^n$ -input Mux

Example:

Using an 8-to-1 multiplexer, design a logic circuit to realize the following Boolean function

$$F(A,B,C) = \Sigma m(1, 2, 4)$$



# Using an $2^{(n-1)}$ -input Multiplexer


- Use a  $2^{(n-1)}$ -input multiplexer to realize a logic circuit for a function with  $2^n$  minterms.
  - $n - 1 = \#$  of control inputs;  $n = \#$  of variables in function
- Group the rows of the truth table, for the function, into  $2^{(n-1)}$  pairs of rows.
  - Each pair of rows represents a product term of  $(n - 1)$  variables.
  - Each pair of rows is mapped to one data input of the mux.
- Determine the logical function of each pair of rows in terms of the remaining variable.
  - If the remaining variable, for example, is  $x$ , then the

# Using an $\underline{2^{(n-1)}}$ -input Mux

Example:  $F(x,y,z) = \Sigma m(1, 2, 6, 7)$

| $x$ | $y$ | $z$ | $F$ |          |
|-----|-----|-----|-----|----------|
| 0   | 0   | 0   | 0   | $F = z$  |
| 0   | 0   | 1   | 1   |          |
| 0   | 1   | 0   | 1   | $F = z'$ |
| 0   | 1   | 1   | 0   |          |
| 1   | 0   | 0   | 0   | $F = 0$  |
| 1   | 0   | 1   | 0   |          |
| 1   | 1   | 0   | 1   | $F = 1$  |
| 1   | 1   | 1   | 1   |          |

(a) Truth table

 


(b) Multiplexer implementation

# Using an $2^{(n-1)}$ -input Mux

Example:  $F(A,B,C,D) = \Sigma m(1,3,4,11,12-15)$

| <i>A</i> | <i>B</i> | <i>C</i> | <i>D</i> | <i>F</i> |          |
|----------|----------|----------|----------|----------|----------|
| 0        | 0        | 0        | 0        | 0        | $F = D$  |
| 0        | 0        | 0        | 1        | 1        |          |
| 0        | 0        | 1        | 0        | 0        | $F = D$  |
| 0        | 0        | 1        | 1        | 1        |          |
| 0        | 1        | 0        | 0        | 1        | $F = D'$ |
| 0        | 1        | 0        | 1        | 0        |          |
| 0        | 1        | 1        | 0        | 0        | $F = 0$  |
| 0        | 1        | 1        | 1        | 0        |          |
| 1        | 0        | 0        | 0        | 0        | $F = 0$  |
| 1        | 0        | 0        | 1        | 0        |          |
| 1        | 0        | 1        | 0        | 0        | $F = D$  |
| 1        | 0        | 1        | 1        | 1        |          |
| 1        | 1        | 0        | 0        | 1        | $F = 1$  |
| 1        | 1        | 0        | 1        | 1        |          |
| 1        | 1        | 1        | 0        | 1        | $F = 1$  |
| 1        | 1        | 1        | 1        | 1        |          |

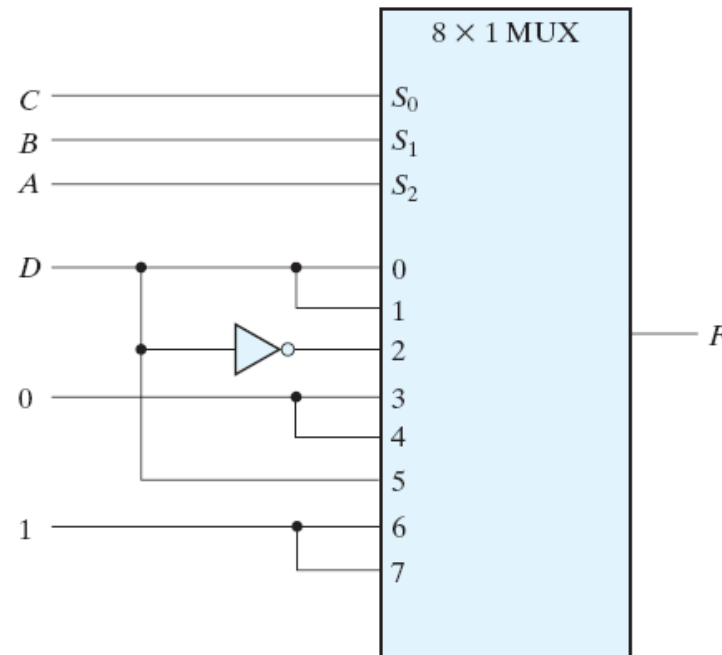

# Using a $\underline{2^{(n-2)}}\text{-input Mux}$

A similar design approach can be implemented using a  $2^{(n-2)}$ -input multiplexer.

# Circuit Design using Decoders

# Using an $n$ -output Decoder

- Use an  $n$ -output decoder to realize a logic circuit for a function with  $n$  minterms.
- Each minterm of the function can be mapped to an output of the decoder.
- For each row in the truth table, for the function, where the output is 1, sum (or “OR”) the corresponding outputs of the decoder.
  - That is, for each minterm in the minterm expansion of the function, OR the corresponding outputs of the decoder.
- Leave remaining outputs of the decoder unconnected.

# Using an $n$ -output Decoder

Example:

Using a 3-to-8 decoder, design a logic circuit to realize the following Boolean function

$$F(A,B,C) = \Sigma m(2, 3, 5, 6, 7)$$

# Using an $n$ -output Decoder

Example:

Using two 2-to-4 decoders, design a logic circuit to realize the following Boolean function

$$F(A,B,C) = \Sigma m(0, 1, 4, 6, 7)$$



# Hierarchical Design

# Hierarchical Design

- Several issues arise when designing large multiplexers and decoders (as 2-level circuits).
  - Number of logic gates gets prohibitively large
  - Number of inputs to each logic gate (i.e. fan-in) gets prohibitively large
- Instead, design both hierarchically
  - Use smaller elements as building blocks
  - Interconnect building blocks in a multi-tier structure

# Hierarchical Design

Exercise:

Design an 8-to-1 multiplexer using 4-to-1 and 2-to-1 multiplexers only.

# Hierarchical Design

Exercise:

Design a 16-to-1 multiplexer using  
4-to-1 multiplexers only.

# Hierarchical Design

Exercise:

Design a 4-to-16 decoder using  
2-to-4 decoders only.

Questions?