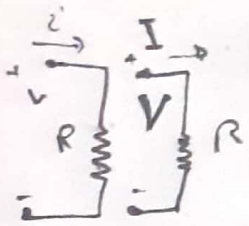



# Phase Relationship for circuit Elements

## Resistor




Time domain  $v = iR$   
 freq. domain  $V = IR$   
 No. Phase difference

## Inductor

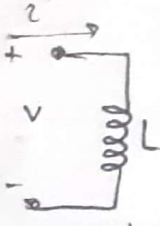


$v = L \frac{di}{dt}$   
 Time domain

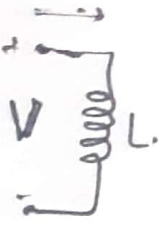


$V = j\omega L I$   
 $V = X_L I$   
 $V = j\omega L I$




## Capacitor

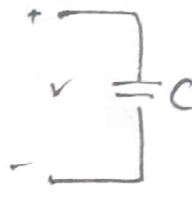

$i = C \frac{dv}{dt}$   
 Time domain

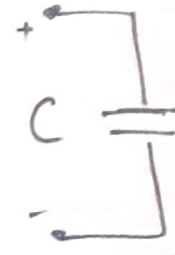

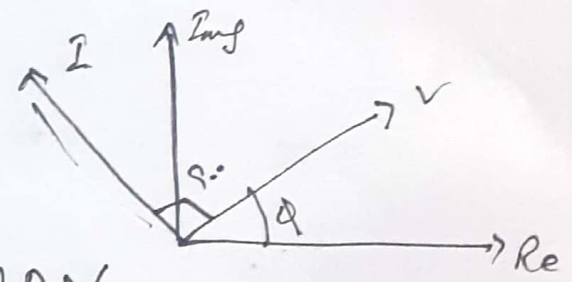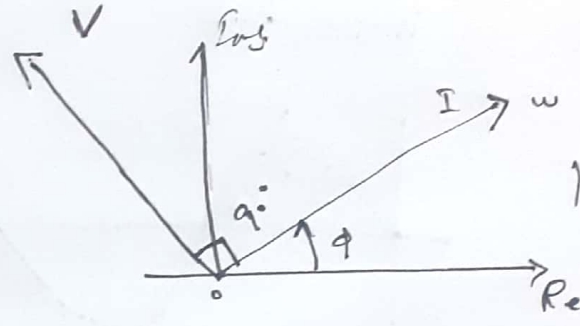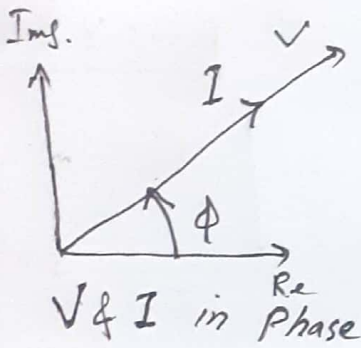$I = C \cdot V \cdot j\omega$   
 $V = \frac{I}{j\omega C}$   
 $V = -\frac{jI}{\omega C}$




Phasor diagram

Remember

Hint


ELI is ICE MAN

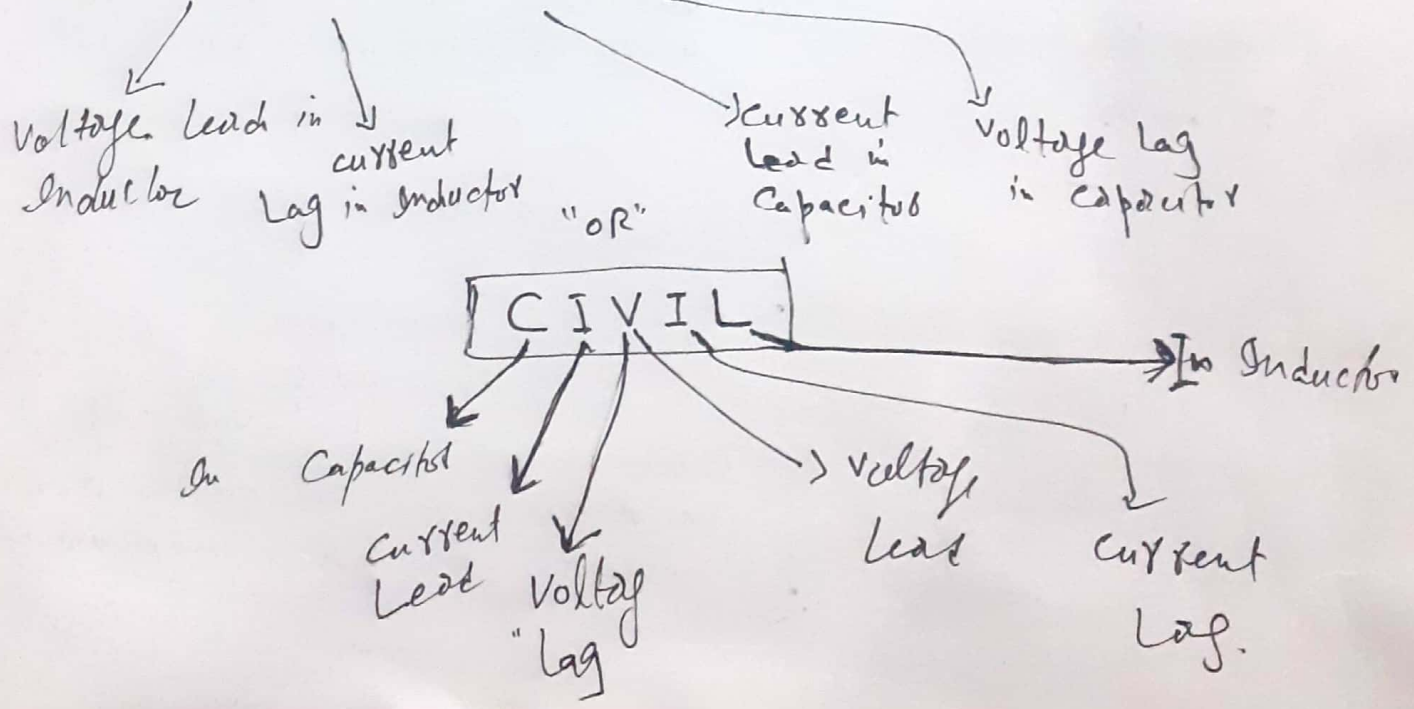


# Summary of Voltage-current Relationship

<u>Element</u>	<u>Time domain</u>	<u>Frequency domain</u>
R	$V = iR$	$V = IR$
L	$V_L = L \frac{di}{dt}$	$V = j\omega L I$
C	$i = C \frac{dv}{dt}$	$I = j\omega C V$ $V = \frac{I}{j\omega C}$


## AC Response of the Basic Elements

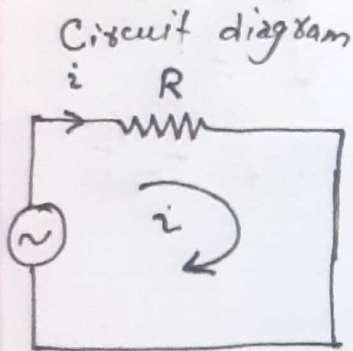

Wave form

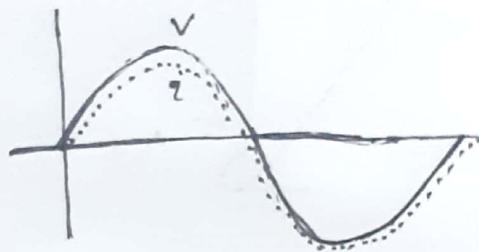

Phasor Diagram

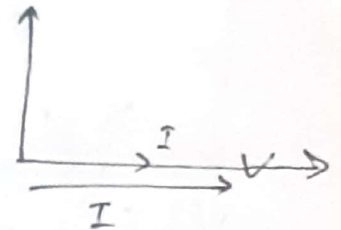

According to Ohm's Law

$$i = \frac{V}{R} \quad \therefore v(t) = V_m \sin(\omega t)$$

$$v = V_m \sin(\omega t)$$

$$i = \frac{V_m \sin(\omega t)}{R}$$

~~$$i = \frac{V_m \sin(\omega t)}{R}$$~~

$$i = I_m \sin(\omega t)$$

$$v = iR$$

$$V_m \sin \omega t = I_m \sin(\omega t) \cdot R$$

$$V_m = I_m \cdot R$$


$$I_m = \frac{V_m}{R}$$

Remember when the value of sine become unity, it mean that time the value of current  $i$  is its maximum value.


As we know that voltage drop across Resistance =  $v = iR$

Putting the value of  $i$


# AC Response of the Inductor :-

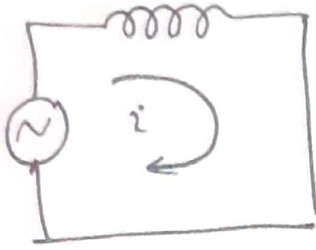

(a) circuit diagram

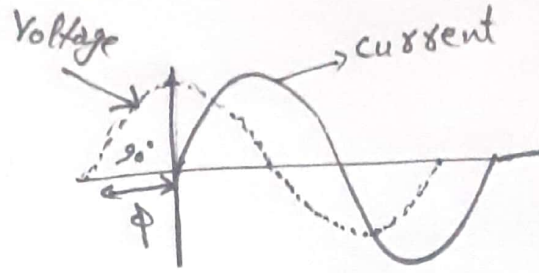

(b) wave forms

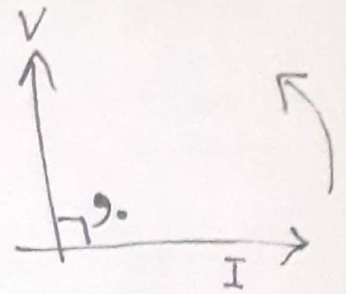

(c) Phasor diagram

→ back EMF due to AC, L/Inductor oppose the change in current  
 Assume ~~current~~ current

$$i = I_m \sin(\omega t) \rightarrow \text{---} \mathbf{I}$$

The voltage Across the Inductor

$$V_L = L \frac{di}{dt}$$

(Putting the value of  $i$  from Equation 1)

$$V_L = L \frac{d}{dt} (I_m \sin \omega t)$$

$$V_L = L I_m \frac{d}{dt} (\sin(\omega t))$$

$$V_L = L I_m \cos(\omega t) \frac{d}{dt} (\omega t)$$

$$V_L = \omega L I_m \cos(\omega t)$$

$$V_L = V_m \cos(\omega t)$$

$$\therefore \left\{ \begin{array}{l} V = IR \\ V_m = I_m R \\ V_m = I_m \cdot L \\ V_m = \omega L I_m \end{array} \right.$$

As we know that

$$\cos(\omega t) = (\sin(\omega t + 90^\circ))$$

$$\text{or } \sin(\omega t + 90^\circ) = \cos \omega t$$

So voltage wave form is cosine where as current wave form is sine.



These ~~for~~ voltage lead  $90^\circ$  by current.

$\therefore$  So the voltage wave form leads by current  $90^\circ$ .

$\therefore$  \_\_\_\_\_



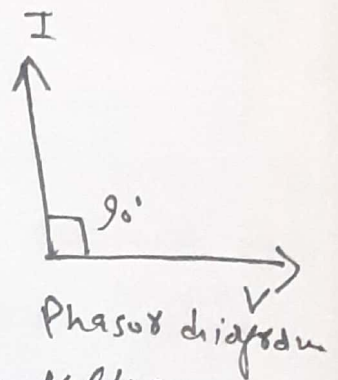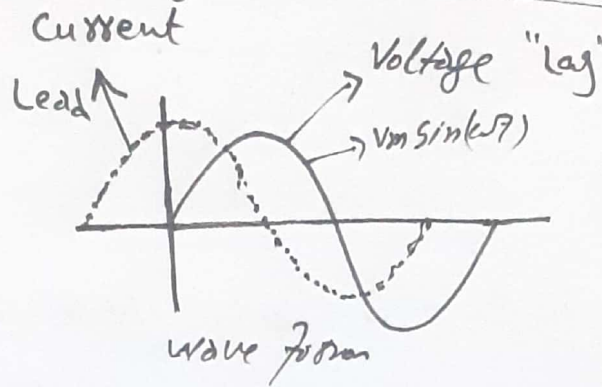describe the AC Response of the capacitor along with circuit diagram, phasor diagram & wave form.



Capacitor don't like the about change in voltage

$$V(t) = V_m \sin(\omega t) \quad \therefore V = V_m \sin(\omega t)$$

The current through the capacitor is

$$i = C \frac{dV}{dt}$$

$$i = C \frac{d}{dt} (V_m \sin(\omega t))$$

$$i = C V_m \frac{d}{dt} (\sin(\omega t))$$

$$i = C V_m \cos(\omega t) \frac{d}{dt} (\omega t)$$

$$i = (\omega C V_m) \cos(\omega t)$$



$$i = I_m \cos(\omega t)$$

As we know that

$$\cos(\omega t) = \sin(\omega t + 90^\circ)$$

$$\therefore i = I_m \sin(\omega t + 90^\circ)$$

Therefore:

we can say that the voltage wave form lags the current wave form by  $90^\circ$ .

"or"

current lead  $90^\circ$  by voltage

$\therefore$  ohm's Law


$$i = \frac{V}{R}$$

$$i = \frac{V}{\frac{1}{C}}$$

$$i = CV$$

# Alternative Concept of Phasors of Basic Elements


Consider axis

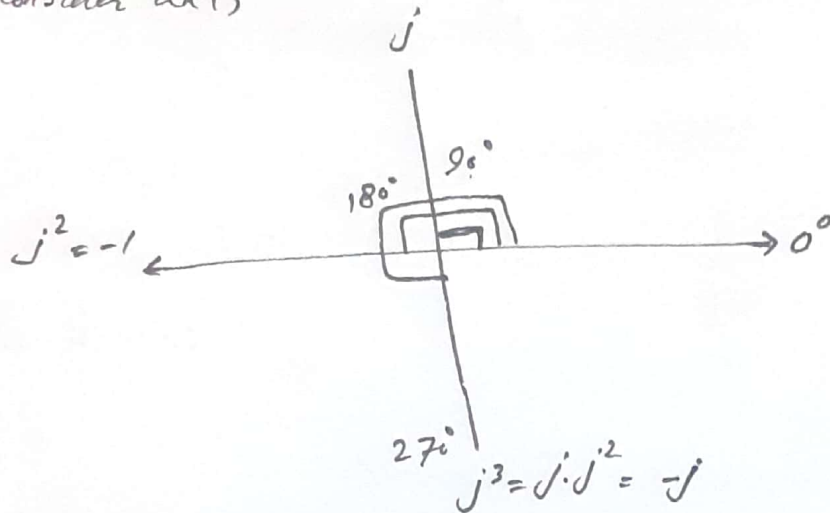

We can say, if Any term containing  $j$ , then that term lead  $90^\circ$ .

$\Rightarrow$  if  $(-1)$  then  $180^\circ$  lead.

Application in Electrical circuits

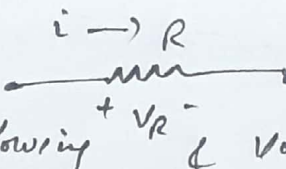① Consider Resistance ( $R$ ) 

$\Rightarrow$  According to Ohm's Law  $\Rightarrow V_R = iR$

Analyze there is no angle between them, so both voltage & current are in phase.

Now

② Consider Inductor


Inductance of Inductor =  $X_L$

Voltage Drop will be =  $V_L$

so  $V_L = iX_L$

$$V_L = j\omega IL$$



$$V_L = jI\omega L$$

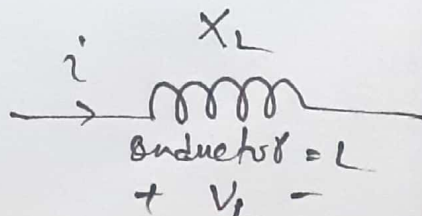


$$\therefore X_L = j\omega L$$

We see from Expression that Inductive voltage is lead  $90^\circ$

# Phasor Diagram

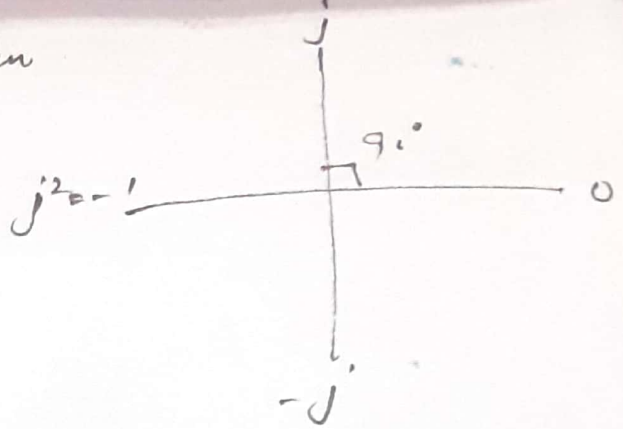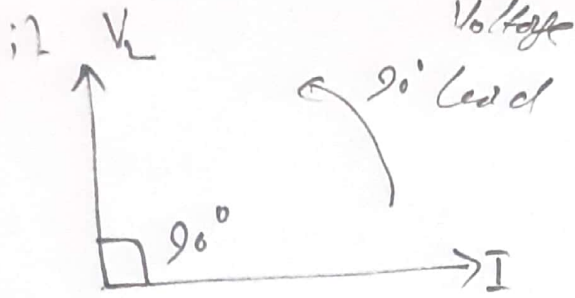

3rd Concept Consider Capacitor

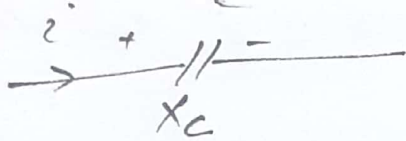

$$X_C = \frac{1}{j\omega C}$$

$$X_C = \frac{1}{j\omega C}$$

Capacitive

~~Impedance~~ = ~~X\_C~~ = ~~1/j\omega C~~  $X_C = \frac{1}{j\omega C}$

Reactance

∴ Voltage drop across capacitor =  $V_C = X_C I$

~~V\_C = \frac{I}{j\omega C}~~

$$V_C = \frac{I}{j\omega C}$$

$$X_C = \frac{1}{j\omega C}$$


Rationalize

$$V_C = \frac{-jI}{\omega C}$$

$$V_C = \frac{-jI}{\omega C}$$

⇒ Current lead & Voltage lag

$V_C$  will lag  $90^\circ$  by current

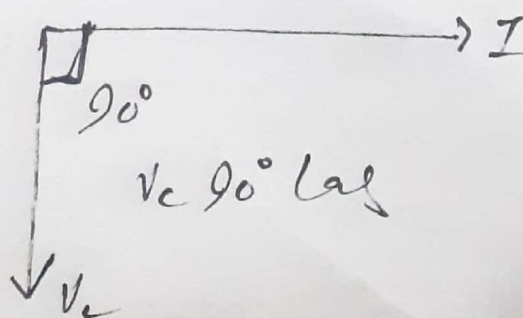




Example 9.8 ... The voltage  $v = 12 \cos(60t + 45^\circ)$  is applied to a  $0.1 \text{ H}$  inductor. Find the Steady State current through the inductor.

Solution

For Inductor  $V = j\omega L I$

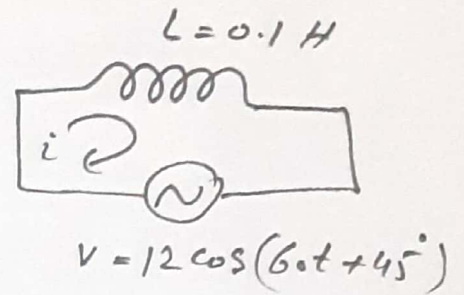where  $\omega = 60 \text{ rad/s}$  &  $V = 12 \angle 45^\circ$



As per formula

$$I = \frac{V}{j\omega L}$$

$$I = \frac{12 \angle 45^\circ}{j \times 60 \times 0.1}$$

$$I = \frac{12 \angle 45^\circ}{1 \angle 90^\circ \times 6}$$

$$I = \frac{2 \angle 45^\circ}{1 \angle 90^\circ}$$

$$I = 2 \angle 45^\circ - 90^\circ$$

$$I = 2 \angle -45^\circ \text{ Amp}$$

Converting this to the time domain

$$i(t) = 2 \cos(60t - 45^\circ) \text{ A}$$


$i(t) = i = j$

$j = \sqrt{-1}$  but in E.E we read as  $1 \angle 90^\circ$

$\therefore \int \dots = 4 \int dx = 4x = j \Rightarrow j4 \Rightarrow 4 \angle 90^\circ$   
 $\frac{d}{dt} \dots = \frac{d}{dt} 4 = 0$   $90^\circ$  Shift

$V = L \frac{di}{dt}$   
 $V = L j\omega I$   
 $I = \frac{V}{j\omega L}$

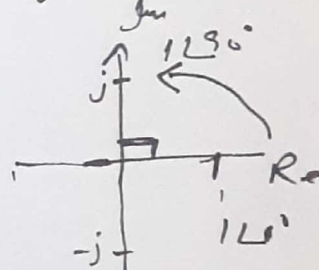$j = 1 \angle 90^\circ$   
 $90^\circ$  Lead  
 $j^0 = 1$   
 $j^1 = j = 1 \angle 90^\circ$   
 $-j = 1 \angle -90^\circ$



$i = \sqrt{-1}$   
 $j = \sqrt{-1}$   
 $j = (-1)^{1/2}$   
 $1 \angle 90^\circ$   
 $90^\circ$  Shift

Example Practice Problem 9.8

If voltage  $v = 10 \cos(100t + 30^\circ)$  is applied to a 50  $\mu\text{F}$  Capacitor, calculate the current through the capacitor?

Solution


$$v = 10 \cos(100t + 30^\circ)$$

$$V = 10 \angle 30^\circ$$

$$\omega = 100 \text{ rad/s}$$

$$C = 50 \times 10^{-6} \text{ F}$$

$$I = ?$$

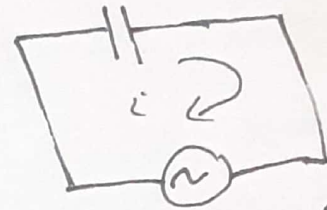

$$v = 100 \cos(100t + 30^\circ)$$

So Putting formula

$$I = j\omega C \cdot V$$

$$I = 1 \angle 90^\circ \cdot 100 \times 50 \times 10^{-6} \times 10 \angle 30^\circ$$

$$I = 10 \angle 90^\circ + 30^\circ \cdot (0.005)$$

$$I = 0.05 \angle 120^\circ \text{ A}$$

$$I = 50 \angle 120^\circ \text{ mA}$$

In time Domain

$$i(t) = 50 \cos(100t + 120^\circ) \text{ mA}$$

∴ As we know that

$$V = X_c I$$

$$V = \frac{1}{j\omega C} I$$

$$V \cdot j\omega C = I$$

$$\therefore 1/j = 1 \angle 90^\circ$$



# Impedance & Admittance

AC Impedance  
voltage-current relationship for the three passive Element

Time Domain

Generalized ohm's Law

$$V = iR \quad [\text{Resistance}]$$

$$V_L = L \frac{di}{dt} \quad [\text{Inductor}]$$

$$\frac{dV}{dt} = \frac{i}{C} \quad [\text{Capacitor}]$$

$$V = \frac{1}{C} \int i \cdot dt$$

$$i = C \frac{dV}{dt}$$

$$V = IR, \quad V = j\omega L I, \quad V_C = \frac{I}{j\omega C}$$

These Equation may be written in term of ratio of the Phasor voltage to the Phasor current

$$\frac{V}{I} = R, \quad \frac{V}{I} = j\omega L, \quad \frac{V}{I} = \frac{1}{j\omega C}$$

$$Z = R$$

$$Z = j\omega L$$

$$Z = \frac{1}{j\omega C}$$

$$Z = -j/\omega C$$

## Definition of Impedance

"The Impedance  $Z$  of a circuit is the ratio of the ~~circuit~~ Phasor voltage ( $V$ ) to the Phasor current ( $I$ ), measured in ohm ( $\Omega$ )  
mathematically

$$Z = \frac{V}{I} \Rightarrow V = I Z$$

"The impedance represents the opposition that the circuit exhibits to the flow of sinusoidal current".

Phasor domain

$$V_R = IR$$

$$V_L = j\omega L I$$

$$V_C = \frac{1}{C} \cdot \frac{I}{j\omega}$$


$$V_C = \frac{I}{j\omega C}$$

$$\left. \begin{array}{l} V = X_L \cdot I \\ V = j\omega L \cdot I \\ \text{OR } V_C = X_C \cdot I \\ V_C = \frac{I}{j\omega C} \end{array} \right\}$$

$$Z_R = R$$

$$Z_L = j\omega L$$

$$Z_C = -\frac{j}{\omega C}$$

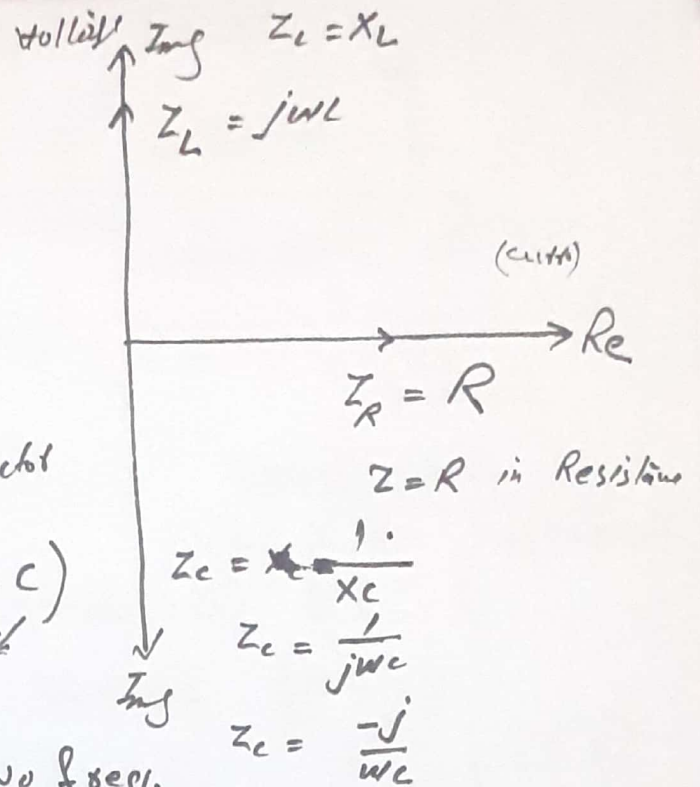

Consider two Extreme cases of angular frequency.


(i) DC Source (behavior of L & C)  
 when  $\omega = 0$

$$Z_L = j\omega L$$


$$Z_L = j2\pi f L \quad \text{as DC has no freq.}$$

$Z_L = 0$  So  $X_L = 2\pi f L$ , No Inductive Reactance

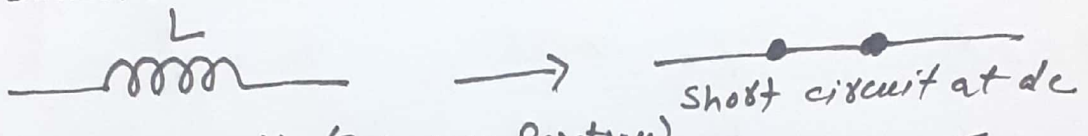So the Inductor acts like a short circuit at dc.



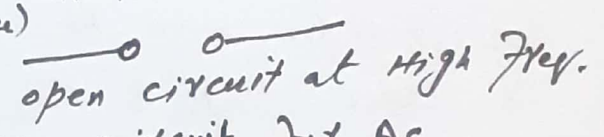if  $f$  is high then  $X_L$  (Inductive Reactance) will be high, then impedance will also very high  $f$  act as open circuit for AC





(ii) when  $\omega_c \rightarrow \infty$  i.e.  $\omega = 0$  in capacitive Reactance

$$X_C = \frac{1}{2\pi f C} = X_C = \frac{1}{0} = \infty$$

$$Z_C = \frac{1}{j\omega C} \Rightarrow Z_C = \frac{1}{0} = \infty$$

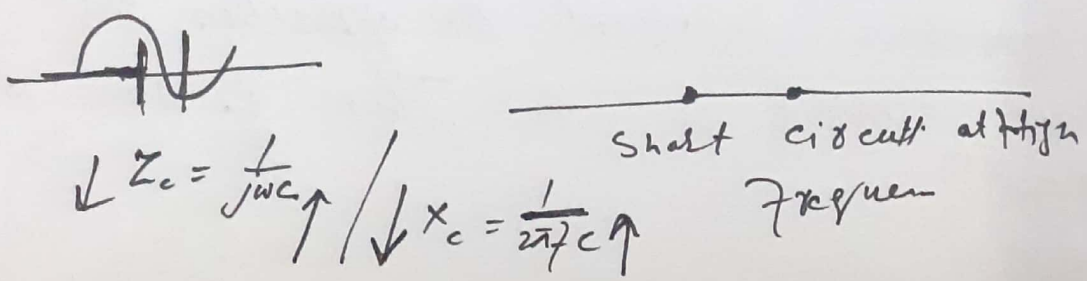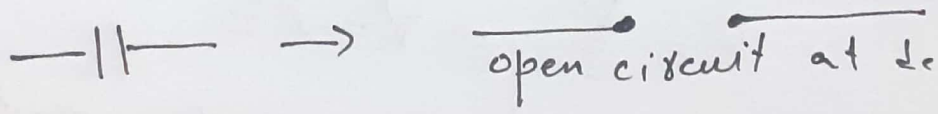The Capacitor acts like an open circuit at dc because of infinite capacitive impedance.



$$\downarrow Z_C = \frac{1}{j\omega C} \uparrow \quad \downarrow X_C = \frac{1}{2\pi f C} \uparrow$$

## Admittance (Y)

"The admittance (Y) is the reciprocal of impedance, measured in Siemens (S)  $\rightarrow$   $\frac{1}{\Omega}$ "

$$\therefore Y = \frac{1}{Z}$$

<u>Element</u>	<u>Impedance</u>	<u>Admittance</u>
R	$Z = R$	$Y = \frac{1}{Z}$
L	$Z = j\omega L$	$Y = \frac{1}{j\omega L}$
C	$Z = \frac{1}{j\omega C}$	$Y = j\omega C$

$\therefore$   $Z = R + jX$   
Real  $\leftarrow$   $\rightarrow$  Imaginary

$Z = R + jX$  is Inductive /

$Z = R - jX$  is capacitive

$\therefore$  Admittance =  $Y = \frac{1}{Z} = \frac{1}{R + jX}$


$Y = G + jB$

Conductance  $G = \frac{1}{R}$   
~~S~~ susceptance  $= jB$



Example 9.9 Find  $v(t)$  and  $i(t)$  in the circuit

Shown in Fig. below

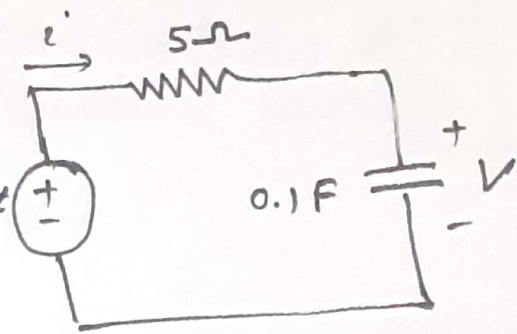

Data

$$V_s = 10 \cos 4t$$

$$\omega = 4$$

$$C = 0.1 \text{ F}$$

As Required  $I = \frac{V}{Z}$

First, we will find the 'Z' Impedance

$$Z = R + X_c$$

$$Z = R + \frac{1}{j\omega C}$$

$$Z = 5 + \frac{j}{j^2 \times 4 \times 0.1}$$

$$Z = 5 - \frac{j}{0.4}$$

$$Z = 5 - j2.5 \text{ } \Omega$$

Hence the current  $\Rightarrow I = \frac{V_s}{Z}$

$$I = \frac{10 \angle 0^\circ}{5 - j2.5}$$


$$I = \frac{10}{5 - j2.5} \times \frac{5 + j2.5}{5 + j2.5}$$

$$I = \frac{50 + j25}{25 - j^2 6.25}$$

$$I = \frac{50 + j25}{25 + 6.25} = \frac{50}{31.25} + \frac{j25}{31.25}$$

$$I = 1.6 + j0.8$$

Convert into Polar form

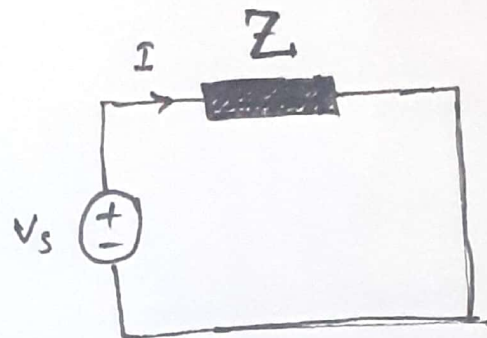

Convert into Polar directly

$$\underline{I = 1.789 \angle 26.57^\circ \text{ A}}$$

→ The Voltage across the Capacitor is

$$V = I Z_c$$

$$\therefore Z_c = \frac{1}{j\omega C}$$

$$V = \frac{I}{j\omega C}$$

$$V = \frac{1.789 \angle 26.57^\circ}{1.29 \times 4 \times 0.1}$$

$$V = \frac{1.789 \angle 26.57^\circ}{0.4 \angle 90^\circ}$$

$$V = \frac{1.789}{0.4} \angle 26.57^\circ - 90^\circ$$

$$V = 4.47 \angle -63.43^\circ \text{ V}$$

$$\begin{aligned} \therefore i &= C \frac{dv}{dt} \\ \left( \frac{i}{C} \right) &= \left( \frac{d(v)}{dt} \right) \\ \frac{1}{C} \int i dt &= V \\ V &= \frac{I}{j\omega C} \end{aligned}$$

Converting  $I$  &  $V$  into the time domain

$$i(t) = 1.789 \cos(4t + 26.57^\circ) \text{ A}$$

$$V(t) = 4.47 \cos(4t - 63.43^\circ) \text{ V}$$

Notice that  $i(t)$  leads  $v(t)$  by  $90^\circ$  as expected.

# Practice Problem 9.9

Determine  $v(t)$  &  $i(t)$  and also write your analysis or comments.

Data  $R = 4 \Omega$   
 $L = 0.2 \text{ H}$   
 $V_s = 20 \sin(10t + 30^\circ) \text{ V}$

first of all convert sin into cosine



$$V_s = 20 \cos(10t + 30^\circ - 90^\circ)$$

$$V_s = 20 \cos(10t - 60^\circ)$$

in Phasor Domain

$$V_s = 20 \angle -60^\circ \quad \omega = 10$$
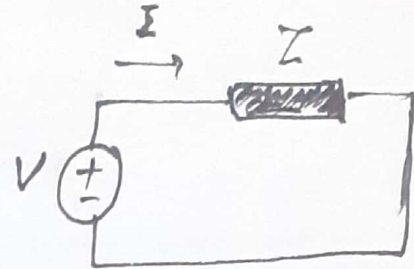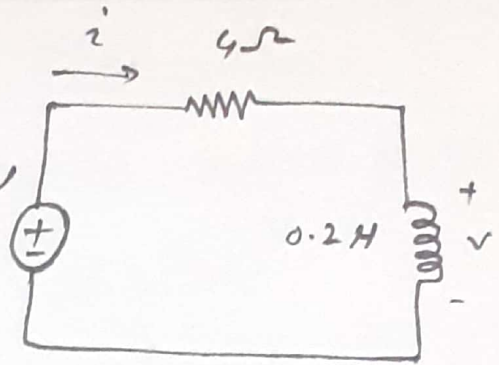
$$\cos(\omega t - 90^\circ) = \sin \omega t$$



The required formula is

$$I = \frac{V}{Z} \quad \therefore \text{first we will find } Z$$

The Impedance =  $Z = R + jX_L$

$$Z = R + j\omega L$$

$$Z = 4 + j \cdot 10 \times 0.2$$

$$Z = 4 + j2 \Omega$$

$$\therefore \sin(\omega t + 90^\circ) = \cos \omega t$$

Hence the current is

$$I = \frac{V}{Z} = \frac{20 \angle -60^\circ}{4 + j2}$$

$$I = \frac{20 \angle -60^\circ}{4.47 \angle 26.56^\circ}$$

$$I = \frac{20}{4.47} \angle -60^\circ - 26.56^\circ$$

$$I = 4.472 \angle -86.56^\circ \text{ A}$$

No write in time domain as required in question

$$i(t) = 4.472 \cos(10t - 86.56^\circ) \text{ A}$$

$$i(t) = 4.472 \sin(10t - 86.56^\circ + 90^\circ) \text{ A}$$

$$i(t) = 4.472 \sin(10t + 3.44^\circ) \text{ A}$$

Convert from Rectangular into Polar

$$Z = 4 + j2$$

$$Z = \sqrt{(4)^2 + (2)^2}$$

$$Z = \sqrt{16 + 4}$$

$$Z = \sqrt{20}$$

$$Z = 4.47$$

$$\theta = \tan^{-1}\left(\frac{2}{4}\right)$$

$$\theta = 26.56$$



Now we can find the voltage across the Inductor.

$$V = I Z_L$$

$$Z_L = j\omega L$$

$$V = 4.472 \angle -86.56^\circ \times j\omega L$$

$$V = 4.472 \angle -86.56^\circ \times 1 \angle 90^\circ \times 10 \times 0.2$$

$$V = 4.472 \angle -86.56^\circ \times 2 \angle 90^\circ$$

$$V = 8.944 \angle 3.44^\circ \text{ V}$$

in time domain

~~V(t) =~~

$$v(t) = 8.944 \cos(10t + 3.44) \text{ V}$$

The Answer should be in given question format  
if in sine then answer will be in sin  
i.e.  $\Rightarrow$  convert into ~~sin~~ sin.

$$v(t) = 8.99 \sin(10t + 3.44 + 90^\circ)$$

$$v(t) = 8.99 \sin(10t + 93.44^\circ) \text{ V} \quad \therefore \sin(\omega t + 90^\circ) = \cos \omega t$$

Extra

Analysis of this P.P. 9.9

$$i(t) = 4.72 \sin(10t + 3.44^\circ) \text{ Amp}$$

$$v(t) = 8.944 \sin(10t + 93.44^\circ) \text{ Volts}$$

Notice/Analyze that the voltage is lead  
 $90^\circ$  by current, as expected.

## Kirchhoff's Law in the frequency Domain

KCL (current Law)

KVL (Voltage Law)

**KCL**

"In any network the algebraic sum of the current meeting at a point (or Junction) is zero."

**"OR"**


"The sum of the current flowing towards a point is equal to the sum of those following away from it"

**"OR"**

The algebraic sum of the currents entering to a Node equals to the sum of the current leaving it


$$i_1 + i_4 = i_2 + i_3 + i_5$$

$$i_1 + i_4 - i_2 - i_3 - i_5 = 0$$

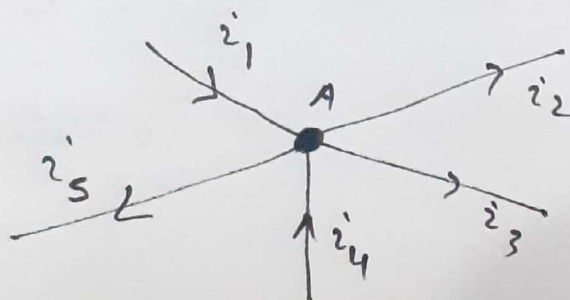

In coming current = out going current  
mathematically
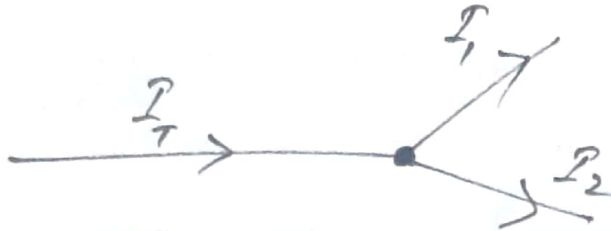
$$\sum I(\text{entering}) = \sum I(\text{leaving})$$



$$I_T = I_1 + I_2$$


∴ Consider all current into a point as positive & all current directed away from that point as negative

$$i_1 + i_3 = i_2 + i_4$$

$$\text{Sum of } \theta^\circ = \text{Sum } \theta^\circ$$

in phasor domain
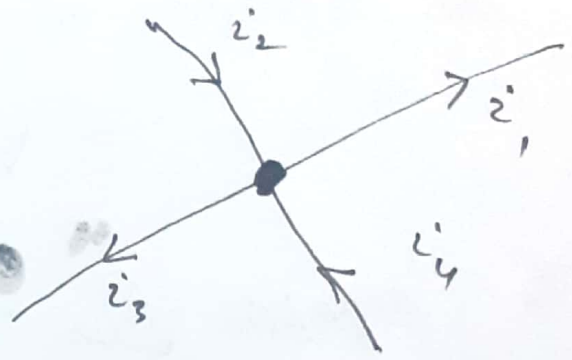
$$I_1 \angle \theta^\circ + I_3 \angle \theta = I_2 \angle \theta^\circ + I_4 \angle \theta$$



$$\Rightarrow I_1 (\cos \theta + j \sin \theta) + I_3 (\cos \theta + j \sin \theta) = I_2 (\cos \theta + j \sin \theta) + I_4 (\cos \theta + j \sin \theta)$$

$$Z = \delta (\cos \theta + j \sin \theta)$$

$$Z = I (\cos \theta + j \sin \theta)$$

$$\Rightarrow I_1 \cos \theta + j I_1 \sin \theta + I_3 \cos \theta + j I_3 \sin \theta = I_2 \cos \theta + j I_2 \sin \theta + I_4 \cos \theta + j I_4 \sin \theta$$

separate Real & Imag. Part

$$(I_1 + I_3) \cos \theta + j(I_1 + I_3) \sin \theta = (I_2 + I_4) \cos \theta + j(I_2 + I_4) \sin \theta$$

Real  $\leftarrow$  Imaginary

similarly we

$$V_1 \angle \theta + V_2 \angle \theta = V_3 \angle \theta$$

$$V_1 (\cos \theta + j \sin \theta) + V_2 (\cos \theta + j \sin \theta) = V_3 (\cos \theta + j \sin \theta)$$

$$(V_1 + V_2) \cos \theta + j(V_1 + V_2) \sin \theta = V_3 \cos \theta + j V_3 \sin \theta$$

Real  $\leftarrow$  Imaginary



Application of KCL & KVL in Impedance, Combination, Nodal & Mesh Analysis and also in Superposition & Source Transformation

Definition of KVL

Kirchoff's Voltage Law

"In any closed path (or circuit) in a network, the algebraic sum of all the voltage is equal to zero"

$$\sum V = 0$$

The Algebraic Sum <sup>"OR"</sup> of the Voltages around any closed path is zero

<sup>'OR'</sup>  
In any closed loop, the algebraic sum of the voltage, applied is equal to the algebraic sum of the voltage drop in the element

$$V_1 + V_2 + \dots + V_n = 0$$

Each voltage may be written in cosine

$$V_{m1} \cos(\omega t + \theta_1) + V_{m2} \cos(\omega t + \theta_2) + \dots + V_{mn} \cos(\omega t + \theta_n)$$