

Chapter #08:- → TRVU:-

Second Order circuit

↳ 2nd ODE → 2nd order RLC.

↳ 1st ODE (contains only single energy storage element either capacitor or inductor).


Introduction:- (RLC)

A second order circuit characterized by 2nd order differential equation - It consists of resistor and combination of two energy storage elements (L & C)

(pg# 314 - 315)

→ active elements produce gain while passive element not produces gain.

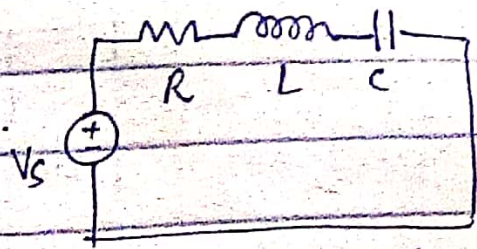→ How to obtain the initial condition for circuit variable.



8.2 Finding initial & final values.
 $v(0)$; $i(0)$; $\frac{dv(0)}{dt}$; $i(\infty)$; $v(\infty)$ → ~~initial~~ final value.

Steps:-

1. Carefully handle polarity of voltage $v(t)$ across the capacitor & direction of current $i(t)$ through the inductor.



→ keep in mind that capacitor voltage is always continuous.

$$v(0^+) = v(0^-)$$

$$i(0^+) = i(0^-)$$

• $t < 0$ / $t = 0^-$ (before switching)

• $t > 0$ / $t = 0^+$ (after switching) → permanent switch is there.

• $t = 0 \rightarrow t = 0$ (switching event take place slowly charge & discharge)

→ capacitor's voltage can't change abruptly -

→ current in inductor can't change abruptly -



• At DC → capacitor → open-cct. , inductor → short-cct.

Example #8.1-

switch in fig is closed for a long time. It is open at $t=0$. Find: (a) $i(0^+)$, $v(0^+)$

(b) $\frac{di(0^+)}{dt}$, $\frac{dv(0^+)}{dt}$

(c) $i(\infty)$, $v(\infty)$

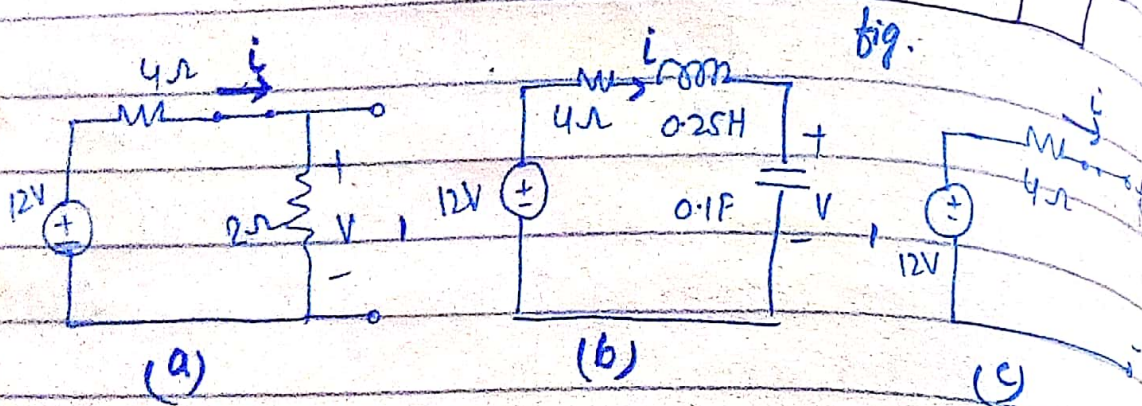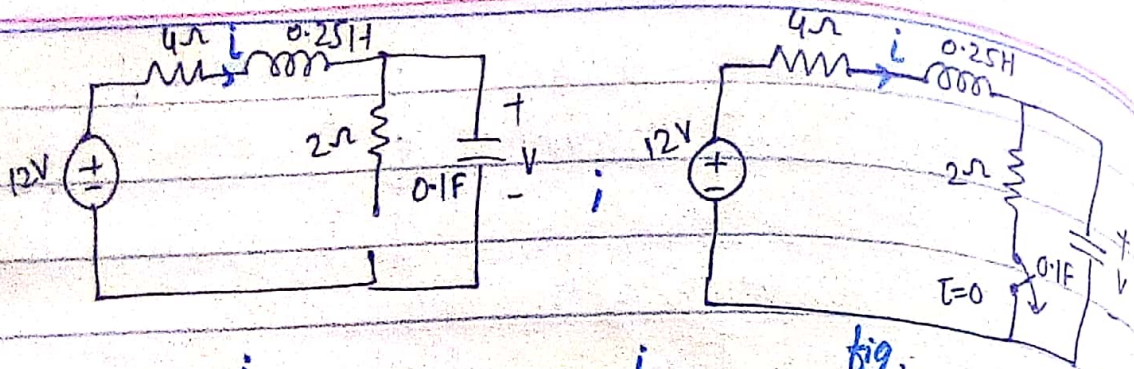

When switch is connected for a long time;
 Then C & L reaches to steady state. Hence;
 Inductor is short & C → open. (a)

i) $\frac{V}{R} = i(0^-) = \frac{12}{4+2} = 2A$

$V(0^-) = 2 \cdot i(0^-) = 2 \times 2 = 4V$

as: $i(0^+) = i(0^-) = 2A$;

$V(0^+) = V(0^-) = 4V$

$t = 0^+$ (after switching)

$i_c(0^+) = i(0^+) = 2A$

$i_c = C \frac{dv}{dt}$

$\frac{dv}{dt} = \frac{i_c}{C} = \frac{2}{0.1} = 20 \text{ V/s}$

ii) $t = 0$ (switch remove) → (b)

$V_L = L \frac{di}{dt} \Rightarrow \frac{di}{dt} = \frac{V_L(0^+)}{L}$

KVL at (b):

$-12 + 4i(0^+) + V_L(0^+) + V_C(0^+) = 0$

$-12 + 4(2) + V_L(0^+) + 4 = 0$

$V_C(0^+) = 4$
 $i(0^+) = 2$

$$V_L(0^+) = 12 - 8 - 4 = 0.$$

$$\frac{di(0^+)}{dt} = \frac{V_L(0^+)}{L} = \frac{0}{0.25} = 0 \text{ A/s.}$$

iii) $t > 0; t \rightarrow \infty$

$$i(\infty) = 0 \text{ A.}$$

$$V(\infty) = 12 \text{ V}$$

8.3 The Source-free Series RLC circuit:-

Natural response of RLC ckt:-

$$\therefore V(0) = V_0$$


$$i(0) = I_0.$$

$$\therefore V_C = V_0$$

KVL:-

$$V_R + V_L + V_C = 0$$
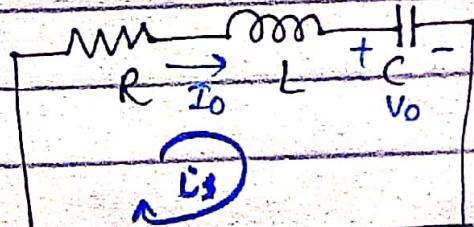
$$iR + L \frac{di}{dt} + \frac{1}{C} \int i dt = 0 \quad (1)$$



Taking derivative on both sides w.r.t 't' to eliminate integral.

$$\begin{aligned} \therefore i &= C \frac{dv}{dt} \\ \int i dt &= \int C dv \\ \frac{1}{C} \int i dt &= v_C. \end{aligned}$$

$$\frac{di}{dt} \cdot R + \frac{d}{dt} \left(L \frac{di}{dt} \right) + \frac{d}{dt} \left(\frac{1}{C} \int i dt \right) = 0.$$

$$\frac{di}{dt} \cdot R + \frac{d^2 i}{dt^2} \cdot L + \frac{1}{C} \cdot i = 0.$$

To remove L-coefficient; divide both sides with 'L':

Eq. be arranged:-

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = 0 \rightarrow 2^{\text{nd}} \text{ order diff. eqn.} \quad (2^{\text{nd}} \text{ ODE})$$

or from eq(1):-

$$iR + L \frac{di}{dt} + V_0 = 0.$$

$$R \cdot i(0) + L \frac{di(0)}{dt} + V_0 = 0.$$

$$L \frac{di(0)}{dt} = -V_0 - Ri_0$$

$$\frac{di(0)}{dt} = \frac{-(V_0 + Ri_0)}{L}$$

let: $i = A e^{st}$

from eq(2) :- (2nd ODE)

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = 0. \quad (1)$$

when: $i = A e^{st}$

$$\frac{di}{dt} = A s e^{st} (s)$$
$$= A s e^{st}$$

so. $\frac{d}{dt} \left(\frac{di}{dt} \right) = \frac{d}{dt} (A s e^{st})$

$$\frac{d^2 i}{dt^2} = A s^2 e^{st}$$

put values in eq(1).

② →

$$(A s^2 e^{st}) + \frac{R}{L} (A s e^{st}) + \frac{(A e^{st})}{LC} = 0$$

Common:-

charac. eqn.

$$A e^{st} \left[s^2 + \frac{R}{L} s + \frac{1}{LC} \right] = 0.$$

$$a=1; b=\frac{R}{L}; c=\frac{1}{LC}$$

$$x = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

put a,b,c in quadratic formula:-

$$S_{1,2} = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

$$= \frac{-\left(\frac{R}{L}\right) \pm \sqrt{\left(\frac{R}{L}\right)^2 - 4(1)\left(\frac{1}{LC}\right)}}{2\left(\frac{1}{LC}\right)}$$

$$S_1 = \frac{-\frac{R}{L} + \sqrt{\left(\frac{R}{L}\right)^2 - 4(1)\left(\frac{1}{LC}\right)}}{2\left(\frac{1}{LC}\right)} \quad S_2 = \frac{-\frac{R}{L} - \sqrt{\left(\frac{R}{L}\right)^2 - 4(1)\left(\frac{1}{LC}\right)}}{2\left(\frac{1}{LC}\right)}$$

$$S_1 = \frac{-R}{2L} + \frac{1}{2} \sqrt{\frac{R^2}{L^2} - \frac{4}{LC}}$$

$$S_2 = \frac{-R}{2L} - \frac{1}{2} \sqrt{\frac{R^2}{L^2} - \frac{4}{LC}}$$

$$S_1 = \frac{-R}{2L} + \frac{1}{2} \sqrt{\left(\frac{R}{L}\right)^2 - \frac{4}{LC}}$$

$$S_2 = \frac{-R}{2L} - \frac{1}{2} \sqrt{\left(\frac{R}{L}\right)^2 - \frac{4}{LC}}$$

$$\text{or } S_1 = \frac{-R}{2L} + \frac{1}{\sqrt{4}} \sqrt{\left(\frac{R}{L}\right)^2 - \frac{4}{LC}}$$

$$S_2 = \frac{-R}{2L} - \frac{1}{\sqrt{4}} \sqrt{\left(\frac{R}{L}\right)^2 - \frac{4}{LC}}$$

$$S_1 = \frac{-R}{2L} + \sqrt{\frac{R^2}{4L^2} - \frac{1}{LC}}$$

$$S_2 = \frac{-R}{2L} - \sqrt{\frac{R^2}{4L^2} - \frac{1}{LC}}$$

$$S_1 = \frac{-R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$$S_2 = \frac{-R}{2L} - \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

let $\alpha = \frac{R}{2L}$

let $\alpha = R/2L$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\omega_0^2 = \frac{1}{LC}$$

$$\omega_0^2 = \frac{1}{LC}$$

so,

$$S_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

so, $S_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$

so,

$$S_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

S_1 & $S_2 \rightarrow$ natural frequencies. ; $\omega_0 =$ resonant freq.
 $\alpha \rightarrow$ damping factor.

$\left. \begin{array}{l} \text{(i) } \alpha > \omega_0 \\ \text{(ii) } \alpha < \omega_0 \\ \text{(iii) } \alpha = 0 \end{array} \right\} \rightarrow \begin{array}{l} \text{Over-damped (roots of eq. are real \& \amp; \text{unequal)} \\ \text{Under-damped} \\ \text{Critical-damped.} \end{array}$

As: $i = A e^{st}$

So, $i_1 = A_1 e^{s_1 t}$ & $i_2 = A_2 e^{s_2 t}$

Total response $i = i_1 + i_2$

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

Case #1 (over-damped)

$\rightarrow (\alpha > \omega_0)$

$\rightarrow b^2 - 4ac = 0$

or $\alpha^2 - \omega_0^2 = 0$

$$\left(\frac{R}{2L}\right)^2 - \frac{1}{LC} = 0$$

$$\therefore \alpha = \frac{R}{2L} \quad \omega_0^2 = \frac{1}{LC}$$

$$\frac{R^2}{4L^2} - \frac{1}{LC} = 0 \Rightarrow \frac{R^2}{4L^2} = \frac{1}{LC}$$

$$1 = \frac{4L}{R^2 C}$$

So, $C = \frac{4L}{R^2} \rightarrow C > \frac{4L}{R^2}$

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

Case #2:- (under-damped) ($\alpha < \omega_0$)

Monday
24-02-2020

→ What is Damping?

To cause a decrease in amplitude of oscillation.

RLC-series:-

over-damped case ($\alpha > \omega_0$):-

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

ii) Critically-damped case:- ($d = \omega_0$)

$$i(\bar{t}) = (A_2 + A_1 \bar{t}) e^{-\alpha \bar{t}}$$

iii) Underdamped case:- ($d < \omega_0$)

$$i(\bar{t}) = e^{-\alpha \bar{t}} (B_1 \cos \omega_d \bar{t} + B_2 \sin \omega_d \bar{t})$$

RLC - parallel:-

i) Over-damped case ($d > \omega_0$):-

$$v(\bar{t}) = A_1 e^{s_1 \bar{t}} + A_2 e^{s_2 \bar{t}}$$

ii) Critically damped case ($\alpha = \omega_0$):-

$$v(\bar{t}) = (A_1 + A_2 \bar{t}) e^{-\alpha \bar{t}}$$

iii) Underdamped case ($d < \omega_0$):-

$$v(\bar{t}) = e^{-\alpha \bar{t}} (A_1 \cos \omega_d \bar{t} + A_2 \sin \omega_d \bar{t})$$

Problem solving strategy:-

1. For $\bar{t} < 0$, we have to find the initial conditions $i(0)$ and $v(0)$.

2. For $\bar{t} > 0$ circuit, write KVL equation and then find v_L .

$$\frac{di}{dt} = \frac{v_L}{L}$$

3. For $\bar{t} > 0$; calculate α, ω_0 & roots $s_{1,2}$. Plug in values of $i(0)$ and $v(0)$ to get $\frac{di}{dt} \Big|_{\bar{t}=0}$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

4. Based on value of α and ω_0 , choose eqn. for current $i(\bar{t})$ and plug \bar{t} values in it.

5. Calculate value of A_1 & A_2 and plug it in to get final answer.

i) $i(0)$ & $v(0)$

ii) $\frac{di}{dt} \Big|_{t=0}$ Through KVL.

iii) d, ω_0 & $S_{1,2}$


iv) $i(t)$ eqn.

v) A_1 & A_2 .

RLC-series:-

2nd order differential eqn.
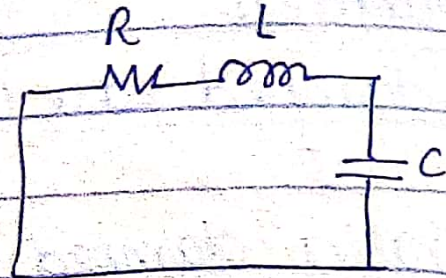
$$\frac{d^2i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = 0$$



$$Ae^{-st} \left[s^2 + \frac{R}{L}s + \frac{1}{LC} \right] = 0$$

→ roots after quadratic formula.

$$\bullet s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$\bullet s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$i(t) = Ae^{st}$; $i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$

$\alpha = \omega_0$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} ; s_1 = s_2 = -\alpha$$

$$i(t) = (A_1 e^{-\alpha t} + A_2 e^{-\alpha t})$$

$$= (A_1 + A_2) e^{-\alpha t}$$

$$= \boxed{A_3 e^{-\alpha t}}$$

→ $\frac{d^2i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = 0$

$$\therefore \alpha = \frac{R}{2L}$$

$$\frac{d^2i}{dt^2} + 2\left(\frac{R}{2L}\right) \frac{di}{dt} + \frac{i}{L\left(\frac{4L}{R^2}\right)} = 0$$

$$\therefore C = \frac{4L}{R^2}$$

$$\frac{d^2i}{dt^2} + 2\alpha \frac{di}{dt} + \frac{i}{4L^2} = 0$$

$$\frac{d^2 i}{dt^2} + 2\alpha \frac{di}{dt} + \left(\frac{R}{2L}\right)^2 i = 0$$

$$\frac{d^2 i}{dt^2} + 2\alpha \frac{di}{dt} + \alpha^2 i = 0$$

splitting

$$\left(\frac{d^2 i}{dt^2} + \alpha \frac{di}{dt}\right) + \left(\alpha \frac{di}{dt} + \alpha^2 i\right) = 0$$

Taking $\frac{d}{dt}$ common:

$$\frac{d}{dt} \left(\frac{di}{dt} + \alpha i \right) + \alpha \left(\frac{di}{dt} + \alpha i \right) = 0$$

Let: $f = \frac{di}{dt} + \alpha i$

So:

$$\frac{d}{dt} (f) + \alpha (f) = 0 \rightarrow \text{1st ODE}$$

$$\because f = A_1 e^{-\alpha t} \rightarrow \text{PUT } f \text{ in eq.}$$

$$\frac{d}{dt} A_1 e^{-\alpha t} + \alpha A_1 e^{-\alpha t} = 0$$

$$\sqrt{A_1 e^{-\alpha t} (-\alpha) + \alpha A_1 e^{-\alpha t} = 0}$$

$$f = \frac{d}{dt} (i) + \alpha i$$

$$A_1 e^{-\alpha t} = \left(\frac{di}{dt} + \alpha i \right) e^{\alpha t}$$

$$A_1 = e^{\alpha t} \frac{di}{dt} + \alpha i e^{\alpha t}$$

apply product formula:-

$$= \frac{d}{dt} (e^{\alpha t} \cdot i)$$

$$= e^{\alpha t} \frac{di}{dt} + \alpha i \cdot e^{\alpha t} \Rightarrow A_1 = \frac{di}{dt} (e^{\alpha t} - i)$$

Integrate on both sides to eliminate derivatives

$$\int A_1 = \int \frac{d}{dt} (e^{\alpha t} \cdot i) dt$$

$$A_1 t + A_2 = e^{\alpha t} \cdot i$$

$$i(t) = (A_2 + A_1 t) e^{-\alpha t}$$

Example # 8.3 :-

$$R = 40 \Omega; \quad L = 4H; \quad C = \frac{1}{4} F; \quad s_{1,2} = ?$$

$$\alpha = \frac{R}{2L} = \frac{40}{2(4)} = 5$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{4 \times \frac{1}{4}}} = 1$$

$5 > 1$
 $\alpha > \omega_0$
over-damped.

So, roots are:-

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$
$$= -5 \pm \sqrt{25 - 1}$$

$$s_1 = -5 + \sqrt{24}; \quad s_2 = -5 - \sqrt{24}$$

$$s_1 = -0.101; \quad s_2 = -9.89$$

P.P# 8.3 :-

$$R = 10 \Omega; \quad L = 5H; \quad C = 2mF; \quad s, \alpha, \omega = ?$$

$$\alpha = \frac{R}{2L} = \frac{10}{2(5)} = 1$$

$$\omega = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{5 \times (2 \times 10^{-3})}} = 10$$

$\omega > \alpha$
under-damped.

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$
$$= -1 \pm \sqrt{1 - 100}$$

$$s_{1,2} = -1 \pm j9.95$$

Example # 8.4 :-

find $i(t)$; assume that circuit has reached steady state $t=0$.

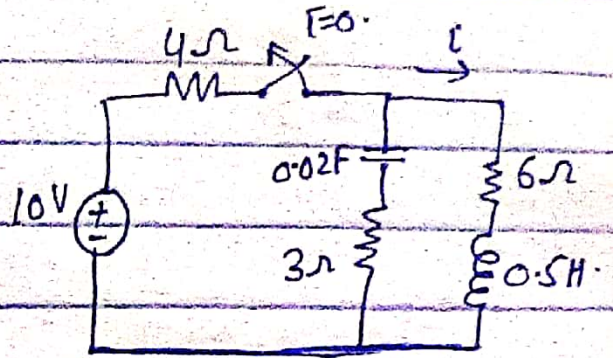


Fig-1.

Solution:-

- STEPS
- 1- $i(0)$ and $v(0)$
 - 2- $di/dt|_{t=0}$ through KVL
 - 3- d, ω, S, \dots
 - 4- $i(t)$ eqn.
 - 5- A_1 & A_2 .

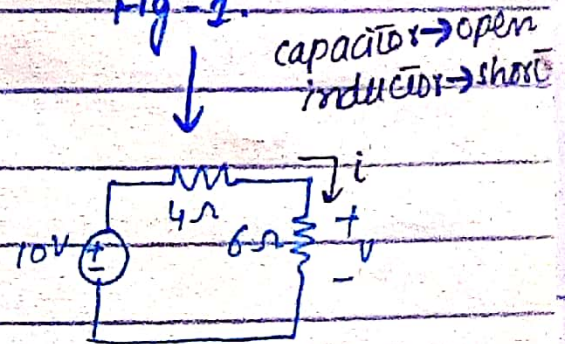


Fig-2.

Solution:-

step#1: Fig2 $\Rightarrow i(0) = \frac{V}{R} = \frac{10}{10} = 1A$.

$$v(0) = i R_{eq}$$

$$= (1)(6)$$

$$v(0) = 6V$$

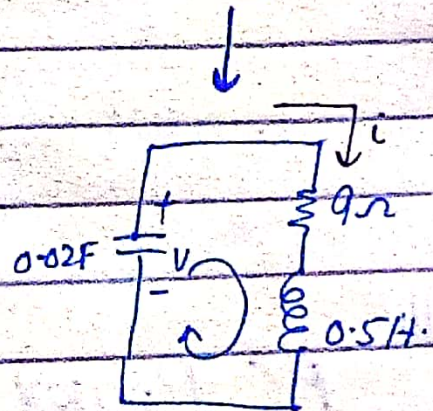


Fig-3.

Fig#3 \rightarrow step#2

$$V_L = L \frac{di}{dt}$$

$$\left. \frac{di}{dt} \right|_{t=0} = \frac{V_L}{L}$$

KVL on fig#3 to find V_L :-

$$-V_C + V_R + V_L = 0$$

$$V_L(0) = V_C(0) - V_R(0)$$

$$V_L(0) = 6 - i(0)R$$

$$= 6 - 1(9)$$

$$\boxed{V_L(0) = 6 - 9 = -3} \rightarrow \text{put in eq:-}$$

$$\left. \frac{di}{dt} \right|_{t=0} = \frac{-3}{0.5}$$

$$= -6 \text{ A/s}$$

STEP #3 $\alpha = \frac{R}{2L} = \frac{9}{2(0.5)} = 9$

$$\omega = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{0.5(0.02)}} = 10$$

$\alpha < \omega$
under-damped.

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega^2}$$

$$= -9 \pm \sqrt{81 - 100}$$

$$= -9 \pm j 4.359$$

STEP #4 So, $i(t) = e^{-\alpha t} (A_1 \cos 4.359j + A_2 \sin 4.359j)$

Ex. 8.1 pp. 8-1 → 8-10, 8-16
6 → 10, 16 → imp.

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

$$\omega_d = 4.359$$