


# Practical 1

To measure the unknown resistance of coil using carey foster bridge

# Carey Foster bridge

- In [electronics](#), the **Carey Foster bridge** is a [bridge circuit](#) used to measure medium resistances, or to measure small differences between two large resistances. It was invented by [Carey Foster](#) as a variant on the [Wheatstone bridge](#). He first described it in his 1872 paper "On a Modified Form of Wheatstone's Bridge, and Methods of Measuring Small Resistances"

# Diagram

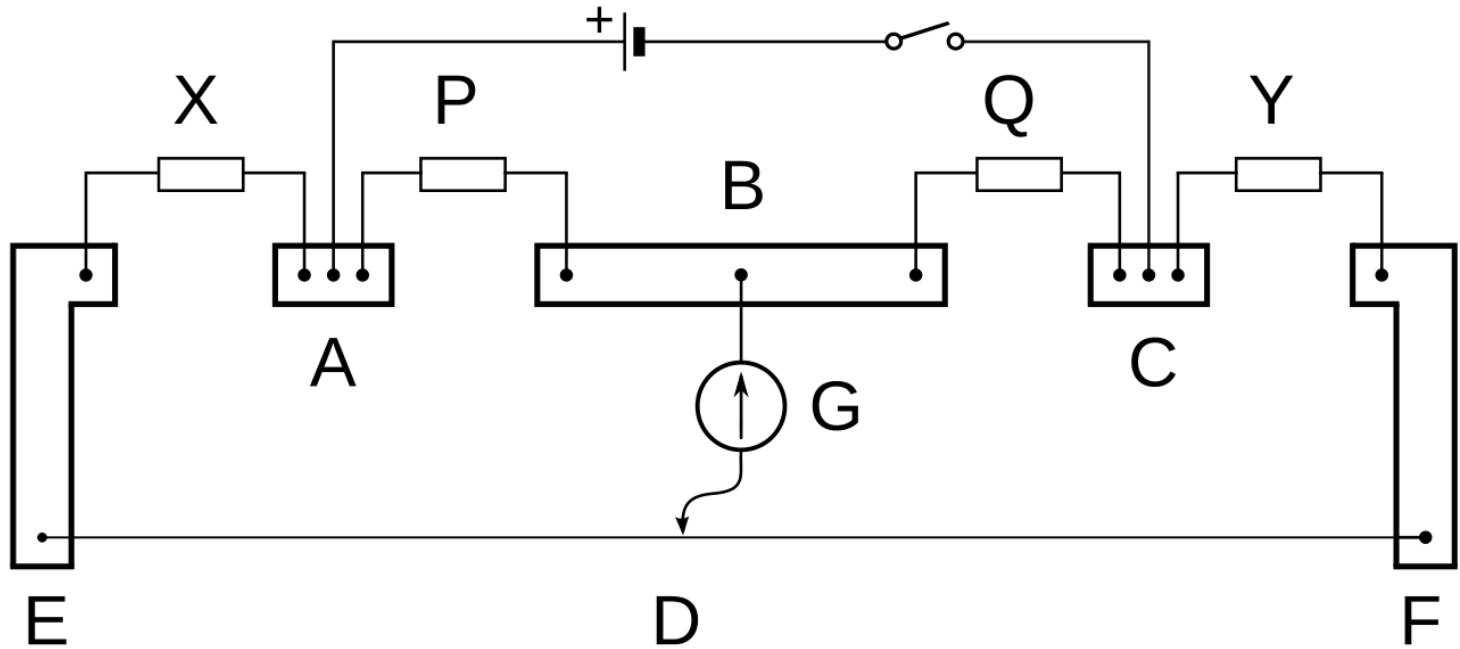

# Use:

- In the adjacent diagram, X and Y are resistances to be compared. P and Q are nearly equal resistances, forming the other half of the bridge. The bridge wire EF has a jockey contact D placed along it and is slid until the galvanometer G measures zero. The thick-bordered areas are thick copper busbars of almost zero resistance.
- Place a known resistance in position Y.
- Place the unknown resistance in position X.

- Adjust the contact D along the bridge wire EF so as to null the galvanometer. This position (as a percentage of distance from E to F) is  $\ell_1$ .
- Swap X and Y. Adjust D to the new null point. This position is  $\ell_2$ .
- If the resistance of the wire per percentage is  $\sigma$ , then the resistance difference is the resistance of the length of bridge wire between  $\ell_1$  and  $\ell_2$
- $$X - Y = \sigma (\ell_2 - \ell_1)$$

- To measure a low unknown resistance  $X$ , replace  $Y$  with a copper busbar that can be assumed to be of zero resistance.
- In practical use, when the bridge is unbalanced, the galvanometer is shunted with a low resistance to avoid burning it out. It is only used at full sensitivity when the anticipated measurement is close to the null point.

# To measure resistance

- To measure the unit resistance of the bridge wire EF, put a known resistance (e.g., a standard 1 ohm resistance) that is less than that of the wire as X, and a copper busbar of assumed zero resistance as Y.