

# **Bipolar Junction Transistor (BJT)**

Operation Theory

# Contents

1. BJT Formation
2. BJT Terminals
3. Biasing of BJT
4. BJT Currents
5.  $\alpha$  of BJT





# Transistors

- Transistors are used for amplification or gain in a circuit.
- When a small variation in voltage or current is used to create a large variation. Like small valve in large water system.
- Two important kinds of transistors are
  - I. BJT----bipolar junction transistor(Bi polar-two polarities)
  - II. FET----Field Effect transistor (Mostly using in I.C)

# BJT, Bipolar Junction Transistor

- Three terminal semiconductor device containing two PN junctions
- Formed from a bar of material that has been doped in such a way that it changes from N to P & back to N.
- When transistor is formed by sandwiching a single P region between two N regions, it is called an NPN type.
- Middle region of each transistor is called base, other two regions are emitter & collector.



# Formation of BJT

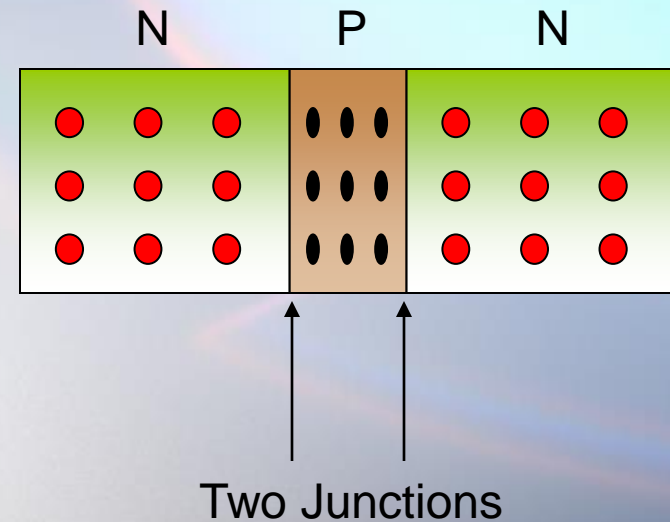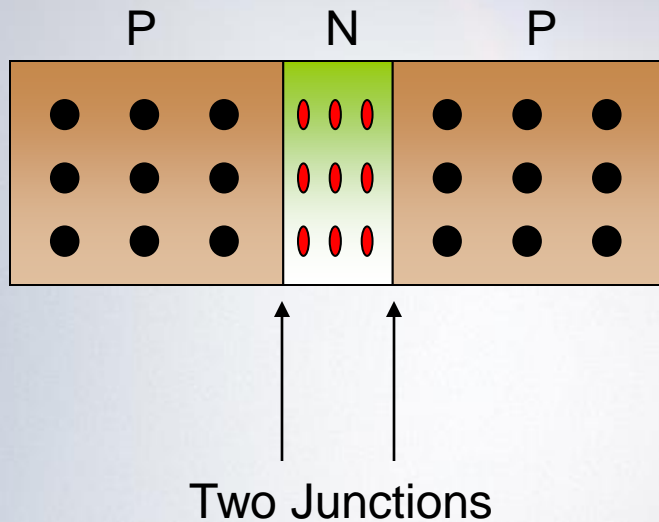







N-Type material has excessive free electrons and P-Type material has excessive holes

NPN and PNP BJTs have same characteristics. The only difference is in their polarities of applied voltages. The polarities are reversed for the two types of transistor.

# BJT Terminals

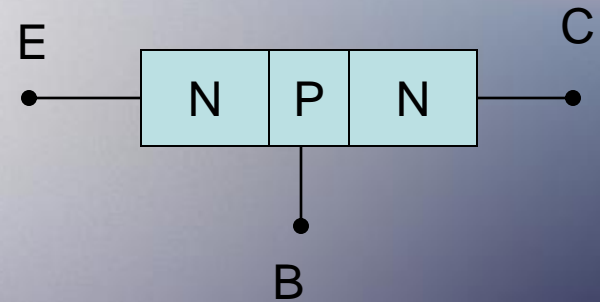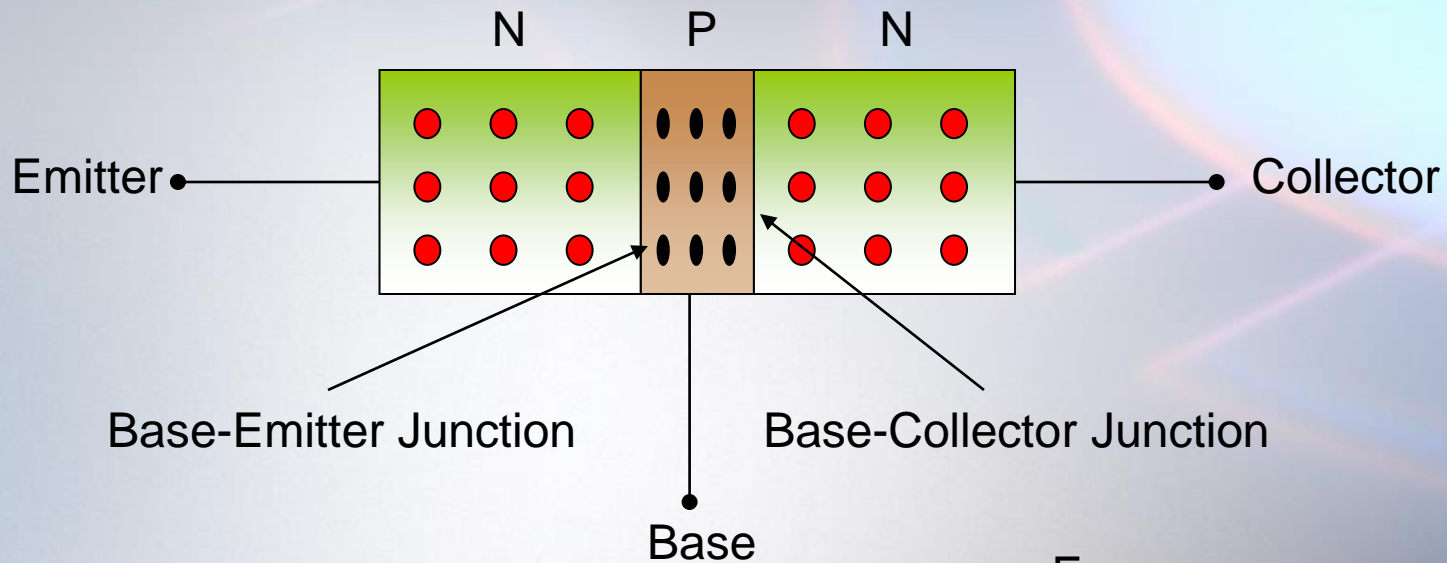

# BJT Circuit Symbols

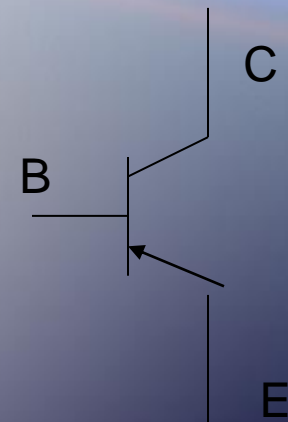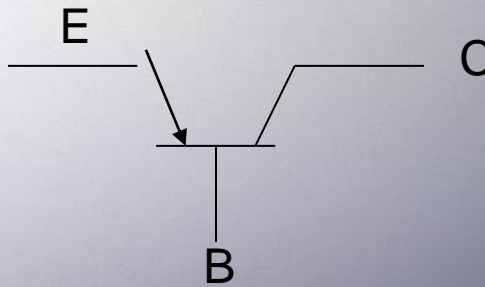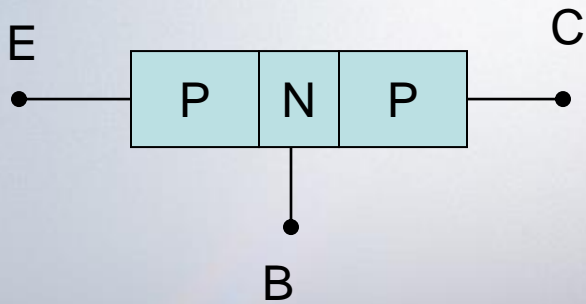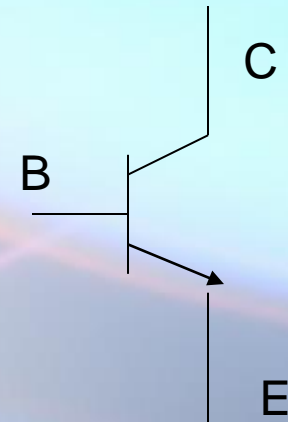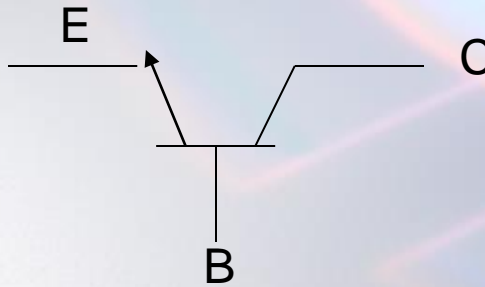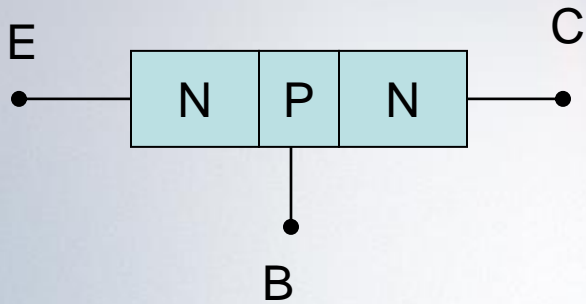


# BJT

- Base region is much more lightly doped and thinner than E & C.
- Emitter is usually heavily doped.
- Biasing is necessary for both PN junctions to obtain normal transistor action.




# Forward Biased Junction Operation

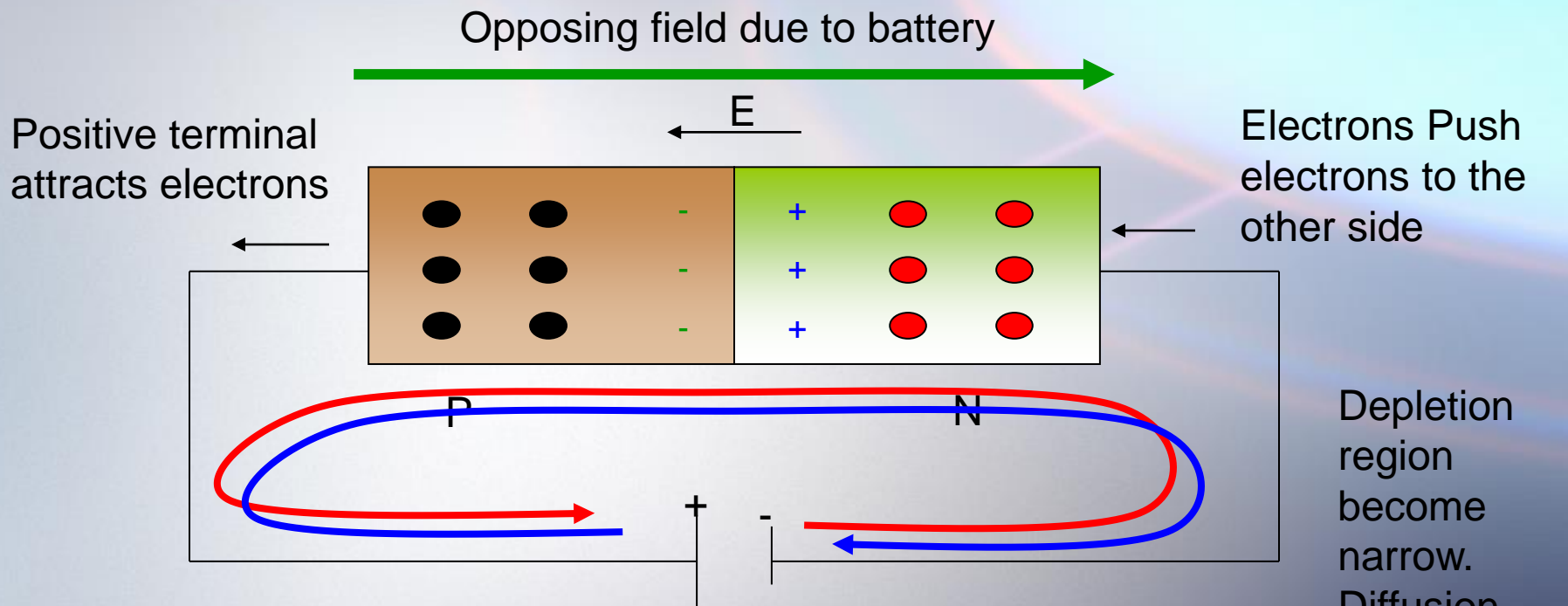


Flow of electron current (diffusion current); but in semiconductor electronics the flow of positive or conventional current is considered

# Reverse Biased Junction Operation

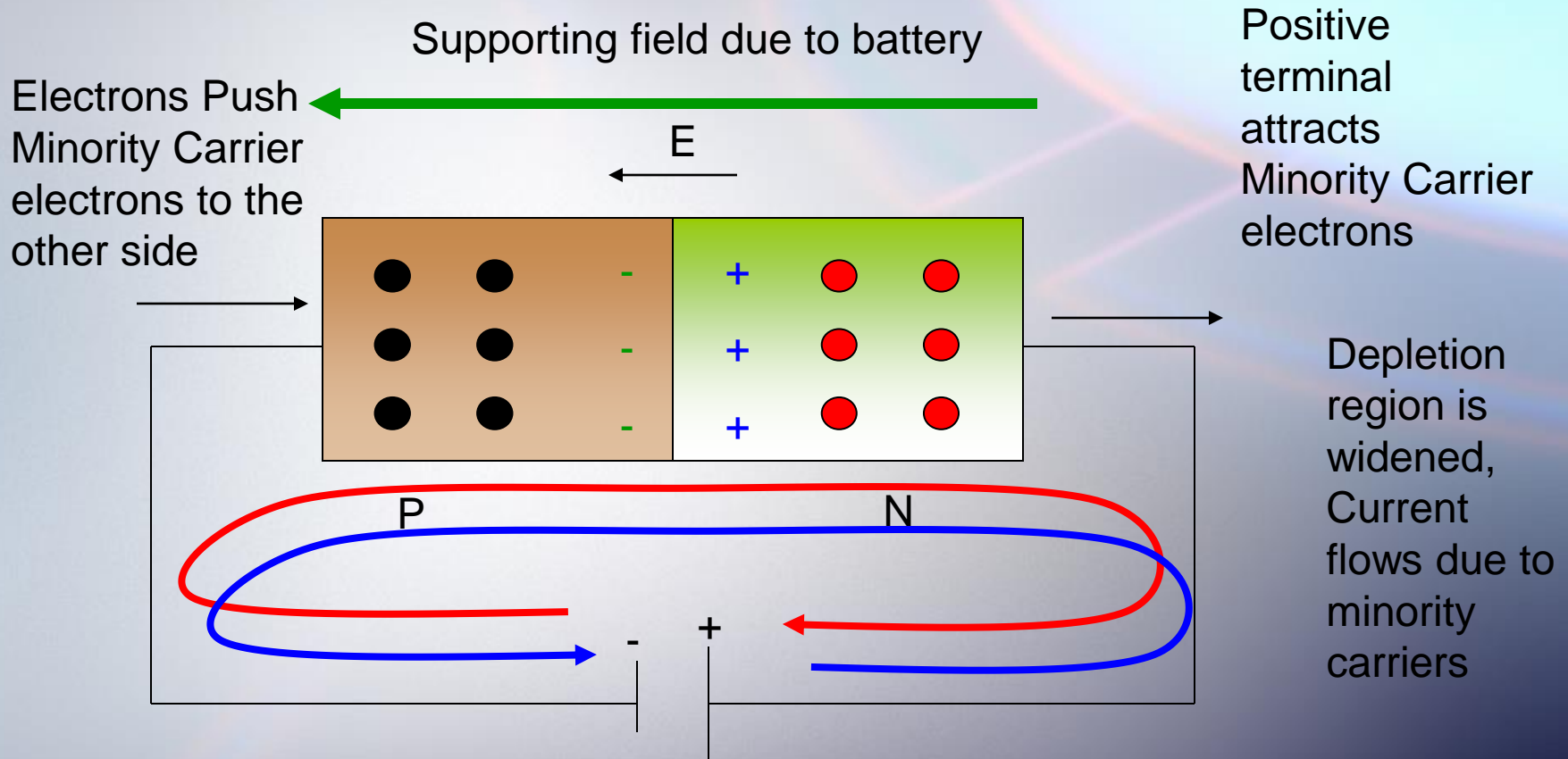

# BJT Biasing

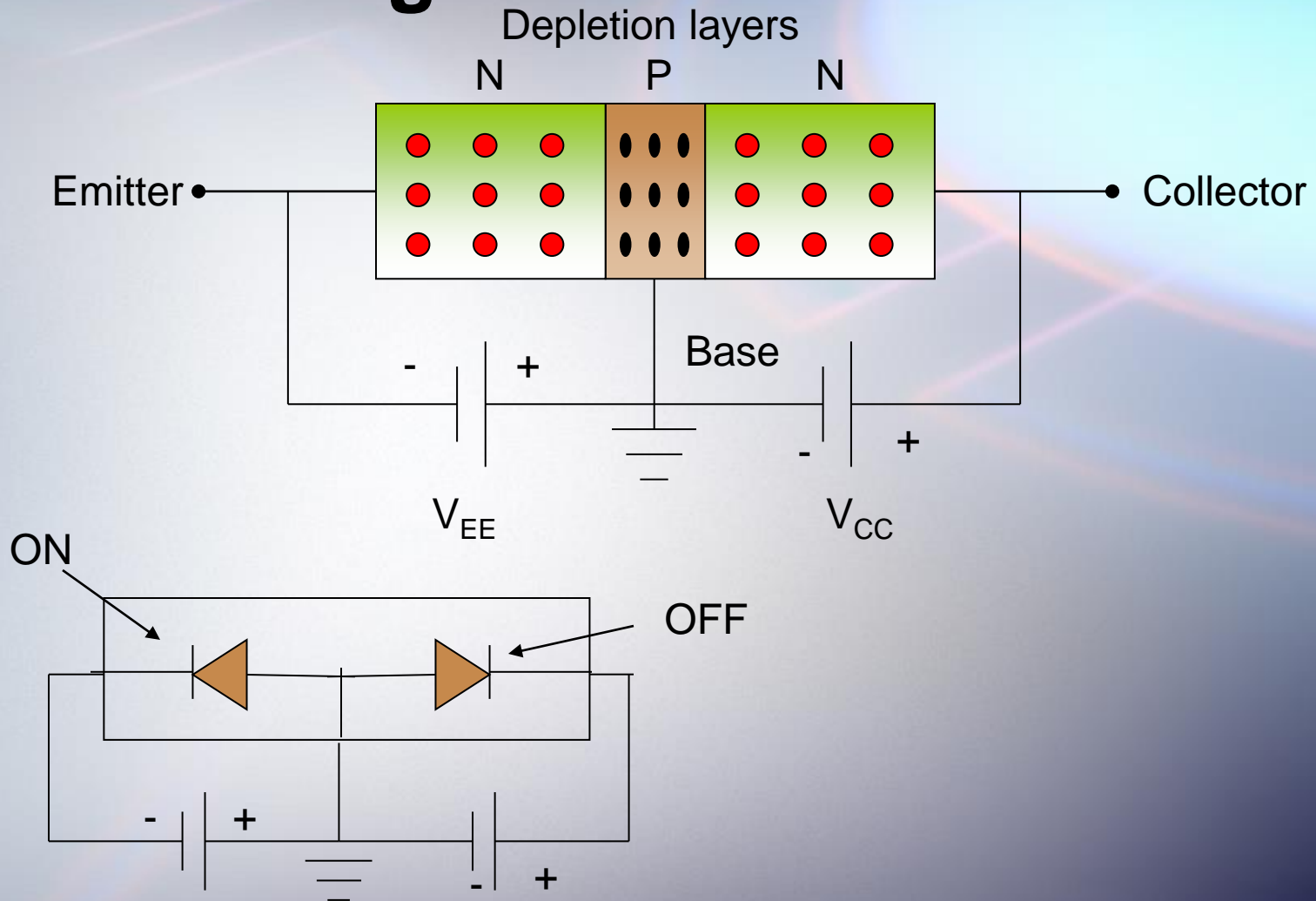

# BJT


- Base is very thin & lightly doped, very few of the electrons injected into the base from the emitter recombines with holes, they diffuse to the reverse-biased base-collector junction.
- Electrons injected into the base become minority carriers in that P-type region.
- Depletion region widens at BC junction. Only current flow due to minority carriers. i.e due to electrons
- Electron flow constitute the dominant current type in an NPN transistor, for PNP hole is the dominant type.
- Most of the electrons injected into the base cross into the collector, a few of them do combine with holes in the base.
- Each electron that combines with the hole, an electron leaves the base region via the base terminal known as base current, about 2% or less of the electron current from emitter to collector.
- Universal rule for biasing transistors for normal operation (ACTIVE MODE); The base emitter junction must be forward biased & the

# BJT


- For both NPN & PNP

$$I_E = I_C + I_B$$


# BJT Currents

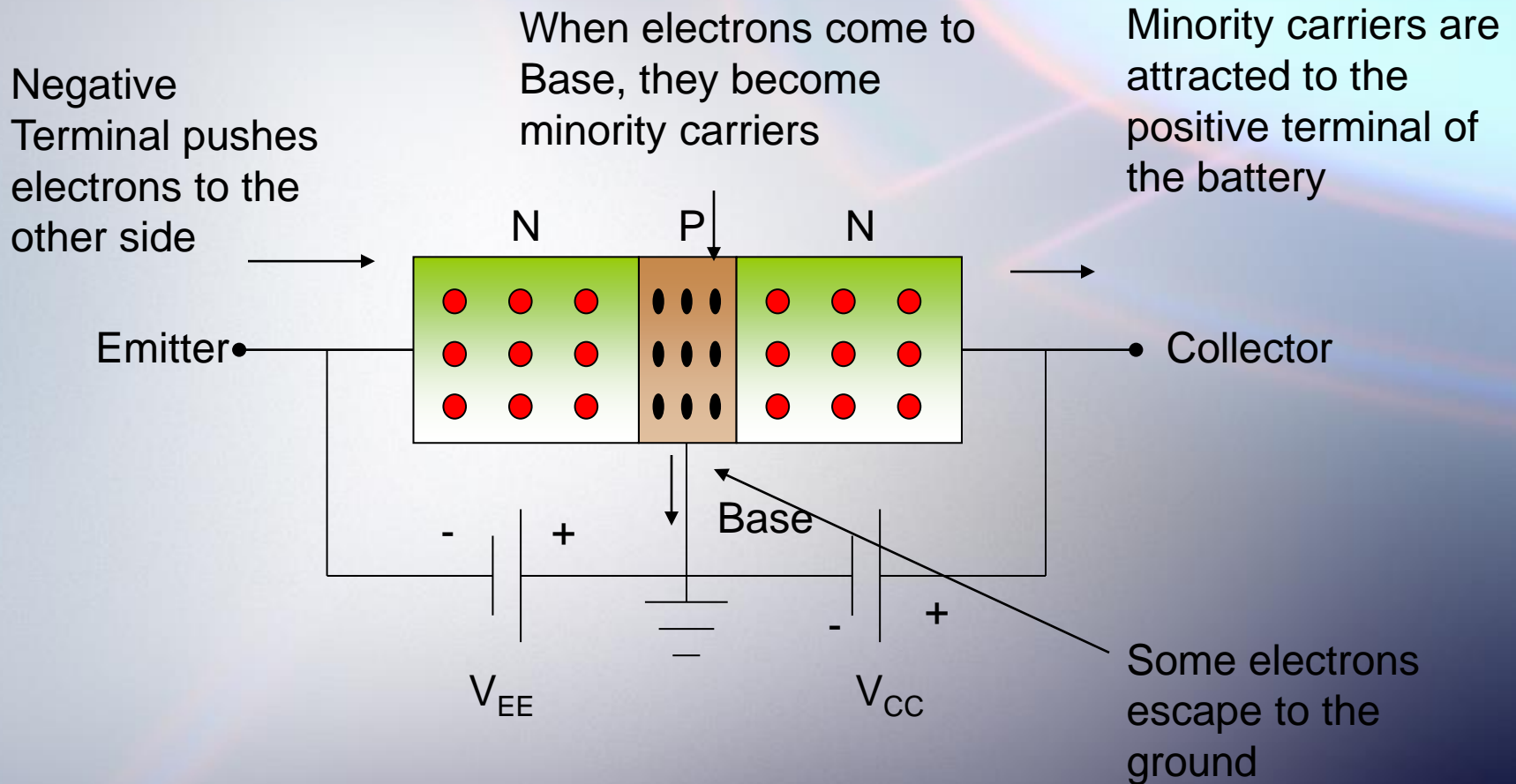

# BJT Currents

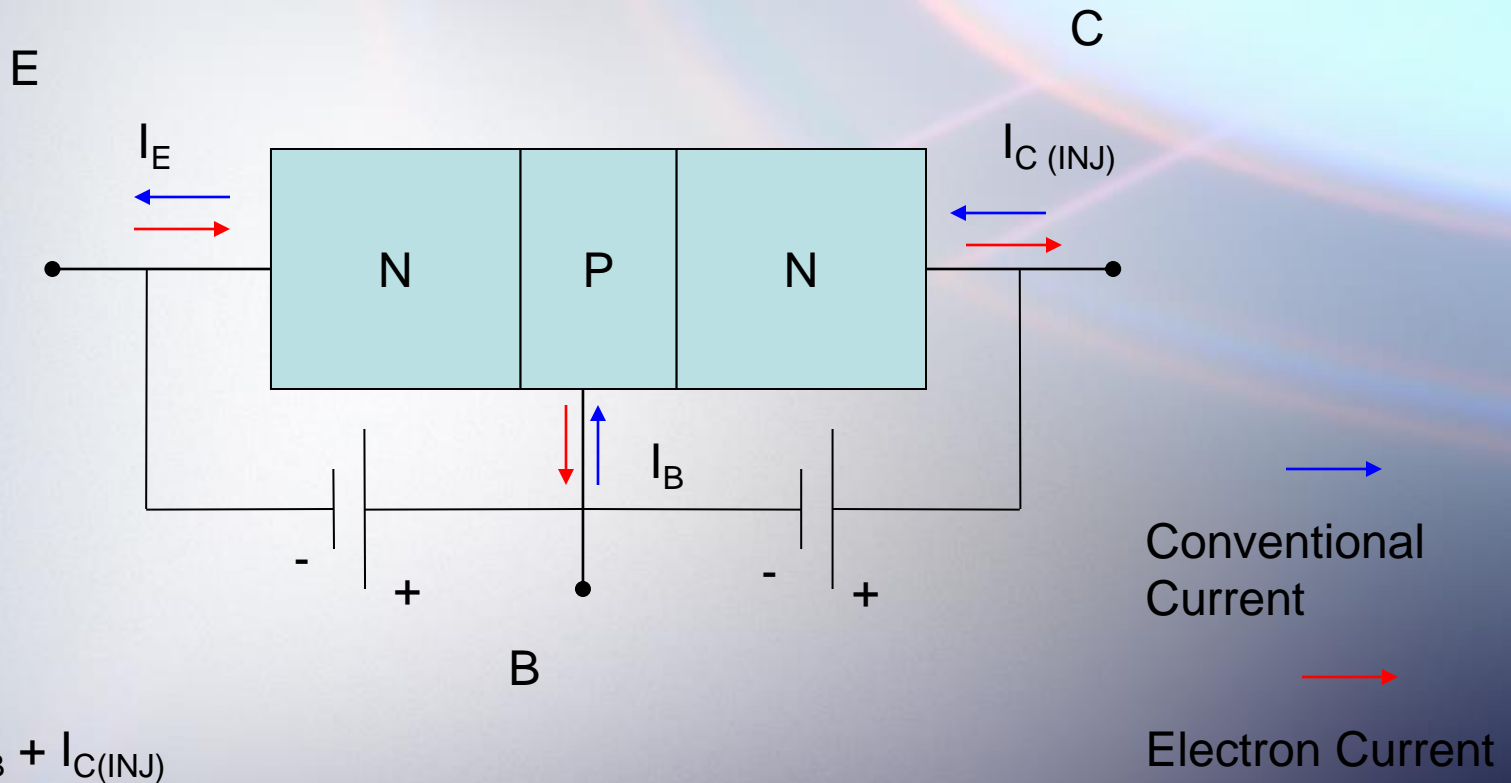

# Collector-Base Reverse Current

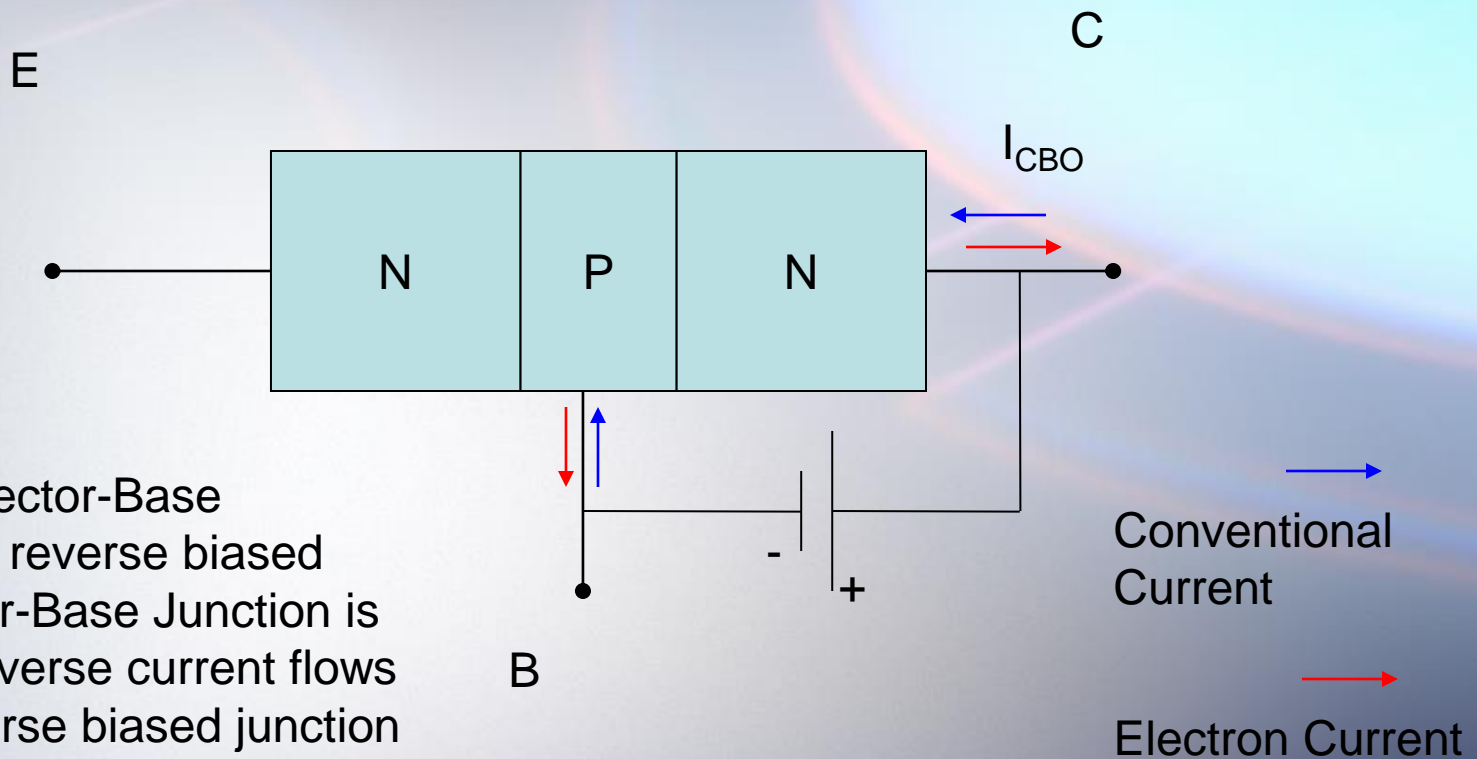

When Collector-Base Junction is reverse biased and Emitter-Base Junction is Open, a reverse current flows in this reverse biased junction which is called  $I_{CBO}$

$$\text{Total Collector current is } = I_C = I_{C(INJ)} + I_{CBO}$$



# $I_{CBO}$ Reverse Current

- Collector current is the sum of two components, the injected minority carriers & the thermally generated minority carriers.
- If the base & emitter are left open & the Collector-Base junction is reverse bias, the only current that flow must be “reverse” component due to thermally generated carriers. This current is called  $I_{cbo}$  (The collector to base current with the emitter open)

$$I_C = I_{C(INJ)} + I_{CBO}$$

- Transistor parameter, Alpha, is defined as “The ratio of the collector current resulting from carrier injection to the total emitter current”

$$\alpha = I_{C(INJ)} / I_E$$

- Alpha measures the portion of the emitter current that survives after passage through base.
- Alpha is always less than “1”

# $I_{CBO}$ Reverse Current

- The greater the value of Alpha, the better the transistor.
- Typical transistor have values of Alpha range from 0.95 to 0.995

$$I_C = \alpha I_E + I_{CBO}$$

- $I_{CBO}$  in modern transistors is so small that it can be neglected.  $I_{CBO}$  is exactly the same as the reverse diode current ( $I_s$ )
- $I_{CBO}$  is negligible small in most practical situations, we can set it equal to 0.

$$I_C = \alpha I_E$$

$$\alpha = I_C / I_E$$

# $\alpha$ of BJT

$$\alpha = I_{C(INJ)} / I_E$$

$$I_C = I_{C(INJ)} + I_{CBO} \quad I_{CBO} \ll I_{C(INJ)}$$

$$I_C = I_{C(INJ)}$$

$$\alpha = I_C / I_E$$



Any Questions?

