

Ch#11:-

AC Power Analysis

(P# 450)

11.1: Introduction:-

- i) Yet now, we have calculated voltage & current.
- ii) in this chapter, our major concern is Power.
- iii) Power is most important quantity in:-
 - a) Utilities (Electricity)
 - b) Electronic & Communication.
 - c) Home Appliance.
 - Pressing iron,
 - Bulbs,
 - Fans,
 - Motors,
 - Charger, TV etc.

①
 → We prefer AC over DC bcz generation and transmission of AC is easy and we can step-up/down it (AC-power).

$$P = VI = \frac{V^2}{R} = I^2 R$$

11.2 Instantaneous Power:-

Instantaneous power (in watts) is power at any instant of time.

$$p(t) = v(t) \cdot i(t) \quad \text{--- ①}$$

→ Power we get normally is average power that is 220V, actually it is 310V.

→ Product of voltage & current at an instant is instantaneous power.

$$\begin{aligned} v(t) &= V_m \cos(\omega t + \theta_v) \\ i(t) &= I_m \cos(\omega t + \theta_i) \end{aligned} \quad \text{--- put in ①}$$

$$\text{②} \quad p(t) = (V_m \cos(\omega t + \theta_v)) (I_m \cos(\omega t + \theta_i))$$

$$p(t) = V_m I_m \cdot \cos(\omega t + \theta_v) \cdot \cos(\omega t + \theta_i)$$

$$2CC = C+C \rightarrow CC = \frac{1}{2}(C+C)$$

So,

$$\cos A \cos B = \frac{1}{2} [\cos(A-B) + \cos(A+B)]$$

So, $p(t)$ will be:

$$p(t) = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i)$$

$$\text{or } p(t) = V_m I_m \cdot \frac{1}{2} [\cos(\omega t + \theta_v + \omega t + \theta_i) + \cos(\omega t + \theta_v - \omega t - \theta_i)]$$

$$p(t) = V_m I_m \cdot \frac{1}{2} [\cos(2\omega t + \theta_v + \theta_i) + \cos(\theta_v - \theta_i)]$$

or $f = \frac{1}{T}$

$$p(t) = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i)$$

$$T = \frac{2\pi}{\omega}$$

pg# 11

→ ch# 1 ref

time independent

time-dependent

→ As instantaneous power is changing at every instant, we can't measure easily. Hence, we measure average power.

↳ average power (in watts) is average of instantaneous power over one period. Thus, average power is-

put p(t) value $P = \frac{1}{T} \int_0^T p(t) dt$

$$P = \frac{1}{T} \int_0^T \left[\frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i) \right] dt$$

or separate :-

$$P = \frac{1}{T} \int_0^T \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) dt + \frac{1}{T} \int_0^T \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i) dt$$

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \cdot \frac{1}{T} \int_0^T 1 dt + \frac{1}{2} V_m I_m \cdot \frac{1}{T} \int_0^T \cos(2\omega t + \theta_v + \theta_i) dt$$

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + 0$$

sin over a complete cycle 2π is zero.
 $\int_0^{2\pi} \sin u du$
 $(\sin 2\pi - \sin 0)$
 $0 - 0 = 0$

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

or
 Phasor →


$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

→ ① $\theta_v = \theta_i$ ⇒ $P = \frac{1}{2} V_m I_m \cos(0^\circ) \Rightarrow P = \frac{1}{2} V_m I_m$ (resistive load) → in-phase.

→ ② $\pm 90^\circ$ ⇒ $P = \frac{1}{2} V_m I_m \cos(90^\circ) \Rightarrow P = 0$ → no power absorbed.

→ A resistive load (R) absorbs power all the time, while reactive load (L or C) absorbs zero power.

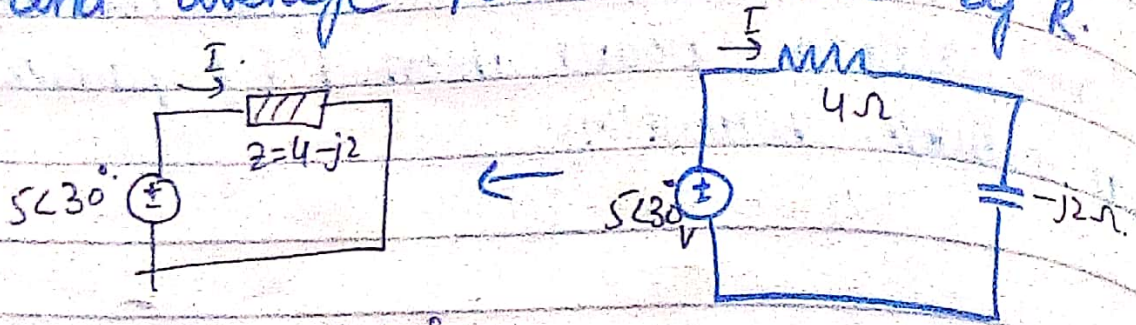Ex #11.3 :- Find avg. power supplied by source and average power absorbed by R.



$$\rightarrow I = \frac{V}{Z} = \frac{5\angle 30^\circ}{4-j2}$$

$$I = 1.11\angle 56.5^\circ \text{ A}$$

avg. power supplied by voltage source.

$$\rightarrow P = \frac{1}{2}(5)(1.11)(\angle 30 - 56.5^\circ)$$

$$\rightarrow V_R = \frac{4}{4-j2} (5\angle 30^\circ)$$

$$P = 2.77\angle -26.5^\circ \text{ W}$$

avg. power absorbed by R

$$V_R = 4.47\angle 56.56^\circ \text{ V}$$

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

$$= \frac{1}{2} (4.47)(1.11) \cos(56.56^\circ - 56.56^\circ)$$

$$P = \frac{1}{2} (4.47)(1.11) \cos(0^\circ)$$

$$P = 2.48 \text{ W}$$

Ex #11.4 :- Determine avg. power generated by each source & avg. power absorbed by each passive element in ckt.

mesh #1 :-

$$I_1 = 4 \text{ A}$$

mesh #2 :-


$$j10(I_2 - I_1) - j5I_2 + 60\angle 30^\circ \text{ V} = 0$$

$$\therefore I_1 = 4$$

$$(j10 - j5)I_2 + j10(4) + 60\angle 30^\circ = 0$$

$$j5I_2 = -60\angle 30^\circ + j40$$
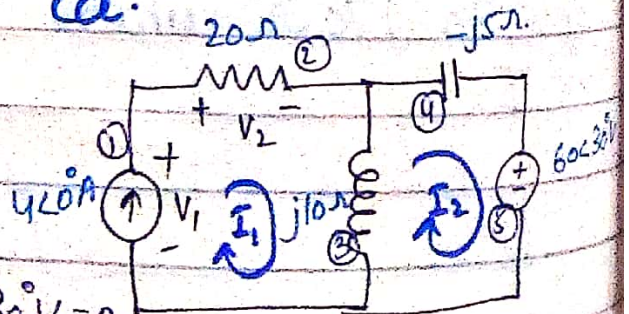
$$I_2 = -12\angle -6^\circ + 8 = 10.58\angle 79.1^\circ \text{ A}$$



for voltage source

$$P_s = \frac{1}{2} V_m I_m \angle \theta_v - \theta_i$$

$$P_s = \frac{1}{2} (60)(10.58) \angle 30 - 79.10^\circ$$

$$P_s = 283 \angle 33.9^\circ \text{ W} \rightarrow \text{const.}$$

Absorbed by the source

for current source

$$I_1 = 4 \angle 0^\circ \text{ A}$$

$$V_1 = 20I_1 + j10(I_1 - I_2) = 20(4) + j10(4) - j10I_2$$

$$V_1 = 80 + j40 - j10(2 + j10 \cdot 31)$$

$$V_1 = 184.2 + j20 = 184.2 \angle 6.23^\circ \text{ V}$$

$$\rightarrow P = -\frac{1}{2} (184.2)(4) \angle 6.21^\circ - 0^\circ$$

$$P_1 = -367.2 + j39.8 \text{ W}$$

$$\text{or } P_1 = \ominus 367.2 \angle 6.21^\circ \text{ W}$$

passive sign convention \rightarrow I-source supplies power to ca.

for resistor

$$I_1 = 4 \angle 0^\circ \text{ A}, \quad V = 20I_1 = 20(4) = 80 \angle 0^\circ$$

$$\text{So, } P_2 = \frac{1}{2} (80)(4) \angle 0 - 0^\circ$$

$$P_2 = 160 \text{ W}$$

for capacitor

$$I_2 = 10.58 \angle 79.10^\circ \text{ A}, \quad V = (-j5)I_2 = (-j5)(10.58 \angle 79.10^\circ)$$

$$V = 52.9 \angle -10.9^\circ \text{ V}$$

$$\text{So, } P_4 = \frac{1}{2} (52.9)(10.58) \angle -10.9^\circ - 79.10^\circ$$

$$P_4 = \frac{1}{2} (52.9)(10.58) \angle -90^\circ$$

$$P_4 = 0$$

for inductor

$$I_1 - I_2 = (4) - (2 + 10.31j) = 2 - 10.31j \text{ A} = 10.51 \angle -79.1^\circ$$

$$V = j10(I_1 - I_2) = 10.51 \angle -79.1^\circ \times 10 \angle 90^\circ = 105.02 \angle 10.9^\circ \text{ V}$$



$$\text{So, } P_3 = \frac{1}{2} (10.51)(105.02) \angle -79.1 - 10.9$$

$$P_3 = 0$$

\rightarrow L & C absorbs zero avg. power & power supplied by I-source is equal to power absorbed by V & R

11.3 Maximum Average Power Transfer:-

Transfer:-

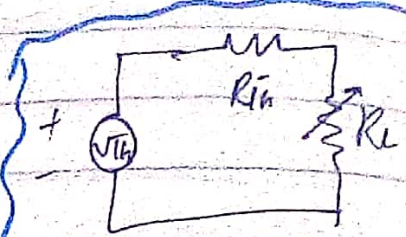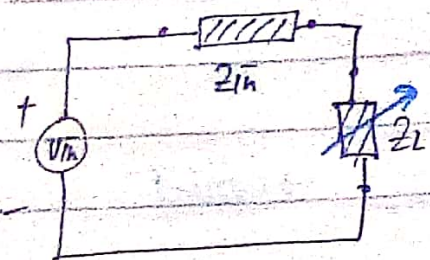

$$Z_{th} = R_{th} + jX_{th} \quad \text{--- (1)}$$

$$Z_L = R_L + jX_L \quad \text{--- (2)}$$

To prove :-

$$Z_{th} = Z_L$$

$$I = \frac{V}{R} = \frac{V_{th}}{Z_{th} + Z_L} \quad \text{--- (3)}$$

putting values from (1) & (2) in (3).

so,

$$I = \frac{V_{th}}{(R_{th} + jX_{th}) + (R_L + jX_L)}$$

Real = $\frac{V_{th}}{R_{th} + R_L}$

Imaginary = $\frac{jX_{th} + jX_L}{R_{th} + R_L}$

Hence;

$$P = \frac{1}{2} I^2 R_L \quad \rightarrow \text{power across load.}$$

put value of I in above eqn.

$$P = \frac{1}{2} \left[\frac{V_{th}}{(R_{th} + jX_{th}) + (R_L + jX_L)} \right]^2 R_L$$

$$\text{or } P = \frac{V_{th}^2 \cdot R_L / 2}{(R_{th} + R_L)^2 + (X_{th} + X_L)^2} \quad \text{--- (4) / 11.15}$$

i) $\frac{\partial P}{\partial R_L}$

ii) $\frac{\partial P}{\partial X_L}$

} \rightarrow partial derivatives.

at: $R_{th} = R_L$

$$I = \frac{V_{th}}{R_{th} + R_L}$$

$$P = I^2 R_L$$

$$P = \frac{V_{th}^2}{(2R_{th})^2} \times R_{th}$$

$$P = \frac{V_{th}^2}{4R_{th}} \rightarrow \text{DC}$$

$$P = \frac{1}{2} \frac{V_{th}^2}{4R_{th}} \rightarrow \text{AC}$$

$$\therefore P = \frac{1}{2} V_m I_m$$

as: $\rightarrow \therefore P = \frac{1}{2} I_m^2 R_o$

$$\therefore P = \frac{1}{2} \frac{V_m}{R_o}$$

take $\frac{dP}{dR_L}$ of eqn. (4) :- (partial derivative w.r.t

$$\frac{dP}{dR_L} = (R_{in} + R_L) + (X_{in} + X_L)^2 \cdot \frac{d}{dR_L} \left(\frac{V_{in}^2 \cdot R_L}{2} \right) - \left(\frac{V_{in}^2 \cdot R_L}{2} \right) \frac{d}{dR_L} \left((R_{in} + R_L) + (X_{in} + X_L)^2 \right)$$

$\frac{dP}{dR_L} =$ Put $\frac{dP}{dR_L} = 0$:-

$$0 = (R_{in} + R_L) + (X_{in} + X_L)^2 \cdot \frac{d}{dR_L} \left(\frac{V_{in}^2 \cdot R_L}{2} \right) - \left(\frac{V_{in}^2 \cdot R_L}{2} \right) \frac{d}{dR_L} \left((R_{in} + R_L) + (X_{in} + X_L)^2 \right)$$

cross-multiply.

So,

$$= (R_{in} + R_L) + (X_{in} + X_L)^2 \cdot \frac{d}{dR_L} \left(\frac{V_{in}^2 \cdot R_L}{2} \right) - \left(\frac{V_{in}^2 \cdot R_L}{2} \right) \frac{d}{dR_L} \left[(R_{in} + R_L) + (X_{in} + X_L)^2 \right]$$

const. w.r.t R_L

$$0 = \frac{V_{in}^2}{2} \cdot (R_{in} + R_L) + (X_{in} + X_L)^2 - \frac{V_{in}^2 \cdot R_L}{2} \left[2(R_{in} + R_L) \frac{d}{dR_L} (R_{in} + R_L) + 0 \right]$$

taking $\frac{V_{in}^2}{2}$ common :-

$$0 = (R_{in} + R_L) + (X_{in} + X_L)^2 - R_L \cdot 2(R_{in} + R_L)$$

$$R_{in}^2 + R_L^2 + 2R_{in} \cdot R_L + (X_{in} + X_L)^2 - 2R_{in} R_L - 2R_L^2 = 0$$

$$R_{in}^2 - R_L^2 + (X_{in} + X_L)^2 = 0$$

$$R_L^2 = R_{in}^2 + (X_{in} + X_L)^2$$

OR

$$R_L = \sqrt{R_{in}^2 + (X_{in} + X_L)^2} \quad \text{--- 11.18 / (5)}$$

Let $X_{in} = -X_L$
 So, $R_L = \sqrt{R_{in}^2 + 0}$
 $R_L = R_{in}$

from 11.18 - 11.5 :-

$$(11.5) \rightarrow P = \frac{V_{th}^2 \cdot R_L / 2}{(R_{th} + R_L)^2 + (X_{th} + X_L)^2}$$

Now partial derivative w.r.t $\delta P / \delta X_L$:-

$$\frac{\delta P}{\delta X_L} = \frac{V_{th}^2 \cdot R_L / 2}{(R_{th} + R_L)^2 + (X_{th} + X_L)^2}$$

$$= (R_{th} + R_L)^2 + (X_{th} + X_L)^2 \frac{\delta (V_{th}^2 \cdot R_L / 2)}{\delta X_L} - (V_{th}^2 \cdot R_L / 2) \frac{\delta [(R_{th} + R_L)^2 + (X_{th} + X_L)^2]}{\delta X_L}$$

$$\text{put } \frac{\delta P}{\delta X_L} = 0 \quad \left[(R_{th} + R_L)^2 + (X_{th} + X_L)^2 \right]^2$$

$$0 = 0 - \frac{V_{th}^2 \cdot R_L / 2 \cdot \delta [(R_{th} + R_L)^2 + (X_{th} + X_L)^2]}{\left[(R_{th} + R_L)^2 + (X_{th} + X_L)^2 \right]^2}$$

cross multiply $\left[(R_{th} + R_L)^2 + (X_{th} + X_L)^2 \right]^2$

$$0 = - \frac{V_{th}^2 \cdot R_L}{2} \left[\frac{\delta (R_{th} + R_L)^2}{\delta X_L} + \frac{\delta (X_{th} + X_L)^2}{\delta X_L} \right]$$

$$0 = \frac{1}{2} \cdot 2 (X_{th} + X_L) (1)$$

$$0 = X_{th} + X_L \rightarrow \text{condition}$$

$$\rightarrow X_{th} = -X_L$$

$$Z_L = R_L + jX_L \quad ; \quad Z_{th} = R_{th} - jX_{th}$$

So, $Z_{th} = Z_L^*$ (conjugate)

put $R_L = R_{th}$ & $X_{th} = -X_L$ in eq. (11.5).

$$P = \frac{V_{th}^2 \cdot R_{th} / 2}{(2R_{th})^2 + (0)}$$

$$P = \frac{1}{2} \cdot \frac{V_{in}^2 \cdot R_{in}}{4 R_{in}^2}$$

$$P = \frac{V_{in}^2}{8 R_{in}} \rightarrow \text{max. average power transfer}$$

EX# 11.5, 11.6 \rightarrow solve.

Section
11.4

$$\cos^2 \theta = \frac{1 + \cos 2\theta}{2}$$

Wednesday
11-03-2020

$$\cos^2 \theta - \sin^2 \theta = \cos 2\theta$$

$$\cos^2 \theta - (1 - \cos^2 \theta) = \cos 2\theta$$

$$2 \cos^2 \theta - 1 = \cos 2\theta$$

$$2 \cos^2 \theta = 1 + \cos 2\theta$$

$$\cos^2 \theta = \frac{1 + \cos 2\theta}{2} ; \sin^2 \theta = \frac{1 - \cos 2\theta}{2}$$

PG# 468, section 11.4 \rightarrow from book.

$$\rightarrow \text{Avg. Power} = P = \frac{1}{2} V_{max} \cdot I_{max} \cdot \cos(\theta_v - \theta_i)$$

$$\text{or } P = \frac{1}{\sqrt{2}} \cdot \frac{1}{\sqrt{2}} \cdot V_{max} \cdot I_{max} \cdot \cos(\theta_v - \theta_i)$$

$$\text{or } P = \frac{V_{max}}{\sqrt{2}} \cdot \frac{I_{max}}{\sqrt{2}} \cdot \cos(\theta_v - \theta_i) \quad \because S = V_{rms} \cdot I_{rms} \quad \left(\frac{VA}{\text{unit}} \right)$$

$$P = V_{rms} \cdot I_{rms} \cdot \cos(\theta_v - \theta_i) \quad \because V_{rms} = \frac{V_{max}}{\sqrt{2}}$$

$$P = S \cos(\theta_v - \theta_i)$$



$$I_{rms} = \frac{I_{max}}{\sqrt{2}}$$

$$\frac{P}{S} = \cos(\theta_v - \theta_i)$$

if $\theta_v - \theta_i = 0 \Rightarrow \theta_v = \theta_i$

So, Power-factor = P.F = $\frac{P}{S} = \cos(0) = 1$ (unity).

Section: 11.5

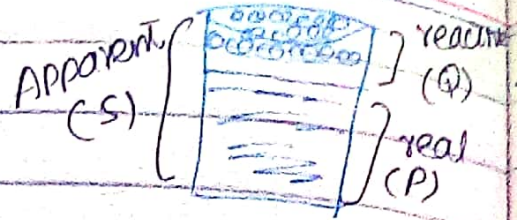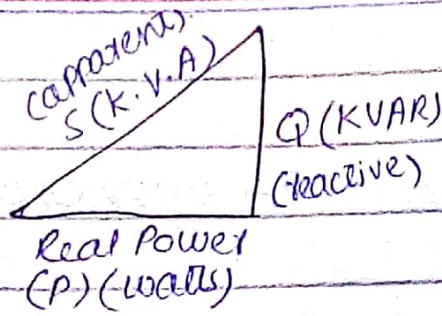

Power-factor:-

"P.F is cosine of phase difference voltage."

or "Ratio of Real Power / To Apparent Power".
true / active.

S = VI (Proof) :-

$$S^2 = P^2 + Q^2$$

or $S = \sqrt{P^2 + Q^2}$


$$S = \sqrt{(VI \cos \theta)^2 + (VI \sin \theta)^2}$$

$$S = \sqrt{V^2 I^2 \cos^2 \theta + V^2 I^2 \sin^2 \theta}$$

$$S = \sqrt{V^2 I^2 (\cos^2 \theta + \sin^2 \theta)}$$

$$S = \sqrt{V^2 I^2 (1)}$$

$S = VI$

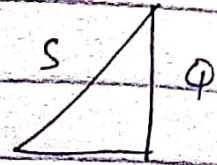

$P = S \cos \theta$
 or $P = VI \cos \theta$ ← $\cos \theta = \frac{P}{S}$
 $\sin \theta = \frac{Q}{S}$
 $Q = S \cdot \sin \theta$ ← $S = VI$
 $Q = VI \sin \theta$

- That is used to do work → ^{P (Watt)} Active / True / real power.
- That is sum of active & reactive power, ^S (KVA) apparent

→ Power which flows back & forth (move in both directions in ckt.) → reactive power. (KVAR)


• $\phi = 0 \rightarrow P.F = 1$ (ideal) → resistive ckt.

• $\phi > 0 \rightarrow P.F$ lags → needs condenser / capacitor / capacitor bank

• $\phi < 0 \rightarrow P.F$ leads → needs capacitor } To improve power factor.

→ Power factor is
unit-less
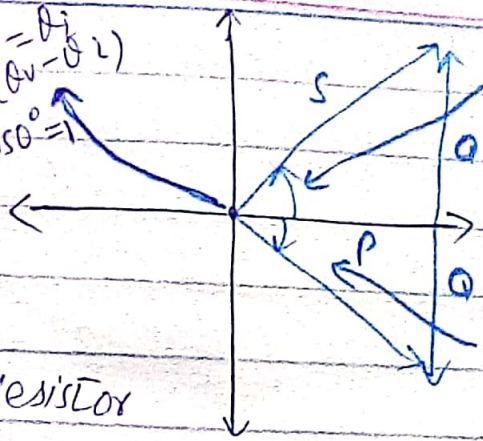
$$\begin{aligned} \cos \phi &= \cos(\theta_v - \theta_i) \\ &= \cos 0^\circ = 1 \end{aligned}$$




$$\begin{aligned} \cos(\theta_v - \theta_i) \\ \phi = \theta_v - \theta_i \\ \phi > 0 \end{aligned}$$

$$\begin{aligned} \cos(\theta_v - \theta_i) \\ \phi = \theta_v - \theta_i \\ \phi < 0 \\ \text{capacitive.} \end{aligned}$$

Sec# 11.4 from start:-

Power absorbed by resistor
in ac ckt. is:-
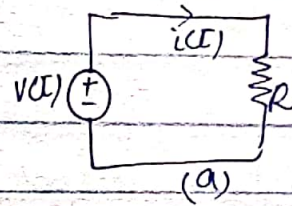
$$P = \frac{1}{T} \int_0^T i^2 R dt = \frac{R}{T} \int_0^T i^2 dt \quad \text{--- (1)}$$




Power absorbed by R in dc ckt.:-

$$P = I_{\text{eff}}^2 \cdot R \quad \text{--- (2)}$$

put (1) in (2) for I_{eff} :-
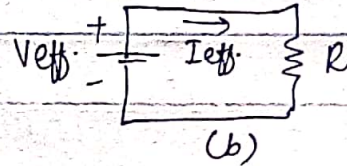
$$I_{\text{eff}}^2 = \frac{R}{T} \int_0^T i^2 dt$$



$$I_{\text{eff}} = \sqrt{\frac{1}{T} \int_0^T i^2 dt} \quad \text{--- (3)}$$

$$\therefore I_{\text{rms}} = I_{\text{eff}}$$

$\therefore v_{\text{eff}}$ is also as:-

$$V_{\text{rms}} = v_{\text{eff}}$$

$$v_{\text{eff}} = \sqrt{\frac{1}{T} \int_0^T v^2 dt} \quad \text{--- (4)}$$

for any periodic function $x(t)$; rms value is:-

$$x_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T x^2 dt} \quad \text{--- (5)}$$

$\therefore i(t) = I_m \cos \omega t \rightarrow$ put in (3).

$$I_{\text{eff}} = I_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T I_m^2 \cos^2 \omega t dt}$$

$$= \frac{I_m^2}{T} \int_0^T$$

$$= \frac{I_m}{\sqrt{2}}$$

$$\therefore \frac{V}{\text{rms}} = \frac{V_m}{\sqrt{2}}$$

Thursday
12-03-2020

III-8] Power factor Correction:-

"The process of increasing the power factor without changing voltage & current is power factor correction."

Three methods:-

- 1 → capacitors bank installed parallel. → here, we deal.
 voltage same &
 to load.
- 2 → Phase advance
- 3 → synchronous condenser.

* Core losses depends upon supply voltage &
* Copper losses depends upon current (load)

1 → Using capacitor bank:-

$$\rightarrow \cos \theta_1 = \frac{P}{S} \Rightarrow \theta_1 = \cos^{-1}\left(\frac{P}{S}\right)$$

$$P_1 = S_1 \cos \theta_1 \text{ (inductive)}$$

new after adding capacitor bank.

$$P_2 = S_2 \cos \theta_2 \text{ (capacitive)}$$

$$\rightarrow \sin \theta_1 = \frac{Q}{S}$$

$$\rightarrow \tan \theta = \frac{Q}{P}$$


$$Q_1 = S_1 \sin \theta_1$$

$$Q_1 = P \tan \theta_1$$

$$\text{new } Q_2 = S_2 \sin \theta_2$$

$$\text{new } Q_2 = P \tan \theta_2$$

$$Q_c = Q_1 - Q_2$$

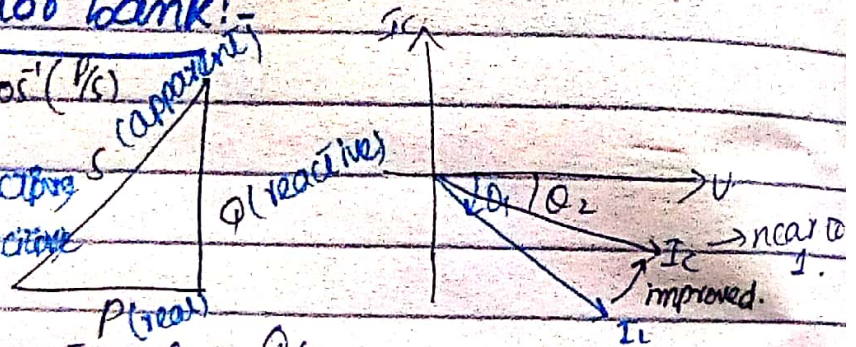

Q. If we have to increase PF; what value of capacitor must be used?

$$\rightarrow Q_c = Q_1 - Q_2$$

$$Q_c = P (\tan \theta_1 - \tan \theta_2)$$

losses $\Rightarrow P = I^2 R$

$$Q = I_{rms}^2 \cdot Z_c$$

$$\text{if } Q_c = I_{rms}^2 \cdot Z_c \text{ (losses)}$$

$$\therefore I_{rms}^2 = \frac{V_{rms}^2}{Z_c}$$

$$Q_c = \frac{V_{rms}^2}{Z_c}$$

Qc

$$\therefore Z_c = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$

$$\text{of } Q_c = \frac{V_{rms}^2}{\left(\frac{1}{\omega C}\right)} = V_{rms}^2 \cdot \omega C$$

$$C = \frac{Q_c}{V_{rms}^2 \cdot \omega}$$

$$\rightarrow Q_c = (\tan \theta_1 - \tan \theta_2) P$$

$$\text{net } Q_c = V_{rms}^2 \cdot \omega C :-$$

$$V_{rms}^2 \cdot \omega \cdot C = P [\tan \theta_1 - \tan \theta_2]$$

$$\theta_1 = \cos^{-1} \left(\frac{P_1}{S} \right) \leftarrow$$

$$C = \frac{P [\tan \theta_1 - \tan \theta_2]}{V_{rms}^2 \cdot \frac{\omega}{2\pi f}}$$

$$\omega = 2\pi f$$

This value of capacitor must be used to increase power factor (P.F).

→ Ch#11. Max. power transfer (Ex#1 PP); Power factor correction (Imp.)

→ why P.F includes cos with it? \rightarrow \sin is 0 at real-axis.

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

$$P_{avg} = \frac{1}{2} V_{rms} I_{rms} \cos(\theta_v - \theta_i) = \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}} \cos(\theta_v - \theta_i) \times$$

$$P = S \cos(\theta_v - \theta_i)$$

$$\frac{P}{S} = \cos(\theta_v - \theta_i)$$

$$\therefore P.F = \frac{P(\text{real})}{S(\text{apparent})}$$

$$P.F = \frac{P}{S} = \cos(\theta_v - \theta_i)$$

at $\theta_v = \theta_i :-$

$$P.F = \cos(0) = 1 \text{ (unity)}$$

$$\therefore P.F = \frac{P}{S}$$

So;

$$P.F = \frac{\frac{1}{2} \cdot V_m \cdot I_m \cos(\theta_v - \theta_i)}{\frac{V_{rms} \cdot I_{rms}}{\sqrt{2} \cdot \sqrt{2}}} = \frac{\frac{1}{2} V_m \cdot I_m \cos(\theta_v - \theta_i)}{\frac{1}{2} V_m I_m}$$

$$P.F = \cos(\theta_v - \theta_i)$$

Ex# 11.15:- When connected to a 120V (rms); 60Hz power line; a load absorbed ^{real} 4kW at a lagging power factor of $\cos \theta_1 = 0.8$. Find value of capacitance necessary to raise P.F to $0.95 \rightarrow \theta_2$

Solution:-

→ If P.F = 0.8 $\Rightarrow \cos \theta_1 = 0.8 \Rightarrow \theta_1 = \cos^{-1}(0.8)$
 $\theta_1 = 36.87^\circ$

$S_1 = \frac{P}{\cos \theta_1} = \frac{4000}{0.8} = 5000 \text{ VA}$

$Q_1 = S_1 \sin \theta_1 = 5000 \sin 36.87^\circ = 3000 \text{ VAR}$

→ $\cos \theta_2 = 0.95 \rightarrow$ capacitive load.

$\theta_2 = \cos^{-1}(0.95) \rightarrow \theta_2 = 18.19^\circ$

$\omega = 2\pi f = 2\pi(60) = 376.99 \approx 377$

So,

$S_2 = \frac{P}{\cos \theta_2} = \frac{4000}{0.95} = 4210.5 \text{ VA}$

$Q_2 = S_2 \sin \theta_2 = (4210.5) \sin 18.19 = 1314.4 \text{ VAR}$

$Q_c = Q_1 - Q_2$

$Q_c = 3000 - 1314.4$

$Q_c = 1685.6 \text{ VAR}$

$Q_c = P(\tan \theta_1 - \tan \theta_2)$
 $V_{rms}^2 \cdot 2\pi f$

$C = \frac{Q_c}{\omega \cdot V_{rms}^2} = \frac{1685.6}{(377)(120)^2}$; $C = 310 \mu\text{F}$

$C = 3.10 \times 10^{-4}$

or $C = 310 \mu\text{F} \rightarrow$ must used.