

Chapter #12: Three-Phase Circuits

112.1] Introduction:-

Single phase two wire system, $\leftarrow V_p \angle \phi$
 where V_p is rms magnitude of source voltage & ϕ is phase.



Poly-Phase:-

"Circuits or systems in which ac-sources operates at same frequency but different phases are known as poly-phase."



or: A three-phase system is produced by generators consisting of 3-sources having same amplitude & frequency but out of phase with each other by 120° .

Importance of 3-phase System:-


1) All electric power is generated & distributed in 3-phase; at operating freq. of 60Hz (or $\omega = 377 \text{ rad/s}$)
 $\omega = 2\pi f \Rightarrow \omega = 2 \times 3.14 \times 60$.

2) The inst. power in 3-phase can be const.

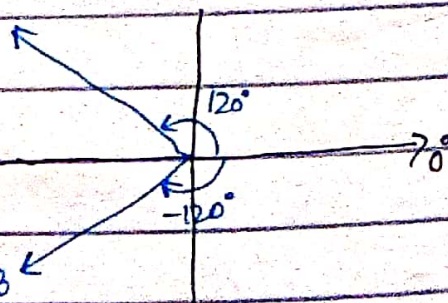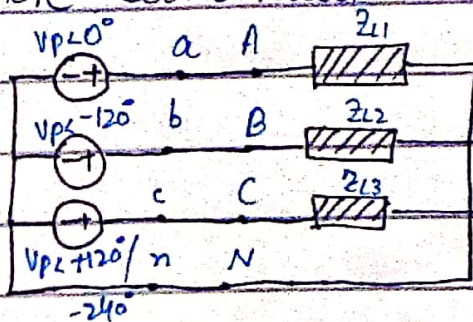
3) For same amount of power, 3-phase system is more economical than single-phase.



Three-phase 4-wire system.

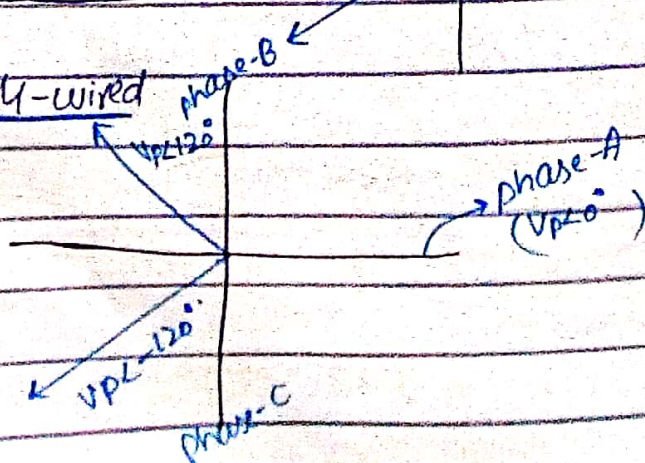

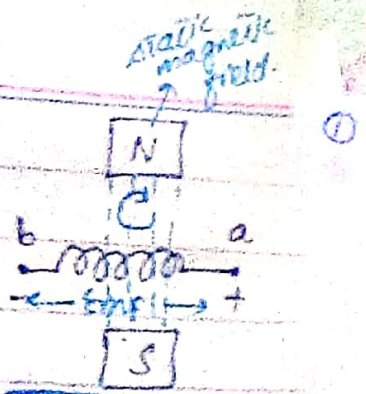→ This emf is alternating in nature - we took static magnetic field & rotating coil/winding.




→ The axis of coil is per to each other - Alternating emf is generated at end of coil.

$$E_{ab} = E_{mf} \sin \omega t$$


b terminals.

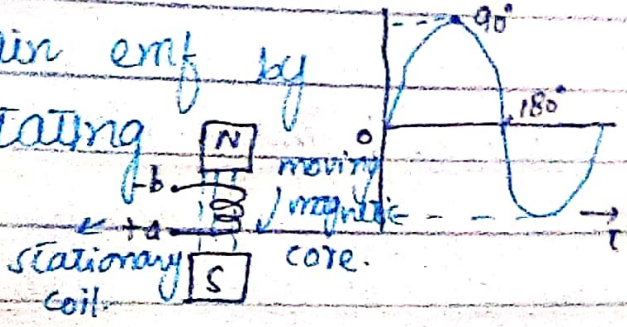→ we can also obtain emf by stationary coil & rotating magnetic field.




→ This is single-phase voltage & we use mostly for domestic/home appliances i.e:- lights, fans, bulbs etc. but single phase has limitations.

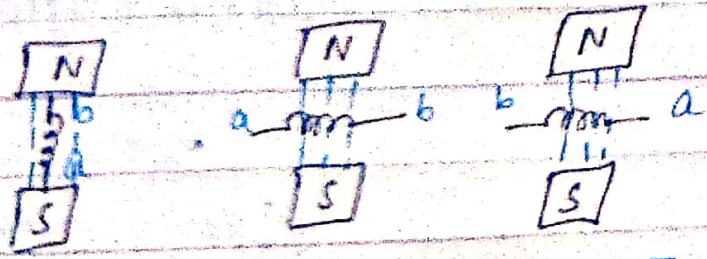1) It can run only small domestic load, but for high-power electric load, we need 3-phase.





3-phase, 4-wire system

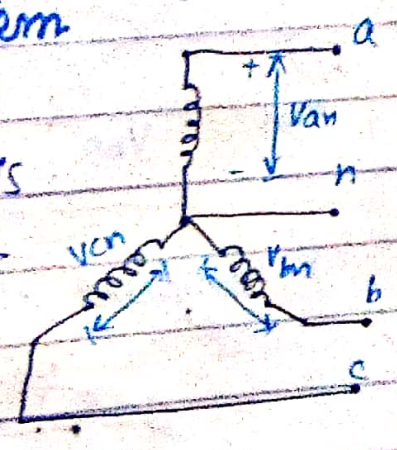→ 3-phase emf can be generated through 3-set of coils - Each coil is displaced at 120° with each other. The 3-coil produces 3-phase emf with phase-diff. of 120° with each other.



→ What does 120° phase difference means?

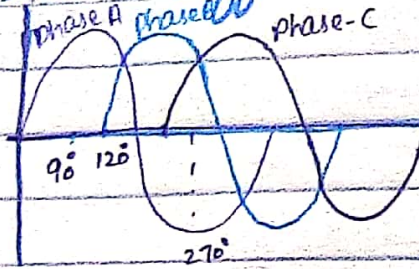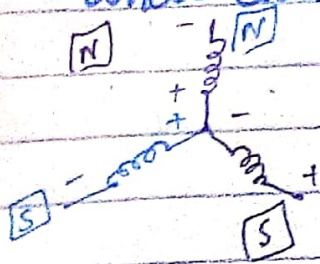

Three-phase single wire → Each sine wave is 120° out of phase.

12.2 Balanced Three-phase Voltages :-


"Balanced 3-phase voltage are equal in magnitude & are out of phase with each other by 120° ."

→ 3-phase voltages are often produced with a 3-phase AC generator (or alternator)


→ Generator consist of rotating magnet (rotor) surrounded by a stationary winding (stator)

→ Three separate windings or coils with terminals a-a', b-b', c-c' are physically placed at 120° apart around stator. (Fig: 12.4 → from book)


Connections -

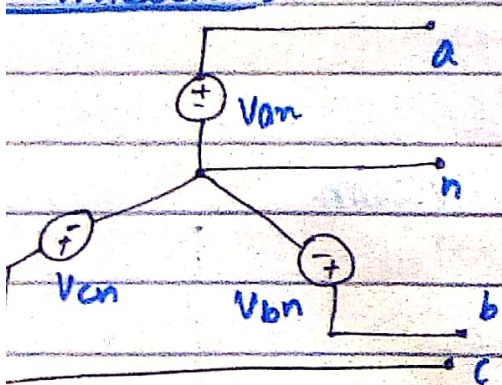


Y-connected sources.

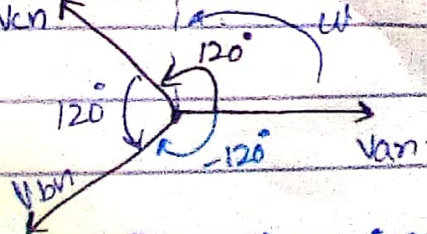

abc / positive phase sequence

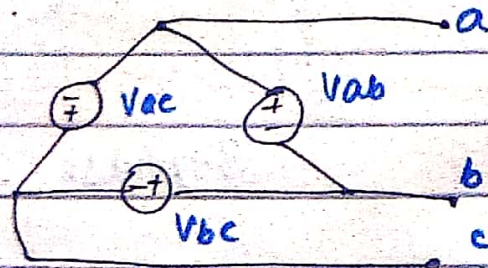

Δ-connected.


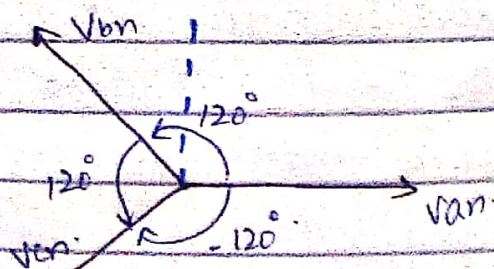


acb / -ve phase sequence

Phase-Sequence:-

Phase sequence mean, that order/arrangement of all 3-phase reaches their max./peak-value. As mentioned in wave-form, the phase-B is lagging 120° by phase of A. Similarly, emf of phase-C is lagging 120° by emf of phase-B.

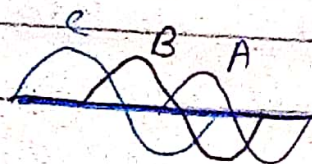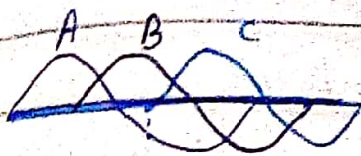→ "order in which phase A, B, C reaches their max. values respectively. This order/arrangement is called phase order/sequence." $A \rightarrow B \rightarrow C$ (ABC)



clock-wise ($A \rightarrow B \rightarrow C$) / ABC

anti-clockwise ($C \rightarrow B \rightarrow A$) / CBA

direction of alternator.

→ if we change direction of alternator, phase-sequence also changes.

→ "Balanced phase voltage are equal in magnitude & out of phase with each other by 120° ." ($V_{an} + V_{bn} + V_{cn} = 0$)

$$V_A = E_A = E_m \sin(\omega t)$$

$$V_B = E_B = E_m \sin(\omega t - 120^\circ)$$

$$V_C = E_C = E_m \sin(\omega t - 240^\circ)$$

→ Phase sequence is order, in which voltage pass through their respective max. values.

→ Since, 3-phase are 120° out of phase, so possible combinations are;

$$V_{an} + V_{bn} + V_{cn} = 0$$

$$|V_{an}| = |V_{bn}| = |V_{cn}|$$

$$V_{an} = V_p \angle 0^\circ; V_{bn} = V_p \angle -120^\circ$$

$$V_{cn} = V_p \angle -240^\circ / V_p \angle +120^\circ$$

→ voltage said to be balanced.

$\therefore V_p = \text{rms. value of phase voltage}$

→ ABC is called +ve-phase sequence. (RYB) → red, yellow, blue.
 → CBA " " -ve-phase sequence. (RBY) → red, blue, yellow.

• $V_{an} + V_{bn} + V_{cn} = 0$

$V_p \angle 0^\circ + V_p \angle -120^\circ + V_p \angle +120^\circ = 0$ (rect. → polar)

$V_p [1 - 0.5 - j0.866 - 0.5 + j0.866] = 0$

$V_p [0] = 0$

$0 = 0$

So, $V_{an} + V_{bn} + V_{cn} = 0$ proved



→ Balanced load:-

"A balanced load is one in which the phase impedances are equal in magnitude & in-phase". for a balanced wye-connected load,

$Z_1 = Z_2 = Z_3 = Z_y$

• Z_y is load impedance per phase for balanced delta-connected load.

$Z_a = Z_b = Z_c = Z_\Delta$

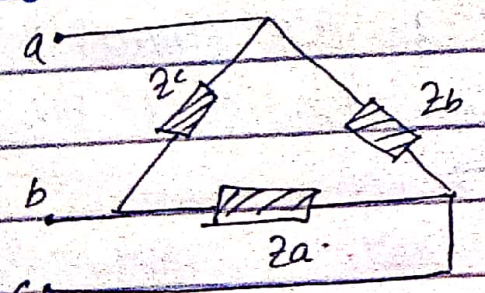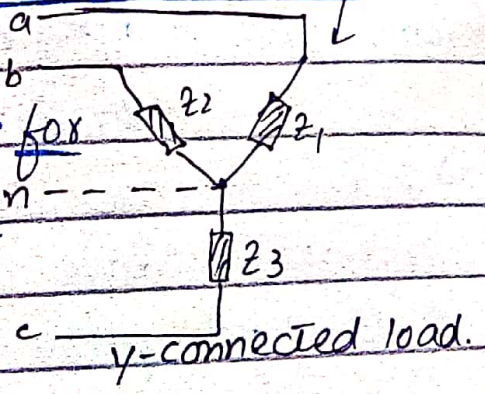

Δ-connected load

→ Z_Δ is load impedance per phase.

ch#9 { 9.69 } $\begin{cases} \bullet Z_\Delta = 3Z_y \text{ or} \\ \bullet Z_y = \frac{1}{3} Z_\Delta \end{cases}$

$Z_\Delta = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_1} = \frac{Z^2 + Z^2 + Z^2}{Z} = \frac{3Z^2}{Z}$

$Z_\Delta = 3Z_y$

→ As we know that, γ -connected load can be transformed into a Δ -connected load or vice versa

$$Z_{\Delta} = 3Z_{\gamma} \quad \text{or} \quad Z_{\gamma} = \frac{1}{3}Z_{\Delta}$$

→ Since both 3-phase source and the 3-phase load can either be γ -or- Δ connected, so we have four possible connections.

1. γ - γ connected i.e. γ -connected load to γ -source
2. γ - Δ connected
3. Δ - γ connected
4. Δ - Δ connected.

→ A balanced delta-connected load is more common than a balanced wye-connected load.

→ This is due to ease, with which loads may be added or removed from each phase of a delta-connected load.

→ A Δ/γ ckt. is said to be balanced if it has equal impedances in all three branches.

$$\gamma\text{-}\Delta: Z_{\Delta} = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_1} = \frac{3Z_{\gamma}^2}{Z_{\gamma}} = 3Z_{\gamma}$$

$$\boxed{Z_{\Delta} = 3Z_{\gamma}} \quad \text{or} \quad \boxed{Z_{\gamma} = \frac{1}{3}Z_{\Delta}}$$

Ex# 12.1:- Determine phase sequence of set of voltages:

$$V_{cn} = 200 \cos(\omega t - 110^\circ)$$

$$V_{an} = 200 \cos(\omega t + 10^\circ); \quad V_{bn} = 200 \cos(\omega t - 230^\circ)$$

Voltages in phasor-form are:-

$$V_{an} = 200 \angle 10^\circ, \quad V_{bn} = 200 \angle -230^\circ, \quad V_{cn} = 200 \angle -110^\circ$$

V_{an} leads V_{cn} by 120° & V_{cn} leads V_{bn} by 120° -
acb sequence here.

PP#12-1:- $V_{bn} = 220 \angle 30^\circ \text{ V}$ & find V_{an} & V_{cn} assuming +ve (abc) sequence.

For abc-sequence; V_{an} leads V_{bn} by 120° & V_{bn} leads V_{cn} by 120° - So,

$$V_{an} = 220 \angle 30^\circ + 120^\circ = \boxed{220 \angle 150^\circ \text{ V}}$$

$$V_{cn} = 220 \angle 30^\circ - 120^\circ = \boxed{220 \angle -90^\circ \text{ V}}$$

$$\boxed{V_{bn} = 220 \angle 30^\circ \text{ V}}$$

12.3 Balanced Wye-Wye connections:-

"A balanced Y-Y system is a 3-phase system with a balanced Y-connected source & a balanced Y-connected load."

$$Z_y = Z_s + Z_l + Z_L \quad \text{--- (12.9)}$$

Z_y = Total impedance per-phase.

Z_s = source " (internal impedance of phase-winding of generator)

Z_l = Line " (Impedance of line joining phase of source with phase of load)

Z_L = Load " "

Z_n = impedance of neutral line

→ (Theory from book pg # 507)

$$Z_y = Z_s + Z_l + Z_L$$

When Z_s & Z_l are small compared to Z_L . So,

$$\boxed{Z_y = Z_L}$$

$$V_{an} = V_p \angle 0^\circ$$

$$V_{bn} = V_p \angle -120^\circ$$

$$V_{cn} = V_p \angle +120^\circ / V_p \angle -240^\circ$$


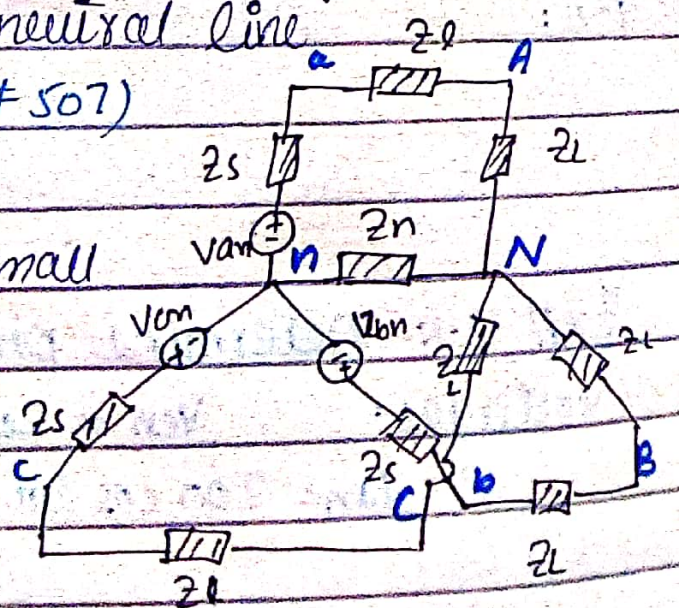
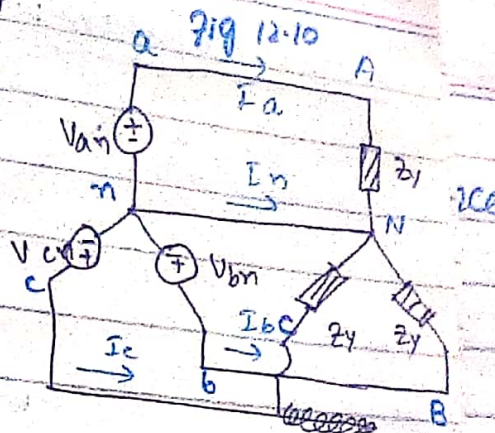


fig # 12.9

→ (Theory from book) pg # 507/508.

$$V_{ab} = V_{an} + (-V_{bn})$$
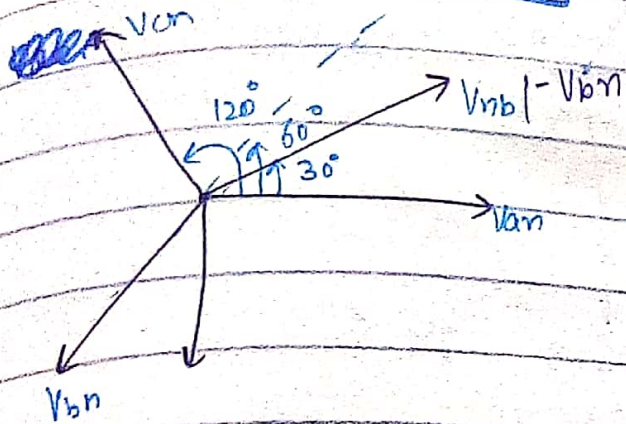
$$= V_p \angle 0^\circ - V_p \angle -120^\circ$$



→ converting from Rectangular to polar:-

$$V_{ab} = V_p [\cos(0) + j \sin(0)] - V_p [\cos(-120^\circ) + j \sin(-120^\circ)]$$

$$V_{ab} = V_p(1 + 0) - V_p[(-0.5) + j(-0.866)]$$

$$V_{ab} = V_p[1 + 0.5 + j0.866]$$

$$V_{ab} = V_p(1.5 + j0.866)$$


$$\therefore V_{ab} = V_p [1.73 \angle 30^\circ] = \sqrt{3} V_p \angle 30^\circ$$

$$V_{ab} = V_L = \sqrt{3} V_p$$

$\therefore V_p = V_{ph} = \text{phase-voltages.}$

Thus, magnitude of line-voltage V_L is $\sqrt{3}$ time the magnitude of phase-voltage (V_p).

$$V_L = \sqrt{3} V_p$$

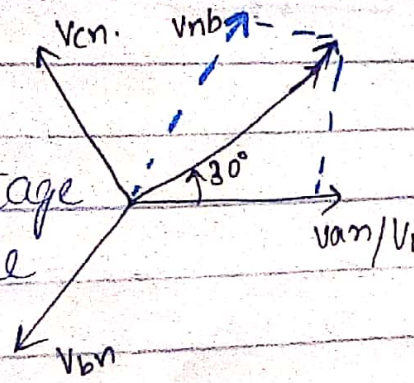

→ Similarly,

$$V_{(phase)} = V_p = |V_{an}| = |V_{bn}| = |V_{cn}|$$


$$\& \ V_{(line)} = V_L = |V_{ab}| = |V_{bc}| = |V_{ca}|$$

$$\text{where, } V_{ab} = \sqrt{3} V_p \angle 30^\circ \rightarrow 12.11(a)$$

$$V_{bc} = \sqrt{3} V_p \angle -90^\circ \rightarrow 12.11(b)$$

$$V_{ca} = \sqrt{3} V_p \angle -210^\circ \rightarrow 12.11(c)$$

Vector diagram:-

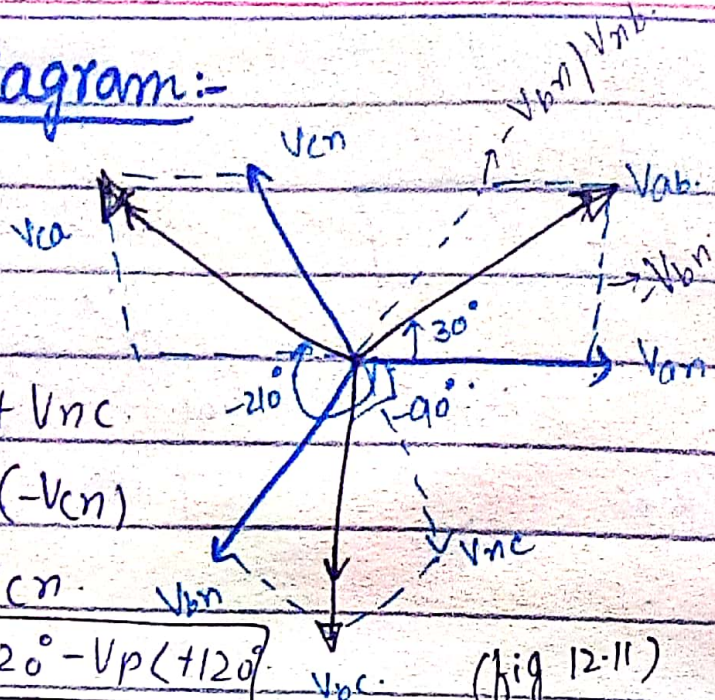

$$V_{bc} = V_{bn} + V_{nc}$$

$$V_{bc} = V_{bn} + (-V_{cn})$$

$$= V_{bn} - V_{cn}$$

$$V_{bc} = V_p \angle -120^\circ - V_p \angle +120^\circ \quad (\text{fig 12-11})$$

$$\text{or } V_{bc} = V_p \angle -120^\circ - V_p \angle +120^\circ \quad (\text{phasor} \rightarrow \text{rect.})$$

$$V_{bc} = V_p [\cos(-120^\circ) + j \sin(-120^\circ)] - V_p [\cos(120^\circ) + j \sin(120^\circ)]$$

$$V_{bc} = V_p [-0.5 - j0.866] - V_p [-0.5 + j0.866]$$

$$V_{bc} = -0.5V_p - jV_p 0.866 + 0.5V_p - jV_p 0.866$$

$$V_{bc} = -jV_p 1.732 = \sqrt{3} V_p \angle -90^\circ$$

$$-j = \angle -90^\circ$$

$$V_{bc} = \boxed{V_L = \sqrt{3} V_p}$$

$$1.732 = \sqrt{3}$$

from fig 12-10 :- (KVL on each phase) :- a $\xrightarrow{I_a}$ A

$$V_{an} = I_a Z_y$$

$$\text{Line current } \bar{I} = I_a = \frac{V_{an}}{Z_y}$$

$$\therefore I_b = \frac{V_{bn}}{Z_y} = \frac{V_{an} \angle -120^\circ}{Z_y}$$

$$\text{So, } I_b = I_a \angle -120^\circ = I_a \angle -120^\circ$$

$$\therefore I_c = \frac{V_{cn}}{Z_y} = \frac{V_{an} \angle -240^\circ}{Z_y} = I_a \angle -240^\circ$$

We can say, line currents add up to zero:-

$$I_a + I_b + I_c = 0 \quad \text{--- 12-16}$$


$$\text{So, } \bar{I}_n = -(I_a + I_b + I_c) = 0 \quad \text{--- 12-17}$$

$$V_{nn} = Z_n \bar{I}_n = 0 \quad \rightarrow \text{voltage across neutral wire}$$

Thus, neutral wire can be removed without affecting system.

→ In fact, in long distance, power transmission conductors in multiples of three are used with earth itself acting as neutral conductor.

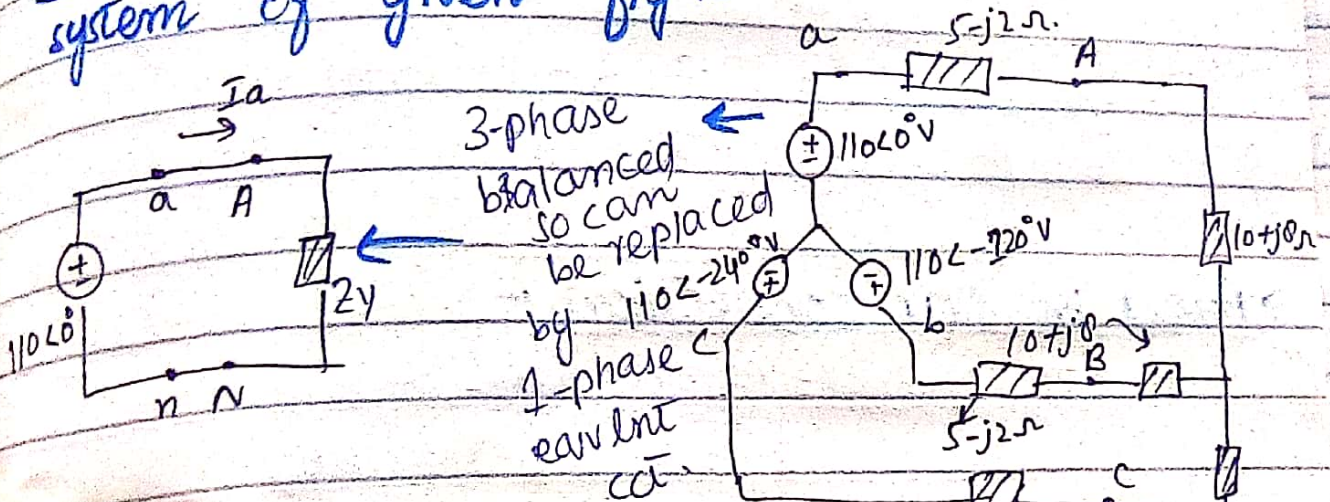Ex#12.2:- calculate line current in 3-wire Y system of given fig:-



$$Z_y = (5-j2) + (10+j8) = 15+j6 = 16.15 \angle 21.8^\circ$$

as: $I_a = \frac{V_{an}}{Z_y}$

$$I_a = \frac{110 \angle 0^\circ}{16.15 \angle 21.8^\circ} = \boxed{6.81 \angle -21.8^\circ \text{ A}}$$

$$I_b = I_a \angle -120^\circ = \boxed{6.81 \angle -141.8^\circ \text{ A}}$$

$$I_c = I_a \angle -240^\circ = \boxed{6.81 \angle 98.2^\circ \text{ A}}$$

PP#12.2:-

a) $V_{ab} = V_{an} - V_{bn} = 120 \angle 30^\circ - 120 \angle -90^\circ = 207.8 \angle 60^\circ \text{ V}$
 V_{ab} leads 30° to V_{an} & has mag. $\sqrt{3}$ time to V_{an} .

So,

$$V_{ab} = \sqrt{3} (120) \angle (30^\circ + 30^\circ) = 207.8 \angle 60^\circ \text{ V}$$

abc sequence $\Rightarrow V_{bc} = 207.8 \angle -60^\circ \text{ V}$

$$V_{ca} = 207.8 \angle +180^\circ \text{ V}$$

b) $I_a = \frac{V_{an}}{Z_y}$

$$Z_Y = (0.4 + j0.3) + (24 + j19) + (0.6 + j0.7)$$

$$Z_Y = 25 + j20 = 32 \angle 38.66^\circ$$

So,

$$I_a = \frac{120 \angle 30^\circ}{32 \angle 38.66^\circ} = 3.75 \angle -8.66^\circ \text{ A}$$

$$I_b = I_a \angle -120^\circ = 3.75 \angle -128.66^\circ \text{ A}$$

$$I_c = I_a \angle -240^\circ = 3.75 \angle 111.34^\circ \text{ A}$$

→ Power in star connection :-

$$\begin{aligned} \text{Total active power} = P &= 3 \times (\text{phase-power}) \\ &= 3 \times (V_{ph} \times I_{ph} \cos \phi) \end{aligned}$$

ϕ = angle b/w phase voltage & phase current

As we know:-

$$\begin{aligned} \text{in } Y-Y \rightarrow V_L &= \sqrt{3} V_{ph} \quad \& \quad I_{ph} = I_L \\ V_{ph} &= \frac{V_L}{\sqrt{3}} \end{aligned}$$

So,

$$P = 3 \times \left[\frac{V_L}{\sqrt{3}} \times I_L \cos \phi \right] = \sqrt{3} \cdot \sqrt{3} \left[\frac{V_L}{\sqrt{3}} \times I_L \cos \phi \right]$$

$$\boxed{P = \sqrt{3} [V_L I_L \cos \phi]} = \text{active / reactive power.}$$

Similarly;

$$\boxed{Q = \text{reactive power} = \sqrt{3} V_L I_L \sin \phi}$$

$$\boxed{S = \text{apparent power} = \sqrt{3} V_L I_L}$$

12.5 Balanced Delta-Delta connection:-

"A balanced Δ - Δ system is one in which both the balance source & balanced load are Δ -connected."

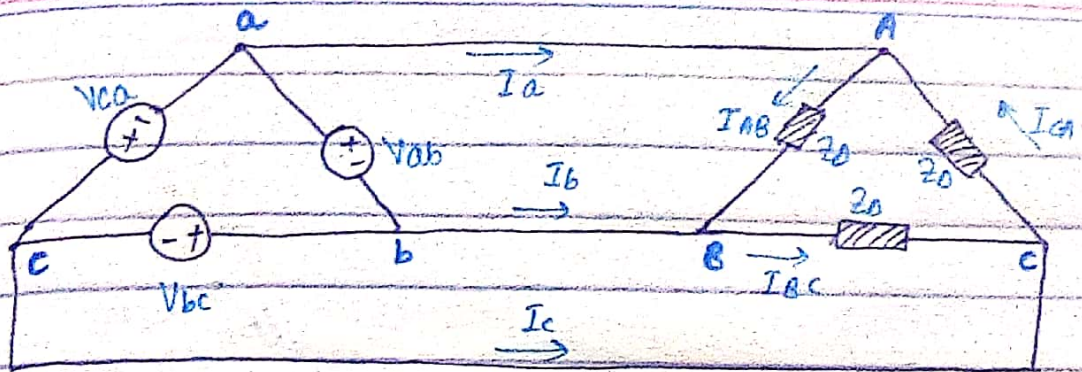


Fig 12.17 (A balanced Δ Connection)

→ Assuming a positive sequence, the phase voltage for a delta-connected source are;

$$V_{ab} = V_p \angle 0^\circ, \quad V_{bc} = V_p \angle -120^\circ, \quad V_{ca} = V_p \angle +120^\circ \quad \rightarrow 12.29$$

* Line voltages are same as phase voltages.

→ Assuming there is no line impedance - phase voltage of Δ -connected source are equal to voltage across impedance.

$$V_{ab} = V_{AB}, \quad V_{bc} = V_{BC}, \quad V_{ca} = V_{CA}$$

Hence, phase current:-

$$I_{AB} = \frac{V_{AB}}{Z_\Delta} = \frac{V_{ab}}{Z_\Delta}$$

$$I_{BC} = \frac{V_{BC}}{Z_\Delta} = \frac{V_{bc}}{Z_\Delta}$$

$$I_{CA} = \frac{V_{CA}}{Z_\Delta} = \frac{V_{ca}}{Z_\Delta}$$

line currents are obtained from phase currents by applying KCL at node A, B & C.

$$I_a = I_{AB} - I_{CA}, \quad I_b = I_{BC} - I_{AB}, \quad I_c = I_{CA} - I_{BC}$$

$$\text{Since; } I_{CA} = I_{AB} \angle -240^\circ$$

$$\text{So, } I_a = I_{AB} - I_{AB} \angle -240^\circ$$

$$\text{or } I_a = I_{AB} (1 - 1 \angle -240^\circ)$$

$$= I_{AB} (1 + 0.5 - j0.866)$$

$$\boxed{I_a = I_{AB} \sqrt{3} \angle -30^\circ} \rightarrow \text{Mag. of } I_L \text{ is } \sqrt{3} \text{ times of } I_{ph}$$


$$I_L = \sqrt{3} \cdot I_{ph}$$

$$I_{ph} = I_p = |I_{AB}| = |I_{BC}| = |I_{CA}|$$

$$I_L = |I_a| = |I_b| = |I_c|$$

$$I_L = \sqrt{3} I_p$$
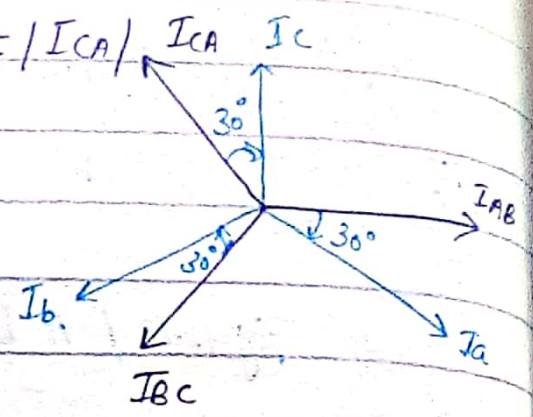
$$\text{or } I_p = \frac{I_L}{\sqrt{3}}$$



Ex#12.3:-

Balanced abc Y connected source with $V_{an} = 100 \angle 0^\circ$ v is connected to Δ

Ex#12.4:-

Balanced Δ -connected load has $Z = 20 - j15 \Omega$ is connected to Δ -connected +ve-sequence generator having $V_{ab} = 330 \angle 0^\circ$ v; calculate I_{ph} of load & line currents.

Solution:-

$$Z_{\Delta} = 20 - j15 = 25 \angle -36.86^\circ$$

Here; $V_{ab} = V_{AB}$; So; $I_{ph}:-$

$$I_{AB} = \frac{V_{AB}}{Z_{\Delta}} = \frac{330 \angle 0^\circ}{25 \angle -36.86^\circ}$$

$$I_{AB} = 13.2 \angle 36.87^\circ \text{ A}$$

$$I_{BC} = I_{AB} \angle -120^\circ = 13.2 \angle -83.13^\circ \text{ A}$$

$$I_{CA} = I_{AB} \angle -240^\circ / +120^\circ = 13.2 \angle 156.87^\circ \text{ A}$$

for delta-load; I_L always lags corresponding I_{ph} by 30° . & has mag. $\sqrt{3}$ times I_{ph} . So, line currents:- $I_a = I_{AB} \cdot \sqrt{3} \angle -30^\circ = (13.2 \angle 36.87^\circ) (\sqrt{3} \angle -30^\circ)$

$$I_a = 22.86 \angle 6.87^\circ \text{ A}$$

$$I_b = I_a \angle -120^\circ = 22.86 \angle -113.3^\circ \text{ A}$$

$$I_c = I_a \angle +120^\circ = 22.86 \angle 126.7^\circ \text{ A}$$

Pr#12.4:- +ve-seq. balance ~~3~~ Δ -connected sources supplies a balanced Δ -connected load. If impedance per phase of load is $18 + j12 \Omega$, $I_a = 9.609 \angle 35^\circ A$, find I_{AB} & V_{AB} .

$$Z_{\Delta} = 18 + j12 \Omega = 21.63 \angle 33.69^\circ$$

$$I_a = 9.609 \angle 35^\circ A = I_{AB} (\sqrt{3} \angle -30^\circ)$$

$$I_{AB} = \frac{9.609 \angle 35^\circ}{\sqrt{3} \angle -30^\circ} = \boxed{5.547 \angle 65^\circ A}$$

$$V_{AB} = I_{AB} \times Z_{\Delta}$$

$$V_{AB} = (5.547 \angle 65^\circ)(21.63 \angle 33.69^\circ)$$

$$V_{AB} = 119.99 \angle 98.69^\circ V$$

$$\text{or } \boxed{V_{AB} = 120 \angle 98.69^\circ V}$$

12.4 Balanced Y- Δ connection:-


"A balanced Y- Δ system consists of a balanced Y-connected source feeding balanced Δ -connected load
 \rightarrow This is most practical 3-phase system used.

$$V_{\text{phase}} = V_{\text{an}} = V_{p \angle 0^\circ}$$

$$V_{bn} = V_p \angle -120^\circ$$

$$V_{cn} = V_p \angle +120^\circ$$
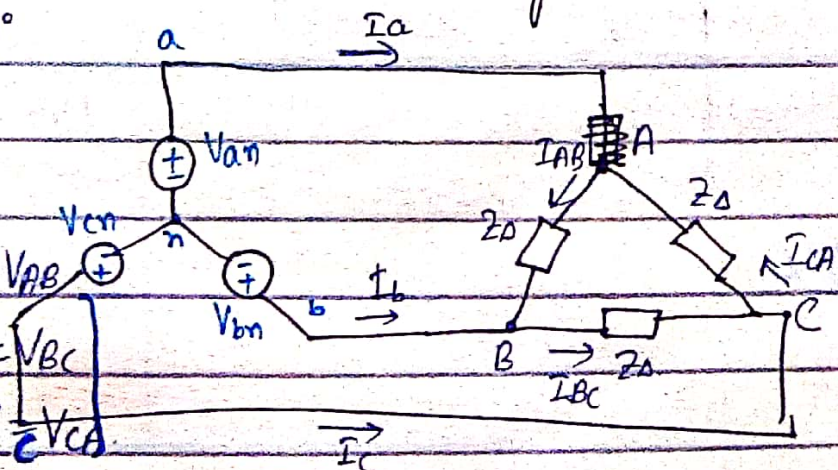
$$\text{as } \begin{cases} V_{ab} = \sqrt{3} V_p \angle 30^\circ = V_{AB} \\ V_{bc} = \sqrt{3} V_p \angle -90^\circ = V_{BC} \\ V_{ca} = \sqrt{3} V_p \angle -120^\circ = V_{CA} \end{cases}$$



$$I_{AB} = \frac{V_{AB}}{Z_{\Delta}} \rightarrow I_{BC} = I_{AB} \angle -120^\circ = \frac{V_{BC}}{Z_{\Delta}}, \quad I_{CA} = \frac{V_{CA}}{Z_{\Delta}} = I_{AB} \angle +120^\circ$$

$$\boxed{I_p = \frac{1}{\sqrt{3}} I_L} \rightarrow \Delta$$

12.6 Balanced Δ -Y connection:- \rightarrow case.

"consists of a balanced Δ -connected source feeding a balanced Y-connected load."

$$Z_b = \frac{1}{3} Z_y$$

Table #12.1

Summary of Phase & Line Current / Voltages for balanced 3-phase system.

(+ve-phase sequence assumed) ∇_{abc}

Connections	Phase voltage/current	Line voltage/current
Y-Y	$V_{an} = V_p \angle 0^\circ$ $V_{bn} = V_p \angle +120^\circ$ $V_{cn} = V_p \angle +120^\circ$ Z_y $I_{\text{phase}} = I_{\text{line}}$	$V_{ab} = \sqrt{3} V_p \angle 30^\circ$ $V_{bc} = \sqrt{3} V_p \angle -90^\circ / V_{ab} \angle -120^\circ$ $V_{ca} = V_{ab} \angle +120^\circ$ $I_a = V_{an} / Z_y, I_b = I_a \angle -120^\circ$ $I_c = I_a \angle +120^\circ$
Y- Δ	$V_{an} = V_p \angle 0^\circ, V_{bn} = V_p \angle -120^\circ$ $V_{cn} = V_p \angle +120^\circ$ $I_{AB} = V_{AB} / Z_\Delta$ $I_{BC} = V_{BC} / Z_\Delta$ $I_{CA} = V_{CA} / Z_\Delta$	$V_{ab} = V_{AB} = \sqrt{3} V_p \angle 30^\circ$ $V_{bc} = V_{BC} = V_{ab} \angle -120^\circ$ $V_{ca} = V_{CA} = V_{ab} \angle +120^\circ$ $I_a = I_{AB} \sqrt{3} \angle -30^\circ, I_b = I_a \angle -120^\circ$ $I_c = I_a \angle +120^\circ$
Δ - Δ	$V_{ab} = V_p \angle 0^\circ, V_{bc} = V_p \angle -120^\circ$ $V_{ca} = V_p \angle +120^\circ$ $I_{AB} = V_{ab} / Z_\Delta$ $I_{BC} = V_{bc} / Z_\Delta$ $I_{CA} = V_{ca} / Z_\Delta$	Line voltages = Phase voltages $(V_L = V_P)$ $I_a = I_{AB} \sqrt{3} \angle -30^\circ$ $I_b = I_a \angle -120^\circ$ $I_c = I_a \angle +120^\circ$
Δ -Y	$V_{ab} = V_p \angle 0^\circ, V_{bc} = V_p \angle -120^\circ$ $V_{ca} = V_p \angle +120^\circ$ phase current = line current	$I_a = \frac{V_p / \sqrt{3}}{Z_y} \angle -30^\circ$ or $I_a = 0.577 V_p \angle -30^\circ / Z_y$ $I_b = I_a \angle -120^\circ$ $I_c = I_a \angle +120^\circ$

Line & phase voltages are same

Ex#12.3 :-

A balanced abc-sequence Y-connected source with $V_{an} = 100 \angle 10^\circ \text{ V}$ is connected to a connected balanced load $(8+4j)\Omega$ per phase; calculate phase & line currents.

Solution:-

$$Z_{\Delta} = (8+4j)\Omega = 8.944 \angle 26.56^\circ \Omega$$

$$V_{an} = V_{ph} = 100 \angle 10^\circ; \quad V_{ab} = V_L = V_{an} \sqrt{3} \angle 30^\circ$$

$$V_{ab} = 173.2 \angle 40^\circ \text{ V} = V_{AB}$$

phase currents:- $I_{AB} = \frac{V_{AB}}{Z_{\Delta}} = \frac{173.2 \angle 40^\circ}{8.944 \angle 26.56^\circ}$

$$I_{AB} = 19.36 \angle 13.44^\circ \text{ A}$$

$$I_{BC} = I_{AB} \angle -120^\circ = 19.36 \angle -106.56^\circ \text{ A}$$

$$I_{CA} = I_{AB} \angle +120^\circ = 19.36 \angle 133.44^\circ \text{ A}$$

line currents:- $I_a = I_{AB} \sqrt{3} \angle -30^\circ = 33.53 \angle -16.57^\circ \text{ A}$

$$I_b = I_a \angle -120^\circ = 33.53 \angle -136.57^\circ \text{ A}$$

$$I_c = I_a \angle +120^\circ = 33.53 \angle 103.43^\circ \text{ A}$$

PP#12.3:- $V_{AB} = 120 \angle -20^\circ \text{ V}$, $Z_{\Delta} = 20 \angle 40^\circ \Omega$ - $I_{ph}=?$, $I_L=?$

phase currents:-

$$I_{AB} = \frac{V_{AB}}{Z_{\Delta}} = \frac{120 \angle -20^\circ}{20 \angle 40^\circ} = 6 \angle -60^\circ \text{ A}$$

$$I_{BC} = I_{AB} \angle -120^\circ = 6 \angle -180^\circ, \quad I_{CA} = I_{AB} \angle +120^\circ = 6 \angle 60^\circ \text{ A}$$

line currents:-

$$I_a = I_{AB} \sqrt{3} \angle -30^\circ = (6)(\sqrt{3}) \angle -30^\circ - 60^\circ = 10.39 \angle -90^\circ \text{ A}$$

$$I_b = I_a \angle -120^\circ = 10.39 \angle -210^\circ \text{ A}$$

$$I_c = I_a \angle +120^\circ = 10.39 \angle 30^\circ \text{ A}$$

Ex#12.5:-

A balanced Y-connected load with phase impedance of $40 + j25 \Omega$ is supplied by a balanced three-phase delta-connected source with $V_L = 210 \text{ V}$. Phase current = ?

$$Z_Y = 40 + j25 \Omega = 47.1609 \angle 32^\circ$$

$$V_{ab} = 210 \angle 0^\circ \text{ V}$$

$$V_{an} = \frac{V_{ab}}{\sqrt{3}} \angle -30^\circ = 121.24 \angle -30^\circ \text{ V}$$

Line currents:- $I_a = \frac{V_{an}}{Z_Y} = \frac{121.24 \angle -30^\circ}{47.17 \angle 32^\circ} = 2.57 \angle -62^\circ \text{ A}$

$$I_b = I_a \angle -120^\circ = 2.57 \angle -182^\circ \text{ A}$$

$$I_c = I_a \angle +120^\circ = 2.57 \angle 58^\circ \text{ A}$$

same as phase currents

PP#12.5:- $V_{ab} = 440 \angle 15^\circ$, $Z_Y = 12 + j15 \Omega$, line currents?

$$Z_Y = 12 + j15 \Omega = 19.21 \angle 51.34^\circ \Omega$$

$$V_{ab} = 440 \angle 15^\circ \text{ V}$$

$$V_{an} = \frac{V_{ab}}{\sqrt{3}} \angle -30^\circ = \frac{440}{\sqrt{3}} \angle -30 + 15 = 254.03 \angle -15^\circ \text{ V}$$

$$I_a = \frac{V_{an}}{Z_Y} = \frac{254.03 \angle -15^\circ}{19.21 \angle 51.34^\circ} = 13.224 \angle -66.34^\circ \text{ A}$$

$$I_b = I_a \angle -120^\circ = 13.224 \angle -186.34^\circ \text{ A}$$

$$I_c = I_a \angle +120^\circ = 13.224 \angle 53.66^\circ \text{ A}$$

Ex#12.7:- $P = 5.6 \text{ kW}$; $V_L = 220 \text{ V}$, $I_L = 18.2 \text{ A}$.

P.f. = ?

$$S = \sqrt{3} V_L I_L = (\sqrt{3})(220)(18.2) = 6935.13 \text{ VA}$$

$$P = S \cos \theta = 5600 \text{ W}$$

$$\text{P.f.} = \cos \theta = \frac{P}{S} = \frac{5600}{6935.13} = 0.8075$$

PP# 12.7:- $P = 30 \text{ kW}$; $P.f = \cos\theta = 0.85$ lagging.

$V_L = 550 \text{ V}$; $I_L = ?$

$$P = S \cos\theta \Rightarrow S = \frac{P}{\cos\theta} = \frac{30,000}{0.85} = 35294.117 \text{ VA}$$

$$S = \sqrt{3} V_L I_L \Rightarrow I_L = \frac{35294.117}{(\sqrt{3})(550)}$$

$$I_L = 37.05 \text{ A}$$

EX# 12.9:- $Z_A = 15 \Omega$, $Z_B = 10 + j5 \Omega$, $Z_C = 6 - j8 \Omega$,
balanced volts = 100V.

$$I_a = \frac{100 \angle 0^\circ}{15} = 6.67 \angle 0^\circ \text{ A}$$

$$I_b = \frac{100 \angle 120^\circ}{10 + j5} = 8.94 \angle 93.44^\circ \text{ A}, \quad I_c = \frac{100 \angle -120^\circ}{6 - j8}$$

$$I_c = 10 \angle -66.87^\circ \text{ A}$$

neutral-line current:-

$$I = -(I_a + I_b + I_c) = 10.06 \angle 178.4^\circ \text{ A}$$