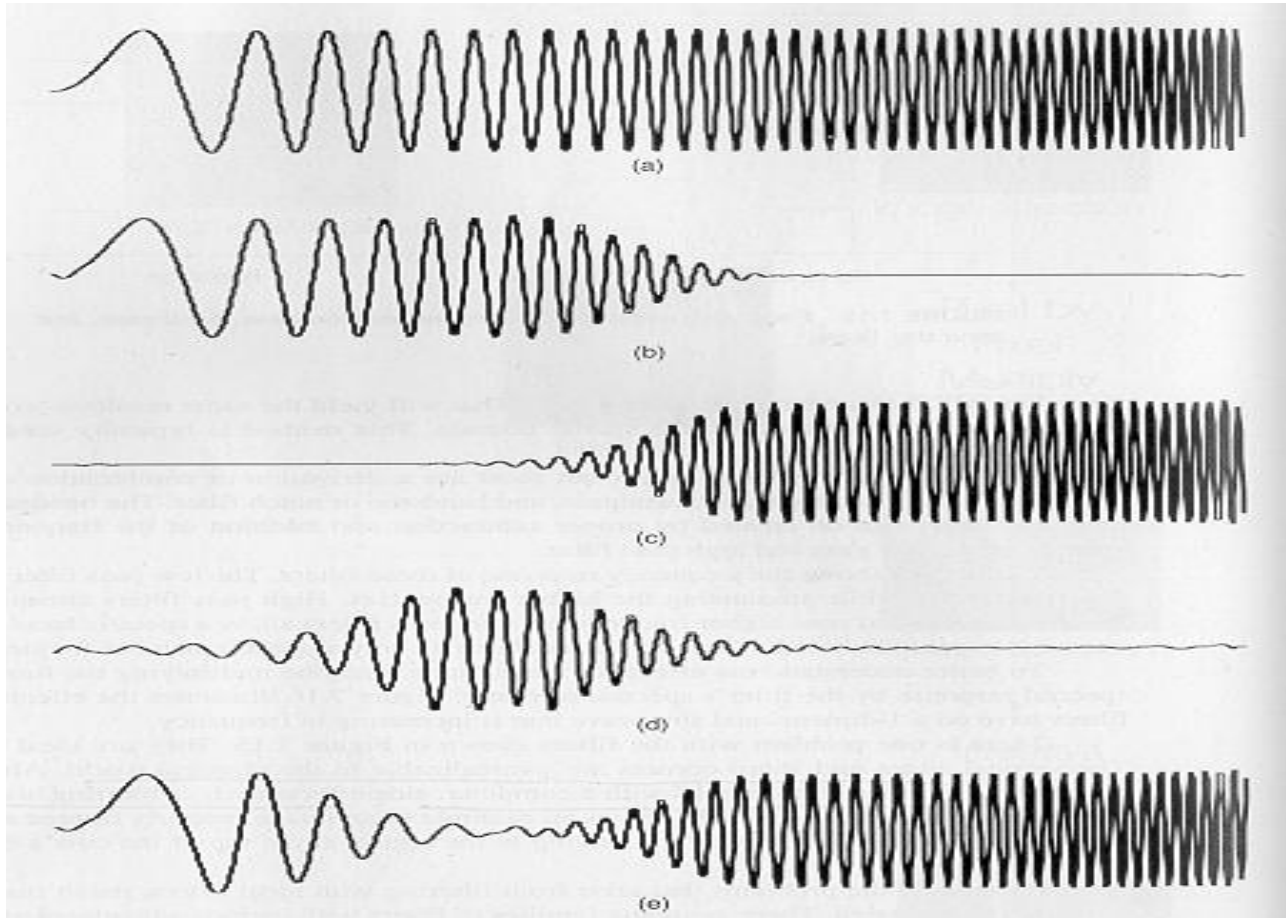





Filters

Major filter categories


- Typically, filters are classified by examining their properties in the frequency domain:
 - (1) Low-pass
 - (2) High-pass
 - (3) Band-pass
 - (4) Band-stop




Low Pass filter

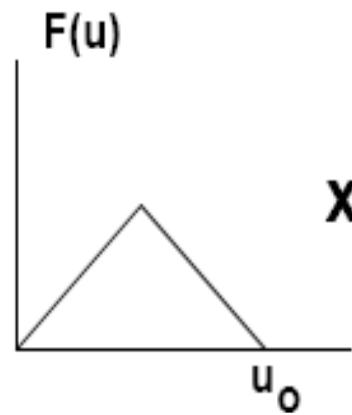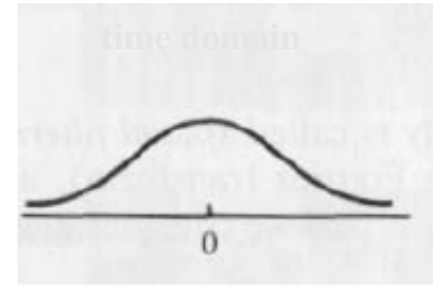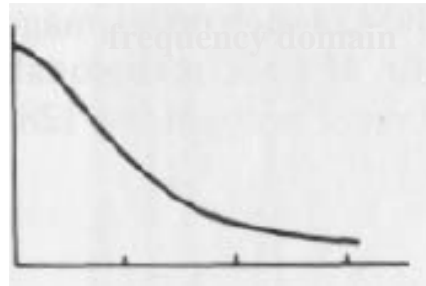

X

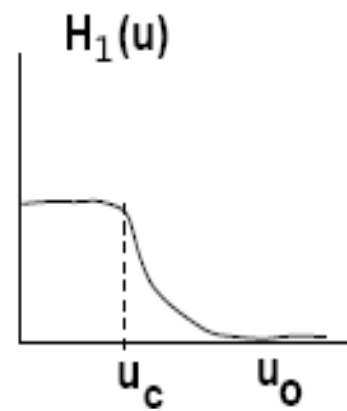


=


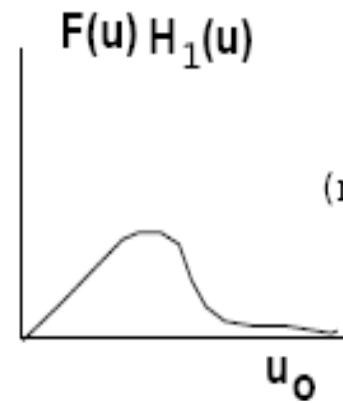


Low-pass filtering
(noise suppression)


High-pass filters

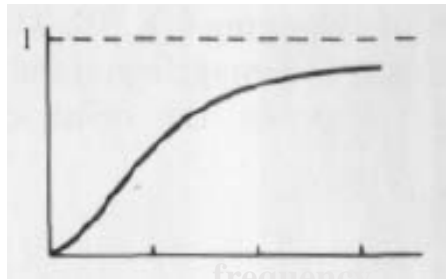


frequency domain

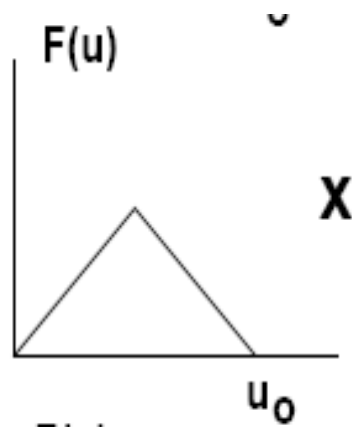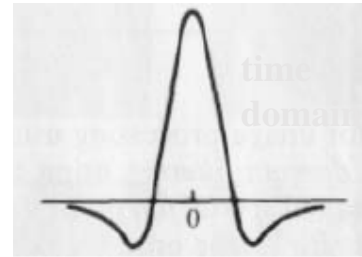

\times



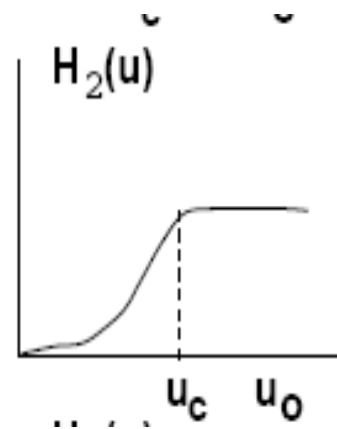


$=$

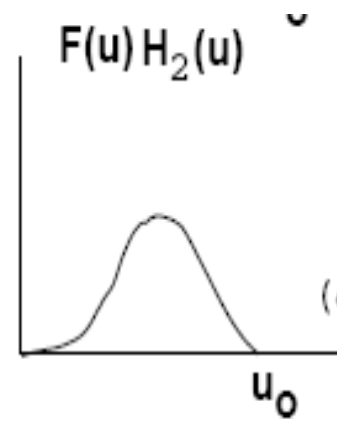


High-pass filtering
(edge detection)


Band-pass filters

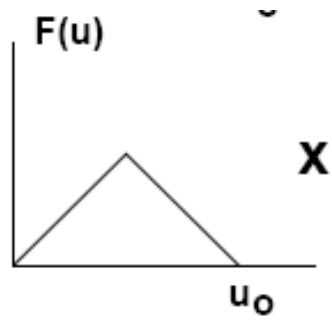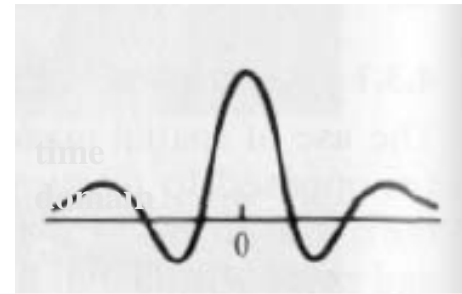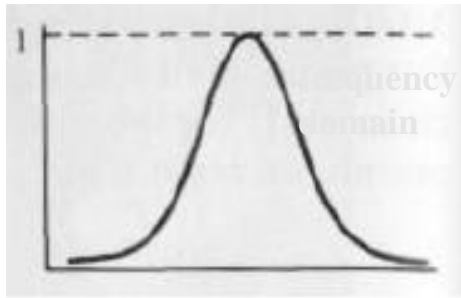

X

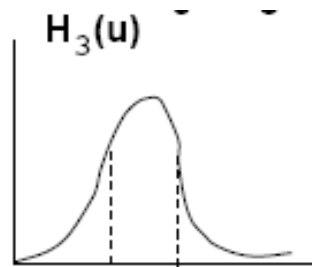


=

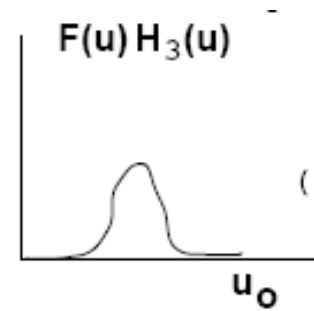


Band-pass filtering
(image restoration)


Lowpass Filter

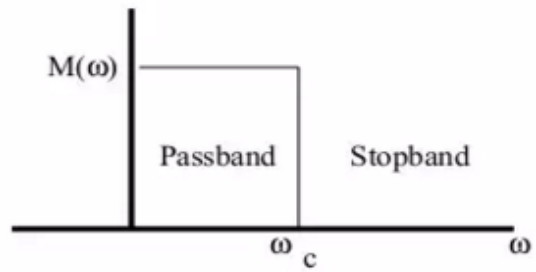


Highpass Filter

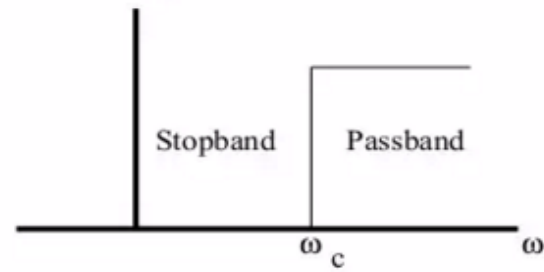


Bandstop Filter

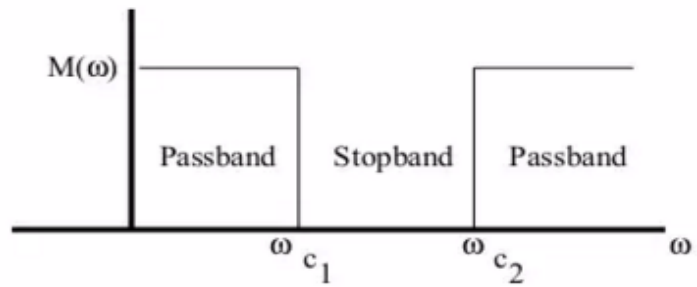


Bandpass Filter

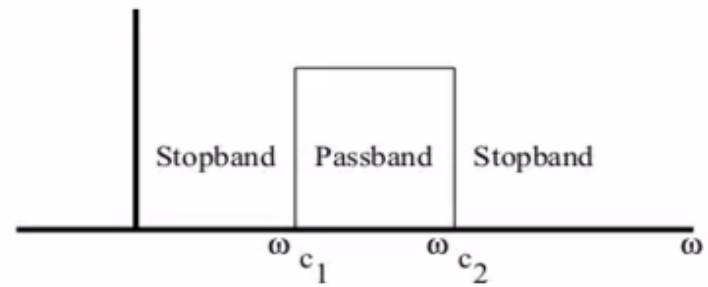


lowpass

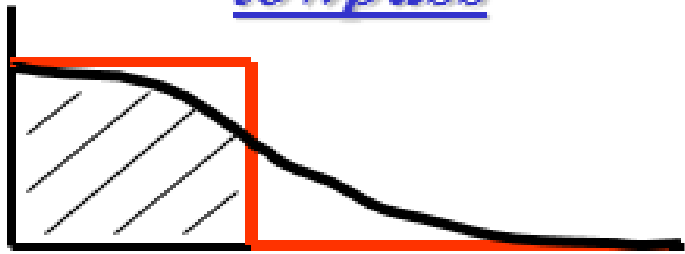


highpass

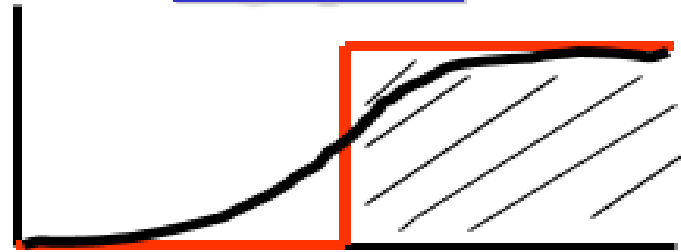

bandpass

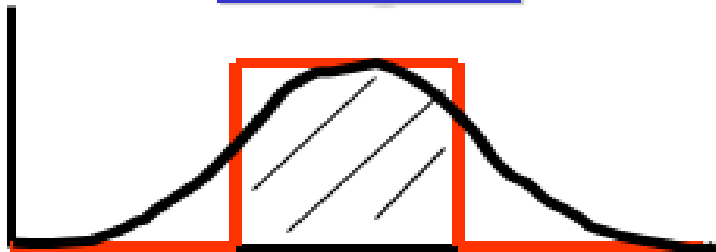


bandstop

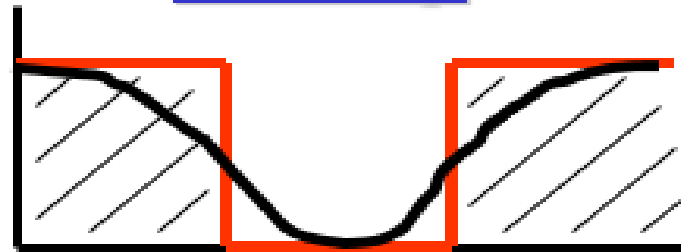

Low Pass Filter


Consider the circuit below.

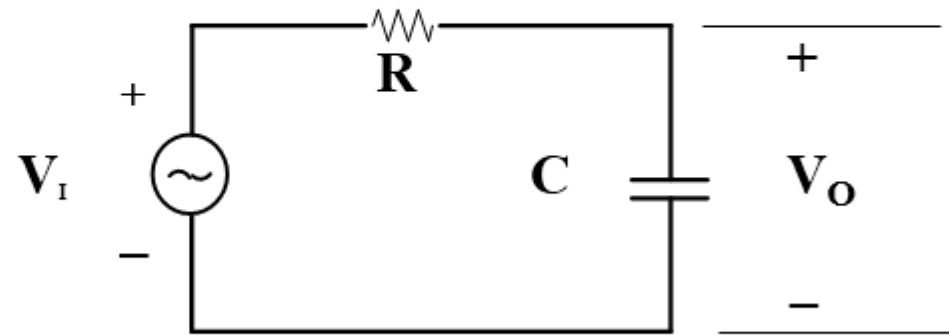

Low pass filter circuit


$$\frac{V_o(j\omega)}{V_i(j\omega)} = \frac{1}{R + \frac{1}{j\omega C}} = \frac{1}{1 + j\omega RC}$$

Low Pass Filter

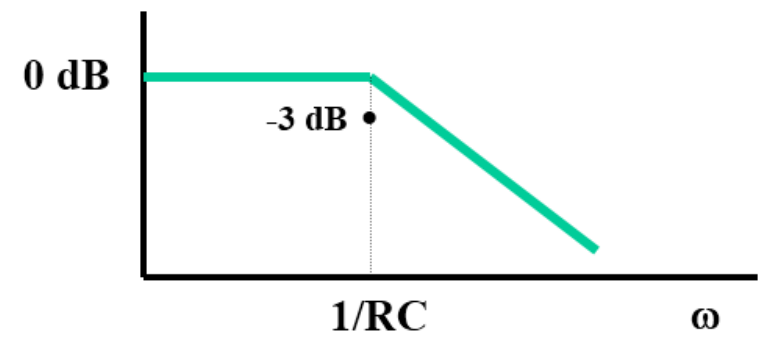

Bode

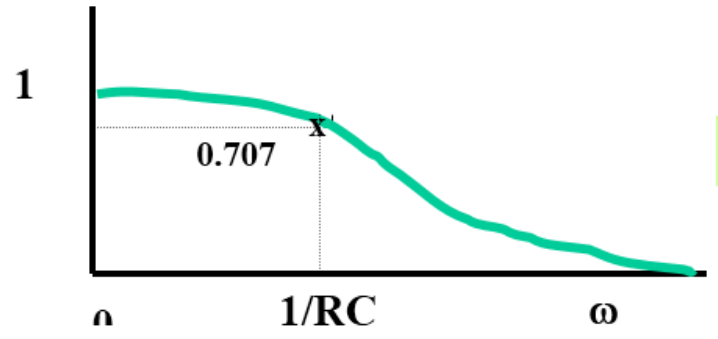
Passes low frequencies
Attenuates high frequencies



Linear Plot

High Pass Filter

Consider the circuit below.

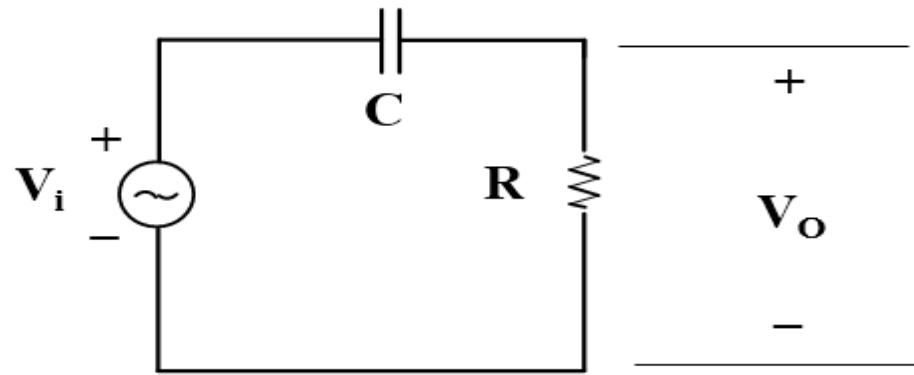

High Pass Filter


$$\frac{V_o(j\omega)}{V_i(j\omega)} = \frac{R}{R + \frac{1}{j\omega C}} = \frac{j\omega RC}{1 + j\omega RC}$$

The **bandwidth** of an **ideal** low-pass filter is equal to **f_c** :

$$BW = f_c$$

The critical frequency of a low-pass RC filter occurs when **$X_C = R$** and can be calculated using the formula below:

$$f_c = \frac{1}{2\pi RC}$$

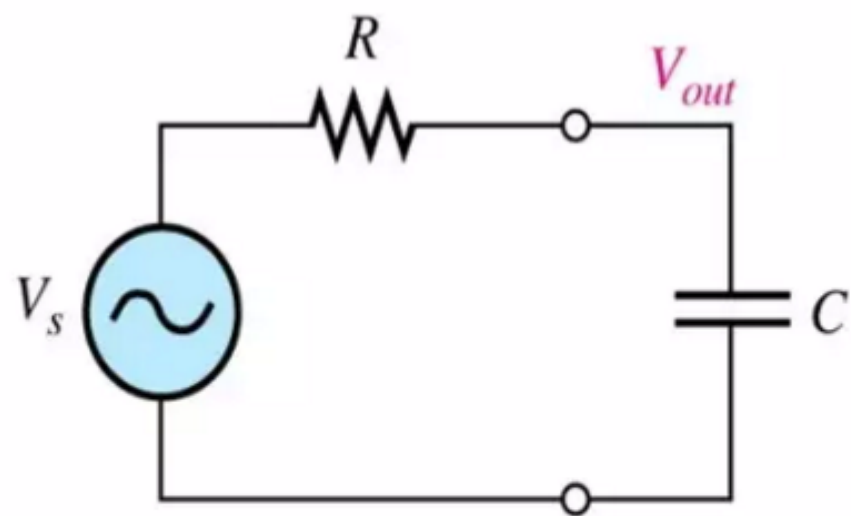

(b) Basic low-pass circuit

At critical frequency,


Resistance = Capacitance

$$R = X_c$$

$$R = \frac{1}{\omega_c C}$$

$$R = \frac{1}{2\pi f_c C}$$


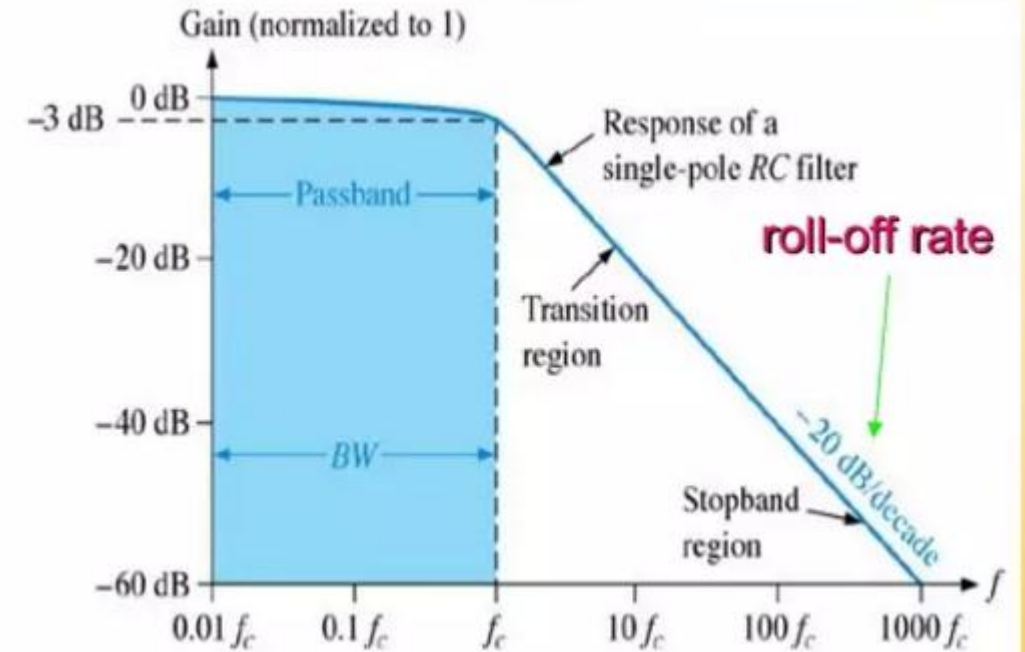
Critical frequency, f_c , (also called the cutoff frequency) defines the end of the passband and normally specified at the point where the response drops -3 dB (70.7%) from the passband response.




Band Pass Filter

Bandpass Pass Filter

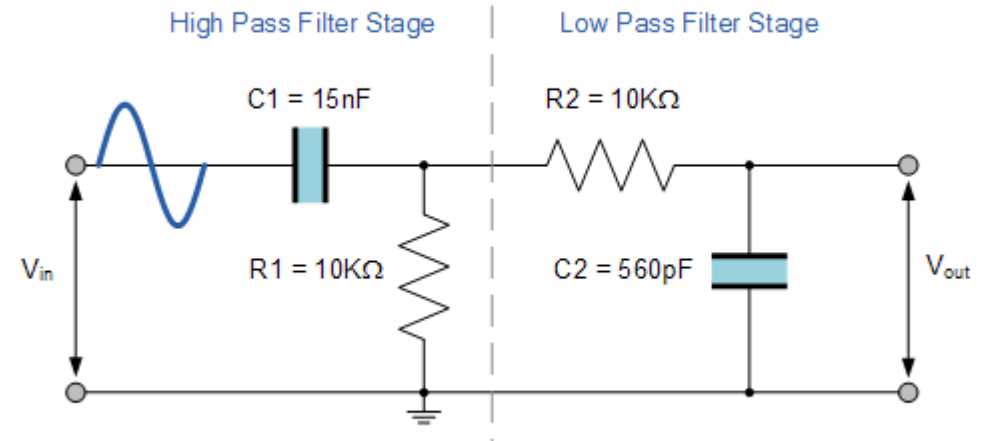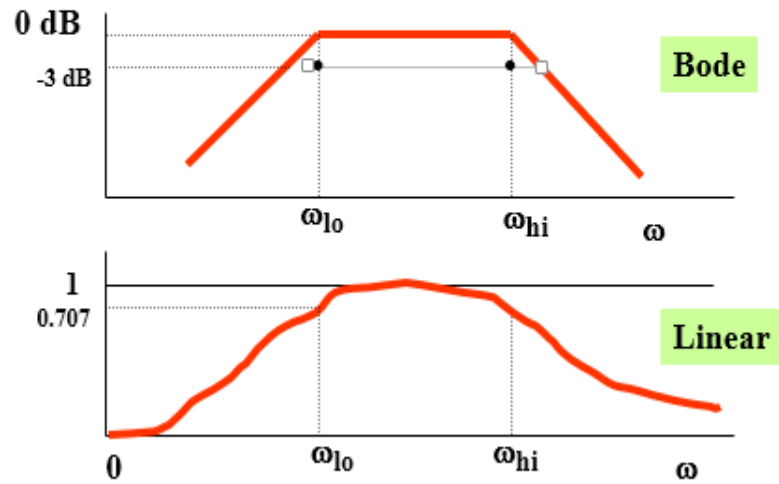
We can make a bandpass from the previous equation and select the poles where we like. In a typical case we have the following shapes.



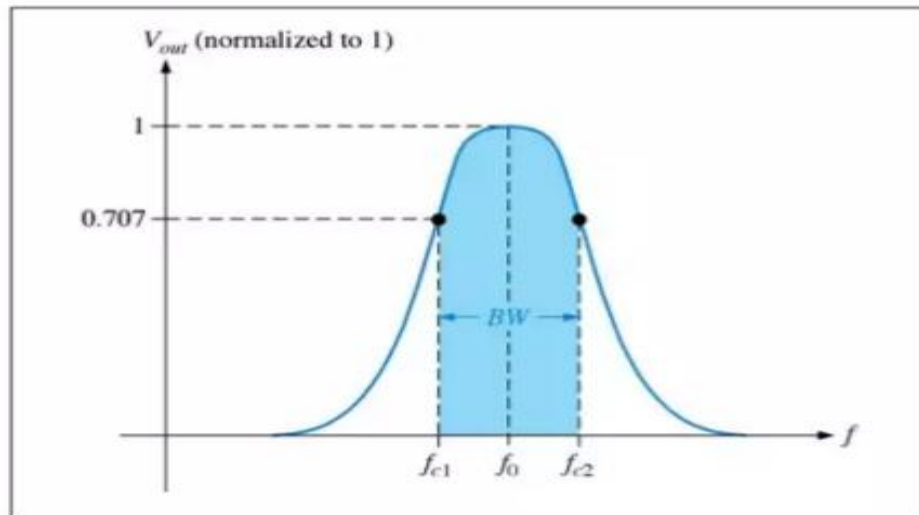
- A **band-pass filter** passes all signals lying within a band between a **lower-frequency limit** and **upper-frequency limit** and essentially rejects all other frequencies that are outside this specified band.



Actual response

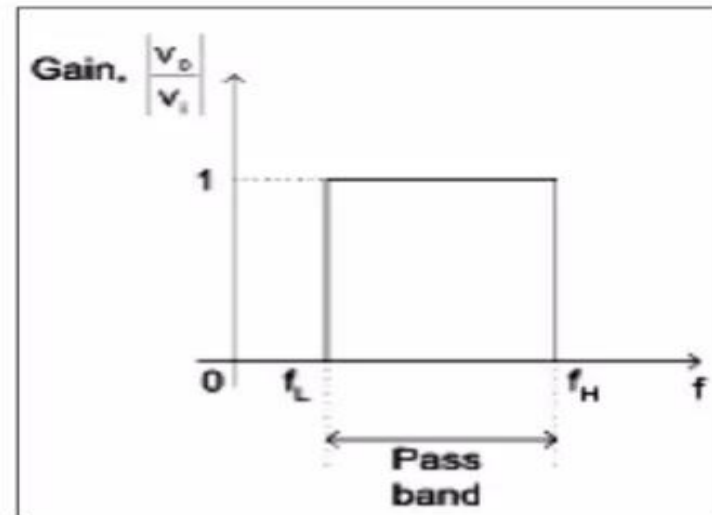

Ideal response

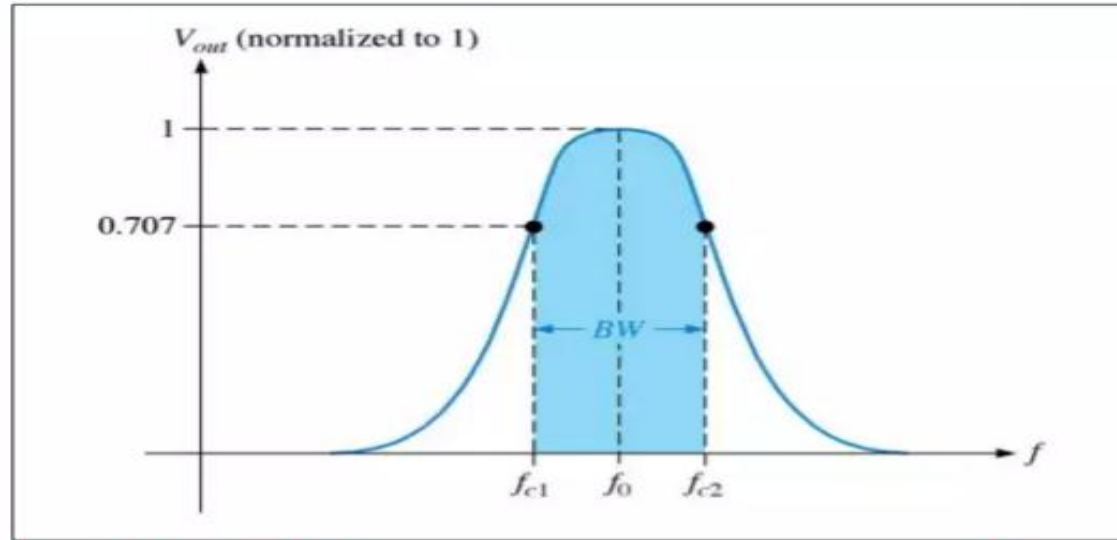


➤ The **bandwidth (BW)** is defined as the **difference** between the **upper critical frequency (f_{c2})** and the **lower critical frequency (f_{c1})**.

$$BW = f_{c2} - f_{c1}$$


➤ The frequency about which the pass band is centered is called the **center frequency, f_o** and defined as the geometric mean of the critical frequencies.

$$f_o = \sqrt{f_{c1}f_{c2}}$$

Band Stop Filter

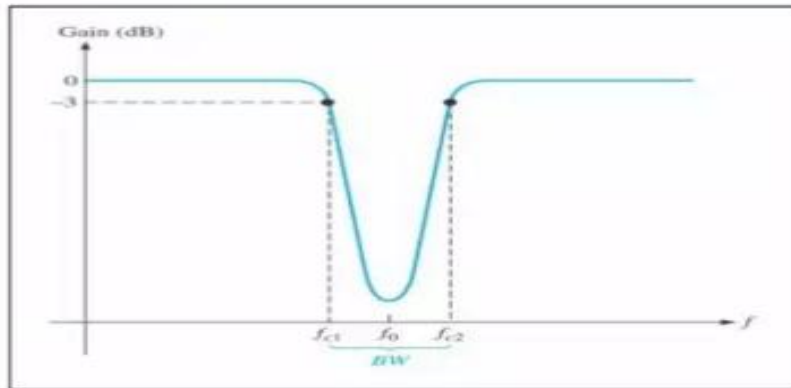


Actual response

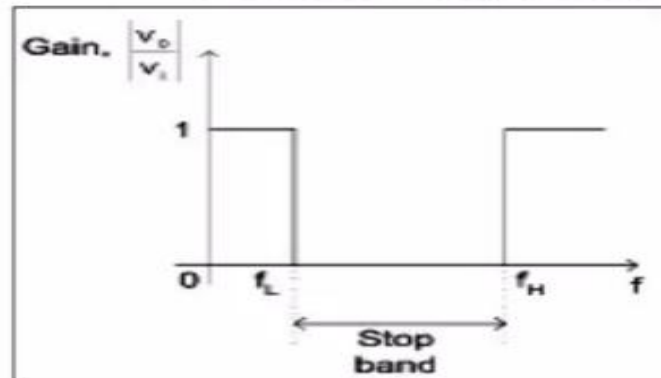


Ideal response

➤ **Band-stop filter** is a filter which its operation is **opposite** to that of the band-pass filter because the frequencies **within** the bandwidth are **rejected**, and the frequencies above f_{c1} and f_{c2} are **passed**.

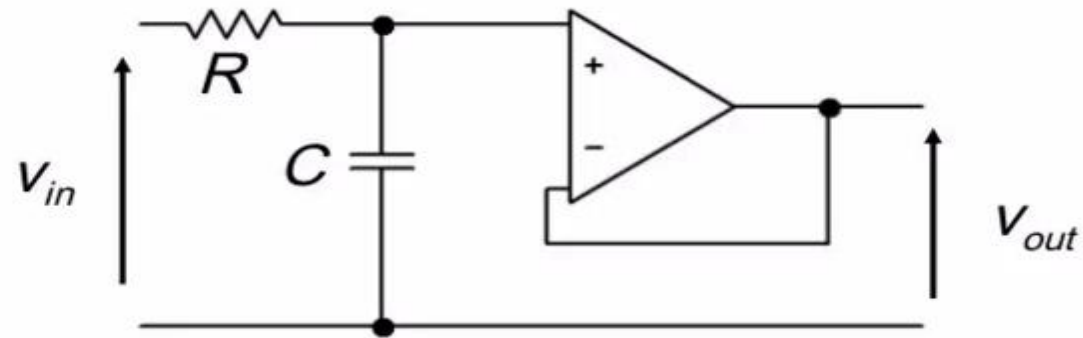
➤ For the band-stop filter, the **bandwidth** is a band of frequencies between the 3 dB points, just as in the case of the band-pass filter response.



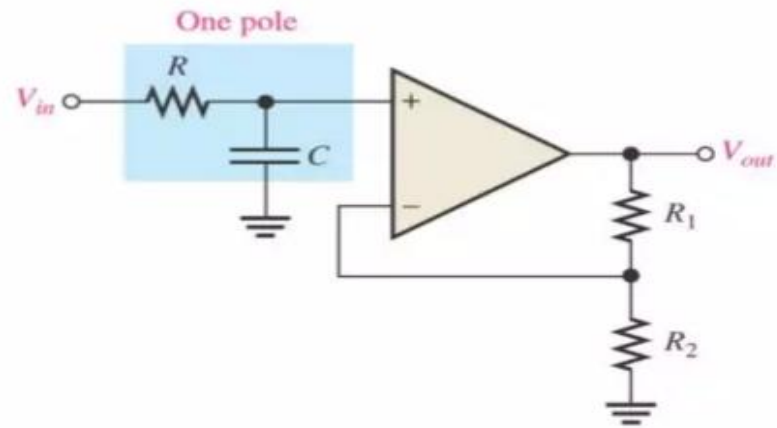- ◆ Same frequency response as passive filter.
- ◆ Buffer amplifier does not load RC network.
- ◆ Output impedance is now zero.



(a)

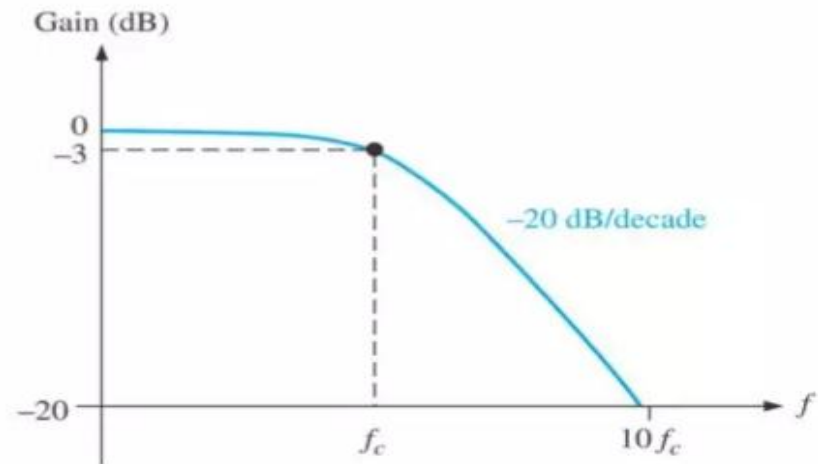


(b)


Single-pole active low-pass filter and response curve.

- This filter provides a roll-off rate of -20 dB/decade above the critical frequency.

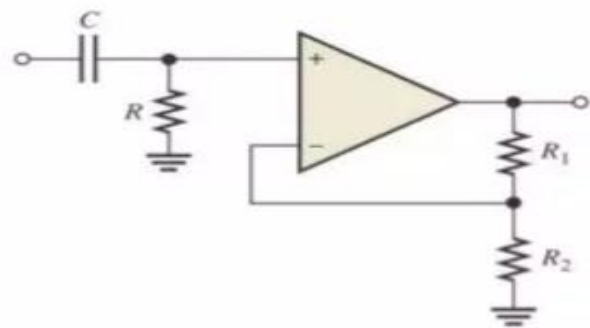
- In high-pass filters, the roles of the **capacitor** and **resistor** are **reversed** in the RC circuits as shown from Figure (a). The negative feedback circuit is the same as for the low-pass filters.
- Figure (b) shows a high-pass active filter with a -20dB/decade roll-off



(a)

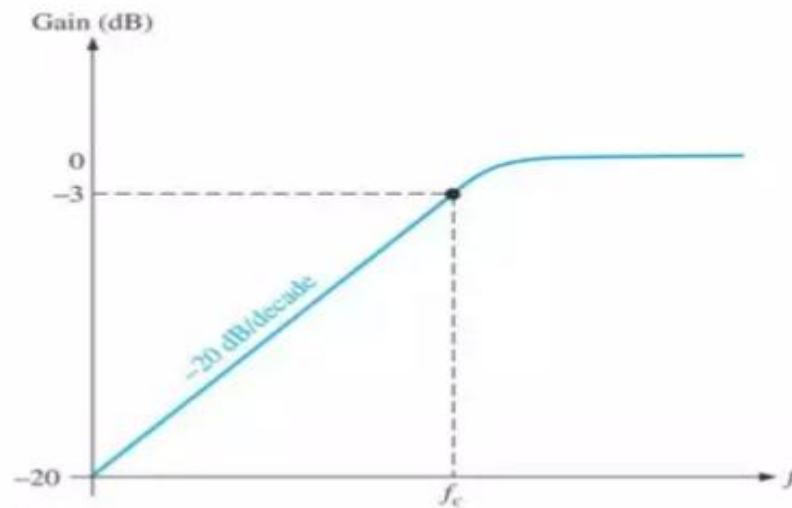


(b)


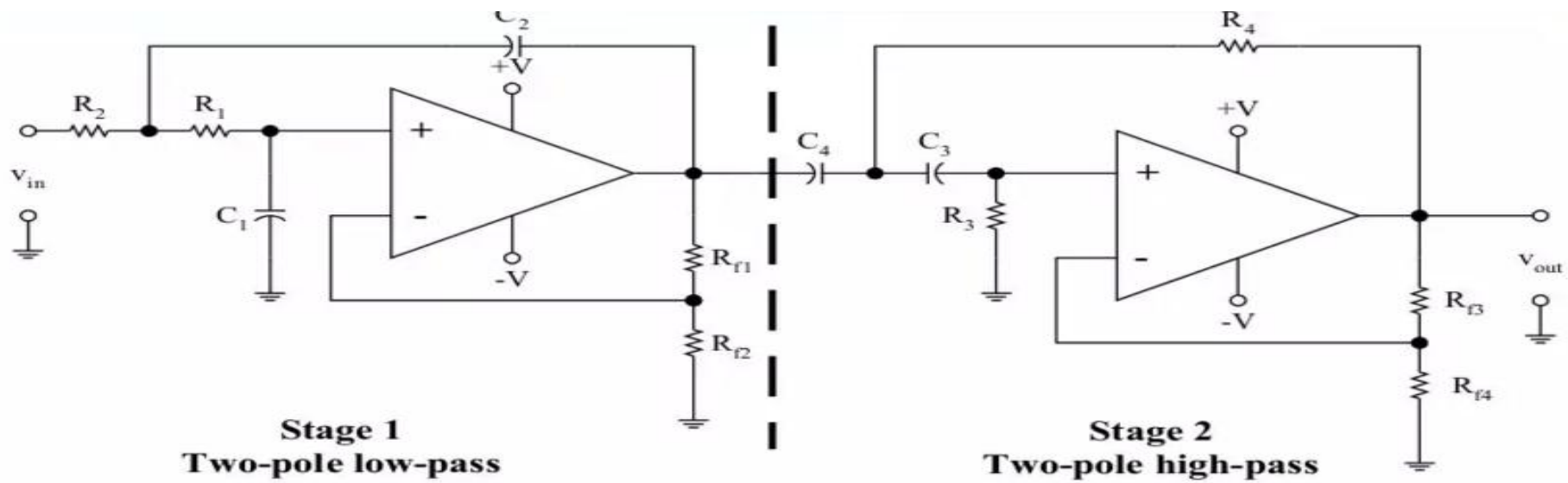


Stage 1
Two-pole low-pass

Stage 2
Two-pole high-pass

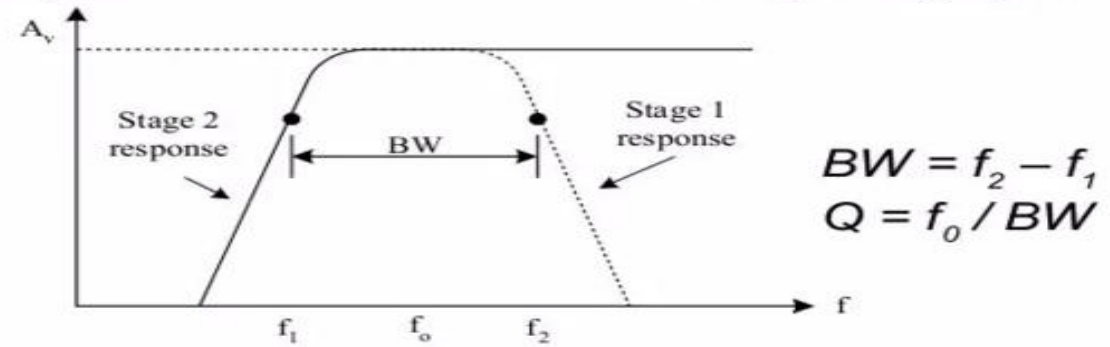

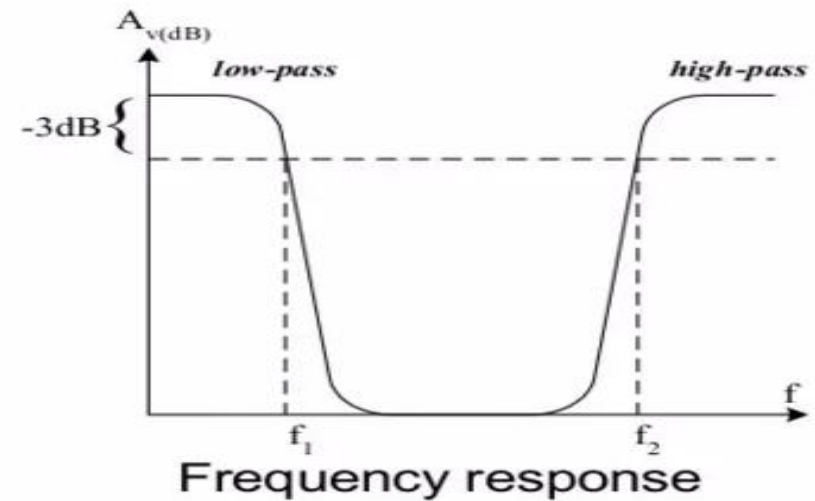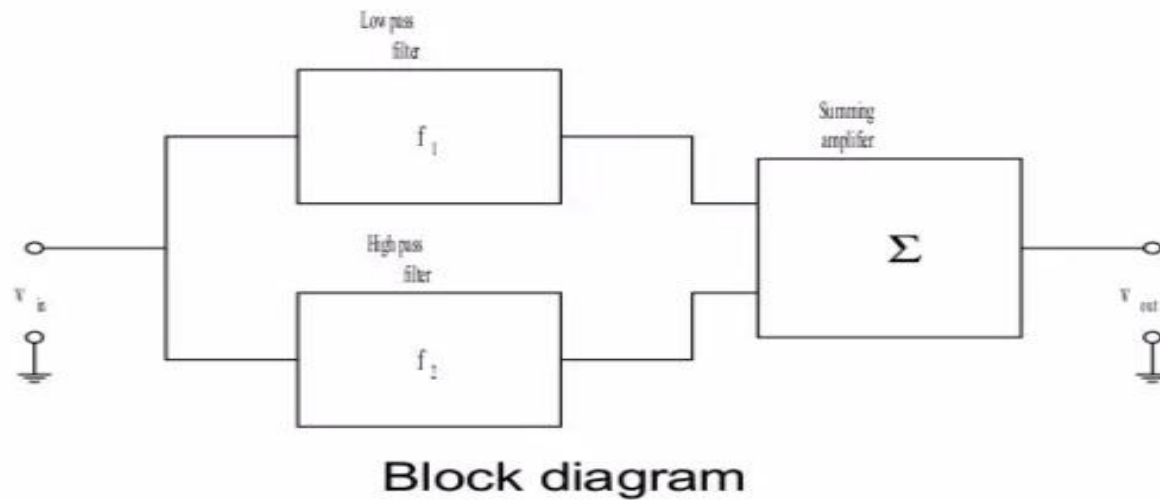The notch filter is designed to block all frequencies that fall within its bandwidth. The circuit is made up of a **high pass filter**, a **low-pass filter** and a **summing amplifier**. The summing amplifier will have an output that is equal to the sum of the filter output voltages.



(I) Low - Pass Filter

$$|H(j\omega)| = 1 \quad f < f_o$$

$$|H(j\omega)| = 0 \quad f > f_o$$

(II) High - Pass Filter

$$|H(j\omega)| = 0 \quad f < f_o$$

$$|H(j\omega)| = 1 \quad f > f_o$$

(III) Band - Pass Filter

$$|H(j\omega)| = 1 \quad f_L < f < f_H$$

$$|H(j\omega)| = 0 \quad f < f_L \text{ and } f > f_H$$

(IV) Band - Stop (Notch) Filter

$$|H(j\omega)| = 0 \quad f_L < f < f_H$$

$$|H(j\omega)| = 1 \quad f < f_L \text{ and } f > f_H$$

(V) All - Pass (or phase - shift) Filter

$$|H(j\omega)| = 1 \quad \text{for all } f$$

has a specific phase response

Advantages of active filters over passive filters (R, L, and C elements only):

1. By containing the op-amp, active filters can be designed to provide required gain, and hence **no signal attenuation** as the signal passes through the filter.
 2. **No loading problem**, due to the high input impedance of the op-amp prevents excessive loading of the driving source, and the low output impedance of the op-amp prevents the filter from being affected by the load that it is driving.
 3. **Easy to adjust over a wide frequency range** without altering the desired response.
-

