

## STATIC CHARACTERISTICS OF TRANSISTOR

### OBJECTIVE

The purpose of the experiment is to study the characteristics of bipolar transistor in common emitter (CE) configuration. From the characteristic curve it is expected to determine the hybrid parameters: input impedance  $h_{ie}$ , output admittance  $h_{oe}$ , forward current gain  $h_{fe}$ , reverse voltage gain  $h_{re}$  and to draw the hybrid equivalent model.

### EQUIPMENT AND COMPONENTS USED

BC107 Bipolar junction transistor  
 (0-30V) Dual Regulated Power Supply  
 330 $\Omega$ , 1k $\Omega$  resistor, ½ W  
 (0 - 30)mA,(0-500) $\mu$ A DC Ammeters  
 (0 - 30)V, (0-1)V DC Voltmeters  
 Breadboard

### THEORY

- Emitter is common or reference to both the input and output terminals.
- The base–emitter circuit is the input network and the collector–emitter circuit is the output network.
- The input and output characteristics describe the behavior of common – emitter configuration.

#### Input characteristics

- The plot between base current  $I_B$  and base emitter voltage  $V_{BE}$  at constant collector-emitter voltage  $V_{CE}$  represents input characteristics.
- Input characteristics resembles that of a forward-biased diode, as the base-emitter section of transistor is a diode.

#### Output characteristics

- The plot between collector current  $I_C$  and collector emitter voltage  $V_{CE}$  at constant base current  $I_B$  represents output characteristics.
- In the cutoff region, a small amount of collector current flows even when base current is zero.
- When  $V_{CE}$  has very low value, the transistor is said to be saturated.
- In active region, for small values of base current, the effect of collector voltage on collector current is small.
- The function of Zener diode is to keep the output voltage fairly constant over a wide variation of load current.

#### Current transfer characteristics

- The current transfer characteristics shows the variation of collector current  $I_C$  with base current  $I_B$  keeping collector emitter voltage  $V_{CE}$  as constant.
- The ratio is referred to as common-emitter current gain  $\beta$  and is always greater than 1.

### Hybrid Parameters

- The quantities  $h_{ie}$ ,  $h_{re}$ ,  $h_{oe}$ ,  $h_{fe}$  are called hybrid parameters and are the components of a small signal equivalent circuit.
- The h-parameters for small signal transistor equivalent circuit in the region of operation for common-emitter configuration can be found using the following equation.

$$h_{ie} = \Delta V_{be} / \Delta I_b \text{ at } V_{CE} \text{ is Constant}$$

$$h_{re} = \Delta V_{be} / \Delta V_{ce} \text{ at } I_B \text{ is Constant}$$


$$h_{fe} = \Delta I_c / \Delta I_b \text{ at } V_{CE} \text{ is Constant}$$

$$h_{oe} = \Delta I_c / \Delta V_{ce} \text{ at } I_B \text{ is Constant}$$


### FURTHER READING

- Theodore F. Bogart, Jeffrey S. Beasley, "Electron Devices and Circuits", PHI
- Robert Diffenderfer, "Electronic Devices", Delmar Cengage Learning, 2005
- Robert Boylestad, Louis Nashelsky, "Electronic Devices and Circuit Theory", PHI, 2008

### CIRCUIT DIAGRAM

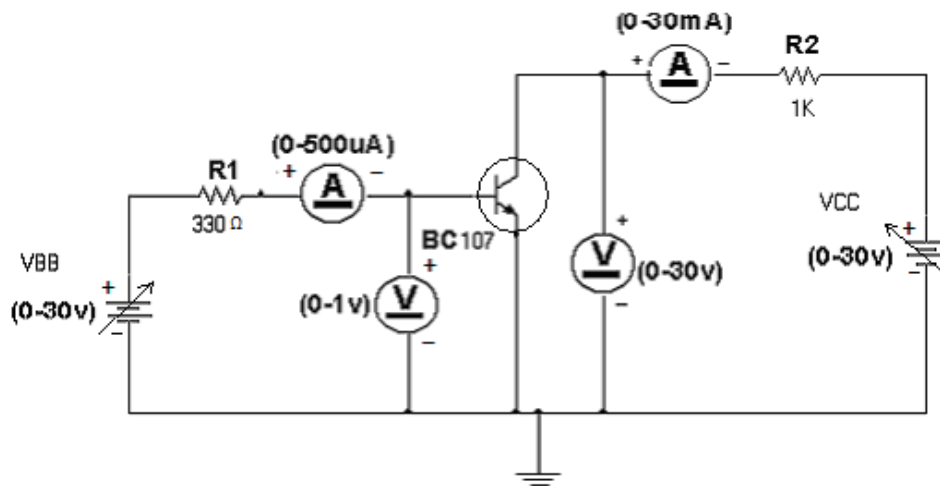


### PIN CONFIGURATION

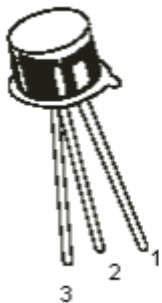


Pin Configuration:


1. Emitter
2. Base
3. Collector

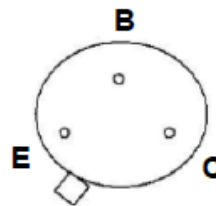


Bottom View

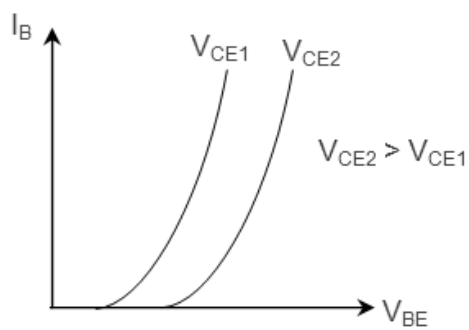**Model Graph**

(a) Input characteristics

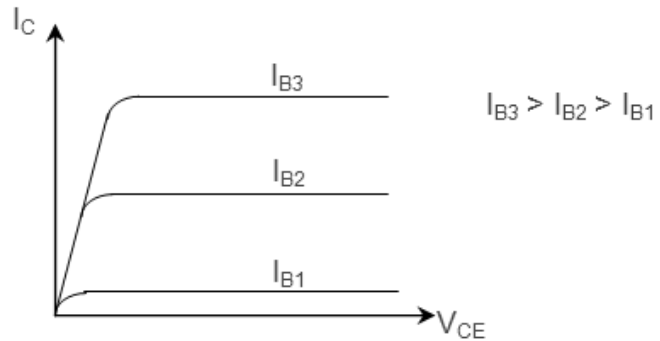

(b) Output characteristics

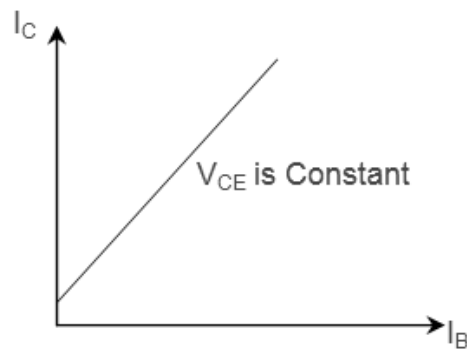

(c) Transfer characteristics

**PRELAB**

1. Read the specifications of BC107 transistor from its datasheet.

**Device Part Number: BC107**

**Device Manufacturer:** \_\_\_\_\_

Maximum Collector to emitter voltage,  $V_{CEO} =$

Maximum Emitter-base voltage,  $V_{EBO} =$

Maximum Collector current,  $I_C =$

Collector-Cut off Current,  $I_{CBO} =$

DC current gain,  $h_{fe} =$

Base Emitter Saturation Voltage,  $V_{BE(Sat)} =$

Collector Emitter Saturation Voltage,  $V_{CE(sat)} =$

Base Emitter On Voltage,  $V_{BE(ON)} =$

Input impedance,  $h_{ie} =$

Reverse Voltage ratio,  $h_{re} =$

Output admittance,  $h_{oe} =$

Total power dissipation,  $P_{tot} =$

Exp. No. :

Date:

**STATIC CHARACTERISTICS OF TRANSISTOR****OBJECTIVE****OBSERVATION**

Circuit Diagram

## Practice Procedure

**Input Characteristics**

1. Keeping the output voltage constant ( $V_{CE} = \text{constant}$ ), vary the input voltage and note down the corresponding  $V_{BE}$  voltage and  $I_B$  current.
2. Repeat the above step for different values of  $V_{CE}$ .
3. Plot the graph:  $I_B$  against  $V_{BE}$  for different values of  $V_{CE}$ .
4. From the plot, find the h-parameters: i)  $h_{fe}$ : forward current gain  
ii)  $h_{ie}$ : input impedance

**Output Characteristics**

1. Keeping the input current ( $I_B$ ) constant ( $I_B = \text{constant}$ ), vary the output voltage ( $V_{CE}$ ) and note down the corresponding collector ( $I_C$ ) current.
2. Repeat the above step for different values of  $I_B$  current.
3. Plot the graph:  $I_C$  against  $V_{CE}$  for different values of  $I_B$ .
4. From the plot, find the h-parameters: i)  $h_{oe}$ : output admittance  
ii)  $h_{re}$ : reverse voltage gain

**Current Transfer Characteristics**

1. Keeping the output voltage constant ( $V_{CE} = \text{constant}$ ), vary the input voltage and note down the  $I_B$  current and corresponding  $I_C$  current.
2. Plot the graph:  $I_C$  against  $I_B$  for constant  $V_{CE}$ .

**Table1: Input Characteristics**

$V_{CE} = 0 \text{ V}$		$V_{CE} = \quad \text{V}$	
$V_{BE}$ (volts)	$I_B$ ( $\mu\text{A}$ )	$V_{BE}$ (volts)	$I_B$ ( $\mu\text{A}$ )

**Table2: Output Characteristics**

$I_B = \quad \mu\text{A}$		$I_B = \quad \mu\text{A}$		$I_B = \quad \mu\text{A}$	
$V_{CE}$ (volts)	$I_C$ (mA)	$V_{CE}$ (volts)	$I_C$ (mA)	$V_{CE}$ (volts)	$I_C$ (mA)

**Table3: Transfer Characteristics**

$V_{CE} = 5 \text{ V}$	
$I_B$ ( $\mu\text{A}$ )	$I_C$ (mA)

$I_B$ ( $\mu\text{A}$ )	$I_C$ (mA)





**RESULTS AND CONCLUSION**

Prepared by:

Name: \_\_\_\_\_

Reg. No.: \_\_\_\_\_

Experiment Date: .....

Report Submission Date: .....

Submission Delay: .....

Signature

**ASSESSMENT**

Student Task	Max. Marks	Graded Marks
Pre-lab Preparation	20	
Inference	10	
Results & Conclusion	10	
Post-lab / Viva-voce	10	
Total	50	